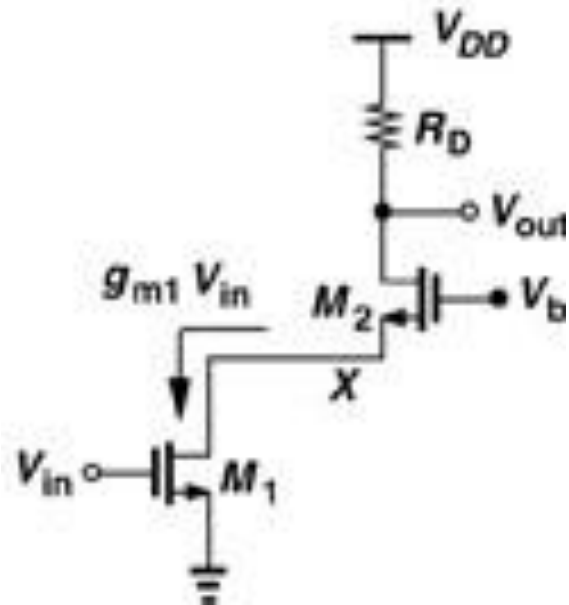


# Lecture 3


## IL2218 Analog electronics, advanced course

- Chapter 3      Cascode amplifiers
- Chapter 4      Differential amplifiers
- Examples

# Cascode amplifier




## Small signal model

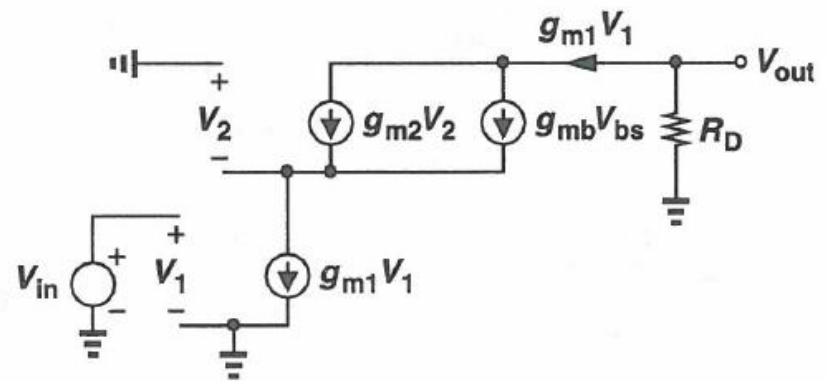


# Differential amplifier

## Why differential?


Single ended output

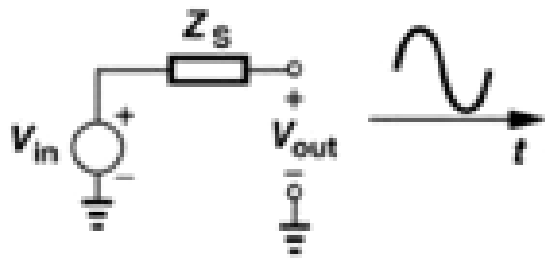


Differential output

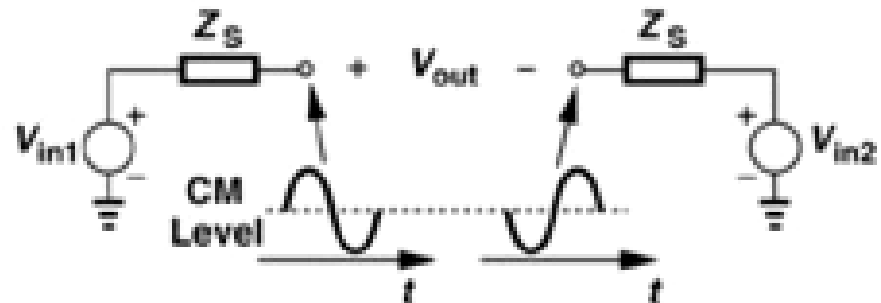

Noisy  $V_{DD}$

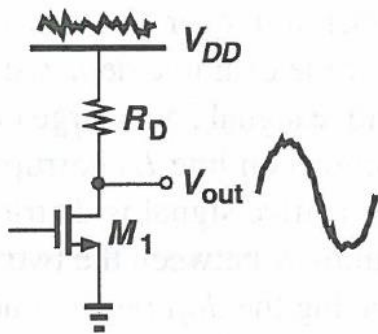


Noise reduction

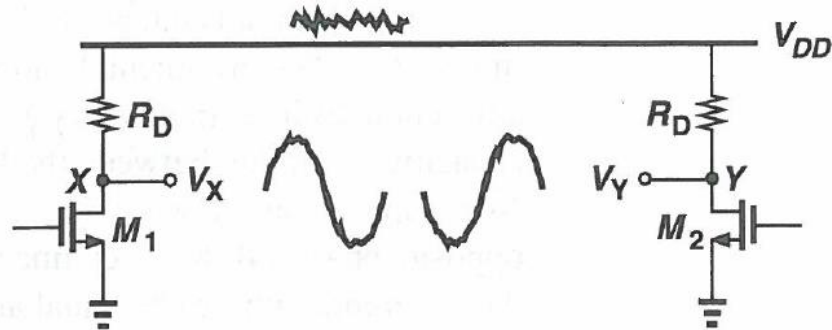


What is wrong in this picture?

# Basic differential pair

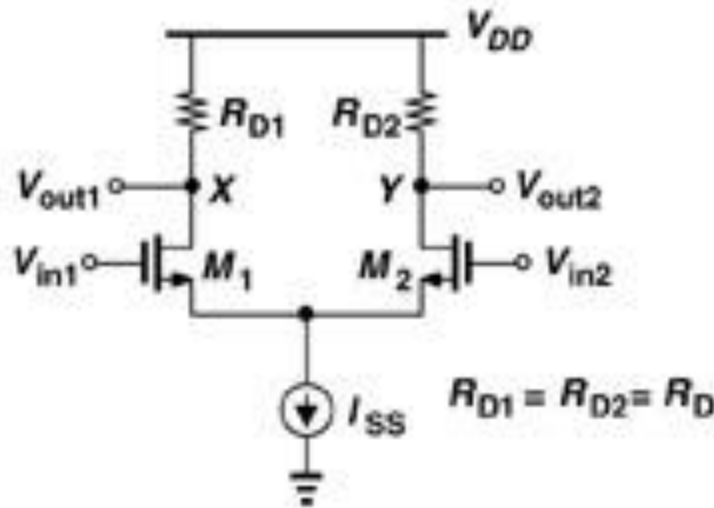

Constant tail current  $I_{SS}$   
 We can increase the current at one side if it is decreased at the other side  $I_{D1} = -I_{D2}$


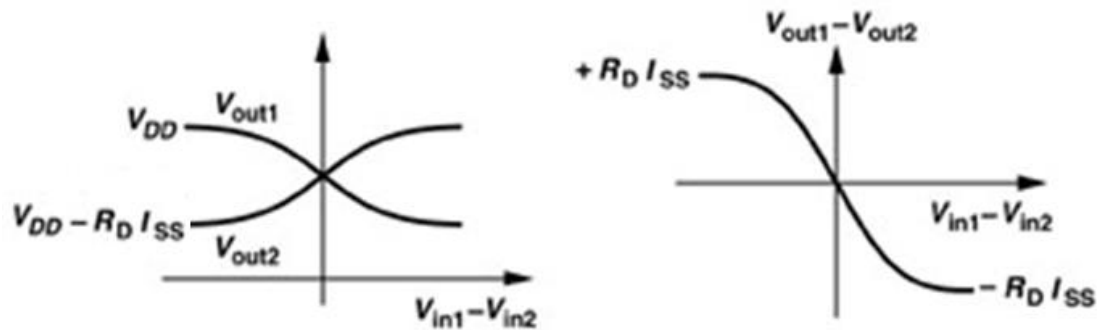
What will happen if  $V_{in1} = V_{in2}$  and the input voltage is increasing?




Input-output characteristics of a differential pair
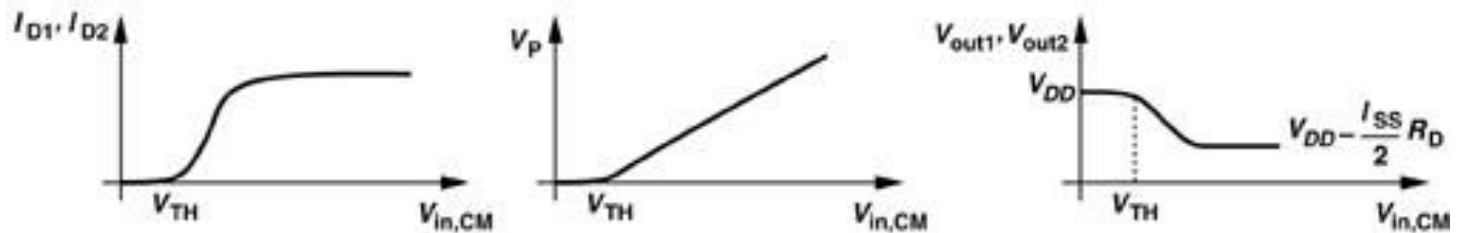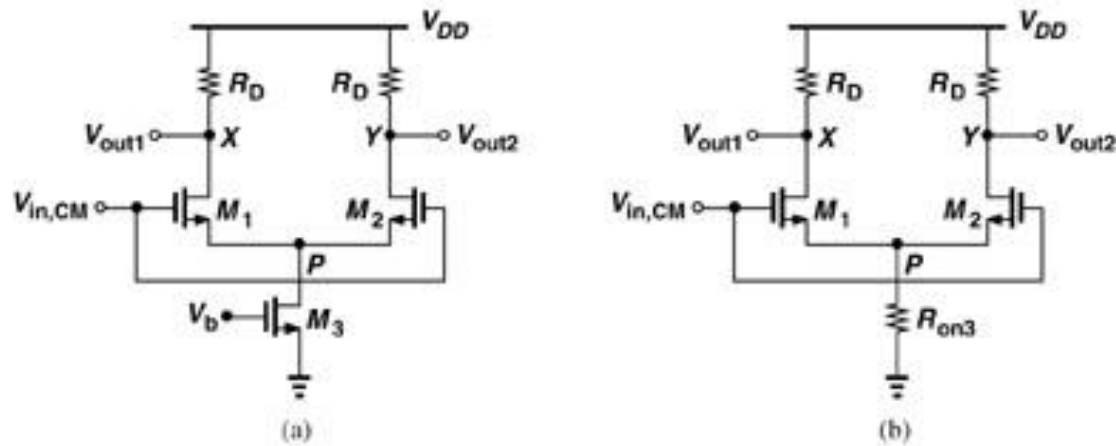
# Common mode response


Tail current source with finite output resistance



# Common mode, output swing

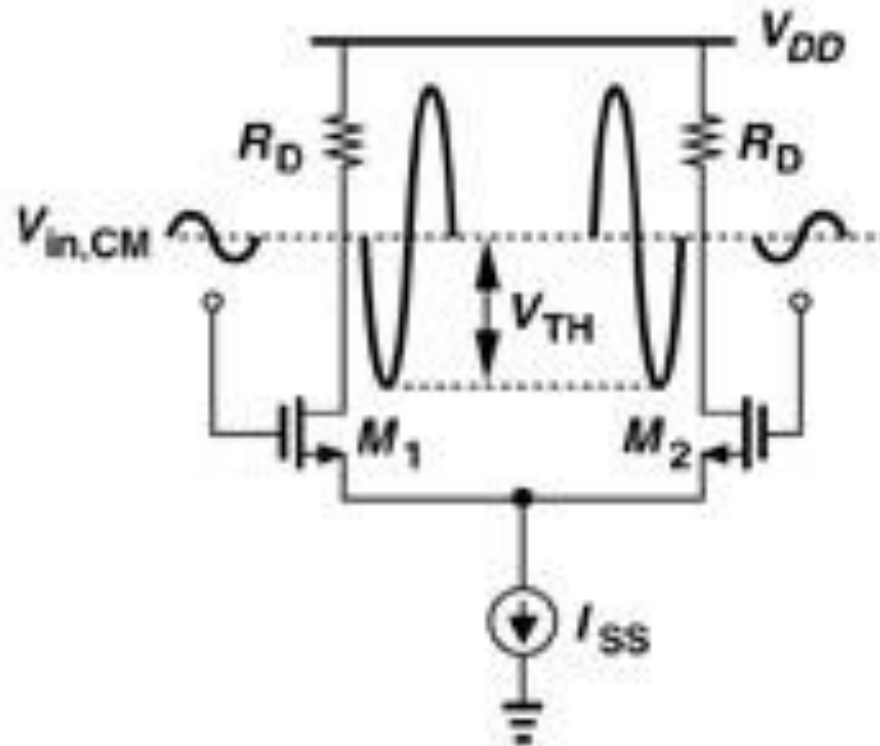

# Differential gain

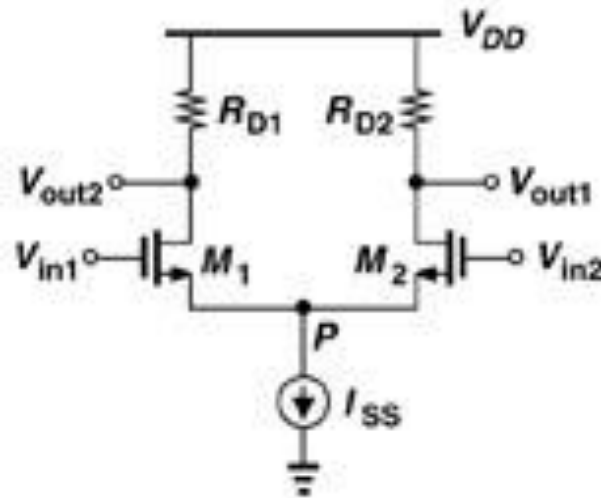


Differential gain

$$A_v = \frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}} = g_m R_D$$

Single ended output

$$A_v = \frac{g_m}{2} R_D$$



# Differential mode gain

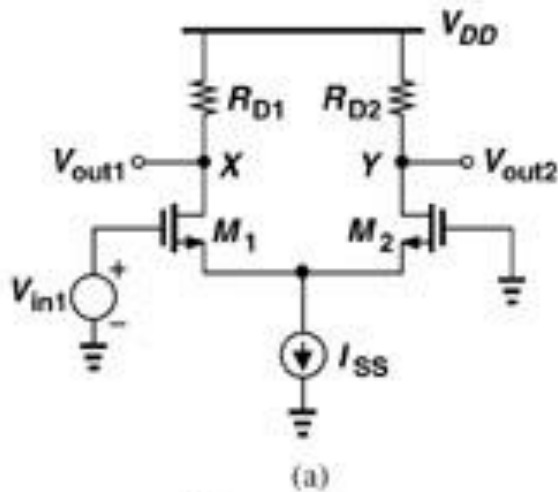

Single ended output

$$A_v = -\frac{g_m R_D}{1 + g_m R_S}$$

$$= -\frac{g_m}{2} R_D$$


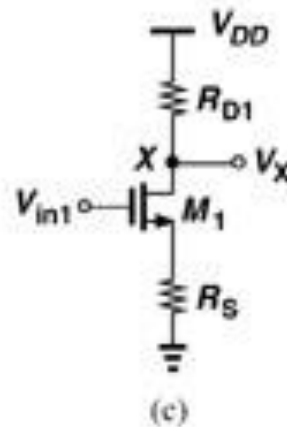
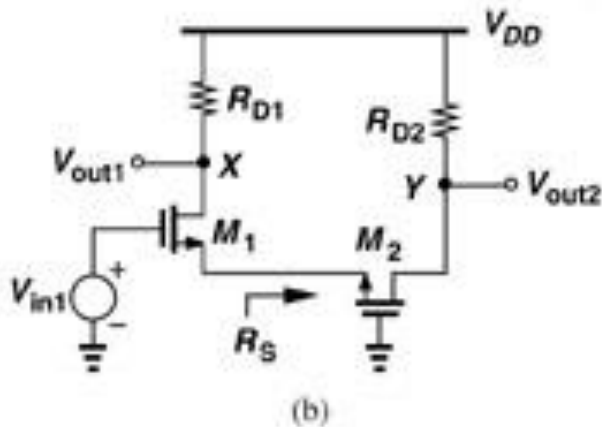


Differential gain

$$A_v = -g_m R_D$$





# Common mode gain

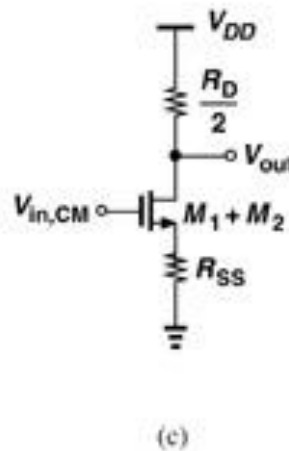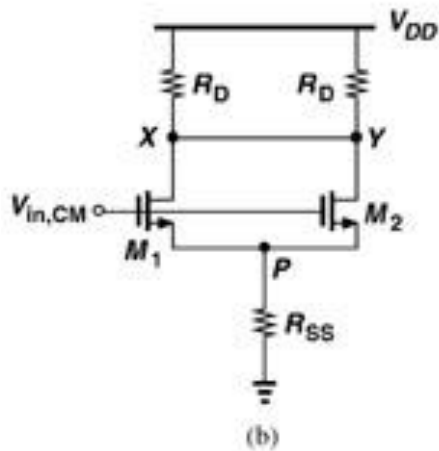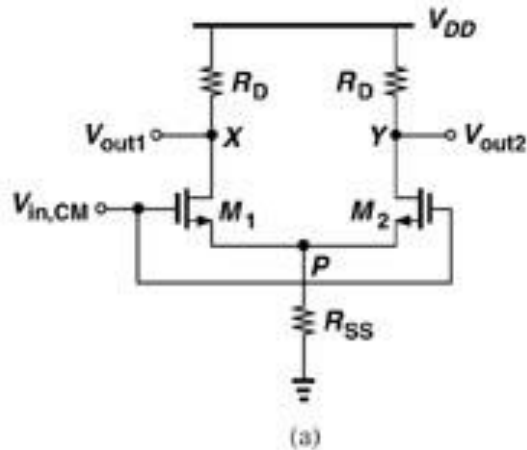

$$A_v = \frac{V_{out}}{V_{in,CM}} = - \frac{R_D / 2}{1 / (2g_m) + R_{SS}}$$

# MOS loads

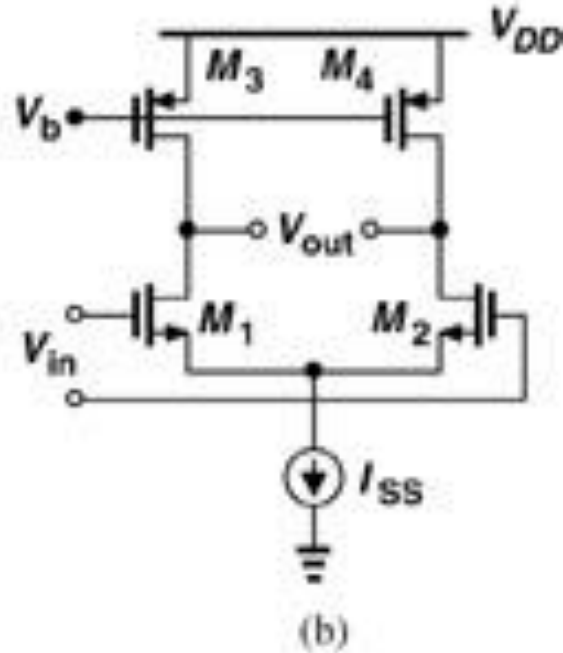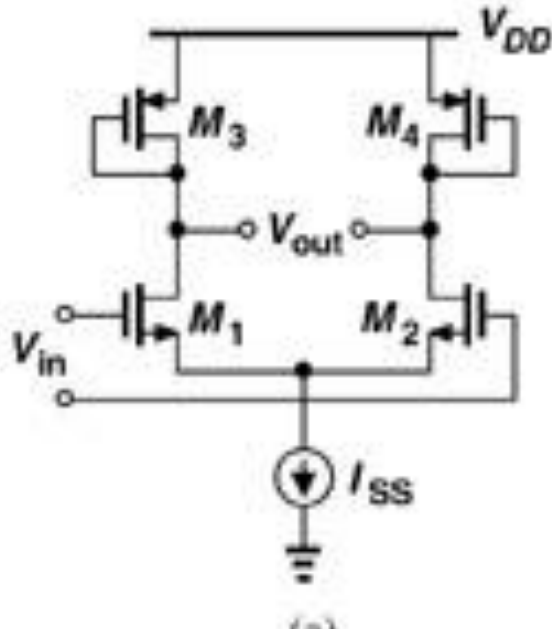


$$A_v = -g_{mN} \left( \frac{1}{g_{mP}} \parallel r_{oN} \parallel r_{oP} \right)$$


$$\approx -\frac{g_{mN}}{g_{mP}}$$

$$A_v = -g_{mN} (r_{oN} \parallel r_{oP})$$


# Variable gain

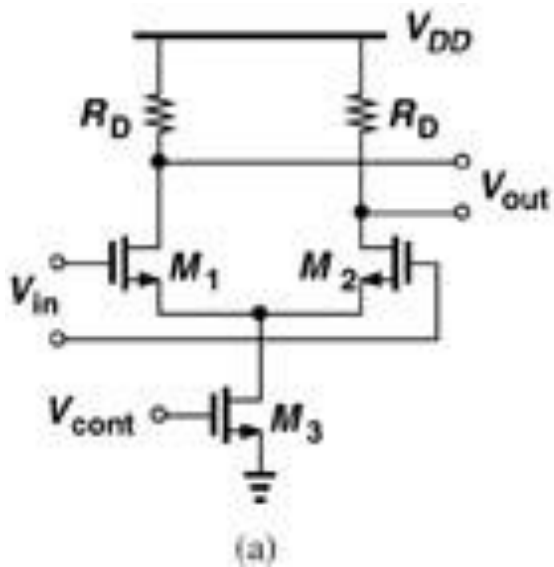

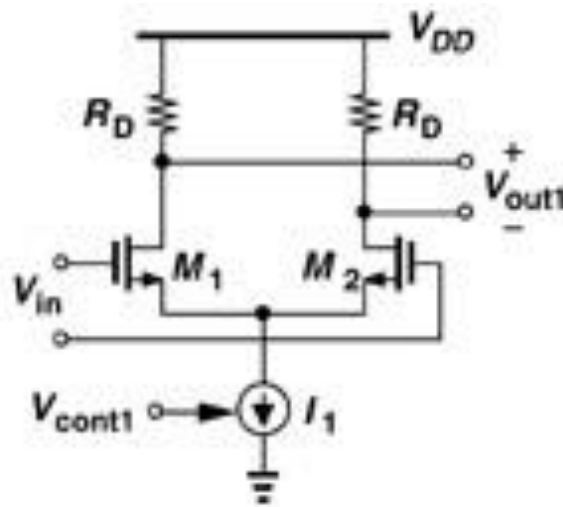Gain varied by control voltage  $V_{cont}$





$$\frac{V_{out1}}{V_{in}} = -g_m R_D$$

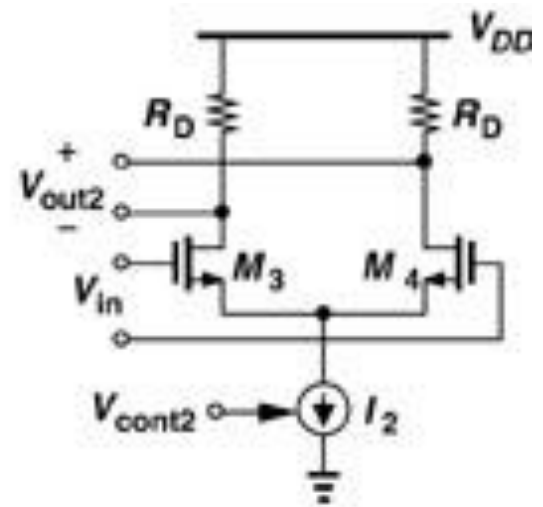

$$\frac{V_{out2}}{V_{in}} = +g_m R_D$$

# Gilbert cell

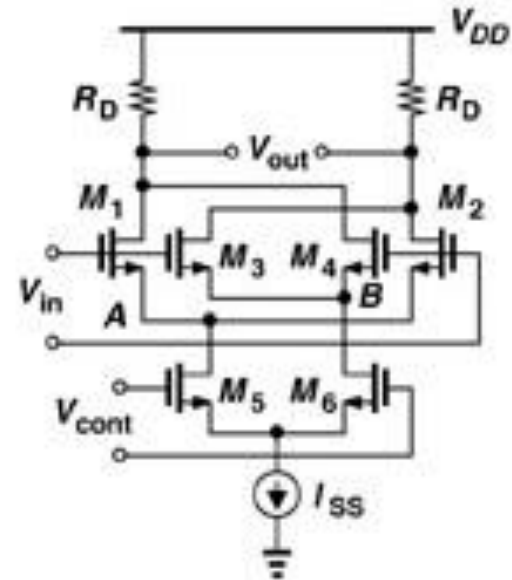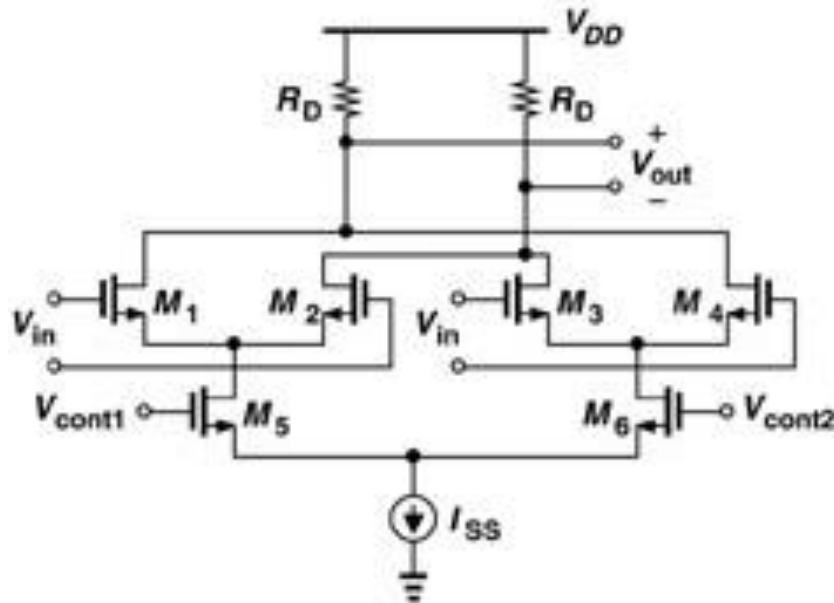

$$V_{OUT} = k V_{in} V_{cont}$$

Widely used in radio circuits as mixer and phase detector