
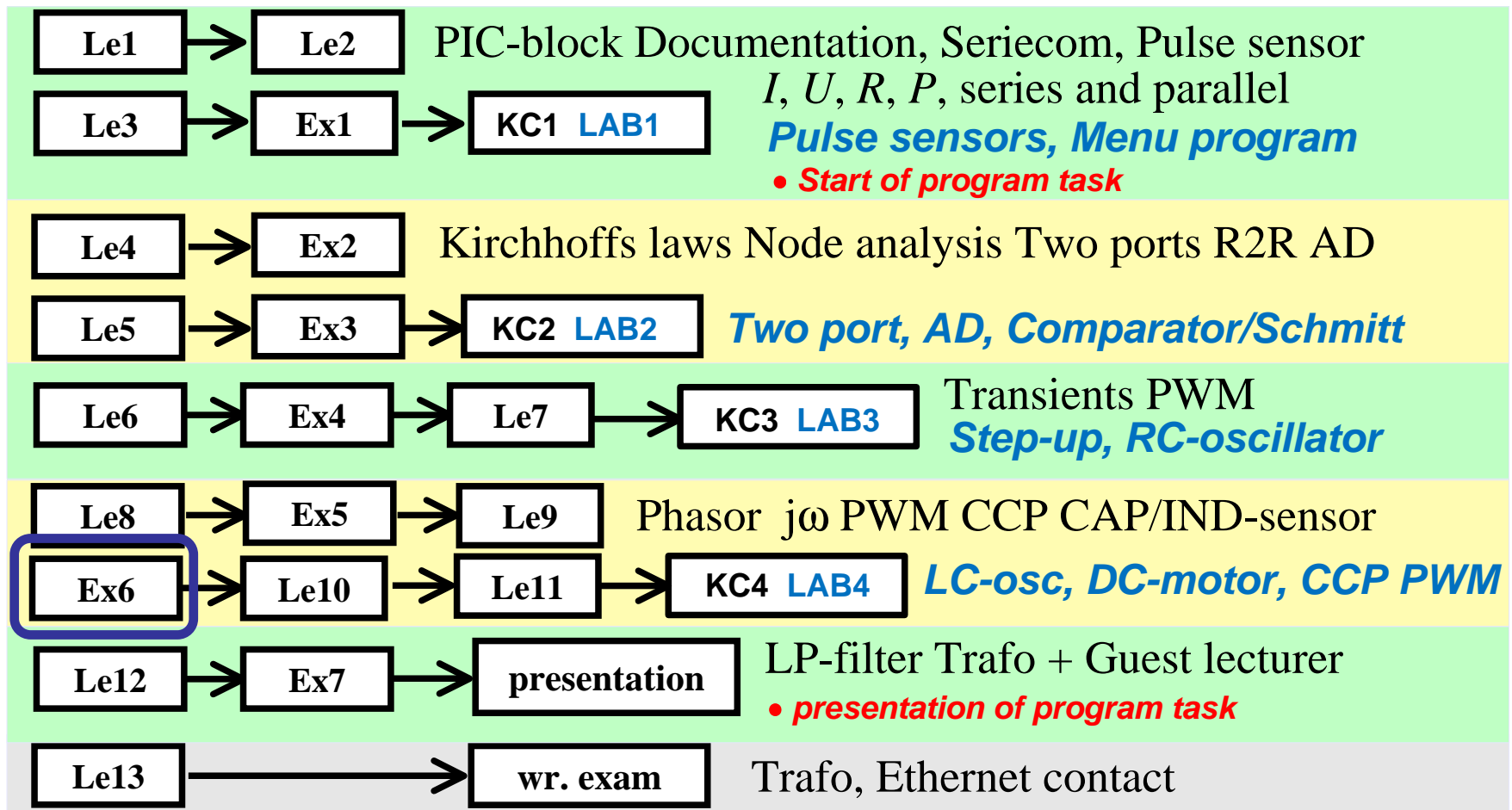


# IE1206 Embedded Electronics

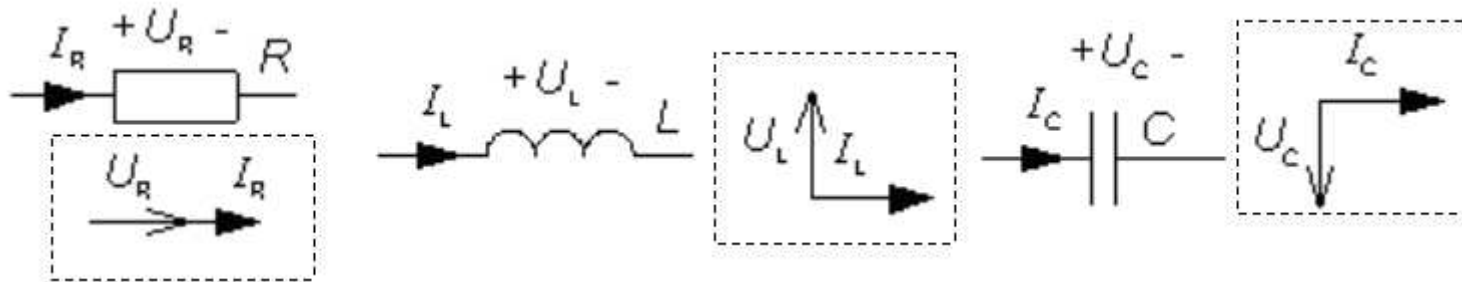

# Phasor - vector



$$\omega = 2\pi f$$

$$|X_L| = \omega \cdot L$$

$$|X_C| = \frac{1}{\omega \cdot C}$$

$$Z = \frac{U}{I}$$

# Complex phasors, $j\omega$ -method

- Complex OHM's law for  $R$   $L$  and  $C$ .

$$\underline{U}_R = \underline{I}_R \cdot R$$

$$\underline{U}_L = \underline{I}_L \cdot jX_L = \underline{I}_L \cdot j\omega L \quad \omega = 2\pi \cdot f$$

$$\underline{U}_C = \underline{I}_C \cdot jX_C = \underline{I}_C \cdot \frac{1}{j\omega C}$$


- Complex OHM's law for  $Z$ .

$$\boxed{\underline{U} = \underline{I} \cdot \underline{Z}} \quad \underline{Z} = \frac{U}{I} \quad \varphi = \arg(\underline{Z}) = \arctan\left(\frac{\text{Im}[\underline{Z}]}{\text{Re}[\underline{Z}]}\right)$$

William Sandqvist [william@kth.se](mailto:william@kth.se)

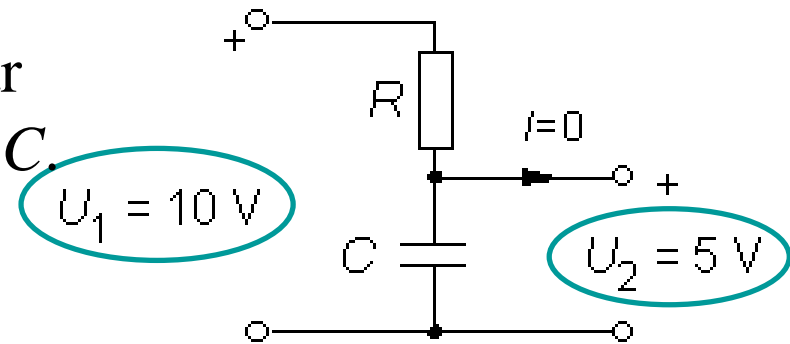
# $\omega$ for half the voltage? (12.3)

$U_1$  is a sine voltage with the angular frequency  $\omega$ . Decide the product  $R \cdot C$ . (No current is consumed at  $U_2$ ).


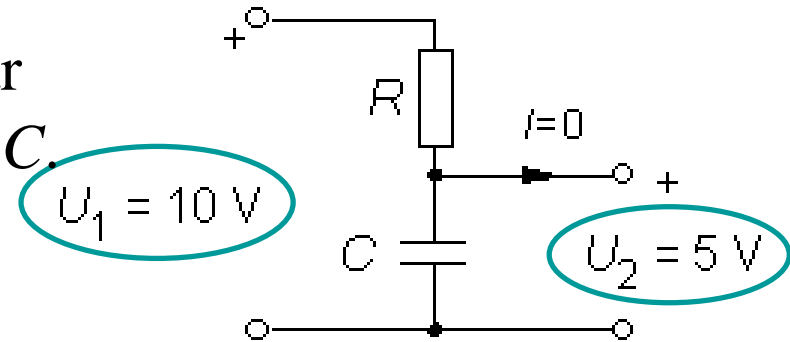
# $\omega$ for half the voltage? (12.3)


$U_1$  is a sine voltage with the angular frequency  $\omega$ . Decide the product  $R \cdot C$ . (No current is consumed at  $U_2$ ).



$$\underline{U}_2 = \underline{U}_1 \cdot \frac{1}{R + \frac{1}{j\omega C}}$$
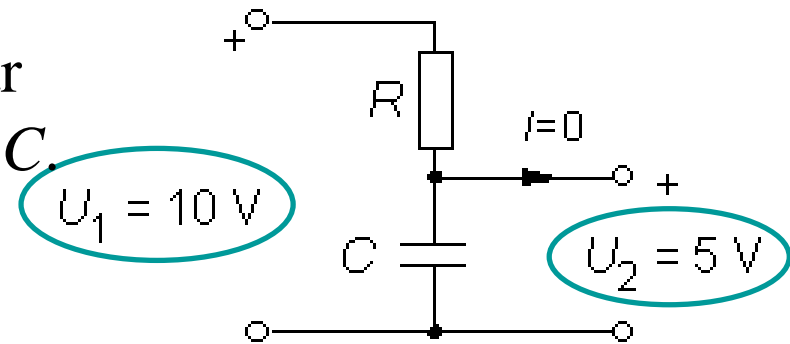
# $\omega$ for half the voltage? (12.3)


$U_1$  is a sine voltage with the angular frequency  $\omega$ . Decide the product  $R \cdot C$ . (No current is consumed at  $U_2$ ).



$$\underline{U}_2 = \underline{U}_1 \cdot \frac{1}{R + \frac{1}{j\omega C}} \cdot \frac{j\omega C}{j\omega C} =$$
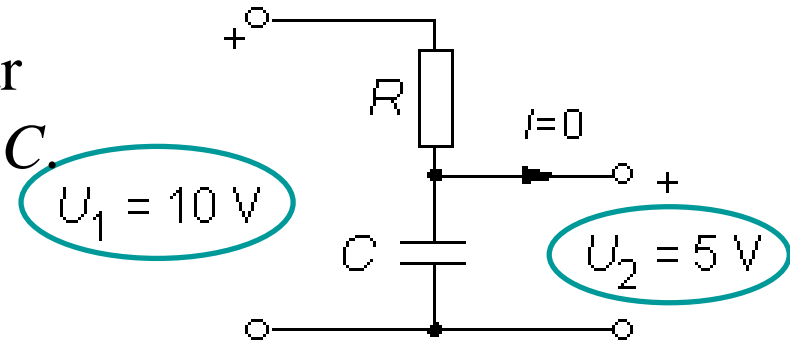
# $\omega$ for half the voltage? (12.3)

$U_1$  is a sine voltage with the angular frequency  $\omega$ . Decide the product  $R \cdot C$ . (No current is consumed at  $U_2$ ).




$$\underline{U}_2 = \underline{U}_1 \cdot \frac{1}{R + \frac{1}{j\omega C}} \cdot \frac{(j\omega C)}{(j\omega C)} = \underline{U}_1 \cdot \frac{1}{1 + j\omega RC}$$


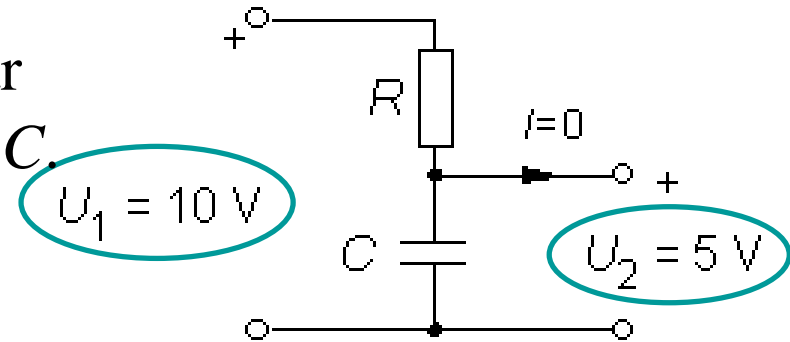
# $\omega$ for half the voltage? (12.3)


$U_1$  is a sine voltage with the angular frequency  $\omega$ . Decide the product  $R \cdot C$ . (No current is consumed at  $U_2$ ).



$$\underline{U}_2 = \underline{U}_1 \cdot \frac{1}{R + \frac{1}{j\omega C}} \cdot \frac{(j\omega C)}{(j\omega C)} = \underline{U}_1 \cdot \frac{1}{1 + j\omega RC} \Rightarrow \frac{U_1}{U_2} = \sqrt{1 + R^2 \omega^2 C^2} = \frac{10}{5} = 2$$
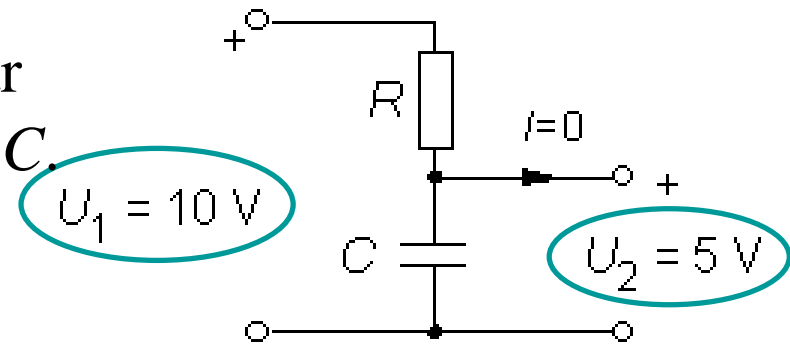
# $\omega$ for half the voltage? (12.3)

$U_1$  is a sine voltage with the angular frequency  $\omega$ . Decide the product  $R \cdot C$ . (No current is consumed at  $U_2$ ).




$$\underline{U}_2 = \underline{U}_1 \cdot \frac{1}{R + \frac{1}{j\omega C}} \cdot \frac{(j\omega C)}{(j\omega C)} = \underline{U}_1 \cdot \frac{1}{1 + j\omega RC} \Rightarrow \frac{U_1}{U_2} = \sqrt{1 + R^2 \omega^2 C^2} = \frac{10}{5} = 2$$

$$1 + R^2 \omega^2 C^2 = 4 \Leftrightarrow R\omega C = \sqrt{3} \Leftrightarrow RC = \frac{\sqrt{3}}{\omega}$$

William Sandqvist [william@kth.se](mailto:william@kth.se)


# Compare serial with parallel (12.5)

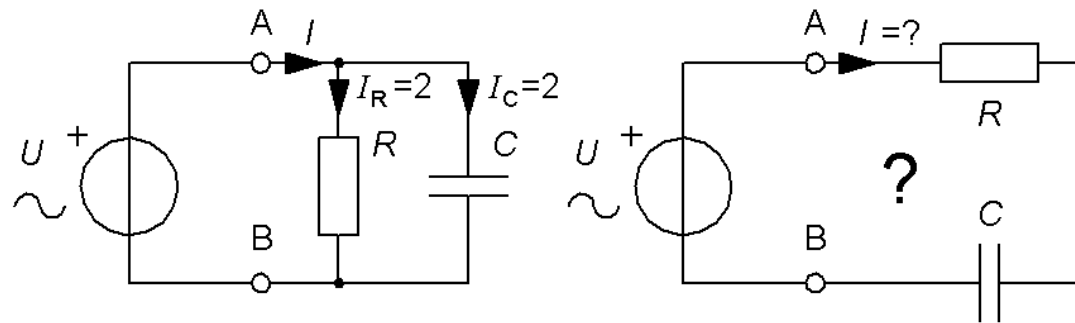

When a resistor  $R$  and a capacitor  $C$  is connected in parallel to a voltage source  $U$  each of them get the current 2A.

How big would the current in the resistor be if the two were series connected to the voltage source?

# Compare serial with parallel (12.5)

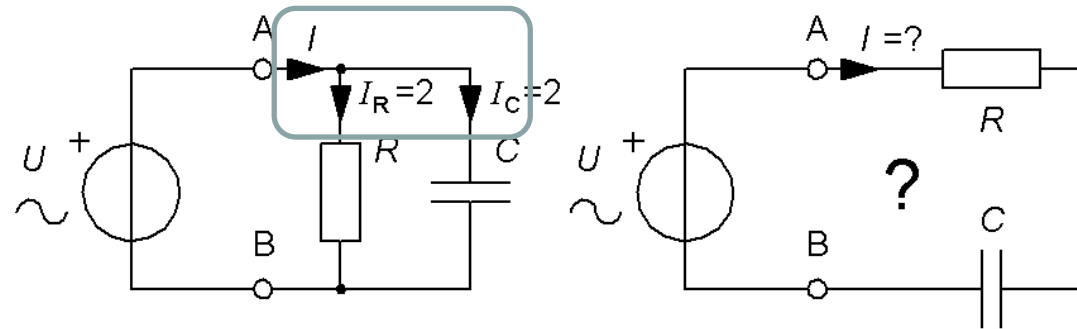


Parallel connection:

$$\underline{I} = \underline{I}_R + \underline{I}_C = \frac{U}{R} + jU\omega C \quad \underline{I} = 2 + 2j$$

$$I_R = \frac{U}{R} = 2 \quad I_C = U\omega C = 2 \quad \Rightarrow \quad R = \frac{1}{\omega C} = \frac{U}{2}$$


# Compare serial with parallel (12.5)

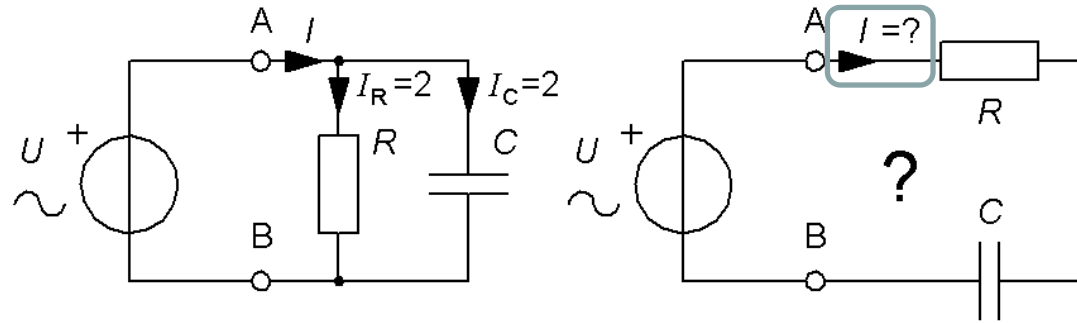

Series connected:

$$\underline{I} = \frac{U}{R + \frac{1}{j\omega C}} \Rightarrow I = \frac{U}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}}$$

# Compare serial with parallel (12.5)

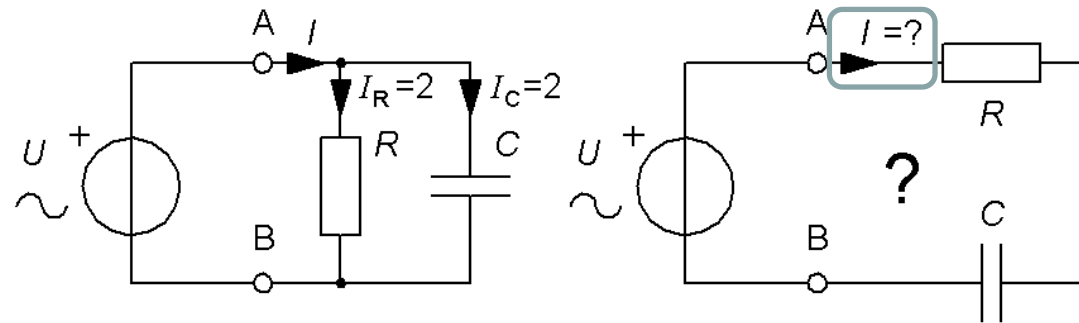


Series connected:

$$\underline{I} = \frac{U}{R + \frac{1}{j\omega C}} \Rightarrow I = \frac{U}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \quad \text{As before ...} \quad R = \frac{1}{\omega C} = \frac{U}{2}$$

$$\Rightarrow I = \frac{U}{\sqrt{\frac{U^2}{2^2} + \left(\frac{U}{2}\right)^2}} = \frac{U}{U \cdot \sqrt{\frac{1}{4} + \frac{1}{4}}} = \sqrt{2} \approx 1,414 \text{ A}$$

# Compare serial with parallel (12.5)

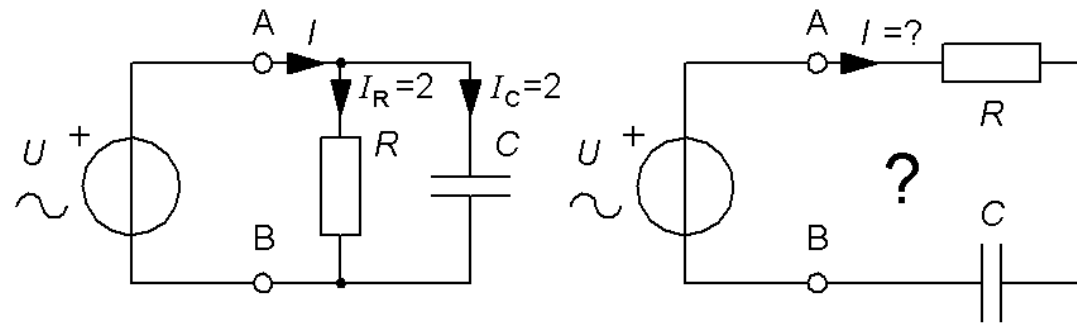

Series connection:

$$\underline{I} = \frac{U}{R + \frac{1}{j\omega C}} \Rightarrow I = \frac{U}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \quad \text{As before ...} \quad R = \frac{1}{\omega C} = \frac{U}{2}$$

$$\Rightarrow I = \frac{U}{\sqrt{\frac{U^2}{2^2} + \left(\frac{U}{2}\right)^2}} = \frac{U}{U \cdot \sqrt{\frac{1}{4} + \frac{1}{4}}} = \sqrt{2} \text{ A}$$


Parallel 2A  
Series 1,4A



William Sandqvist [william@kth.se](mailto:william@kth.se)
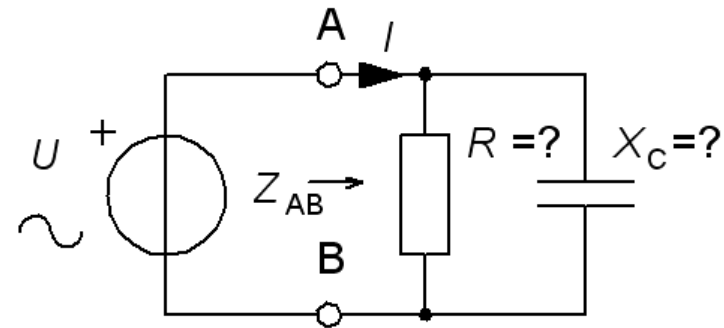
# Try yourself ... (12.1)

Set up the complex expression for current  $I$  expressed with  $U$   $R$   $C$   $\omega$ . Let  $U$  be reference phase, real. Answer with a expression of the form  $a+jb$ .




$$\underline{I} = \underline{I}_R + \underline{I}_C = \frac{U}{R} + \frac{U}{\frac{1}{j\omega C}} = \frac{U}{R} + j\omega C \cdot U$$

William Sandqvist [william@kth.se](mailto:william@kth.se)
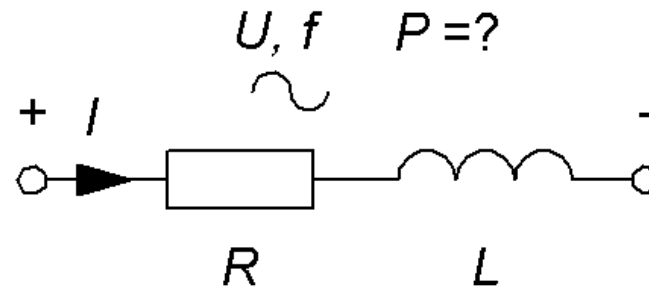
# Active power in impedance

Set up an expression of the active power  $P$  for this impedance. There will only be power in the resistors.




$U$  reference phase, real.

$$P = I^2 \cdot R \quad \underline{I} = \frac{U}{\underline{Z}} = \frac{U}{R + j\omega L} \Rightarrow I = \frac{U}{\sqrt{R^2 + (\omega L)^2}}$$


$$P = R \cdot \frac{U^2}{R^2 + (\omega L)^2} = \frac{RU^2}{R^2 + (\omega L)^2}$$

William Sandqvist [william@kth.se](mailto:william@kth.se)

# SL accesscard (13.7)

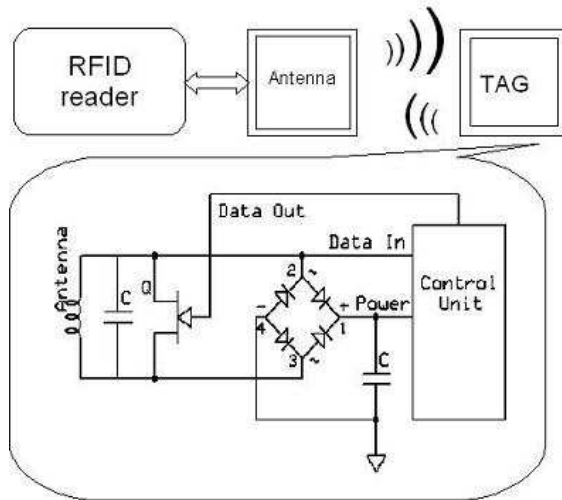

$$R_X = ?$$

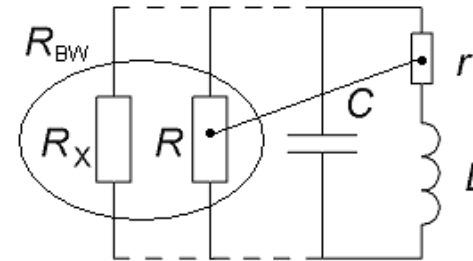

SL access-card contains a RFID-tag that communicates with the turnstyle reader on the frequency 13,56 MHz and uses the data transfer speed of 70 KHz.

To be able to read data in that speed then the resonance circuits inside the reader and the card must have a bandwidth at least twice this data speed:  $2 \cdot 70 = \mathbf{140 \text{ kHz}}$ .


# SL accesscard (13.7)



RFID-tag in the card consists of a parallel resonance circuit

$C||L||R||R_X$ . The processor in the card consumes current from the resonance circuit. This is symbolized with the resistance  $R_X$ .

$$R_X = ?$$

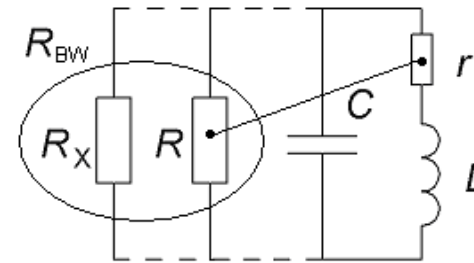

$$f_0 = 13,56 \text{ MHz}$$

$$BW = 140 \text{ kHz}$$

$$L = 2,5 \text{ } \mu\text{H}$$

$$r = 1,5 \text{ } \Omega$$

$$C = 55 \text{ pF}$$

a) Calculate the value of  $R_X$  gives the card the desired bandwidth  $BW$ .

b) How big current at the voltage 3V can the processor ( $R_X$ ) then take from the resonant circuit?

# SL accesscard (13.7)




- The inductor Q-value:

$$Q = \frac{\omega L}{r} = \frac{2\pi f_0 \cdot L}{r} =$$

$$= \frac{2\pi \cdot 13,56 \cdot 10^6 \cdot 2,5 \cdot 10^{-6}}{1,5} = 142$$

$$R_X = ?$$

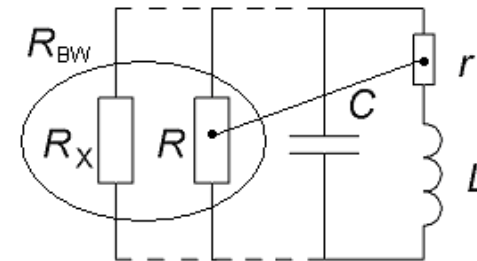

- Transformation of  $r$

$$R = Q^2 \cdot r = 142^2 \cdot 1,5 = 30,25 \text{ k}\Omega$$

- Parallel resistance to give bandwidth 140 kHz

$$Q_{\text{BW}} = \frac{f_0}{\Delta f} = \frac{13,56 \cdot 10^6}{140 \cdot 10^3} = 96,86 \quad Q_{\text{BW}} = \frac{R_{\text{BW}}}{2\pi \cdot f_0 \cdot L} \Rightarrow$$

$$R_{\text{BW}} = Q_{\text{BW}} \cdot 2\pi \cdot f_0 \cdot L = 96,86 \cdot 2\pi \cdot 13,56 \cdot 10^6 \cdot 2,5 \cdot 10^{-6} = 20,63 \text{ k}\Omega$$



# SL accesscard (13.7)



Parallel resistande for bandwidth 140 kHz


$$R_X = ?$$

$$R_{BW} = 20,63 \text{ k}\Omega$$

$$\text{a) } R_{BW} = R_X \parallel R \Rightarrow R_X = \frac{R \cdot R_{BW}}{R - R_{BW}}$$

$$R_X = \frac{30,25 \cdot 20,63}{30,25 - 20,63} \cdot 10^3 = 64 \text{ k}\Omega$$
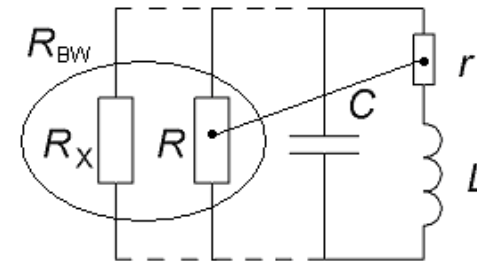
$$\text{b) } U = I \cdot R_X \quad U = 3 \quad I = \frac{U}{R_X} = \frac{3}{64 \cdot 10^3} = 47 \mu\text{A}$$



William Sandqvist [william@kth.se](mailto:william@kth.se)

# To measure Q-value




**Radio controlled clock** is a clock that is automatically synchronized with a time code from a radio transmitter in Germany, on longwave 77,5 kHz. The time signal consists of pulses encoded digitally. The signal strength is weak so such a receiver uses a tuned resonant circuit with  $L$  and  $C$ . The coil has a ferrite core, and this is also used as an antenna.

In a project we have to measure the Q-value this resonance circuit. How will this be done? Other values:

$$L = 1,5 \text{ mH}$$

$$C = 2,8 \text{ nF}$$

# To measure Q-value

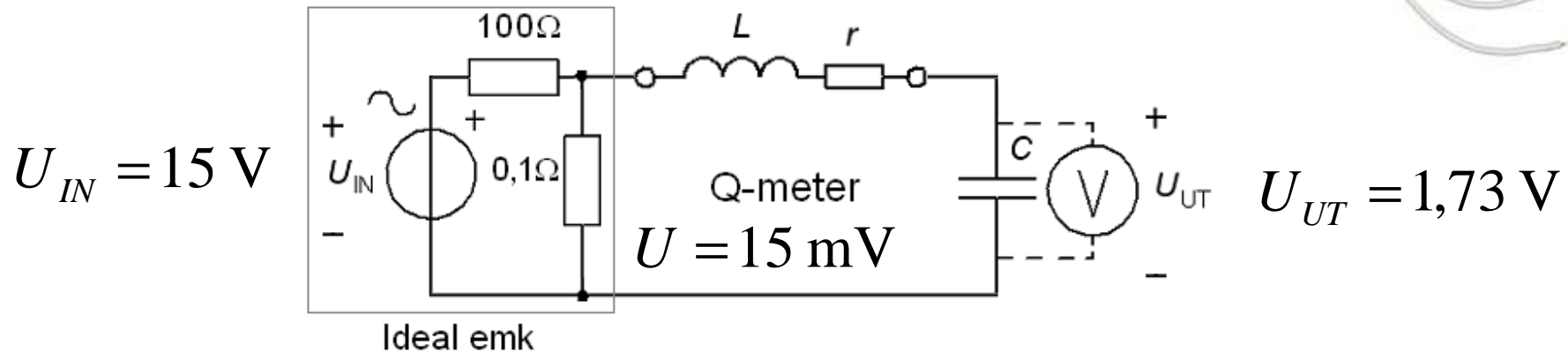


*This is how to measure the inductor's Q-value.*

$U_{IN} = 15 \text{ V}$  is a sine voltage with the frequency 77,5 kHz (the resonance resonansfrequency) which is voltage divided to 15 mV. Over the capacitor we then measures the much bigger voltage  $U_{UT} = 1,73 \text{ V}$ .

- What is the inductor's Q-value?
- What is the value of the inductor's internal resistance  $r$  (will also include other losses)?

# To measure Q-value

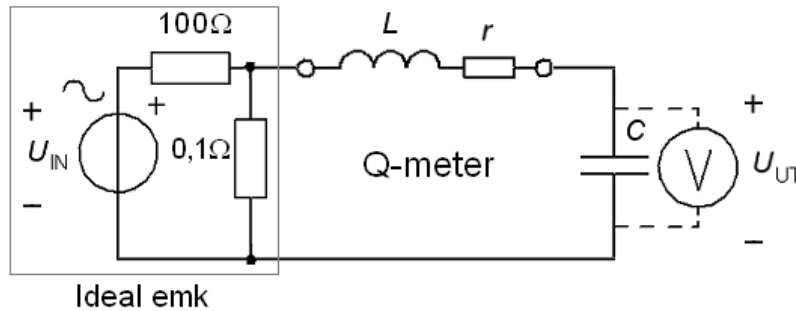

$$f_0 = \frac{1}{2\pi\sqrt{L \cdot C}} = \frac{1}{2\pi\sqrt{1,5 \cdot 10^{-3} \cdot 2,8 \cdot 10^{-9}}} = 77,5 \cdot 10^3$$

Check of resonance frequency 77,5 KHz

The voltage divider:  $U_r = 15 \frac{0,1}{100} = 0,015 \text{ V}$

a)  $Q = \frac{2\pi f \cdot L}{r} \cdot \frac{I}{I} = \frac{U_L}{U_r} = \{U_L = U_C = U_{UT}\} = \frac{U_{UT}}{U_r} = \frac{1,73}{0,015} = 115$

b)  $r = \frac{2\pi f \cdot L}{Q} = \frac{2\pi \cdot 77,5 \cdot 10^3 \cdot 1,5 \cdot 10^{-3}}{115} = 6,33 \Omega$


Big compared with 0,1Ω from voltage divider.

William Sandqvist [william@kth.se](mailto:william@kth.se)

# Thevenin equivalent with inductor (12.4)

Determine the value of the current  $I$ .


Use Thevenin equivalent.

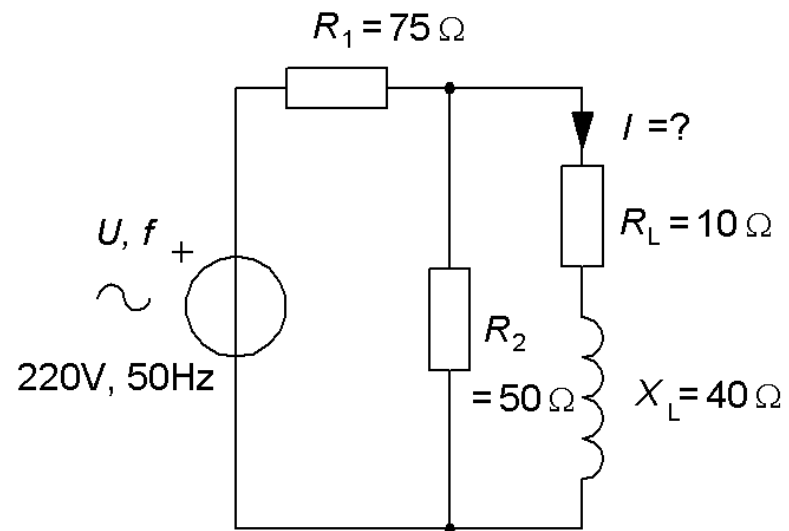

# Thevenin equivalent with inductor (12.4)

Determine the value of the current  $I$ .


Use Thevenin equivalent.

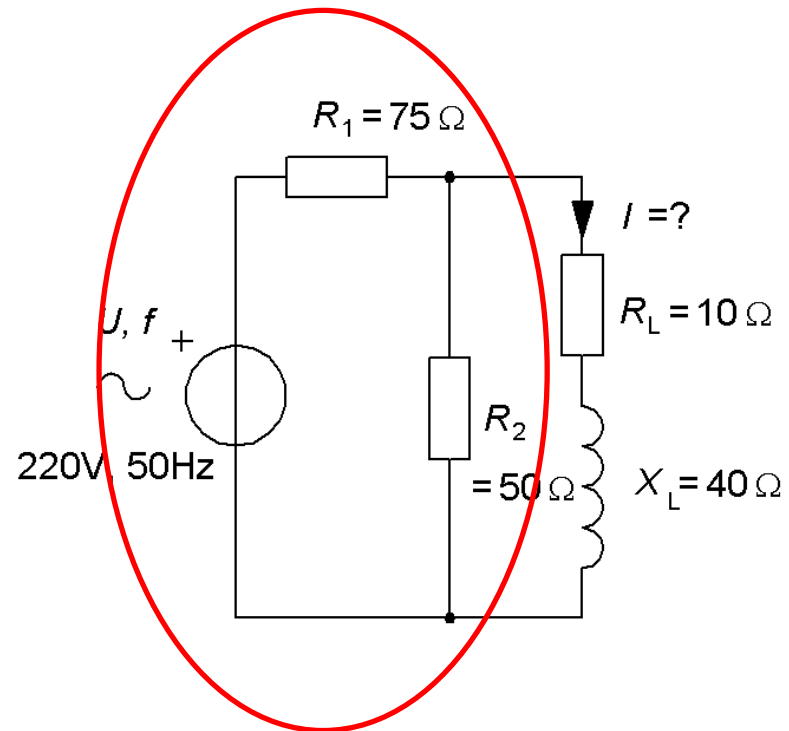




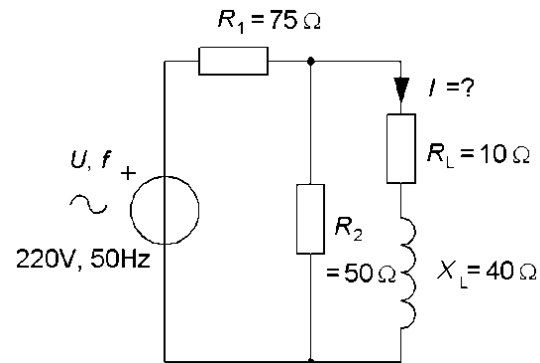
# Thevenin equivalent with inductor (12.4)

Calculate the Thevenin equivalent  $E_0$  and  $R_I$  of this circuit.



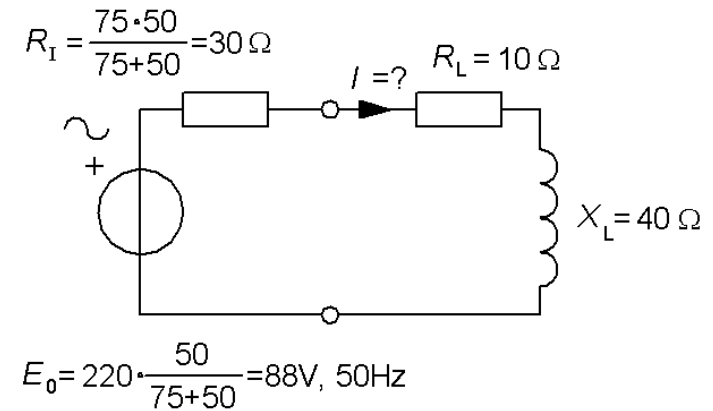
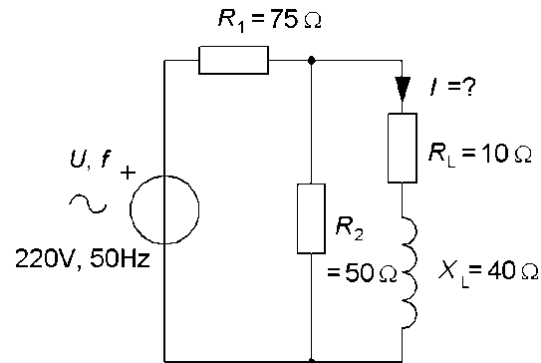
# Thevenin equivalent with inductor (12.4)

Calculate the Thevenin equivalent  $E_0$  and  $R_I$  of this circuit.


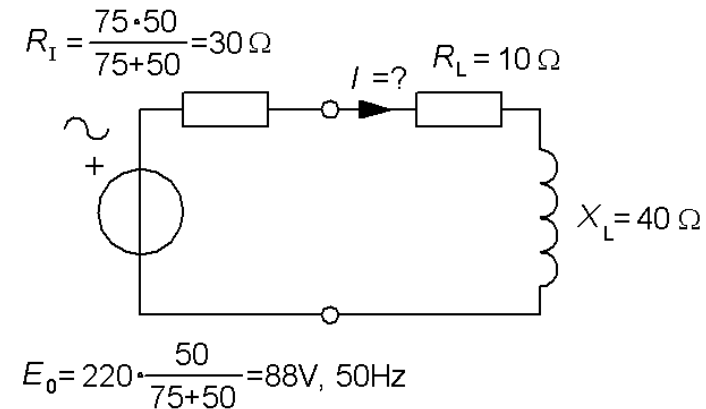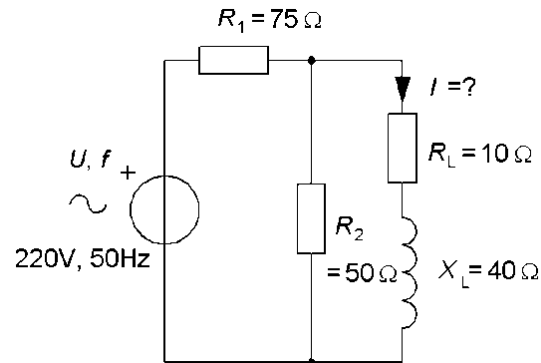
# Thevenin equivalent with inductor (12.4)

Calculate the Thevenin equivalent  $E_0$  and  $R_I$  of this circuit.



The emf and resistors – this time as with DC circuits ...


$$R_I = \frac{75 \cdot 50}{75 + 50} = 30 \Omega \quad E_0 = 220 \frac{50}{75 + 50} = 88 \text{ V}$$

The inductor – now it must be considered an AC circuits ...

$$\underline{I} = \frac{\underline{U}}{\underline{Z}} \Rightarrow I = \frac{88}{|(30 + 10) + j40|} = \frac{88}{\sqrt{(30 + 10)^2 + 40^2}} = 1,56 \text{ A}$$


William Sandqvist [william@kth.se](mailto:william@kth.se)

# Example. Complex equivalent

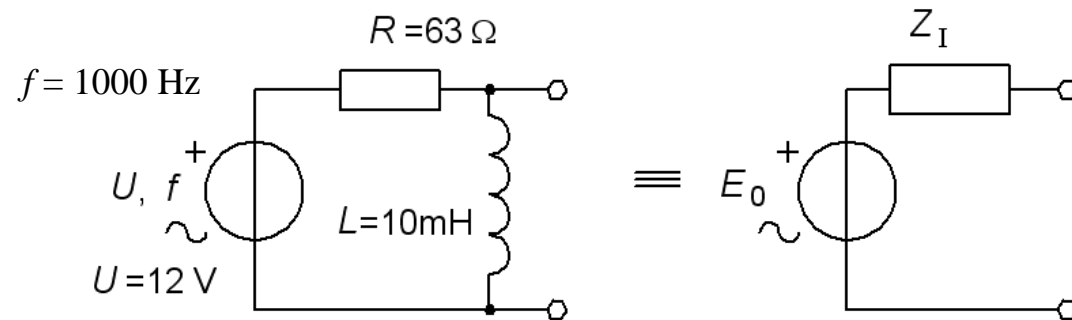

- Derive the equivalent complex circuit with  $E_0 + Z_I$ .
- Suppose that we can load the circuit with an arbitrary chosen impedance – how should this be composed if one wishes the power in the load to be the maximum? (Maximum power transfer theorem).

# Example. Complex equivalent, $E_0$

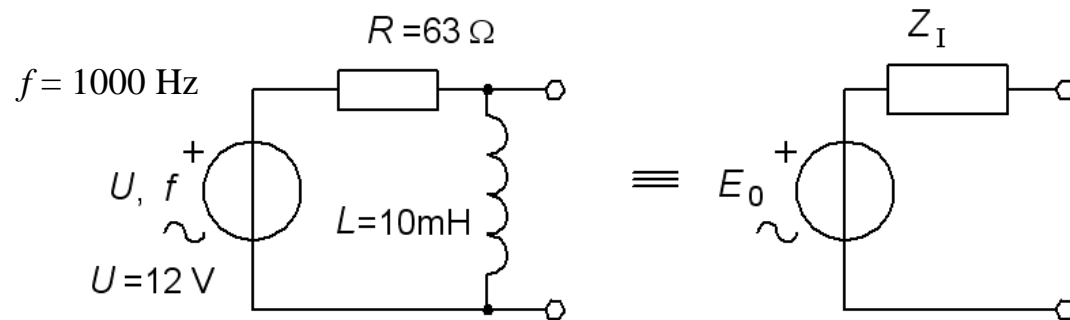


$E_0$  is calculated as the divided voltage. If  $U$  is the reference phase we get  $E_0$  8,47 V and gets the phase  $45^\circ$  to  $U$ .

If there are no other voltage sources or current sources in the circuit then we don't have to keep track on the phase, as  $E_0$  might as well become the network's new reference phase!

$$\underline{E}_0 = U \frac{j\omega L}{R + j\omega L} = 12 \frac{j2\pi 1000 \cdot 0,01}{63 + j2\pi 1000 \cdot 0,01} = 6 + 6j \quad E_0 = \sqrt{6^2 + 6^2} = 8,48 \text{ V}$$

# Example. Complex equivalent, $Z_I$

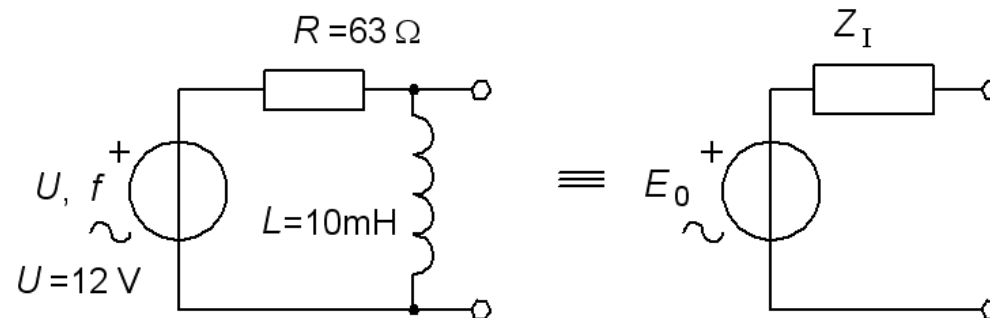


$Z_I$  is the impedance we see if we turn down  $U$ .

$$\underline{Z}_I = \frac{R \cdot j\omega L}{R + j\omega L} = \frac{63 \cdot j2\pi 1000 \cdot 0,01}{63 + j2\pi 1000 \cdot 0,01} = 31,4 + 31,5j$$
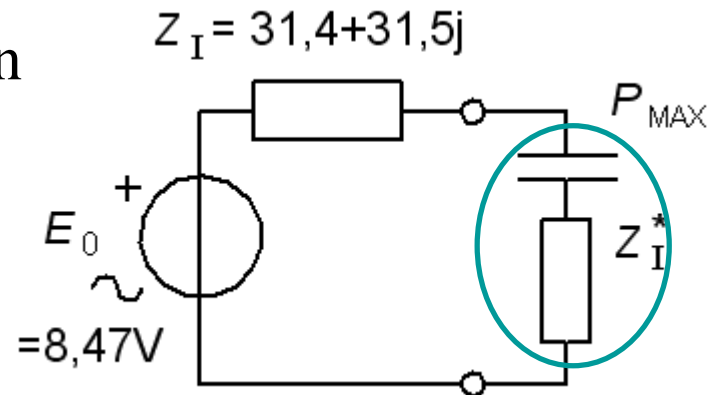
# Maximum power, $X$

The equivalent circuit is 8,57 V an emf with internal impedance  $Z_I = 31,4 + 31,5j$ .



- **Maximum power.**

At resonance inductance and capacitance cancel each other. This will maximize the power in the load. Therefore, the load this time should be capacitive ( $-31,5j$ ).


When the two reactances cancel each other the circuit becomes completely resistive. What load resistance will give the maximum power?


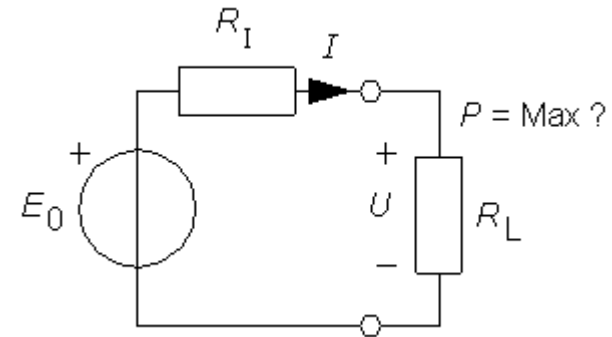
# Maximum power, $R_I$

$$P = R_L \cdot I^2 \quad I = \frac{E_0}{R_I + R_L} \Rightarrow P = E_0^2 \cdot \frac{R_L}{(R_I + R_L)^2}$$

When do  $P(R_L)$  have a maximum? (You get simpler calculations if you turn to the question to "where is  $1/P$  minimum").



$$\frac{1}{P} = \frac{1}{E_0^2} \cdot \left( \frac{R_L^2}{R_L} + \frac{R_I^2}{R_L} + 2 \cdot \frac{R_I \cdot R_L}{R_L} \right) = \frac{1}{E_0^2} \cdot \left( R_L + 2 \cdot R_I + \frac{R_I^2}{R_L} \right)$$


$$\frac{d}{dR_L} \left( \frac{1}{P} \right) = \frac{d}{dR_L} \left( \frac{1}{E_0^2} \cdot \left( R_L + 2 \cdot R_I + \frac{R_I^2}{R_L} \right) \right) = 1 - \frac{R_I^2}{R_L^2} = 0 \Rightarrow R_L = R_I$$

Maximum transferred power if you chose  $R_L = R_I$ .  
( $R_L = 31,4 \Omega$ ).
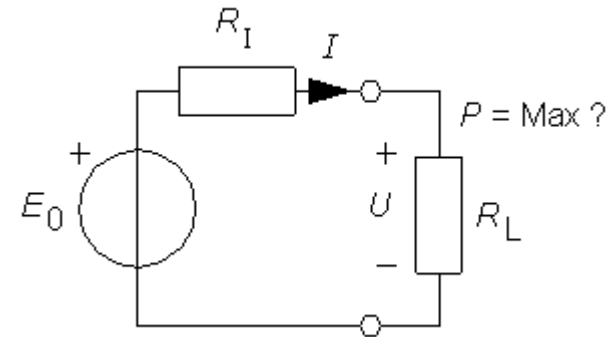
# The maximum power

How big is the power for  $R_L = R_I$   
(Maximum power)?

$$P = E_0^2 \cdot \frac{R_L}{(R_I + R_L)^2} \quad R_I = R_L \quad \Rightarrow \quad P_{MAX} = \frac{E_0^2}{4 \cdot R_I}$$




How big are the losses inside the equivalent circuit?

If  $R_L = R_I$  the power is divided equal between the internal resistance and the load. This means that the Thermal efficiency will be 50% (= bad).

Maximum power transfer, impedance matching, is only used when necessary, such as for radio transmitters.
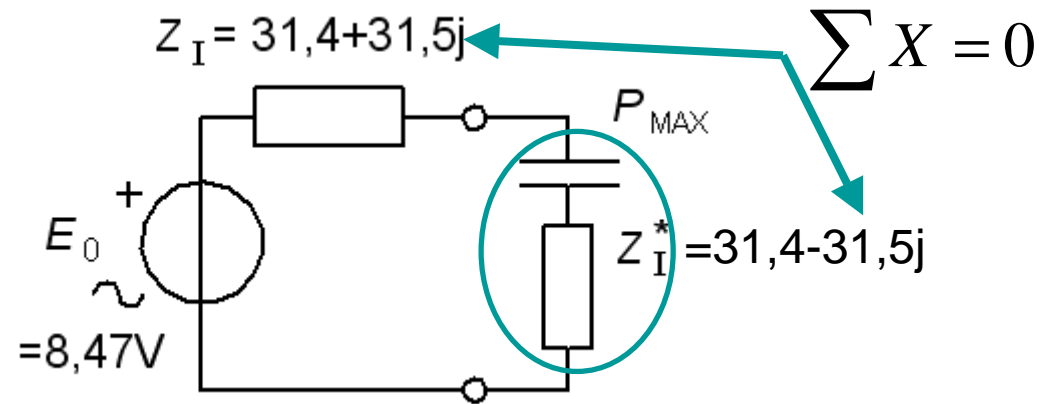
# Maximum power transfer

$$P_{\max} \Rightarrow$$
$$\underline{Z} = \underline{Z}_I^*$$



At power match with a load equal to the complex conjugate of the internal impedance, the effect:

$$P_{\max} = \frac{|\underline{E}_0|^2}{4 \cdot \text{Re}[\underline{Z}_I]}$$

William Sandqvist [william@kth.se](mailto:william@kth.se)