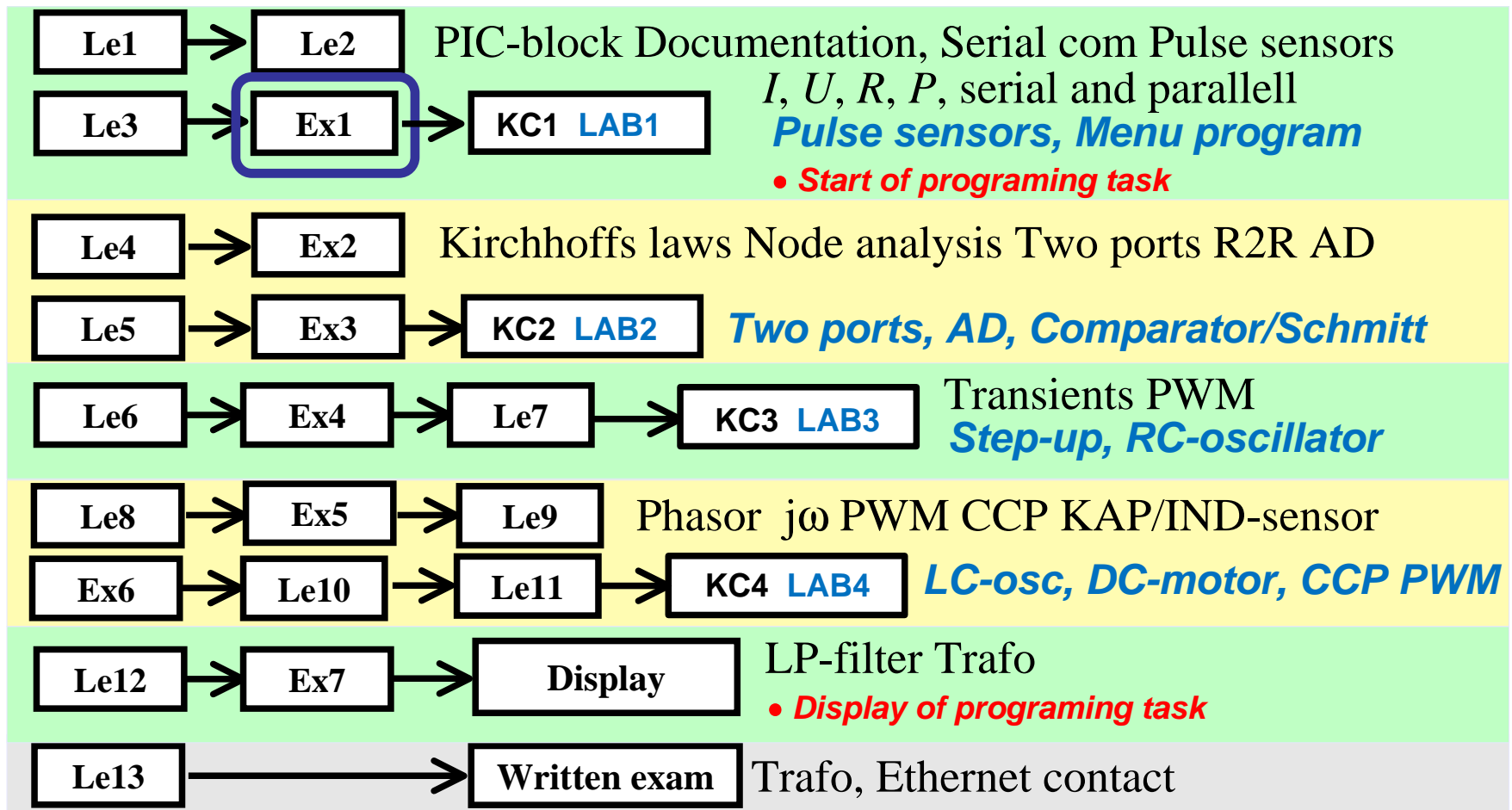


IE1206 Embedded Electronics







Closed circuit?

- **discussion.**

Current can only flow through a circuit on condition there is a closed circuit.


Describe in words the action of circuits a) ... d) when when you operate the two switches.

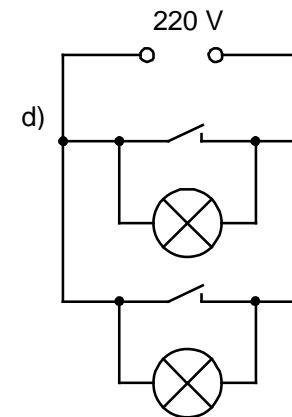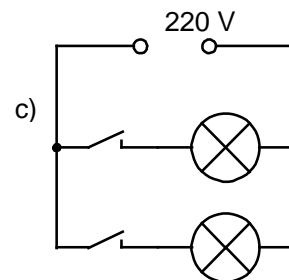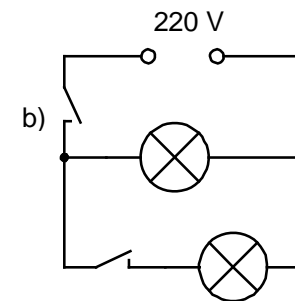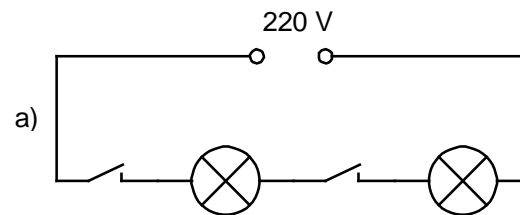(All the circuits are perhaps not as useful ...)




William Sandqvist william@kth.se

Series resistors

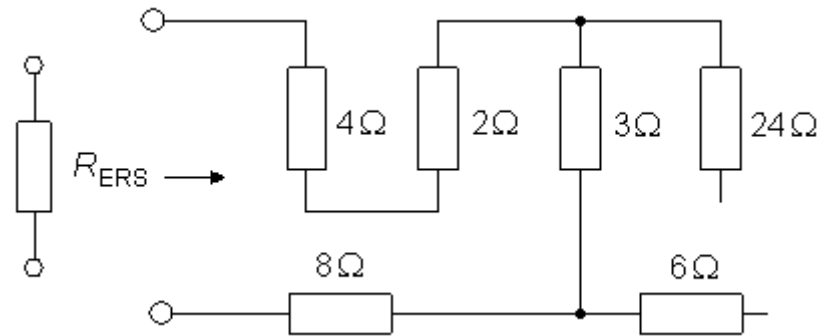


Series resistors

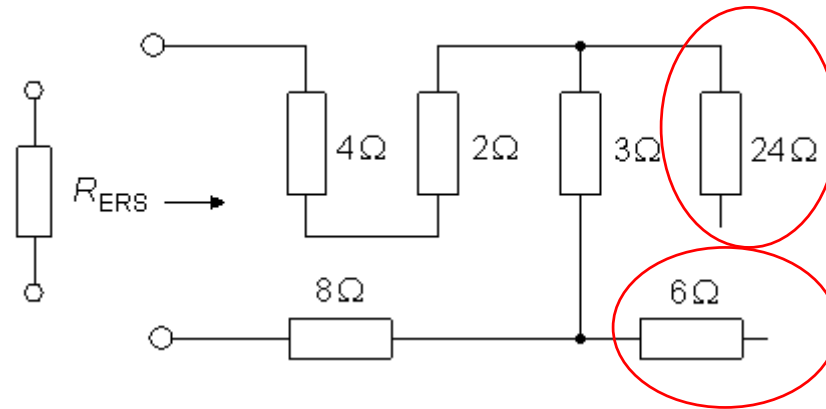

no current =
not included
in circuit!

Series resistors

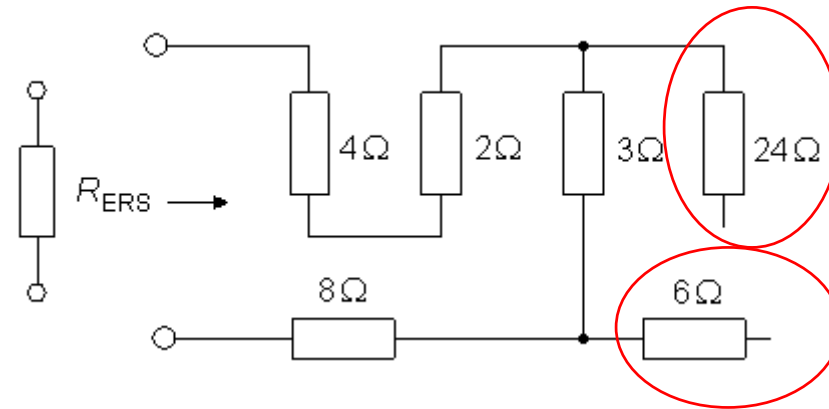


no current =
not included
in circuit!

$$R_{ERS} = 4 + 2 + 3 + 8 = 17$$

William Sandqvist william@kth.se

Two resistors in Parallel

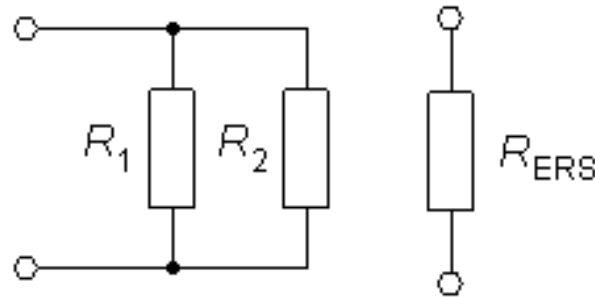

$$\frac{1}{R_{ERS}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_2}{R_2} \cdot \frac{1}{R_1} + \frac{R_1}{R_1} \cdot \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 \cdot R_2}$$

$$R_{ERS} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$


Equivalent resistance (1.2)

$$R_1 = 1 \Omega$$

$$R_2 = 21 \Omega$$

$$R_3 = 42 \Omega$$

$$R_4 = 30 \Omega$$

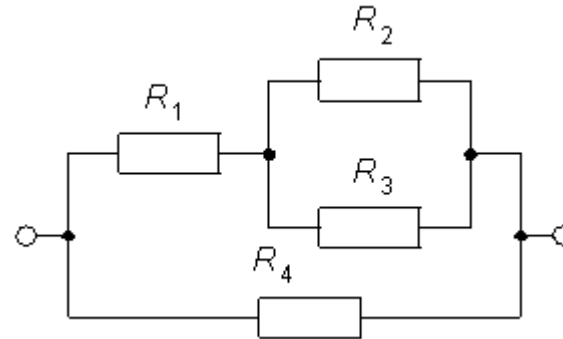


$$R_{ERS} = 30 // (1 + 21 // 42)$$

$$21 // 42 = \frac{21 \cdot 42}{21 + 42} = 14 \Rightarrow (1 + 21 // 42) = 15$$

$$30 // 15 = \frac{30 \cdot 15}{30 + 15} = 10 \Rightarrow R_{ERS} = 10 \Omega$$

William Sandqvist william@kth.se

N same value in parallel

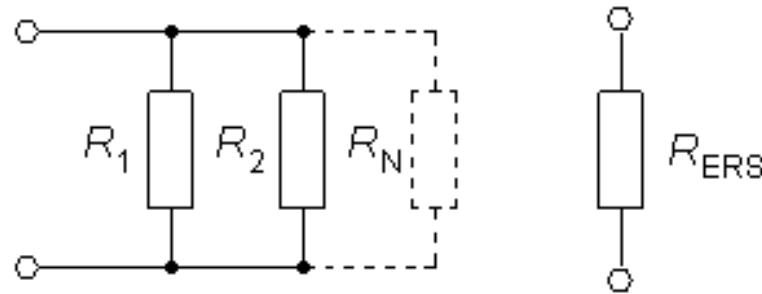


$$R_1 = R_2 = \dots = R_N = R$$


$$\frac{1}{R_{ERS}} = \frac{1}{R} + \frac{1}{R} + \dots = \frac{N}{R}$$

$$R_{ERS}(N) = \frac{R}{N}$$

OK to move ...

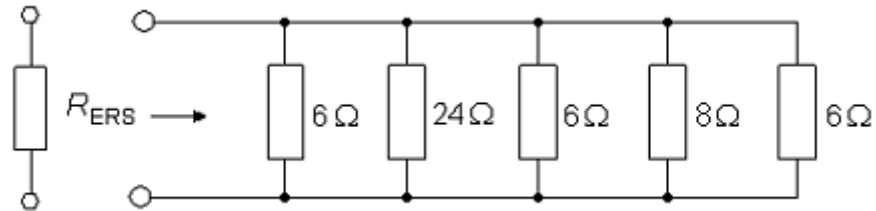

Redrawn:

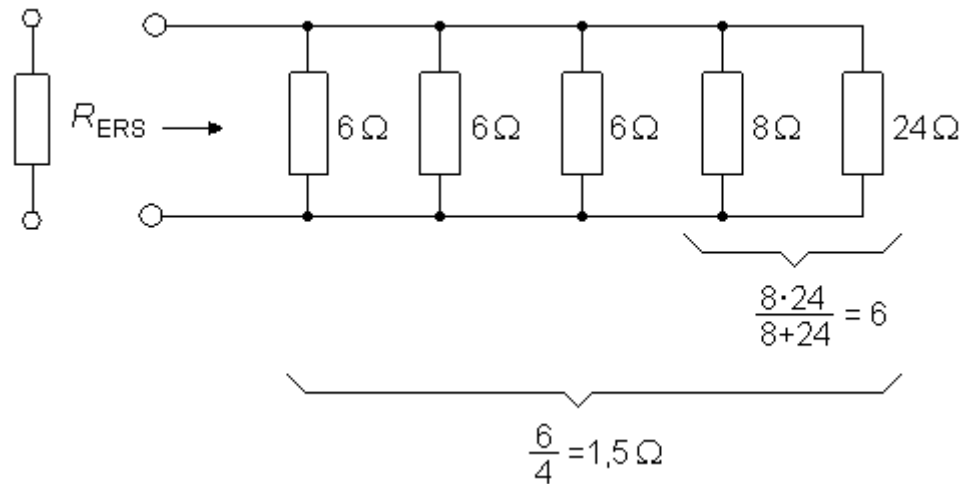

William Sandqvist william@kth.se

Equivalent resistance (1.6)


$$R_{TOT} = 2 + (12 // 12) // (24 // 24)$$

// means parallel connection


$$12 // 12 = 6 \quad 24 // 24 = 12$$

$$(12 // 12) // (24 // 24) = \frac{6 \cdot 12}{6 + 12} = 4$$

$$R_{TOT} = 2 + 4 = 6 \Omega$$

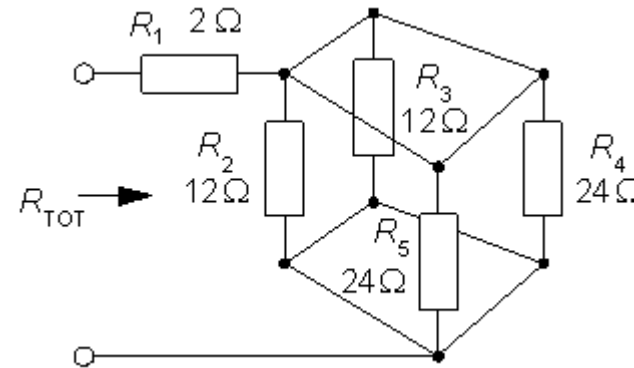


Equivalent resistance (1.1)

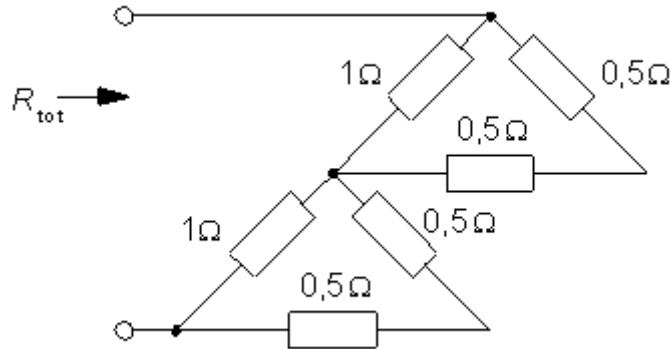

$$R_{TOT} = 1 // (0,5 + 0,5) + 1 // (0,5 + 0,5) = 1 // 1 + 1 // 1 = 0,5 + 0,5 = 1$$

William Sandqvist william@kth.se

Equivalent resistance (1.8)

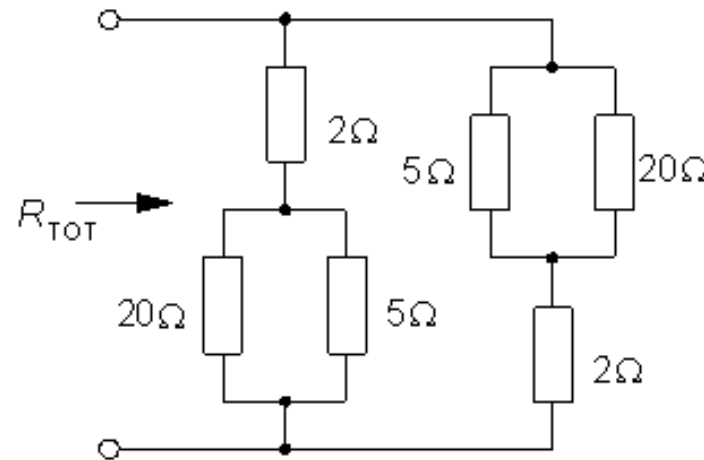



$$R_{TOT} = (2+20//5)//(20//5+2)$$

$$(2 + 20 // 5) = 2 + \frac{20 \cdot 5}{20 + 5} = 2 + 4 = 6 \quad 6 // 6 = 3$$

$$R_{TOT} = 3 \Omega$$


William Sandqvist william@kth.se

Potentiometer

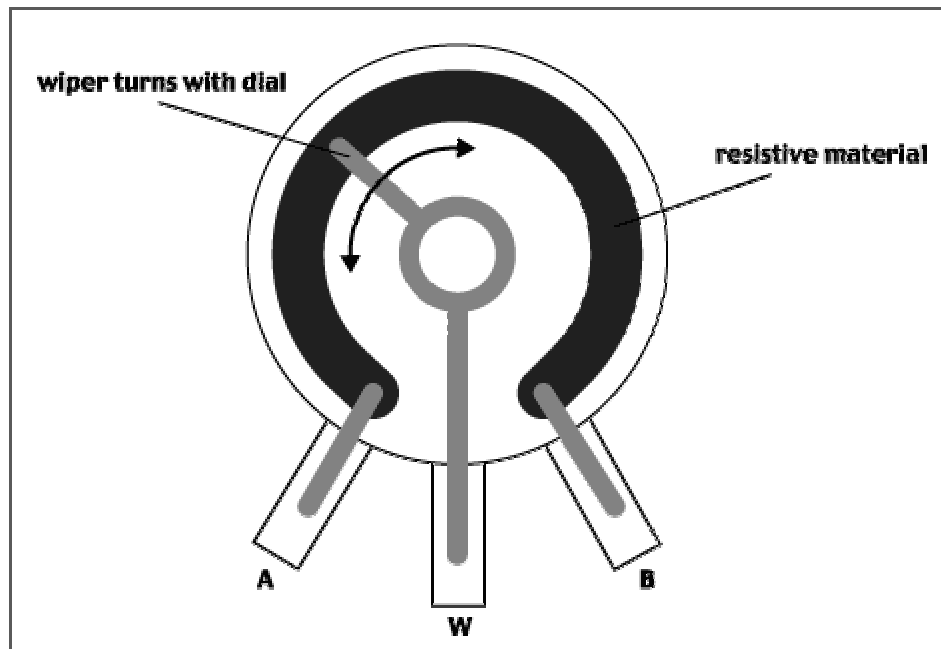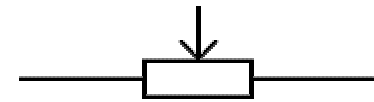


Appearance at our labs.

Equivalent resistance (1.10)

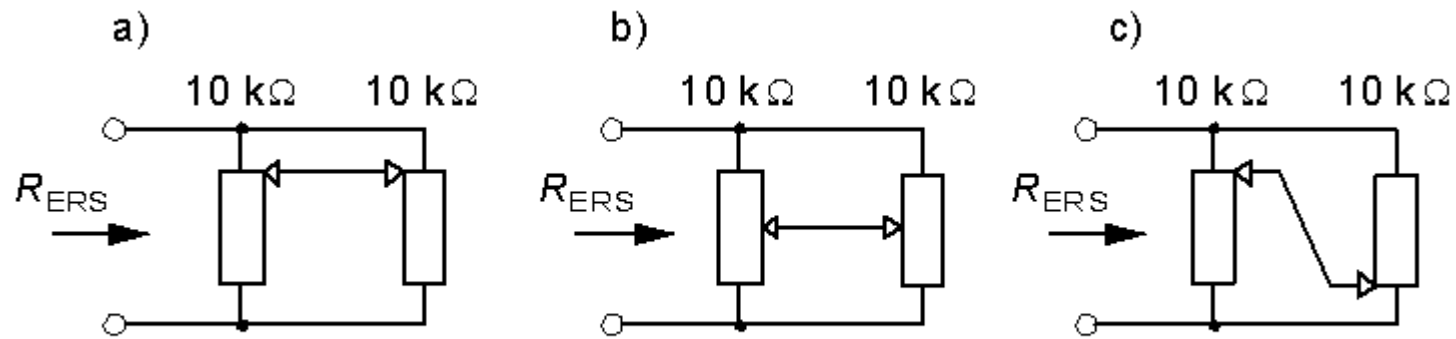


Equivalent resistance (1.10)

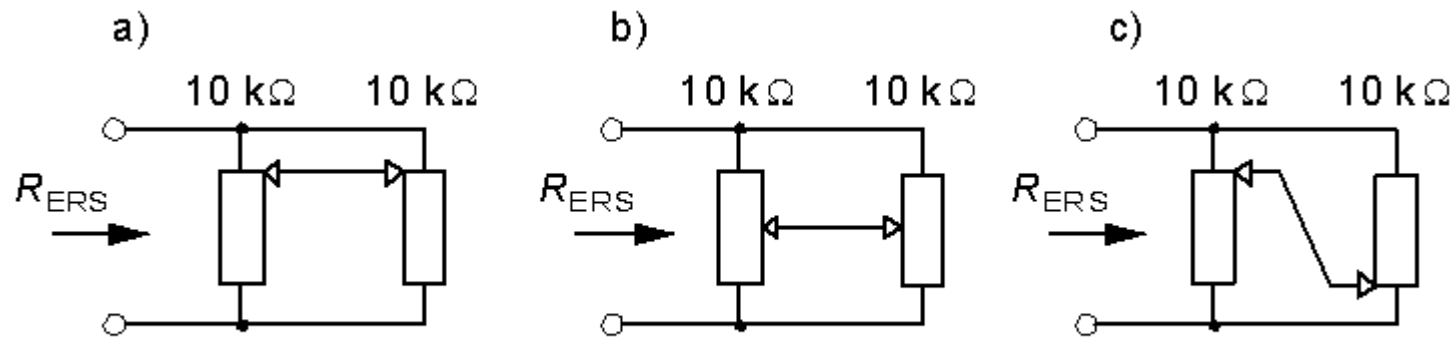

a) $R_{ERS} = 10/2 = 5 \text{ k}\Omega$




Equivalent resistance (1.10)

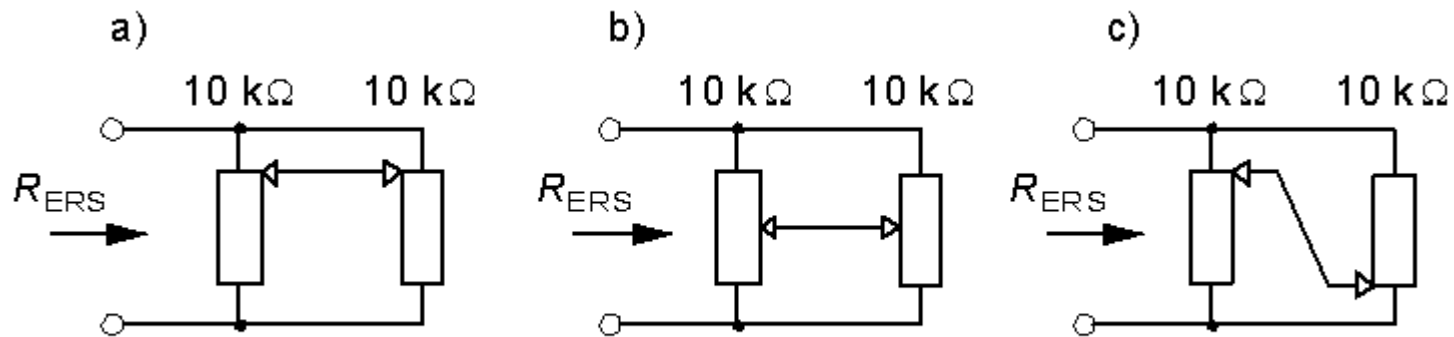


a) $R_{ERS} = 10/2 = 5 \text{ k}\Omega$

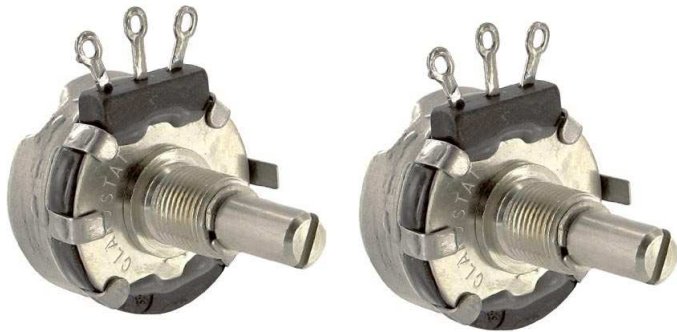b) $R_{ERS} = 5/2 + 5/2 = 5 \text{ k}\Omega$




Equivalent resistance (1.10)

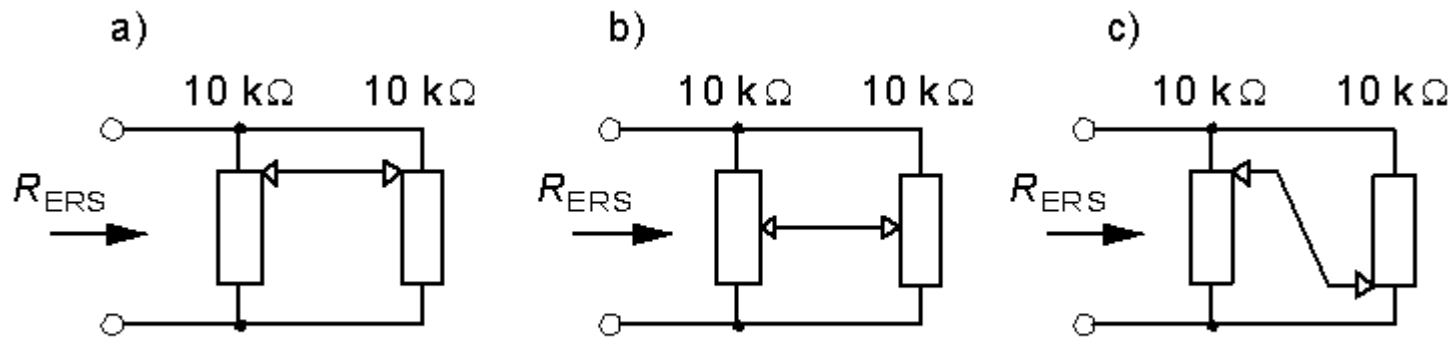

a) $R_{ERS} = 10/2 = 5 \text{ k}\Omega$


b) $R_{ERS} = 5/2 + 5/2 = 5 \text{ k}\Omega$

c) $R_{ERS} = 0 \Omega !$

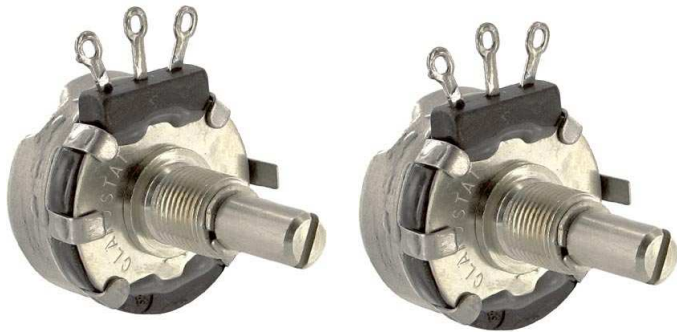


William Sandqvist william@kth.se

Voltage divider

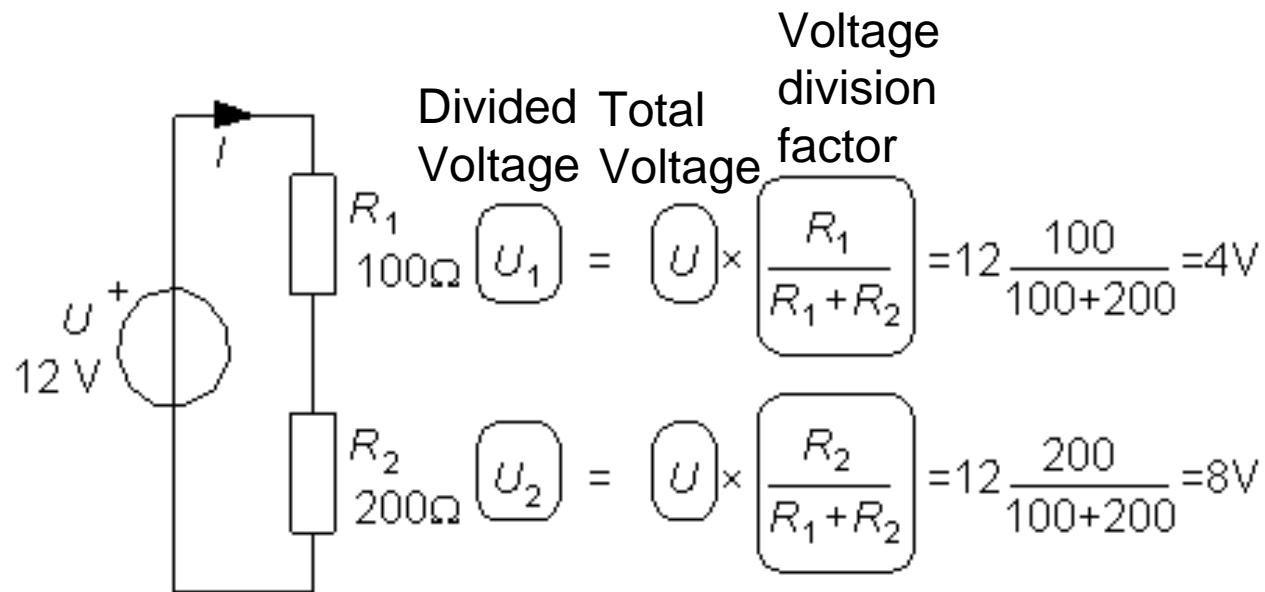

According to the voltage divider formula you get a divided voltage, for example U_1 across the resistor R_1 , by multiplying the total voltage U with a voltage division factor. This voltage division factor is the resistance R_1 divided by the sum of all the resistors that are in the series connection.

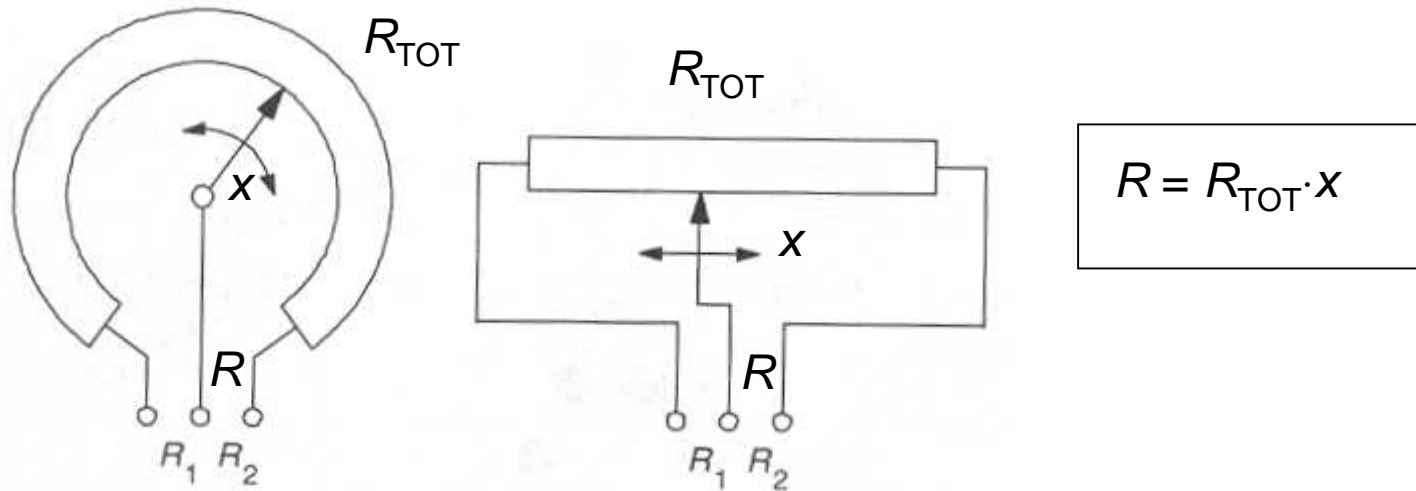
Resistive sensors, rotate and slide resistances



x relative movement/rotation $0 < x < 1$




Potentiometer with load (1.11)

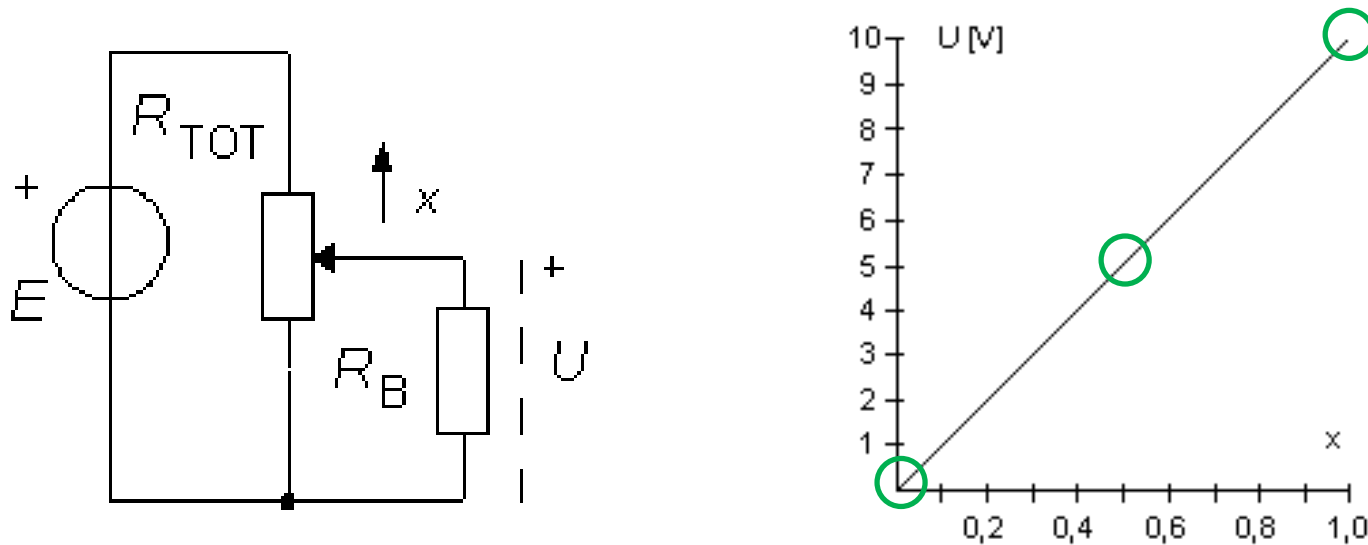

Without R_B

$$U = E \cdot x \quad \{0 \dots x \dots 1\}$$

Potentiometer with load (1.11)

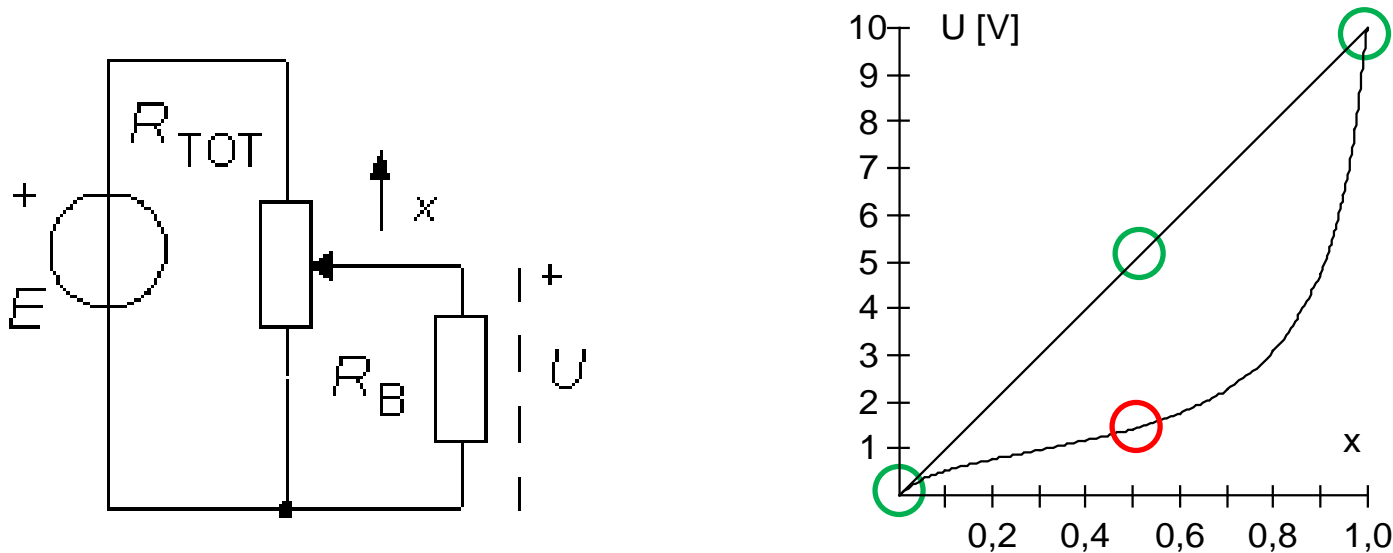


At $x = 0$ and $x = 1$ then $U = 0$ and $U = 5V$.

At $x = 0,5$ the load R_B draws current from the voltage divider and this "reduce" U .

Potentiometer with load ?

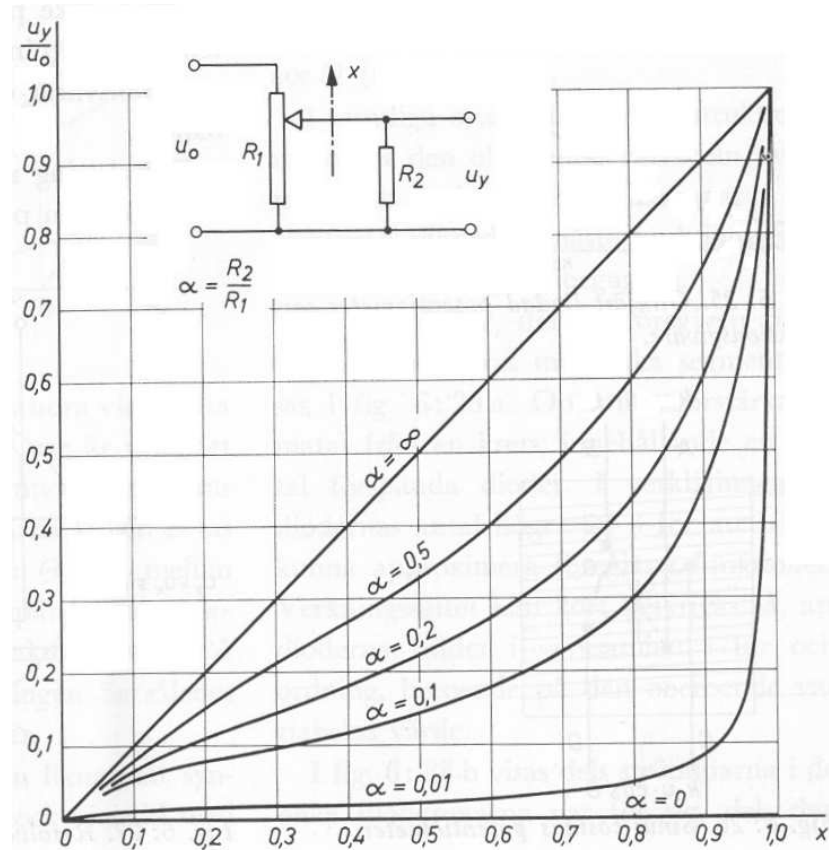
Would you happen to wish for any of the non-linear relationships that exists in the figure, it costs apparently just an extra resistor R_2 !



William Sandqvist william@kth.se


Serial circuit (3.1)

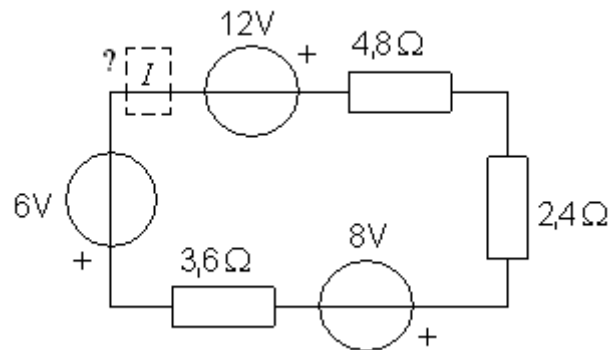Determine the current I , its magnitude and direction.



$$8 + 6 - 12 = 2 \quad 3,6 + 2,4 + 4,8 = 10,8$$


$$I = \frac{2}{10,8} = 0,19 \text{ A}$$

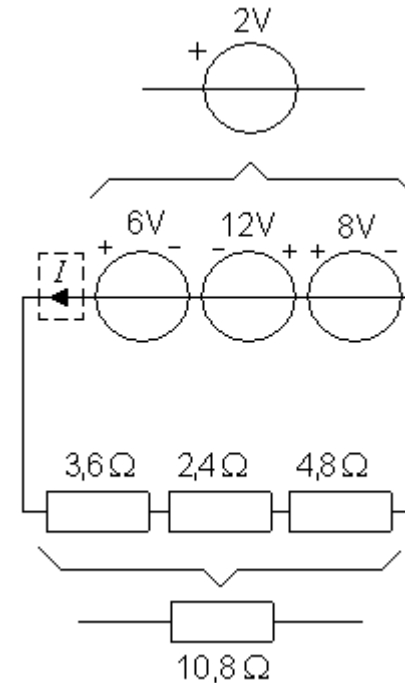

William Sandqvist william@kth.se

Serial – parallel circuits (3.4)

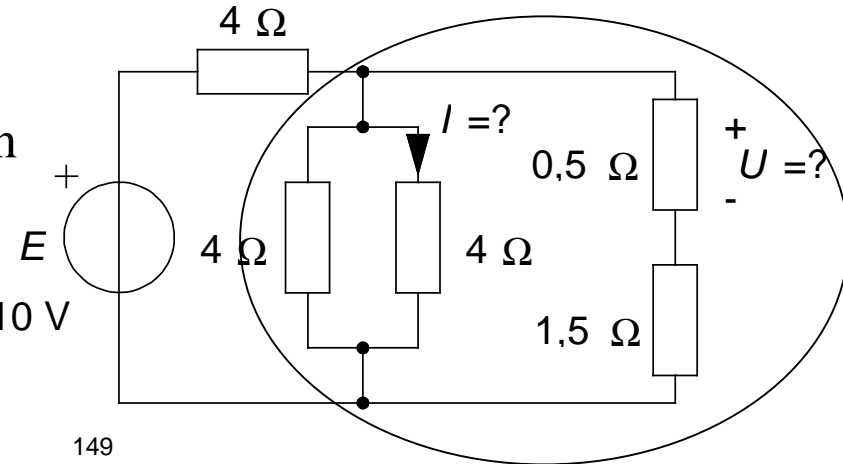Calculate current $I = ?$ And voltage $U = ?$ for the serial-parallel circuit in the figure.



Calculate the equivalent resistance: 10 V

$$R_{ERS} = 2 // (4 // 4) = 2 // 2 = 1 \Omega$$

Calculate voltage over the equivalent resistor U_{RERS}

$$U_{RERS} = 10 \frac{1}{4+1} = 2$$

$$\text{Current } I = U_{RERS} / 4 = 2 / 4 = 0,5 \text{ A}$$


$$\text{Voltage } U = 2 \frac{0,5}{1,5+0,5} = 0,5 \text{ V}$$

William Sandqvist william@kth.se

Serial – parallel circuits (3.3)

Calculate current $I = ?$ And voltage $U = ?$ for the serial-parallel circuit in the figure.

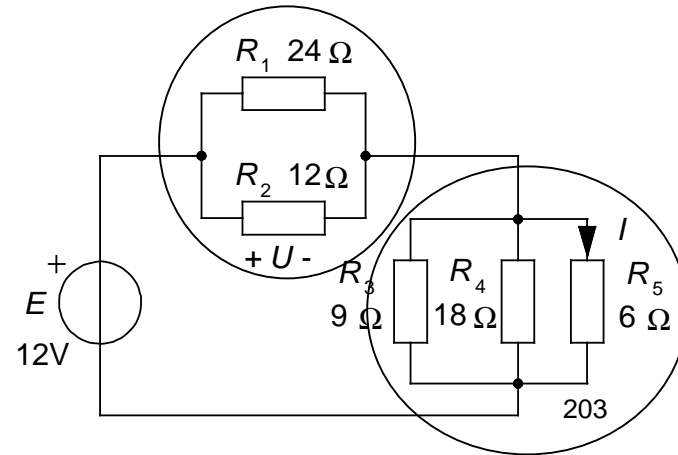We start by calculating two equivalent resistances:



$$R_{1//2} = \frac{24 \cdot 12}{24 + 12} = 8 \quad \frac{1}{R_{3//4//5}} = \frac{1}{9} + \frac{1}{18} + \frac{1}{6} = \frac{2+1+3}{18} = \frac{6}{18} \Rightarrow R_{3//4//5} = \frac{18}{6} = 3$$

Voltage divider:

$$U = 12 \frac{8}{8+3} = 8,73 \Rightarrow U_{3//4//5} = E - U \Rightarrow I = \frac{U_{3//4//5}}{R_5} = \frac{12 - 8,73}{6} = 0,55 \text{ A}$$

William Sandqvist william@kth.se

Serial – parallel circuits (3.5)

Calculate current $I = ?$ And voltage $U = ?$ for the serial-parallel circuit in the figure.

We calculate an equivalent resistance:


$$R_{3//4,5} = \frac{6 \cdot (1+2)}{6+1+2} = 2$$

$U_{R1} = 36 \text{ V}$. $U_{R3} = U_{R3//4,5}$ can be calculated by voltage division:

$$U_{R3} = E \frac{R_{3//4,5}}{R_{3//4,5} + R_2} = 36 \frac{2}{2+4} = 12 \Rightarrow I = \frac{U_{R3}}{R_3} = \frac{12}{6} = 2 \text{ A}$$

U can be calculated by voltage division:
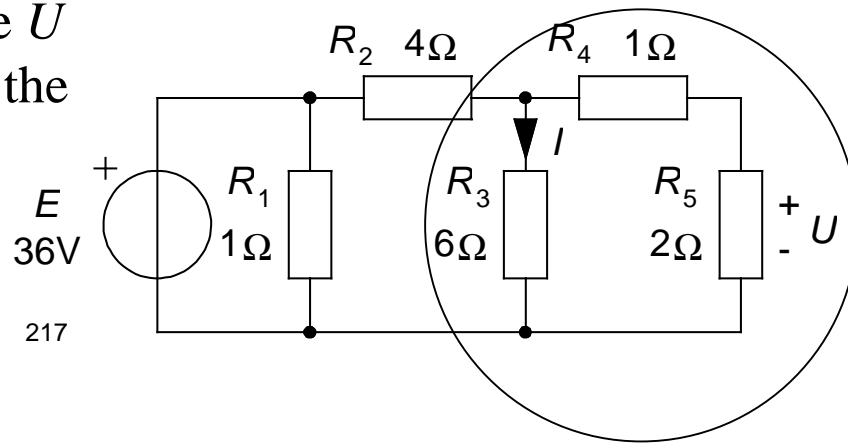
$$U = U_{R3//4,5} \frac{R_5}{R_4 + R_5} = 12 \frac{2}{1+2} = 8 \text{ V}$$



William Sandqvist william@kth.se