
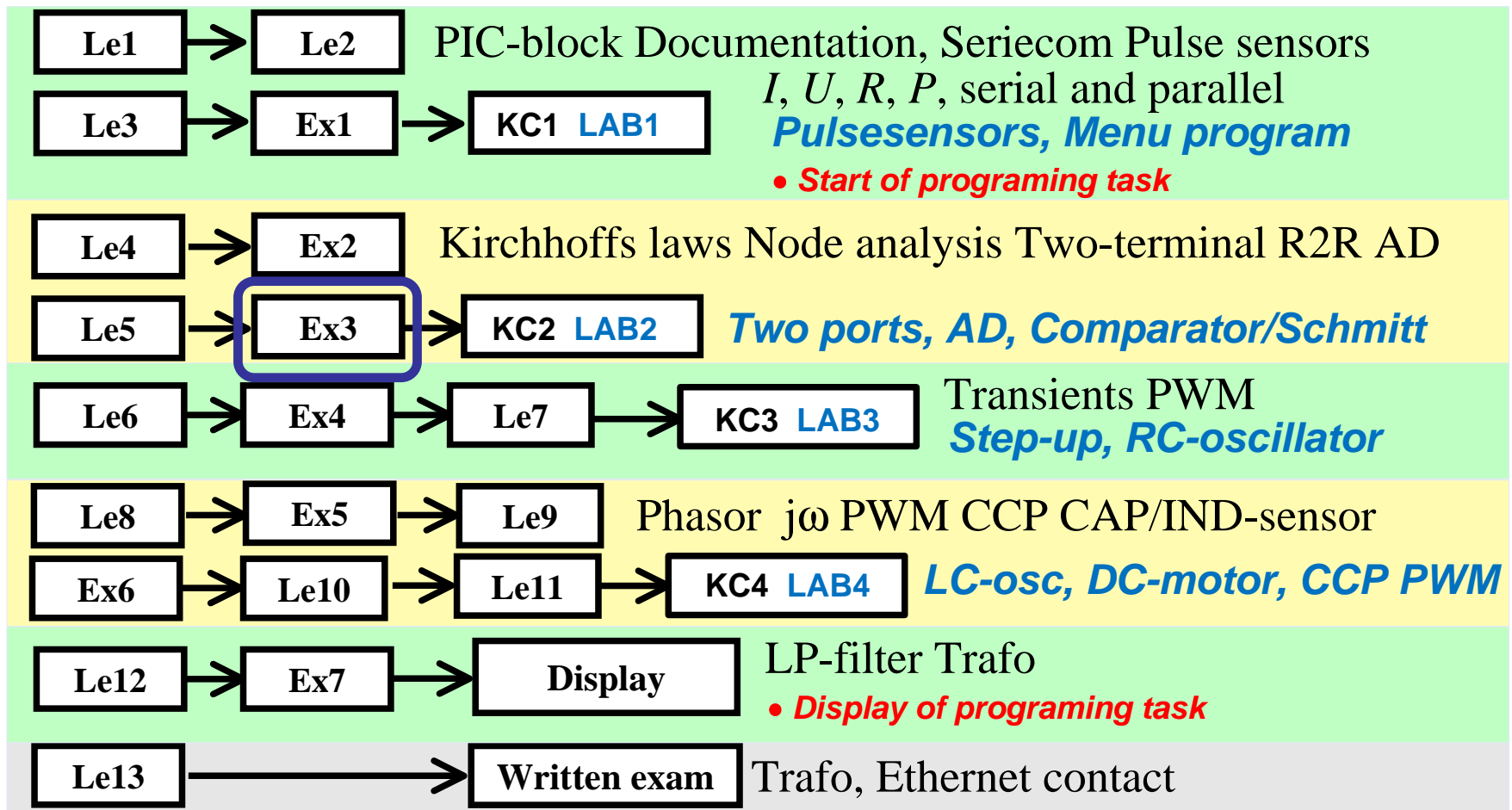


IE1206 Embedded Electronics

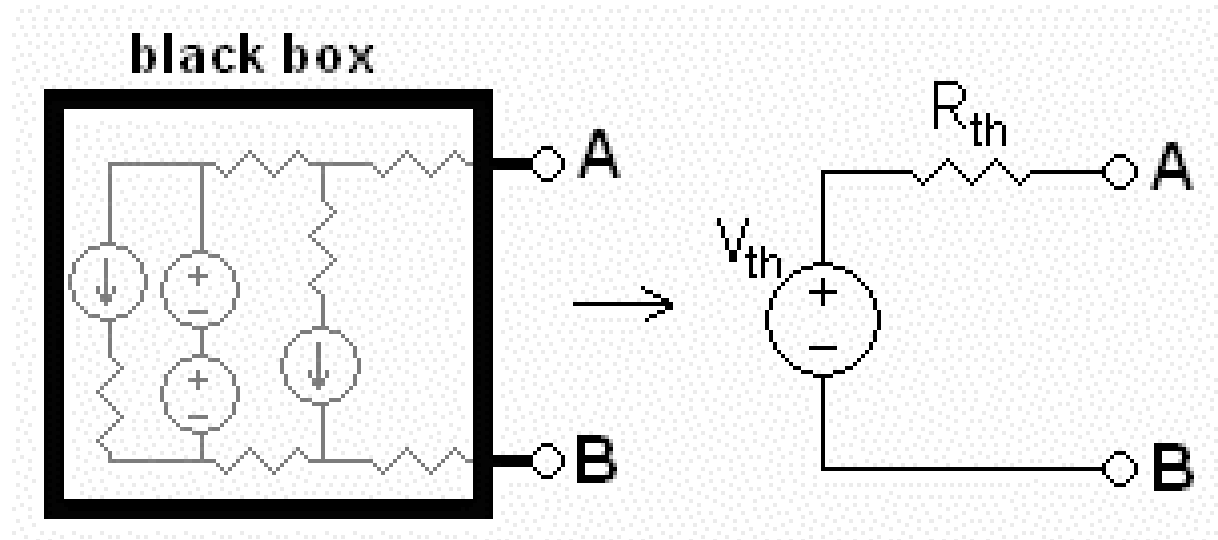


Two port circuits – Black box



? = !

The power supply

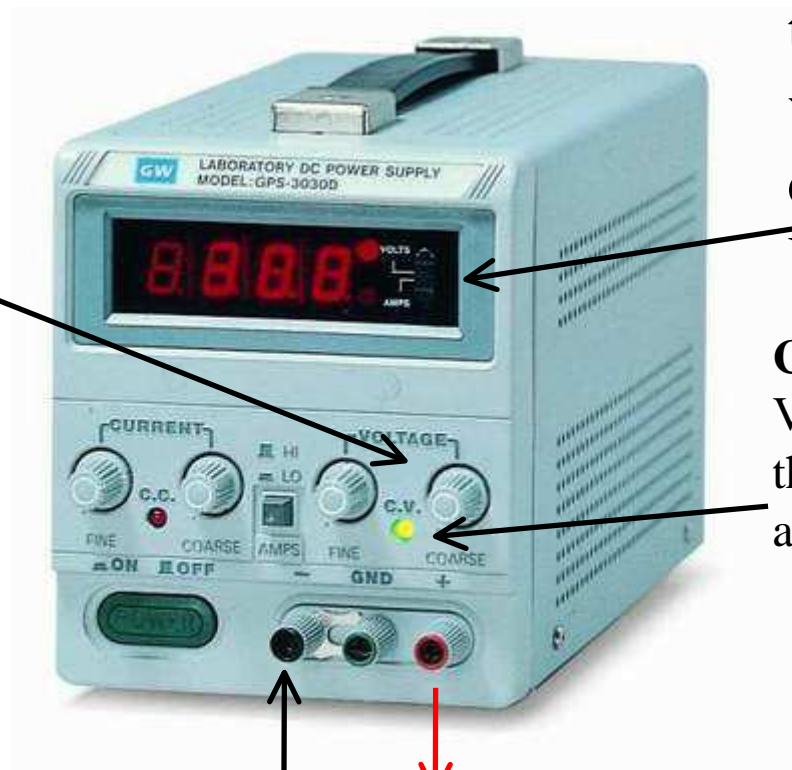VOLTAGE knob to set the constant voltage. Coarse and fine adjustments.



Buttons to select the display of voltage or current.

Voltage / Amps

C.V. Continuous Voltage. Led indicating that the unit operates as a voltage generator.



+ and - poles

(GND is to connect the metal casing to +/- to suppress interference).

The power supply

CURRENT knob to set the current limit. Coarse and fine adjustments.

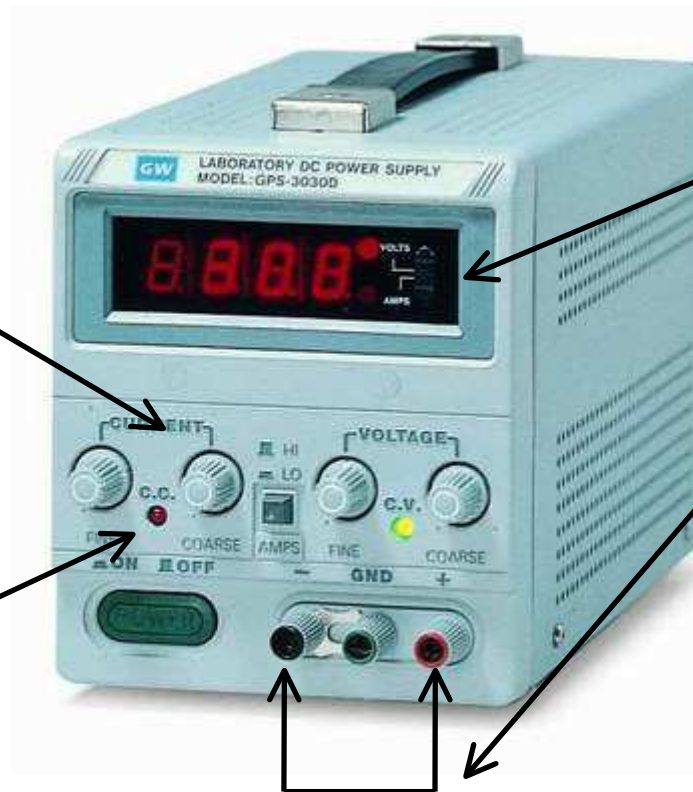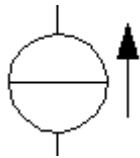C.C. Continuous Current. Led indicating that the unit operates as a current generator.





To set the current limit you show “Amps” and then short voltage poles.

The set current then becomes the maximum current that can occur.




Voltage and Current generator

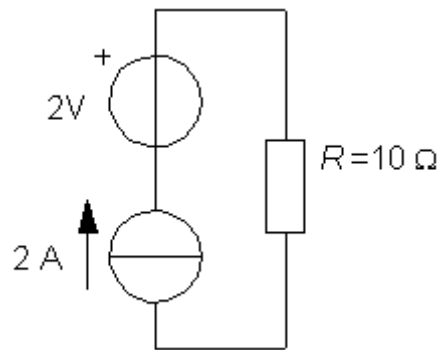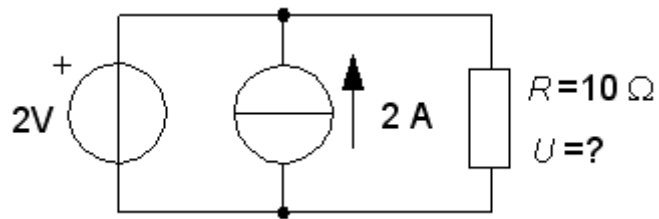(Ex. 8.1) What value will the U get in these idealized and usually unrealistic circuits?







Voltage and Current generator

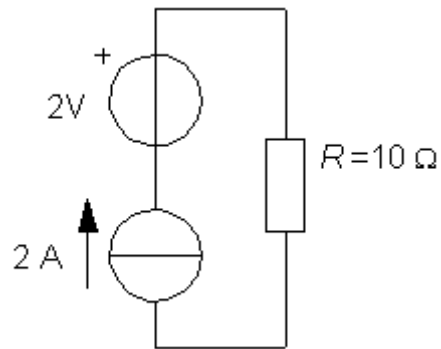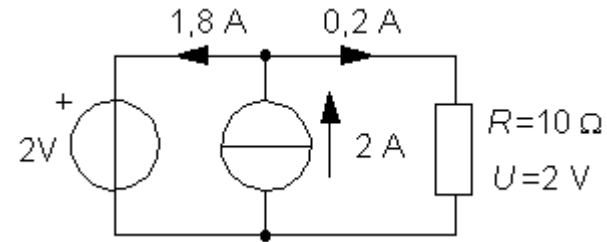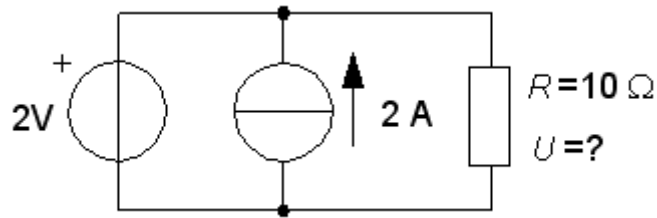(Ex. 8.1) What value will the U get in these idealized and usually unrealistic circuits?





Voltage and Current generator

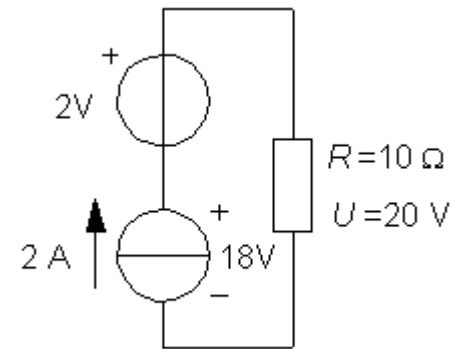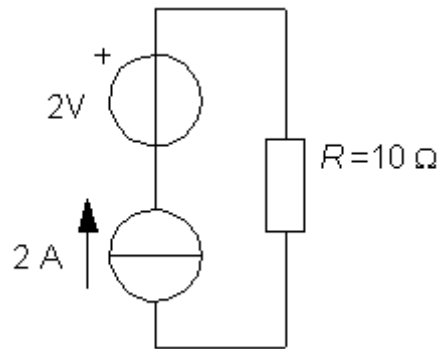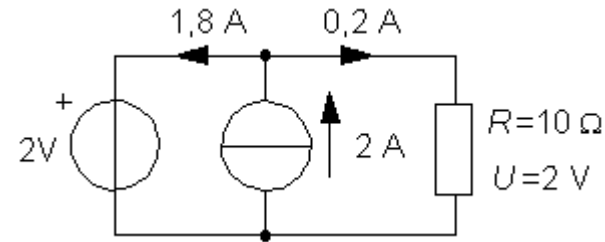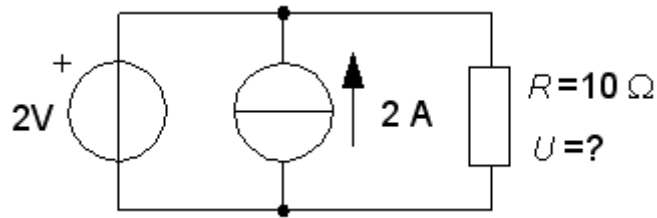(Ex. 8.1) What value will the U get in these idealized and usually unrealistic circuits?





William Sandqvist william@kth.se


Simplify ... (8.2)

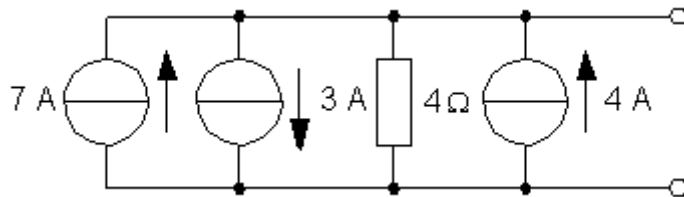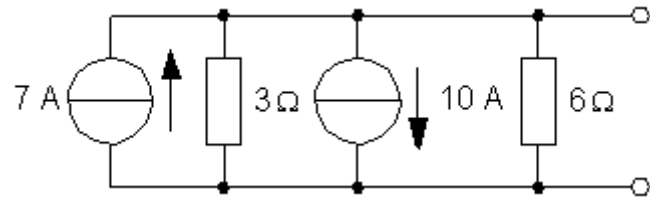

Simplify ... (8.2)


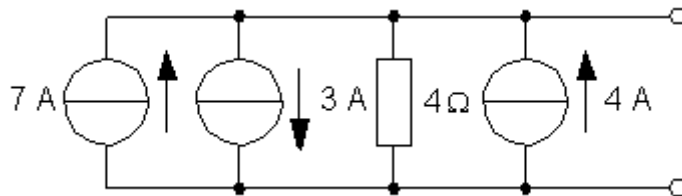
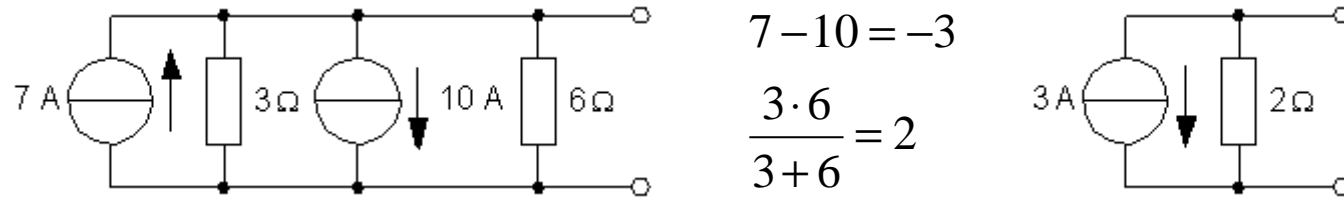


Simplify ... (8.2)

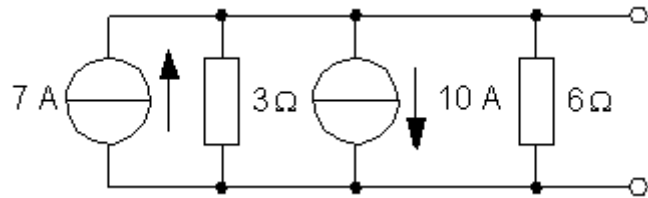

$$7 - 10 = -3$$


$$\frac{3 \cdot 6}{3 + 6} = 2$$

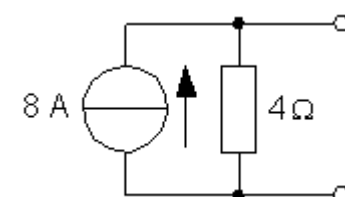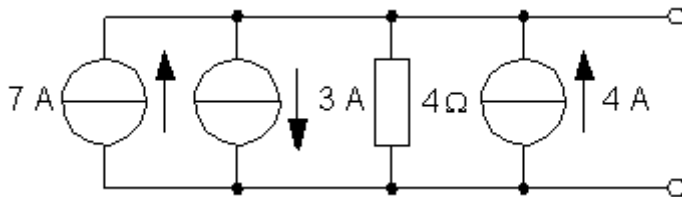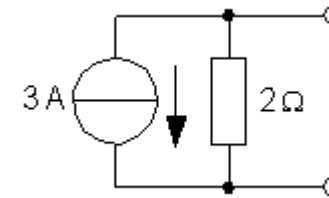

William Sandqvist william@kth.se


Equivalents step by step ...

(8.4) Electronics prefix [V] [k Ω] [mA]

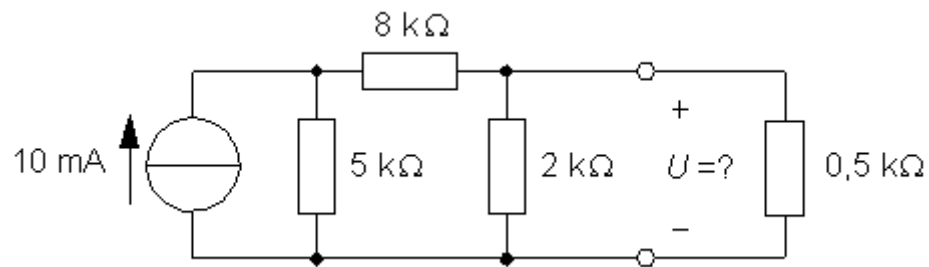


Equivalents step by step ...

(8.4) Electronics prefix [V] [kΩ] [mA]


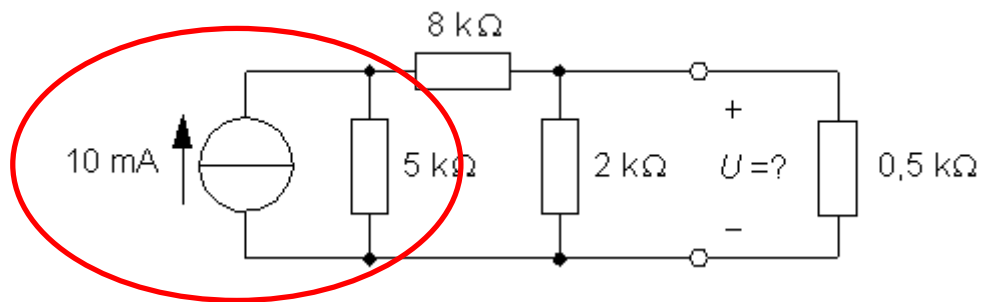


$$10 \cdot 5 = 50$$

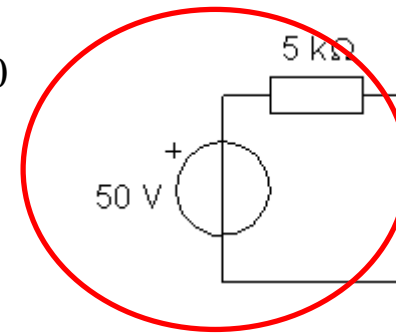


Equivalents step by step ...

(8.4) Electronics prefix [V] [kΩ] [mA]

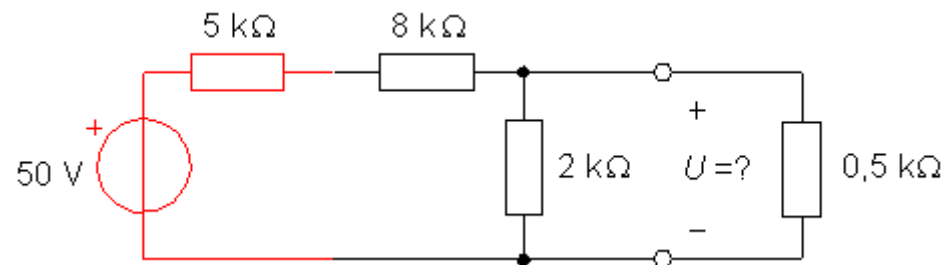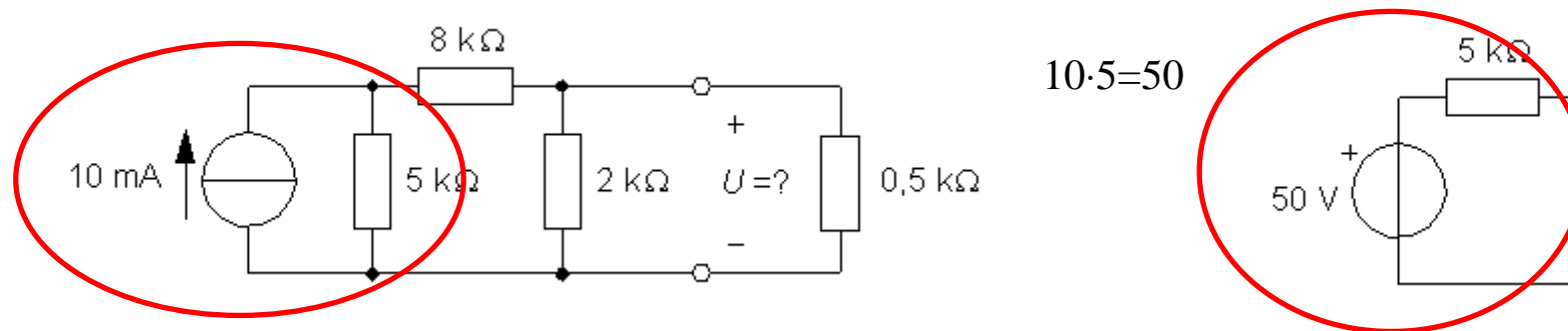


Equivalents step by step ...

(8.4) Electronics prefix [V] [kΩ] [mA]

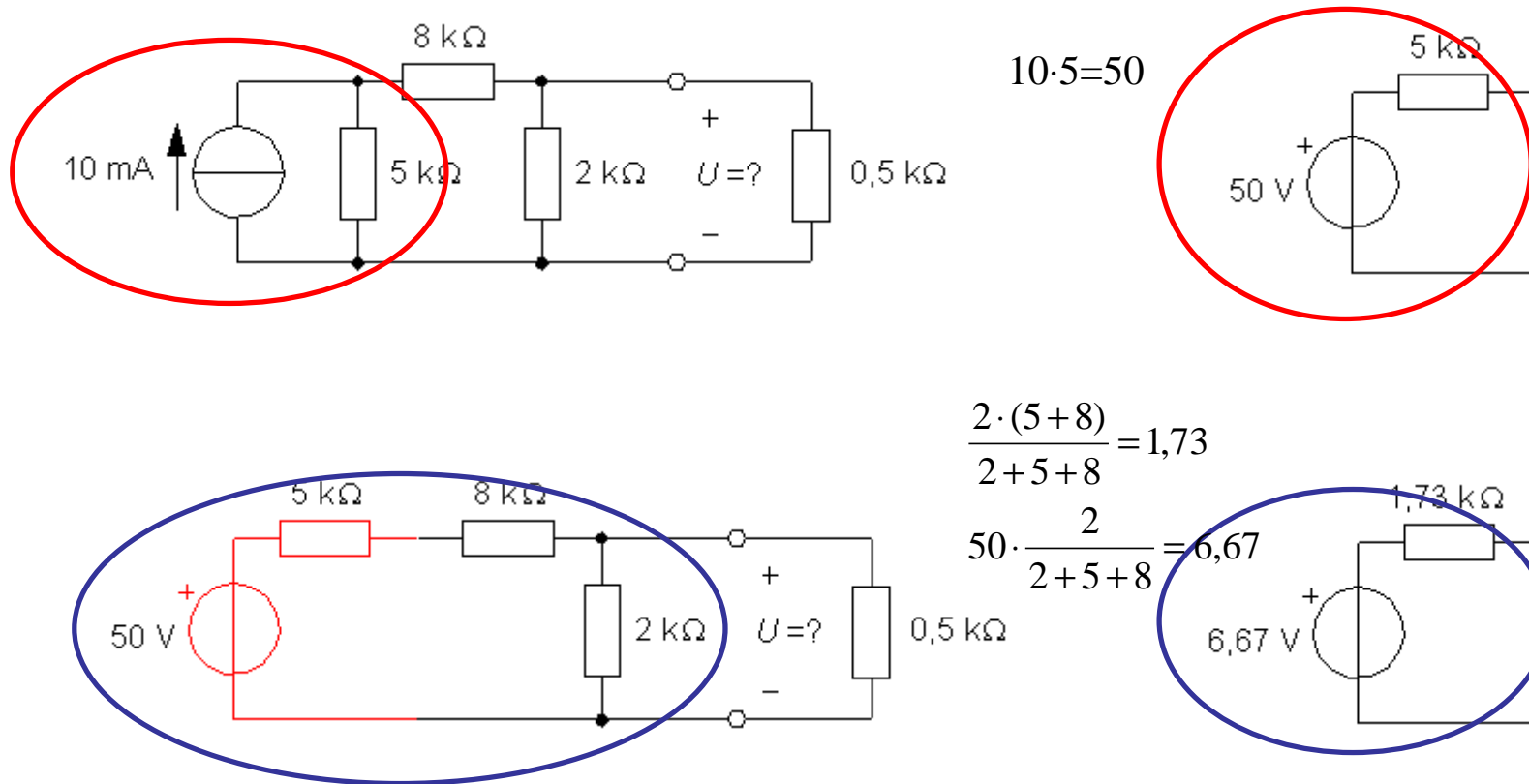

At last ...

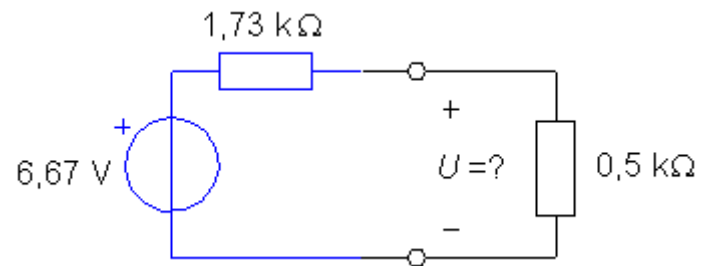


Voltage divider:

$$U = 6,67 \cdot \frac{0,5}{0,5 + 1,73} = 1,49 \text{ V}$$

William Sandqvist william@kth.se


(Wheatstone bridge equivalent)

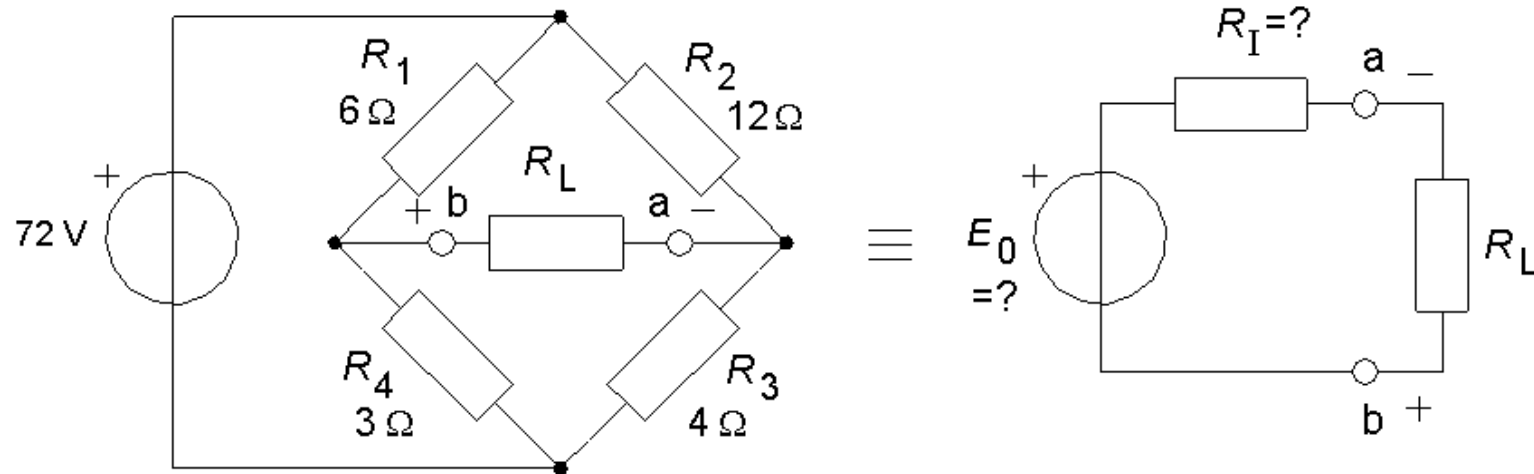

Determine the Wheatstone bridge Thevenin equivalent.


(Determine R_1)

Voltage turned
down to zero

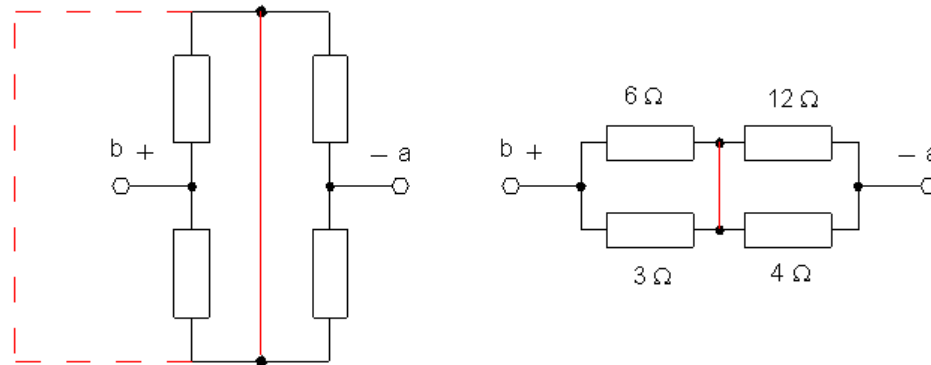

$$R_1 = \frac{6 \cdot 3}{6 + 3} + \frac{12 \cdot 4}{12 + 4} = 5 \Omega$$

(Determine E_0)

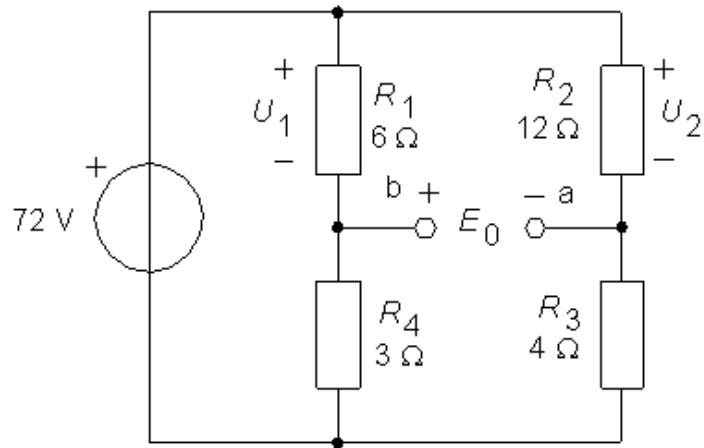


$$U_1 = 72 \cdot \frac{6}{6+3} = 48$$

$$U_2 = 72 \cdot \frac{12}{12+4} = 54$$

$$E_0 = 54 - 48 = 6 \text{ V}$$

(Determine $R_1 E_0$)

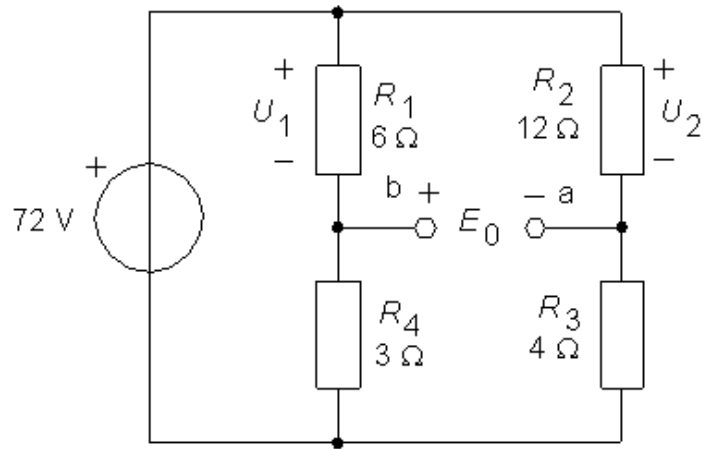


$$U_1 = 72 \cdot \frac{6}{6+3} = 48$$


$$U_2 = 72 \cdot \frac{12}{12+4} = 54$$

$$E_0 = 54 - 48 = 6 \text{ V}$$

Done!

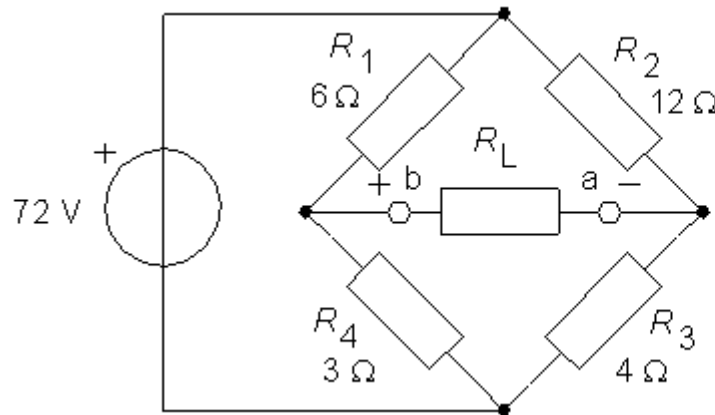


\equiv

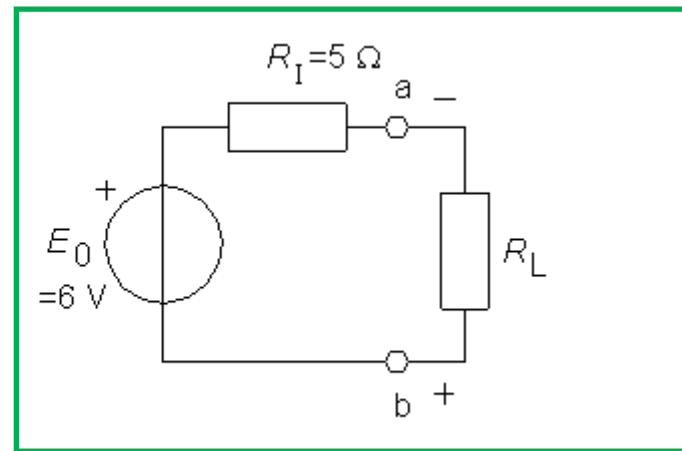


William Sandqvist william@kth.se


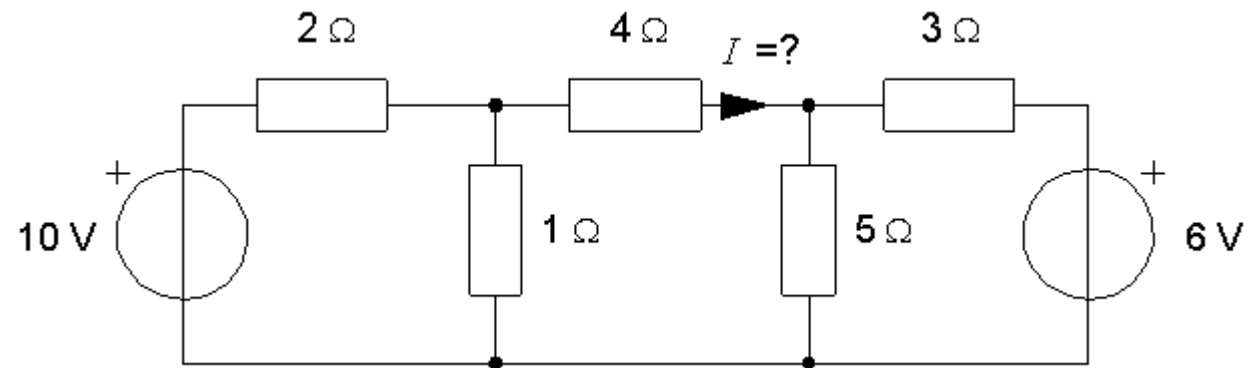
Equivalent circuits (instead of mesh analysis)!




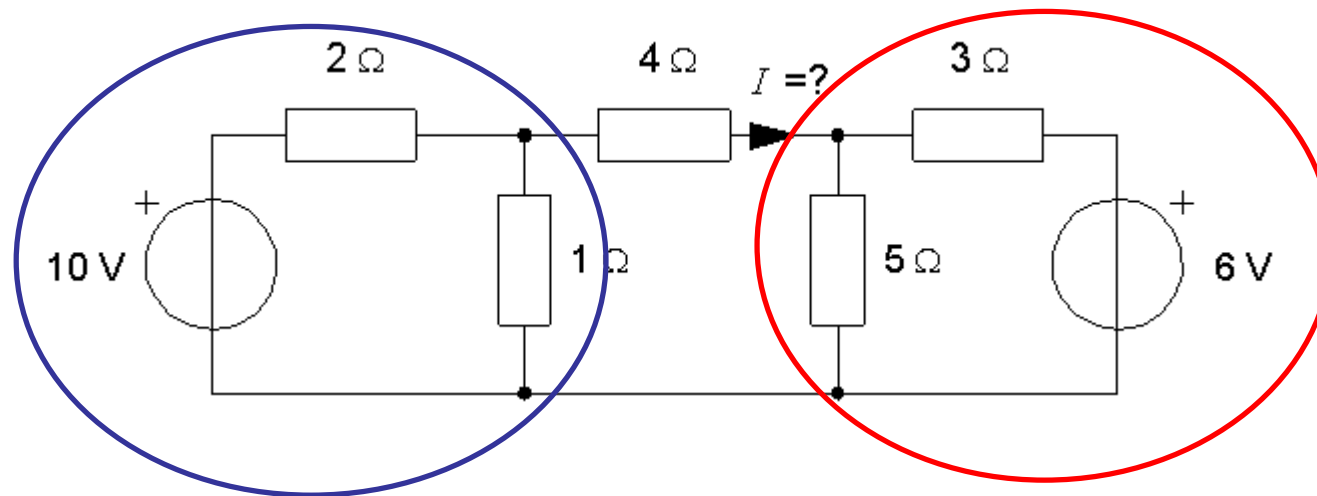
Equivalent circuits (instead of mesh analysis)!



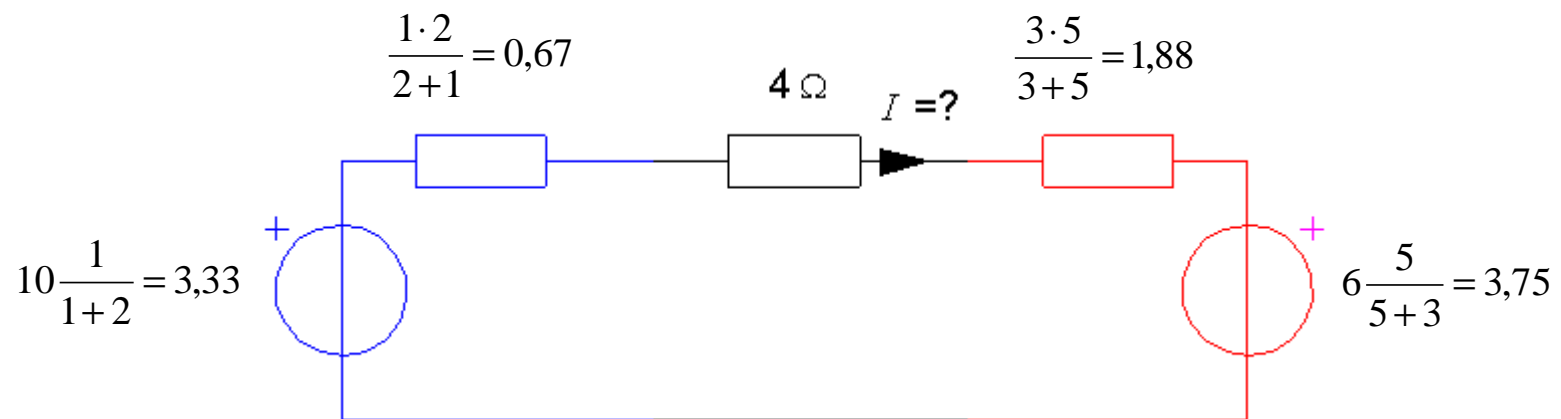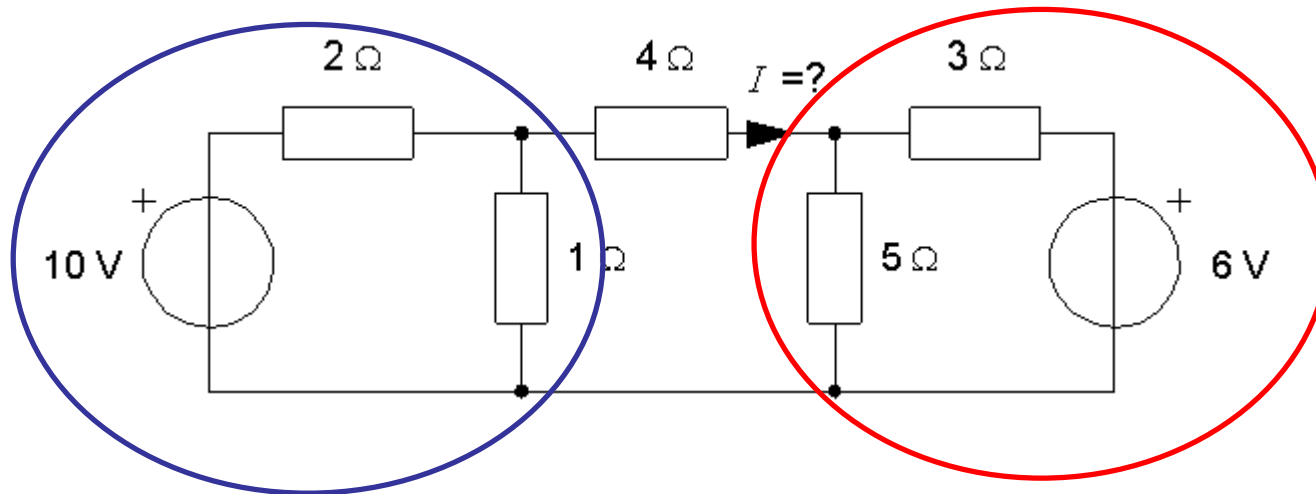Equivalent circuits (instead of mesh analysis)!



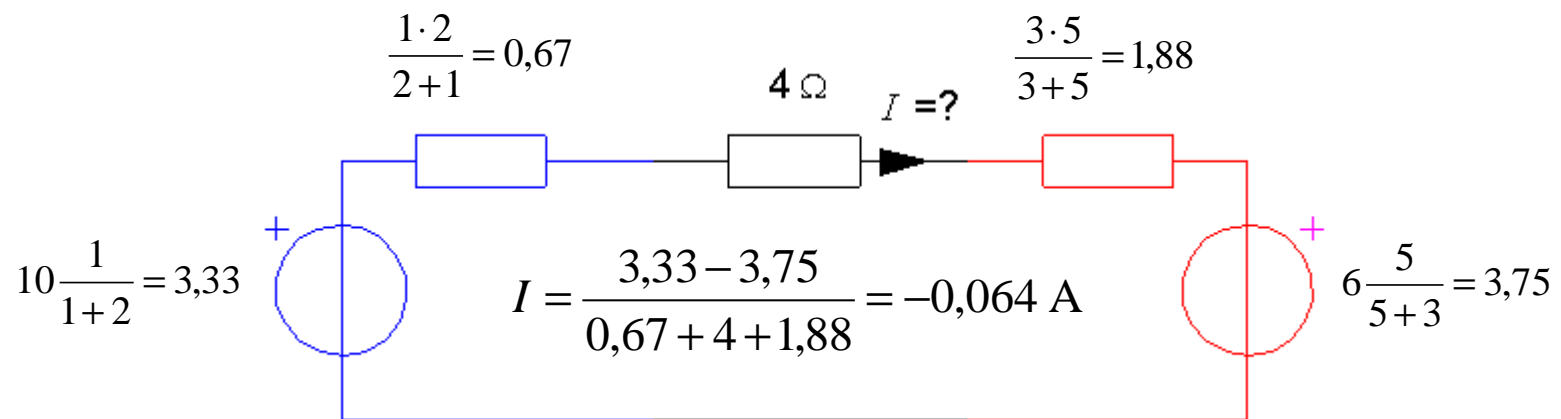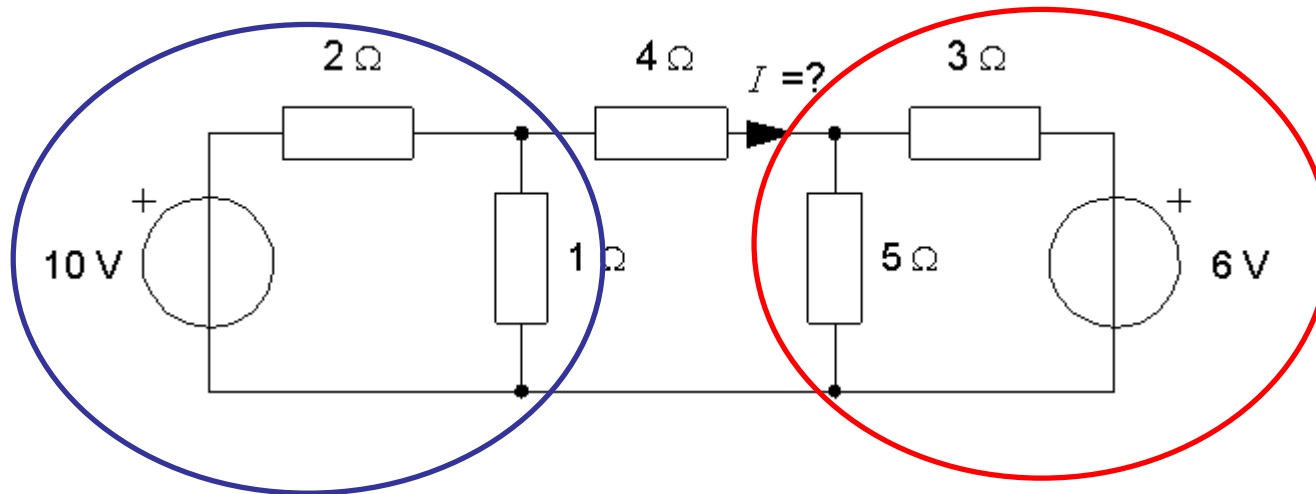Equivalent circuits (instead of mesh analysis)!



William Sandqvist william@kth.se

Ex. current generator at node analysis

(7.2)


$$-I_1 - I_2 + 1 = 0 \quad I_1 + I_2 = 1$$

$$I_2 = \frac{U}{R_2} = \frac{U}{12}$$

$$I_1 = \frac{U - E}{R_1} = \frac{U - 24}{6}$$

$$1 = \frac{U}{12} + \frac{U - 24}{6} = \frac{2 \cdot U - 48 + U}{12} \quad \Leftrightarrow \quad 12 = 3 \cdot U - 48$$

$$U = 20 \text{ V}$$

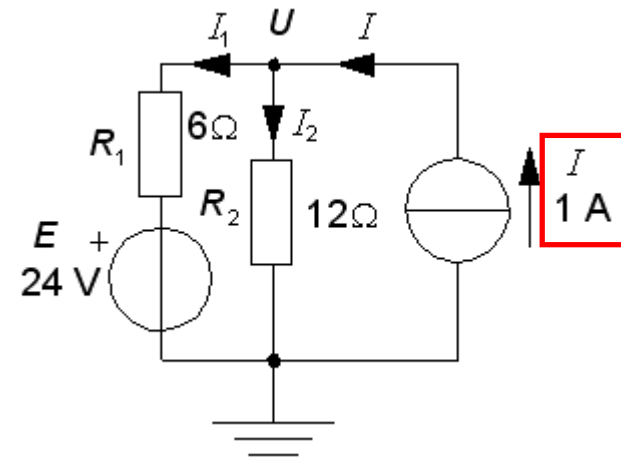


Node analysis – the currents

$$I_2 = \frac{20}{12} = 1,67$$


$$I_1 = \frac{20 - 24}{6} = -0,67$$
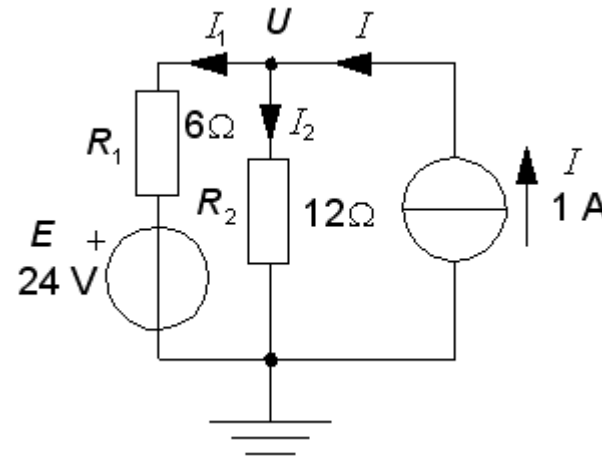
$$I_1 + I_2 = 1 \Rightarrow -0,67 + 1,67 = 1$$




William Sandqvist william@kth.se

Example (8.9)

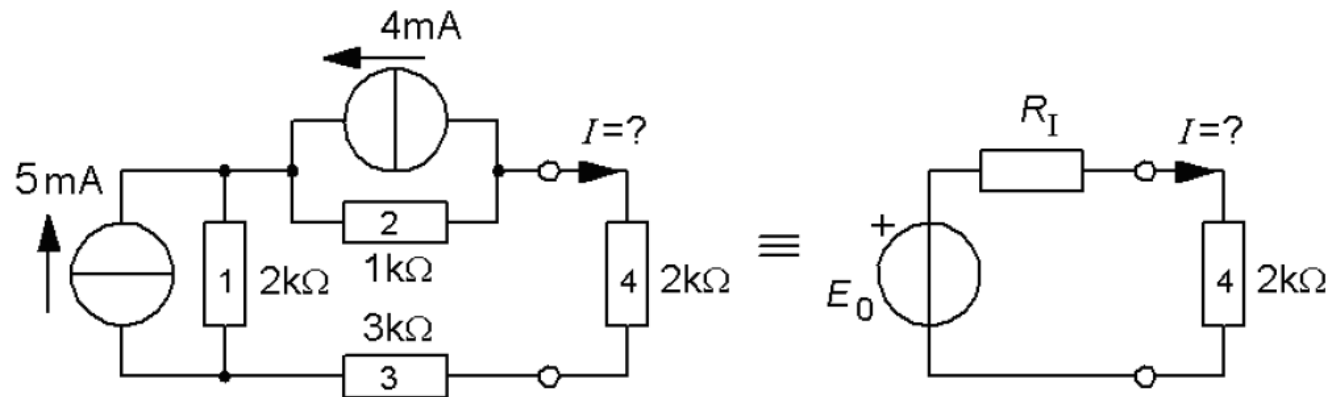

- Derive a Thevenin's equivalent, E_0 R_I , to the circuit with the two current sources.
- Calculate how big the current I would be if you connected a resistor $R_4 = 2 \text{ k}\Omega$ to the circuit (or its equivalent).

Example (8.9)

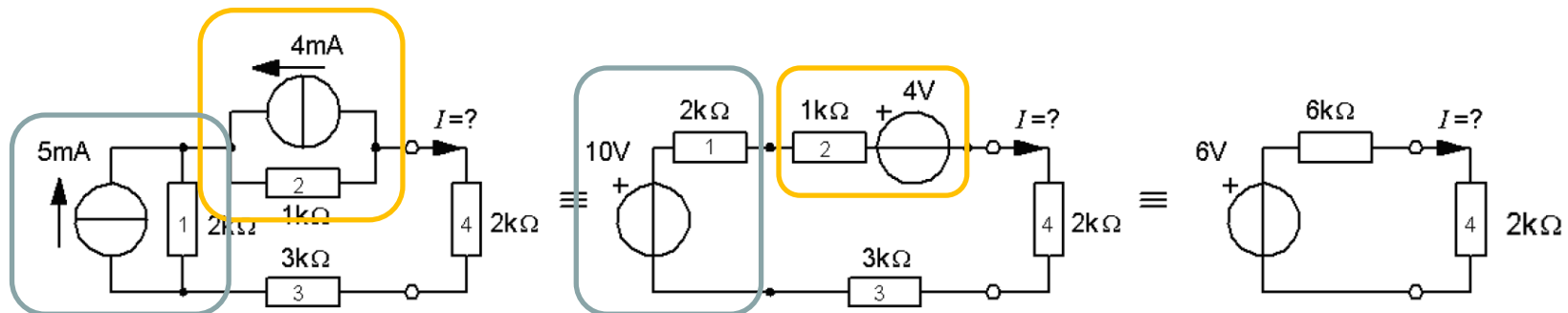


$$5\text{mA} \parallel 2\text{k}\Omega \Leftrightarrow 10\text{V} + 2\text{k}\Omega, \quad 4\text{mA} \parallel 1\text{k}\Omega \Leftrightarrow 4\text{V} + 1\text{k}\Omega \Rightarrow 6\text{V} + 6\text{k}\Omega$$

$$I = \frac{E_0}{R_I + R_L} = \frac{6}{6 + 2} = 0,75 \text{ mA}$$

William Sandqvist william@kth.se


Example (8.10)

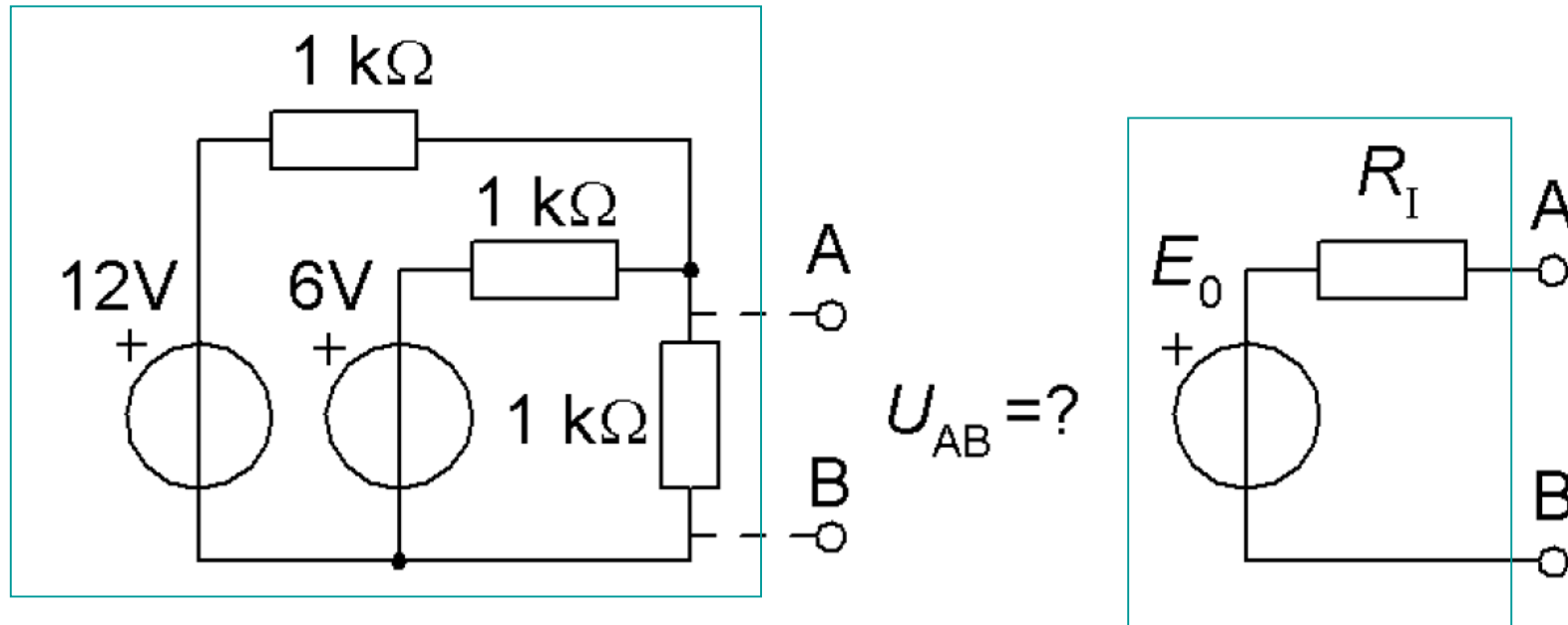

- Derive a Thevenin's equivalent, E_0 R_I , to the circuit with the two voltage sources and the three resistors.
- How big is the voltage drop U_{AB} over $1\text{ k}\Omega$ resistor in the original circuit?

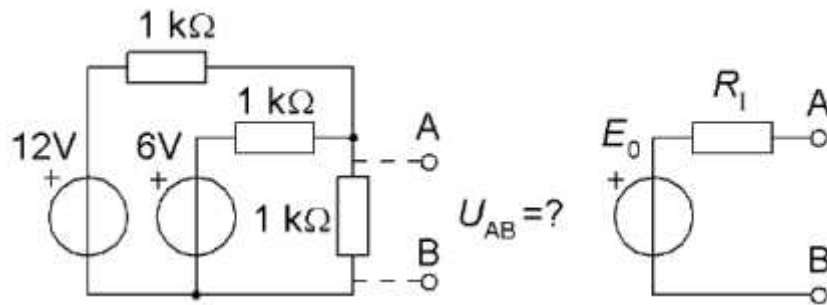Example (8.10)

Let's calculate the voltage drop U_{AB} over the $1\text{ k}\Omega$ resistor in the circuit, from the Thevenin's equivalent, as then U_{AB} will be the same as the E_0 !




R_I is the equivalent resistance when the both voltage sources are turned down to zero:

$$R_I = \frac{1}{\frac{1}{1\text{k}\Omega} + \frac{1}{1\text{k}\Omega} + \frac{1}{1\text{k}\Omega}} = \frac{1}{3} \text{k}\Omega$$

Suppose A and B short circuited. The third $1\text{ k}\Omega$ resistor will then be without current and can be ignored. The short circuit current will come from the two voltage sources through their $1\text{ k}\Omega$ resistors:

$$I_K = \frac{12\text{V}}{1\text{k}\Omega} + \frac{6\text{V}}{1\text{k}\Omega} = 18 \text{ mA}$$

Example (8.10)

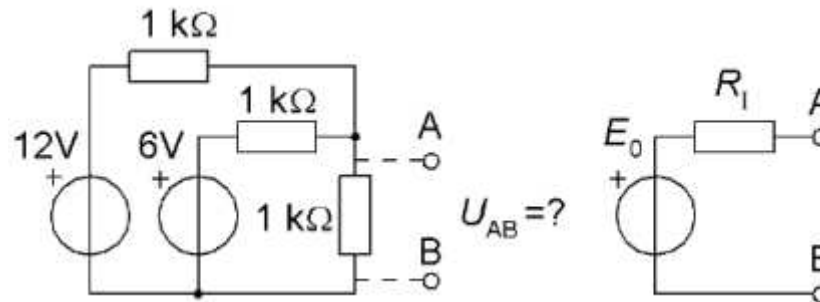


The Thevenin equivalent will have the same short circuit current $I_K = 18$ mA. This makes it easy to calculate E_0 :

$$I_K = \frac{E_0}{R_I} \Rightarrow E_0 = I_K \cdot R_I = 18 \cdot \frac{1}{3} = 6 \text{ V}$$

And the voltage drop U_{AB} is the same E_0 . $U_{AB} = 6 \text{ V}$.


William Sandqvist william@kth.se

Example (8.11)

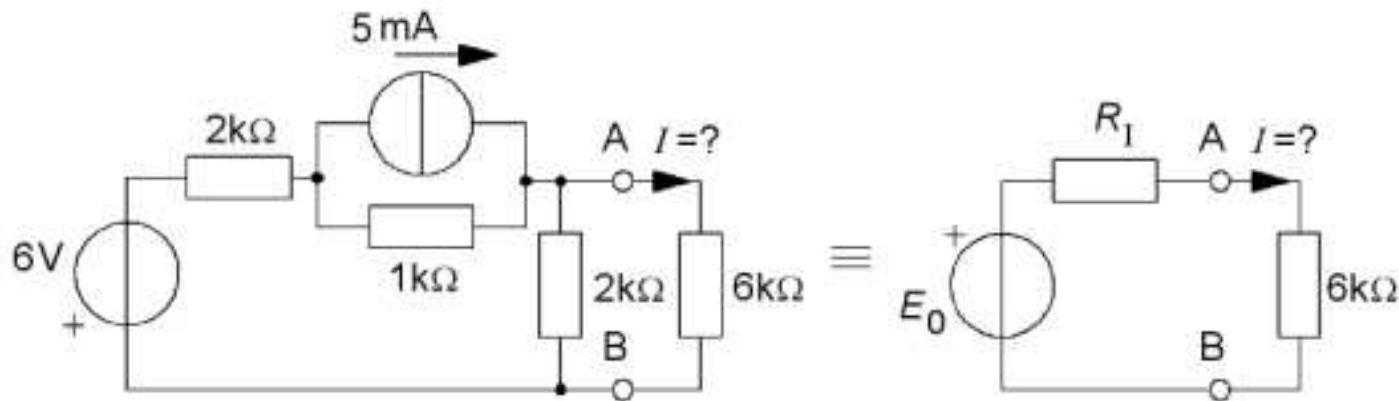

- Derive a Thevenin's equivalent, E_0 R_T , to the circuit with the voltage source and the current source and the three resistors. (The 6 kΩ resistor is not included in the circuit).
- Calculate how big current I would flow in a resistor $R = 6$ kΩ connected to A-B? What direction will the current have?

Example (8.11)

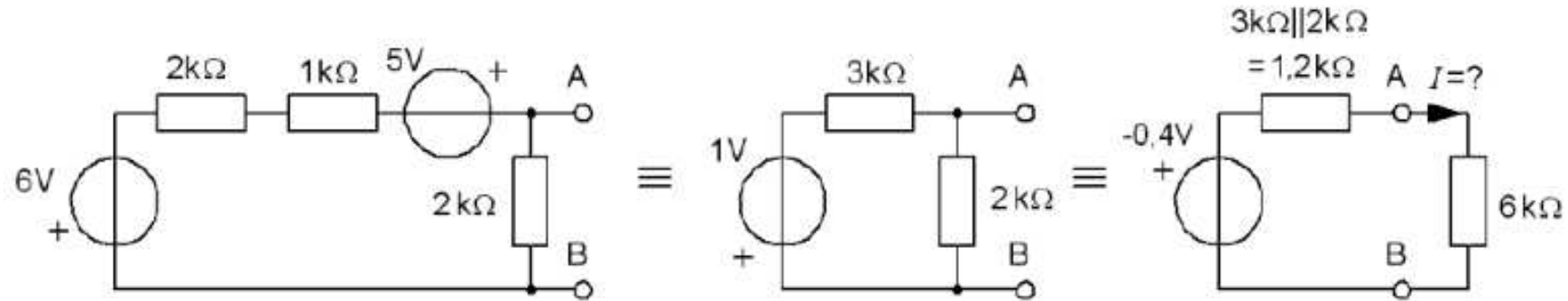

The current source with the $1\text{ k}\Omega$ resistor can be transformed to a voltage source. The circuit then becomes a 1 V voltage source with a voltage divider.

$$E_0 = 1 \frac{2}{3+2} = 0,4\text{ V} \quad R_I = \frac{3 \cdot 2}{3+2} = 1,2\text{ k}\Omega$$

The open circuit voltage is $0,4\text{ V}$, and the internal resistance $3\text{ k}\Omega \parallel 2\text{ k}\Omega = 1,2\text{ k}\Omega$. Note. The voltage source $0,4\text{ V}$ is opposite to the definition of the figure.

William Sandqvist william@kth.se