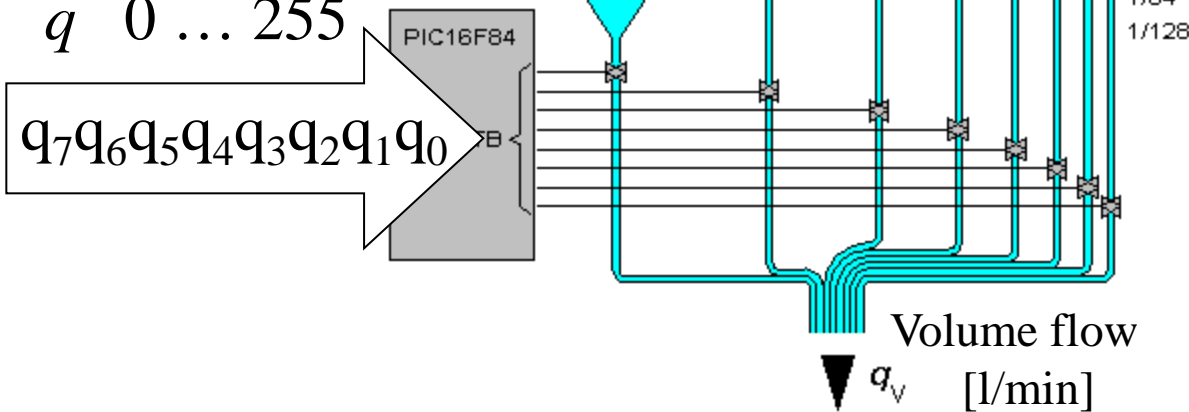



# Digital or Analog

1 1/2 1/4 1/8 1/16 1/32 1/64 1/128  
binary coded funnels

- digitally:  
 $q = 0 \dots 255$



- Digital style*

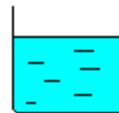

- or analog?




- Old school*

# Digital→Analog converter?

$b_7b_6b_5b_4b_3b_2b_1b_0$

- Binary coded resistor values


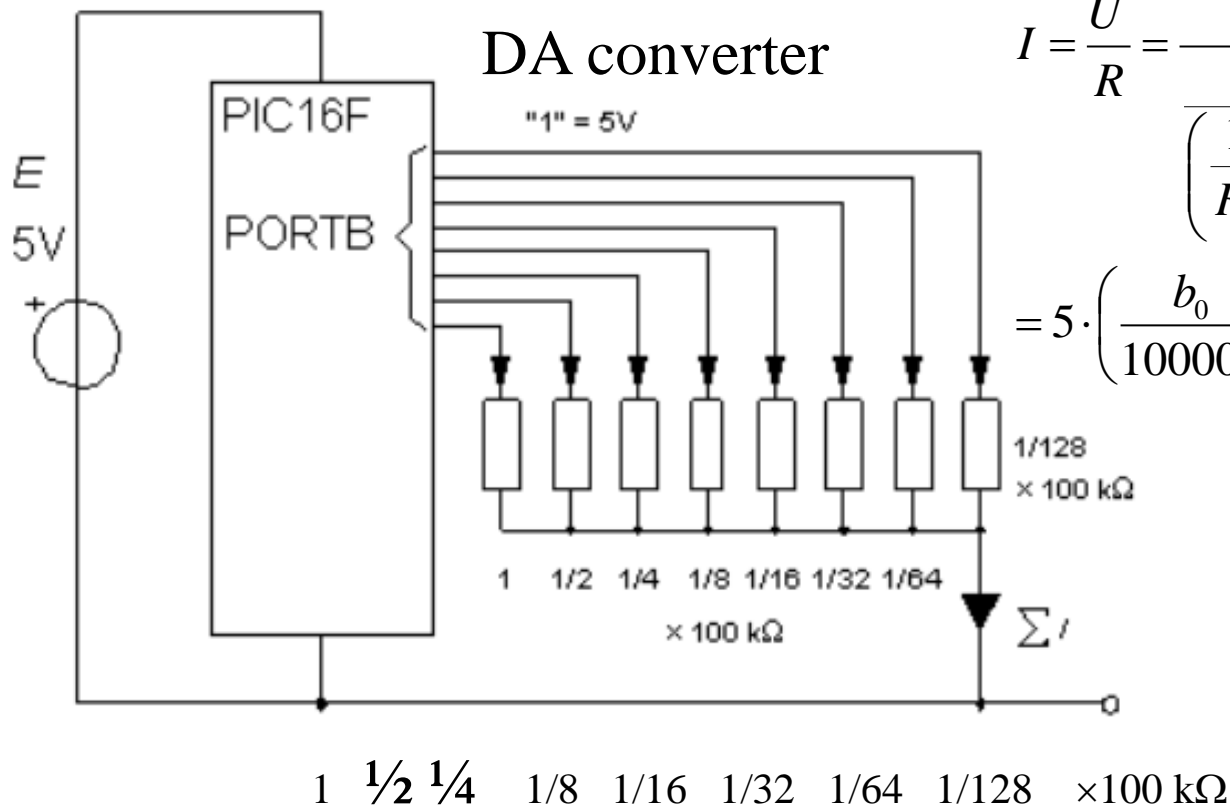


$$I = \frac{U}{R} = \frac{U}{\frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}\right)}}$$

$$= 5 \cdot \left( \frac{b_0}{100000} + \frac{b_1}{50000} + \frac{b_2}{25000} + \dots + \frac{b_7}{781} \right)$$

The current  $I$  is the **sum** of the currents from the "binary coded" resistors.

# Digital→Analog converter?

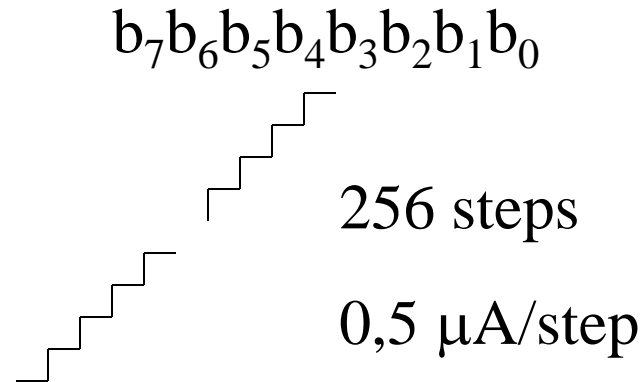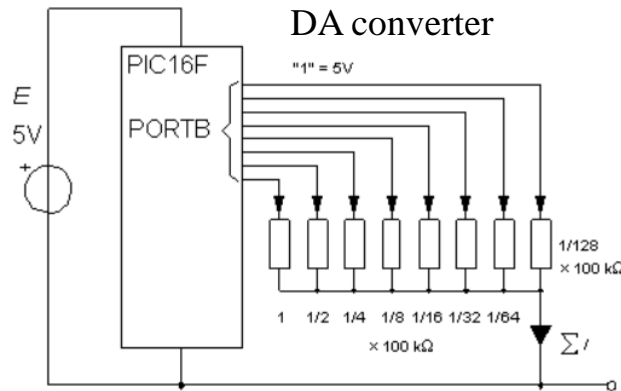

$$I = \frac{U}{R} = 5 \cdot \left( \frac{b_0}{100000} + \frac{b_1}{50000} + \frac{b_2}{25000} + \frac{b_3}{12500} + \frac{b_4}{6250} + \frac{b_5}{3125} + \frac{b_6}{1563} + \frac{b_7}{781} \right)$$

$$I_{\max} = 5 \cdot \left( \frac{1}{100000} + \frac{1}{50000} + \frac{1}{25000} + \frac{1}{12500} + \frac{1}{6250} + \frac{1}{3125} + \frac{1}{1563} + \frac{1}{781} \right) = 128 \mu\text{A}$$

# Problems with tolerances


Binary coded resistors for 8 bit.

Biggest resistor *exactly* **100000  $\Omega$**  and  
smallest resistor *exactly* **781  $\Omega$**  (preferably  
781,25 )?


**It is difficult to manufacture such various resistors with tight tolerances.**

- There is a better solution!


**R2R- method.**

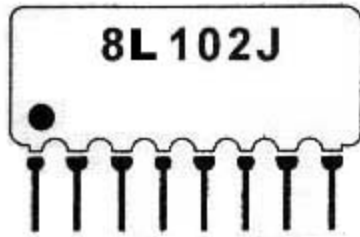

# R-2R-ladder

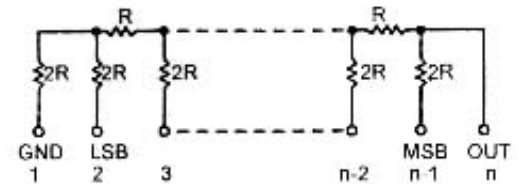

$$b_4 b_3 b_2 b_1 b_0$$

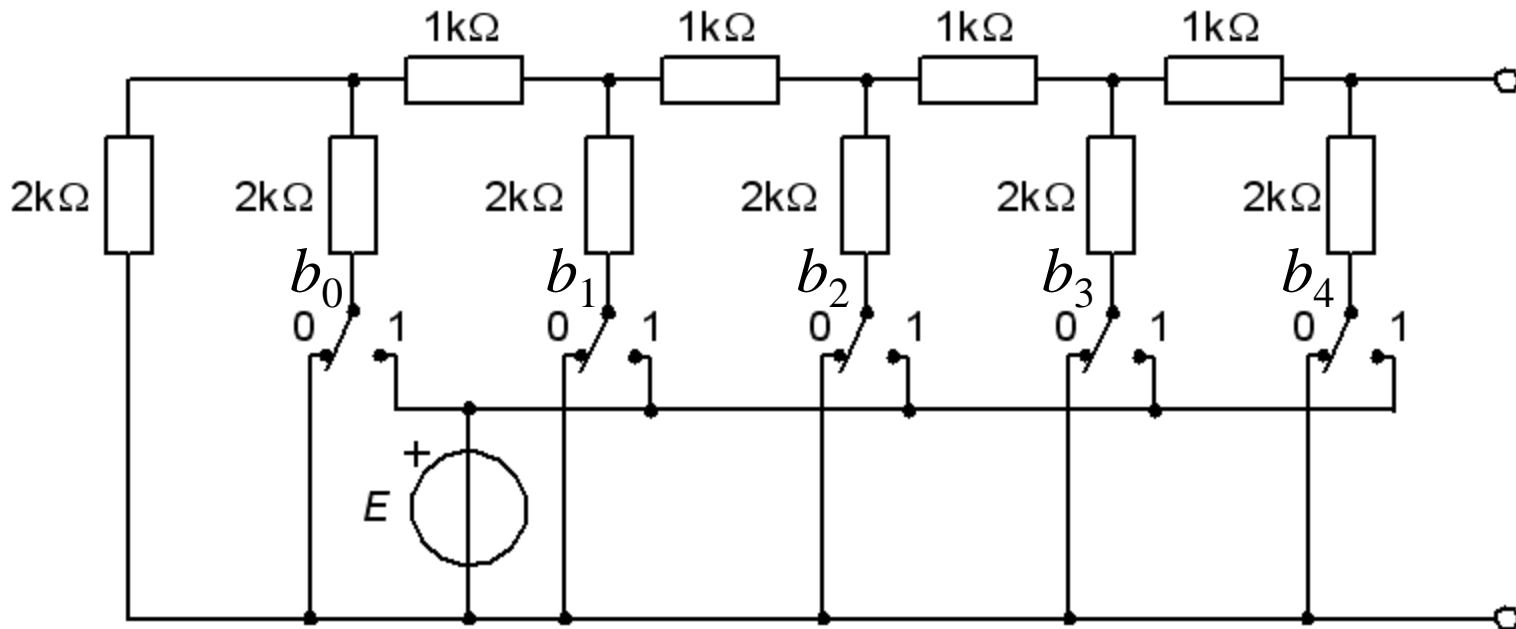


Just one resistance value needs to be manufactured,  $R$ , and then  $R+R=2R$ . One must be able to produce many "equal" resistors - the exact value is no longer important.

# Two-terminal equivalent $R_I$

The R2R-ladder is not that easy to understand ...

Repeated use of two-terminal equivalents and the superposition rule is what is required.


R-2R  $b_0=0$   $R_I=?$

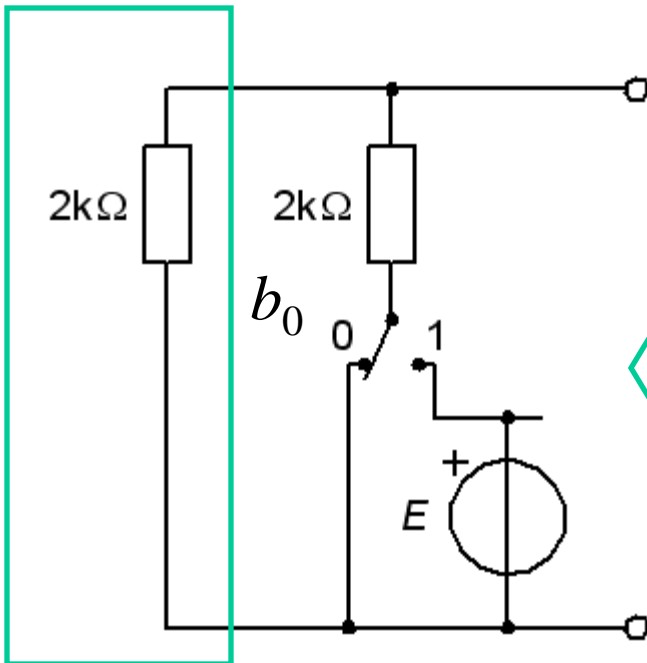

$R_I = ?$

$$R_I = \frac{2 \cdot 2}{2 + 2} = 1 \text{ k}\Omega$$

R-2R  $b_0=1$   $R_I=?$

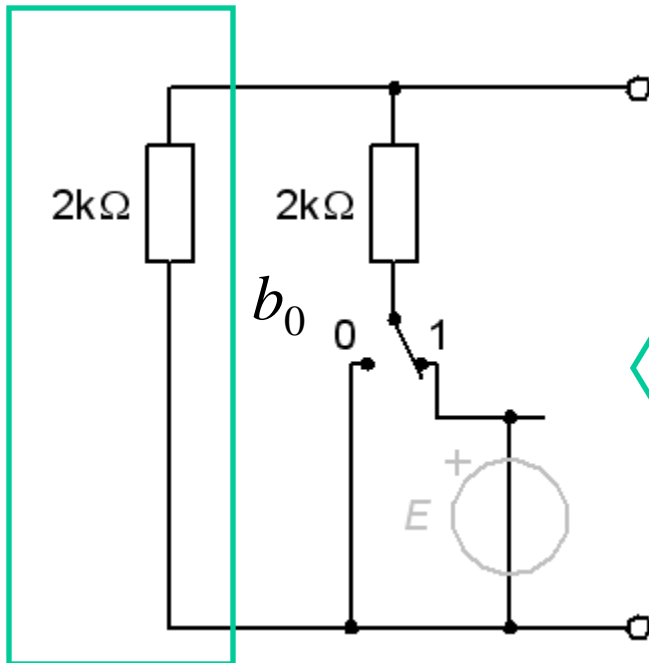


$R_I = ?$

$$R_I = \frac{2 \cdot 2}{2 + 2} = 1 \text{ k}\Omega$$

$b_0$  1 or 0, same internal resistance!




R-2R  $b_0$   $R_I = ?$

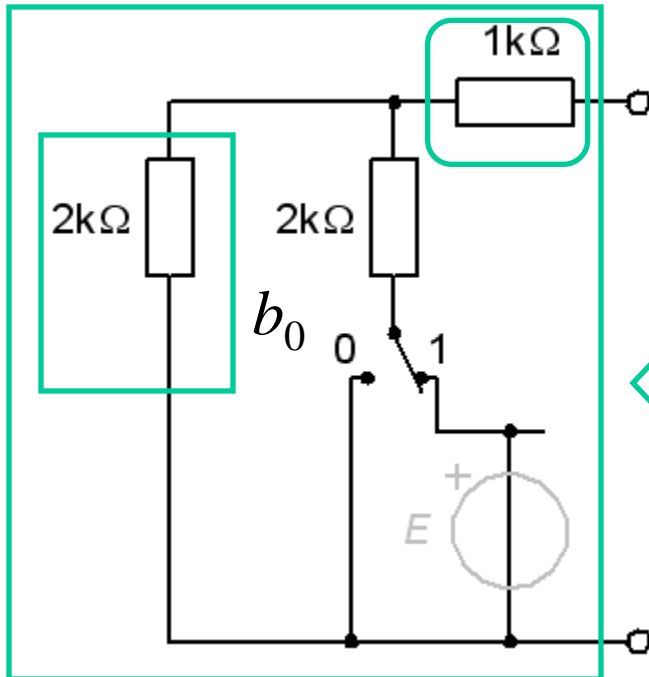

$$R_I = 1 + 1 = 2 \text{ k}\Omega$$

**The total resistance of one stage becomes 2 kΩ.**


R-2R  $b_1=0$   $R_I=?$

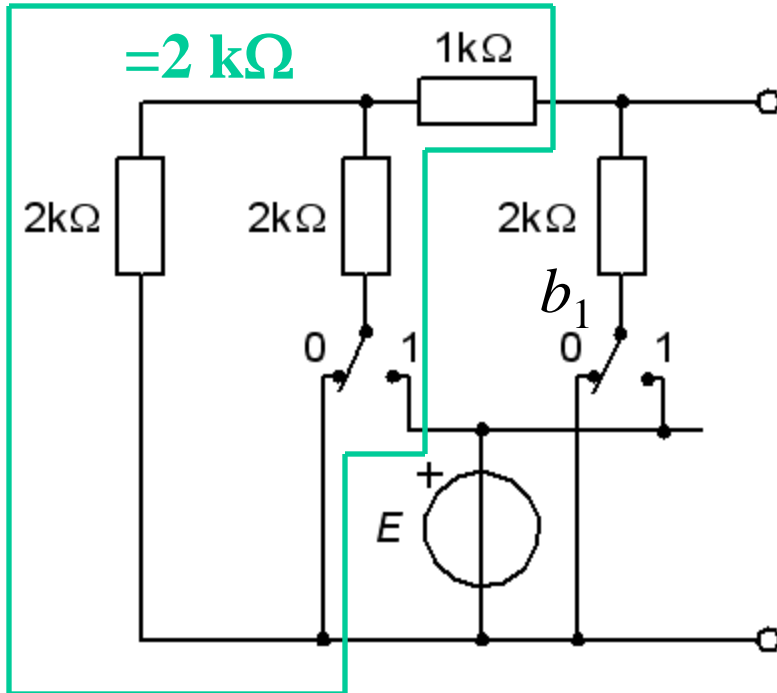

$R_I = ?$

$$R_I = \frac{2 \cdot 2}{2 + 2} = 1 \text{ k}\Omega$$

R-2R  $b_1=1$   $R_I=?$

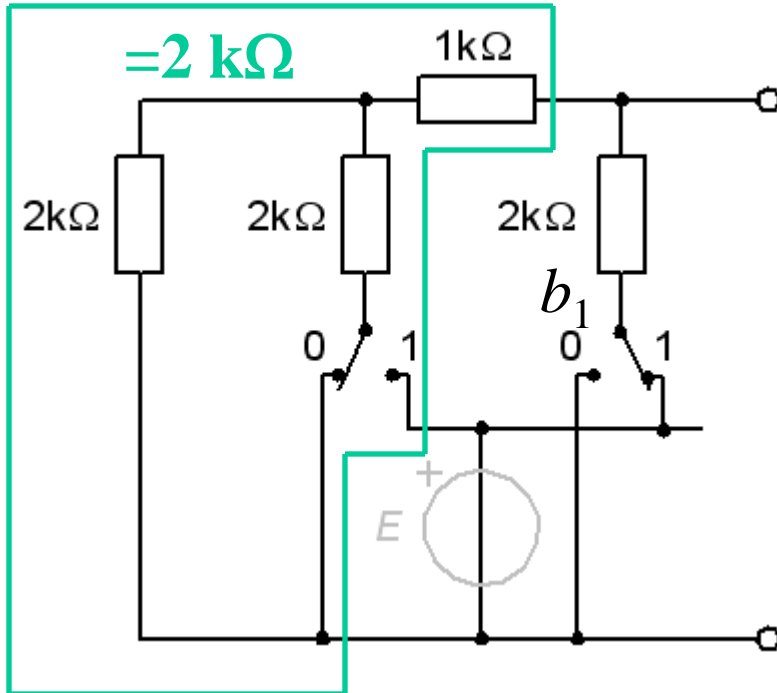


$R_I = ?$

$$R_I = \frac{2 \cdot 2}{2 + 2} = 1 \text{ k}\Omega$$

$b_1$  1 or 0, same  
internal resistance!

# R-2R $b_1$ $R_I = ?$

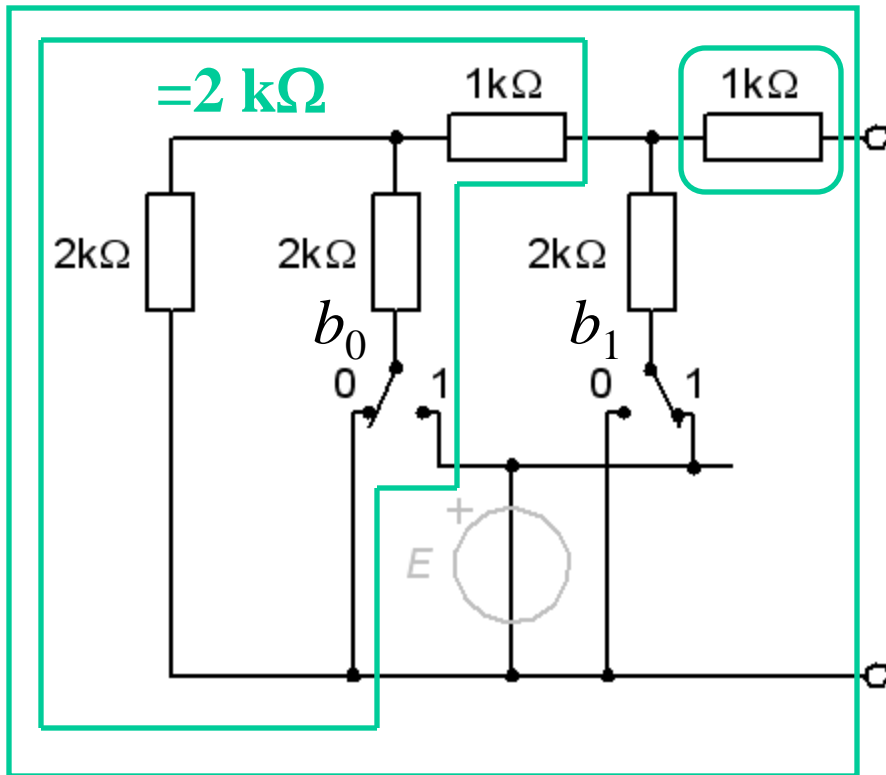


• Conclusion:

$$R_I = 1 + 1 = 2 \text{ k}\Omega$$


Regardless 1's or 0's is the total input resistance from the previous stages always  $2 \text{ k}\Omega$

# Two-terminal equivalent $E_0$

R-2R  $b_4=1$   $E_0=?$

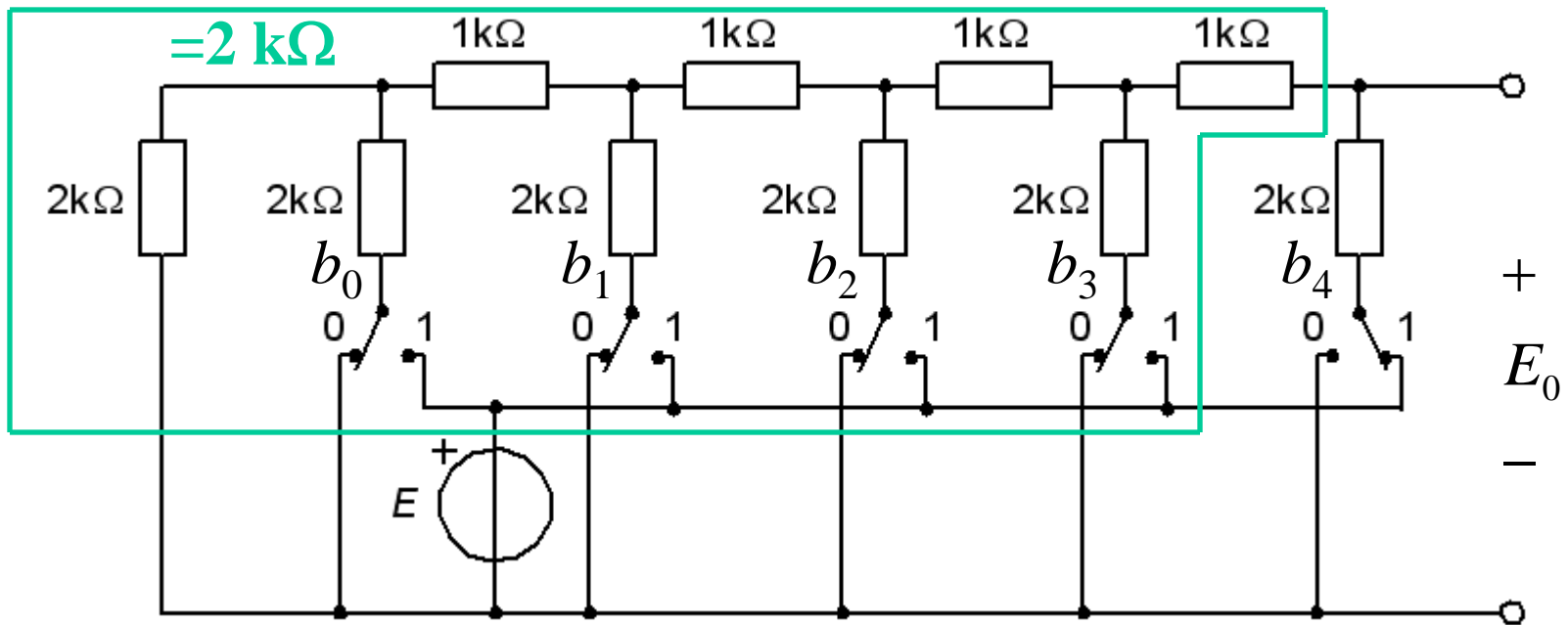


R-2R  $b_4=1$   $E_0=?$

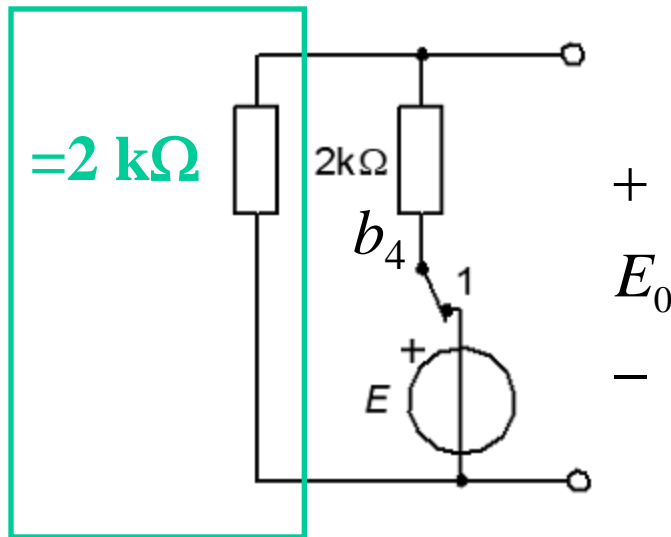

Voltage divider:





$$E_0 = E \frac{2}{2+2} = \frac{E}{2}$$

R-2R  $b_3=1$   $E_0=?$

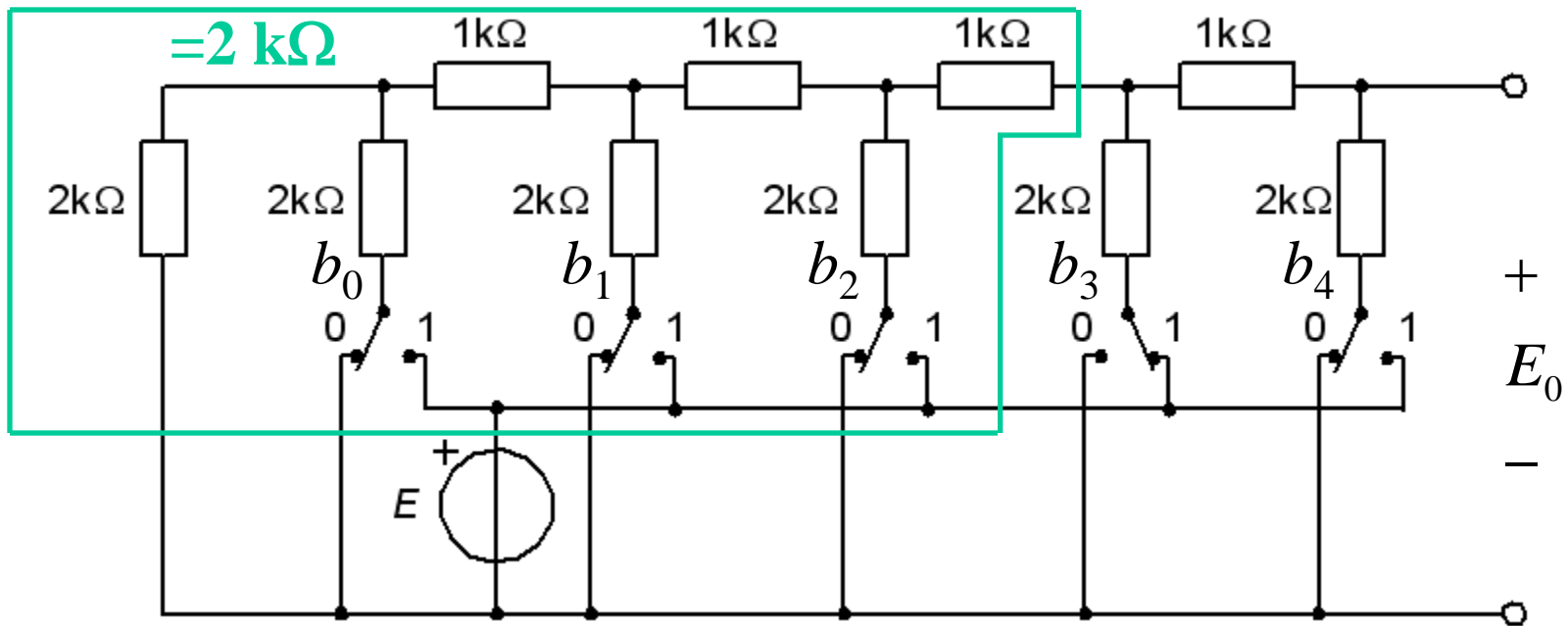




# R-2R $b_3=1$ $E_0=?$

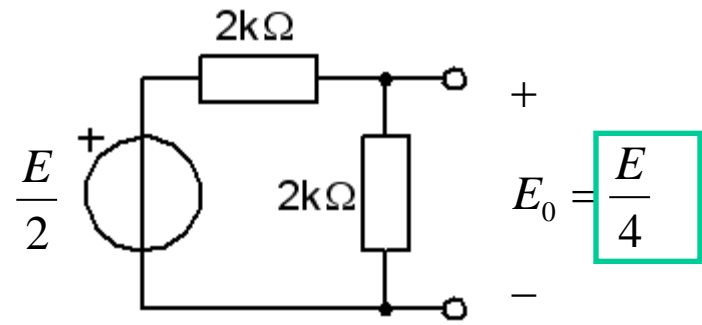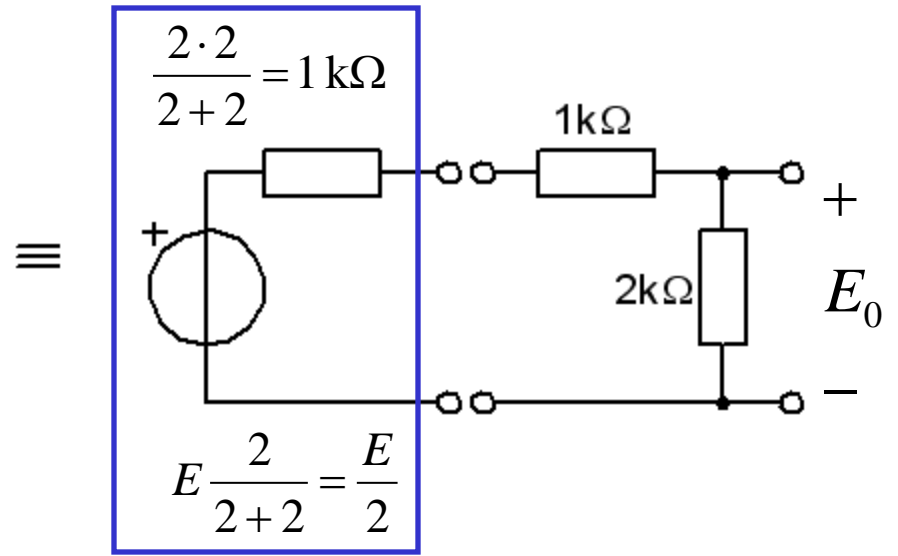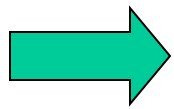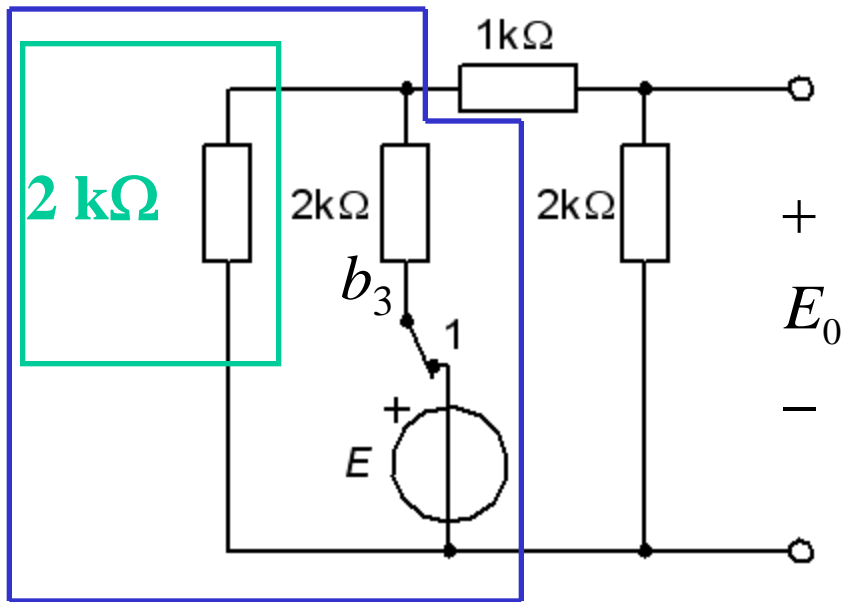


# R-2R conclusion $E_0 \dots$

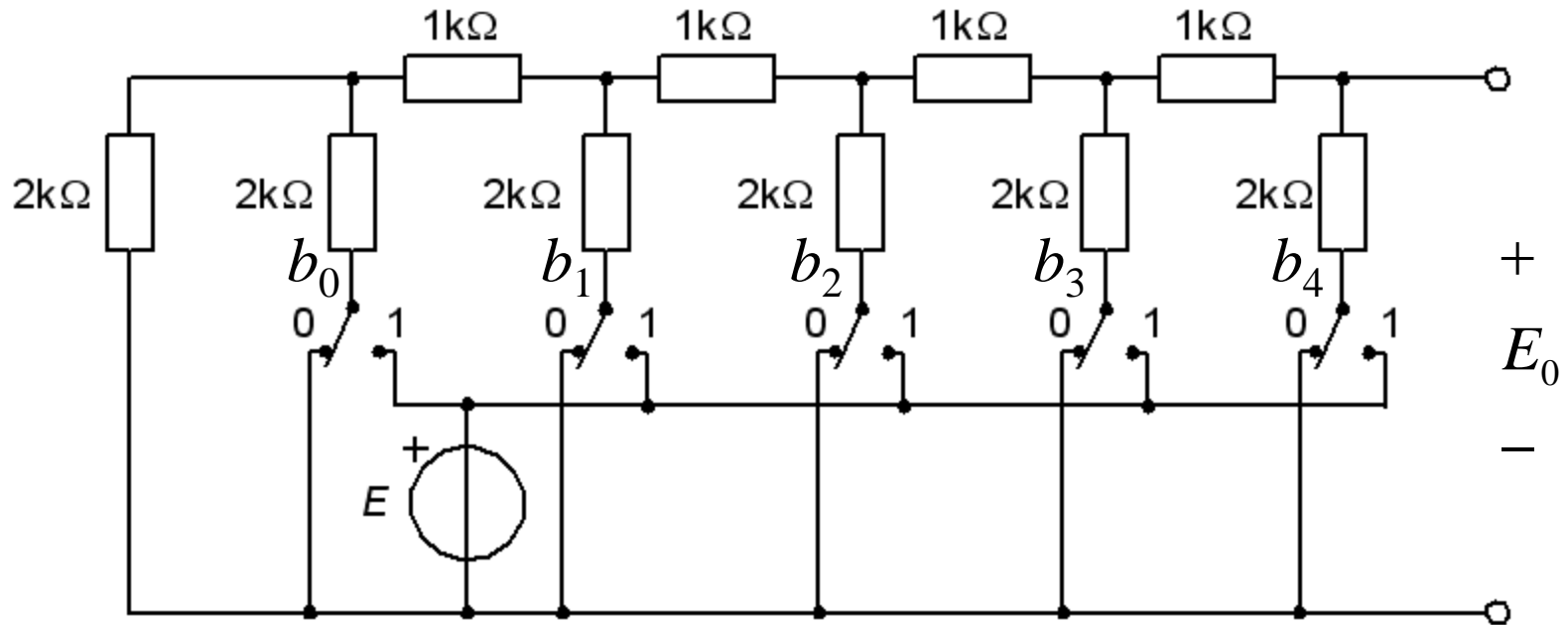

$$b_4 = 1 \Rightarrow \frac{E}{2} \quad b_3 = 1 \Rightarrow \frac{E}{4} \quad b_2 = 1 \Rightarrow \frac{E}{8} \quad \dots$$

- Reasonable guess – is it not?

# R-2R superposition

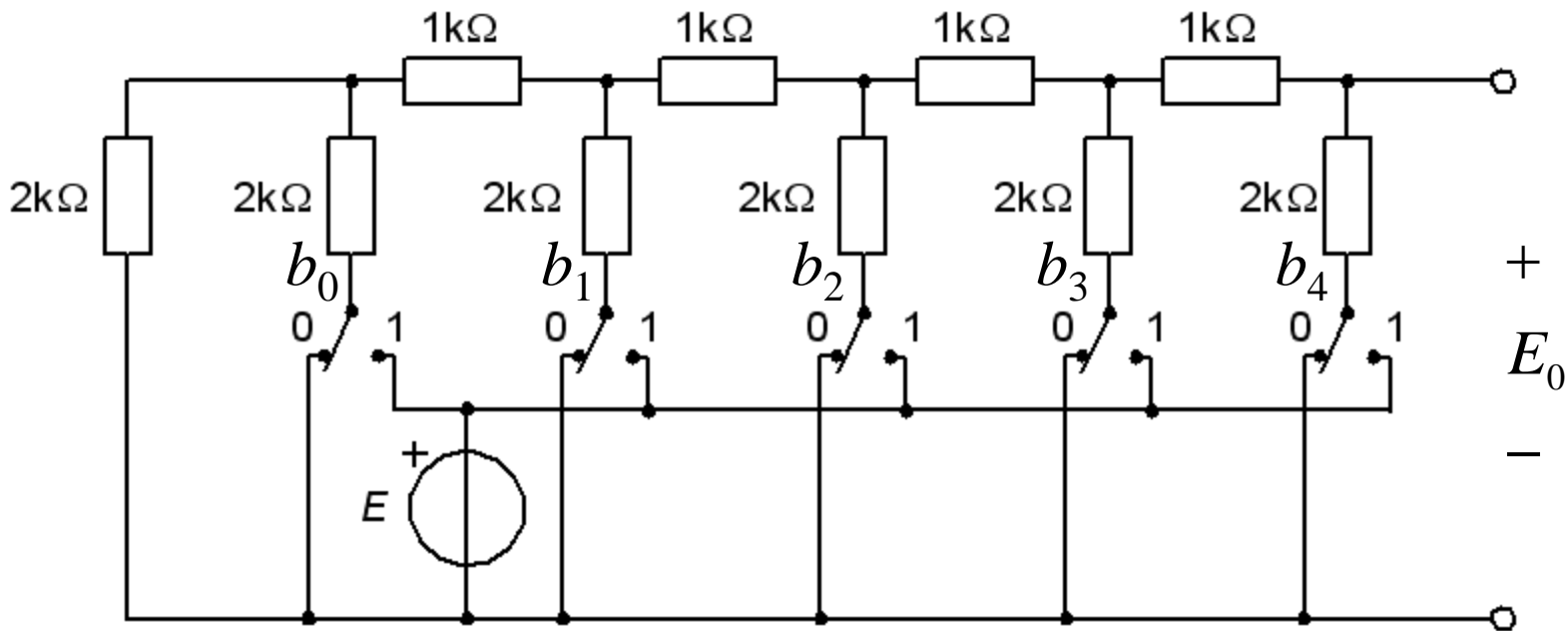


- According to the **superposition** principle, the contributions of  $b_4 b_3 b_2 \dots b_0$  can be added individually:

$$b_4 b_3 b_2 b_1 b_0 \longrightarrow E_0 = E \cdot \left( \frac{b_4}{2} + \frac{b_3}{4} + \frac{b_2}{8} + \frac{b_1}{16} + \frac{b_0}{32} \right)$$

*We have a  
DA-converter!*

# R-2R simulation

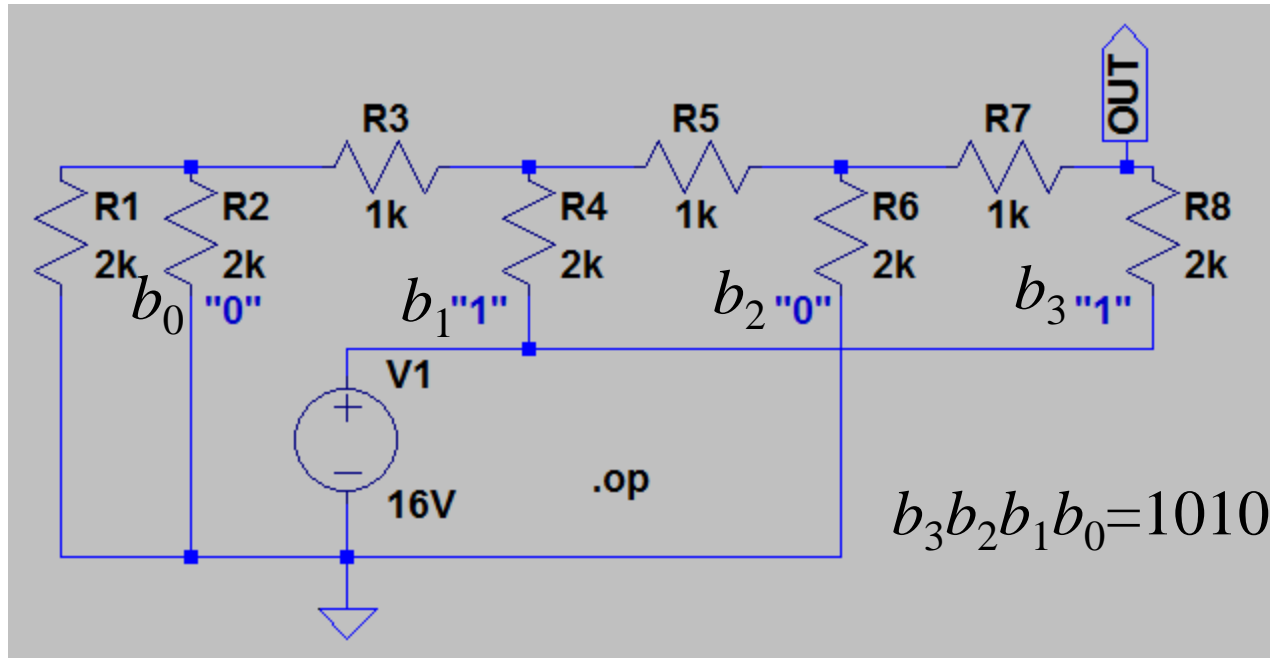


Guess value of voltage OUT?


William Sandqvist [william@kth.se](mailto:william@kth.se)

# AD-converter?



# Successive approximations

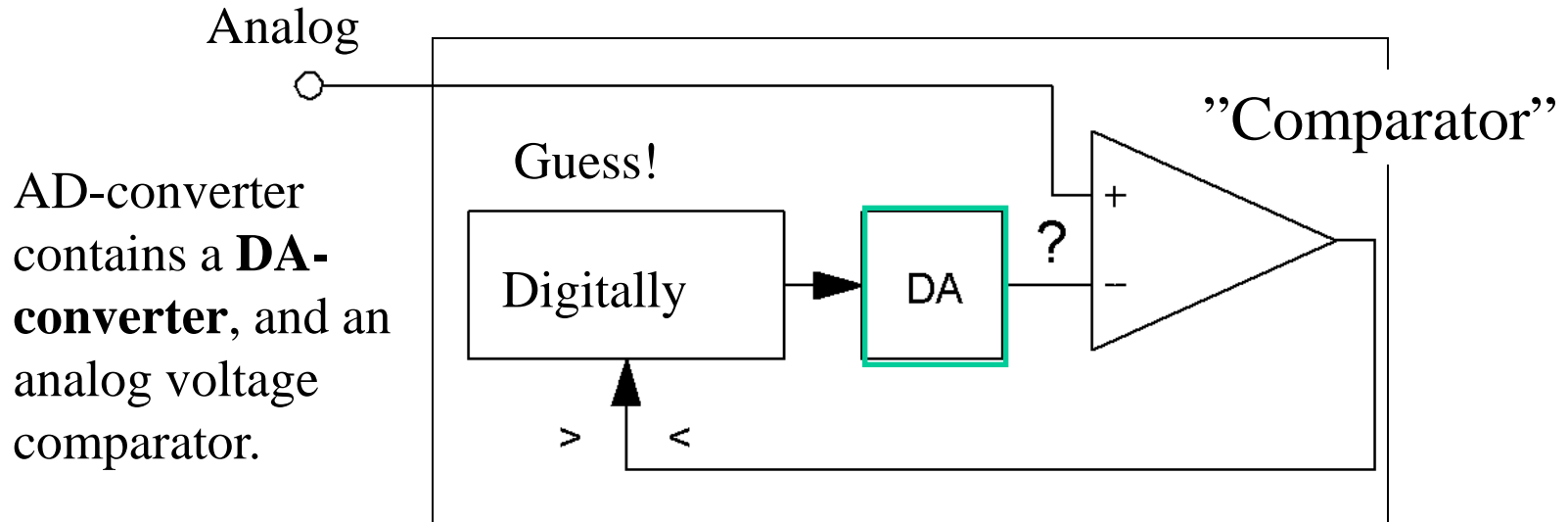

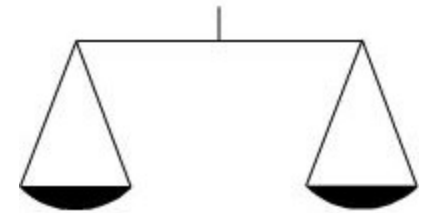*AD conversion according to the method of successive approximations is comparable to weigh an unknown mass with binary weights on a balance. We try step by step to adding binary "weight" if "<" or remove "weight" if ">".*




# Binary weights 8 4 2 1 ...

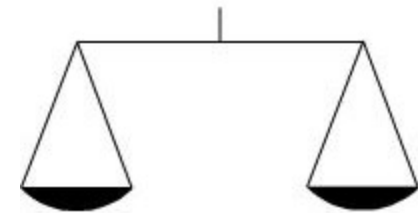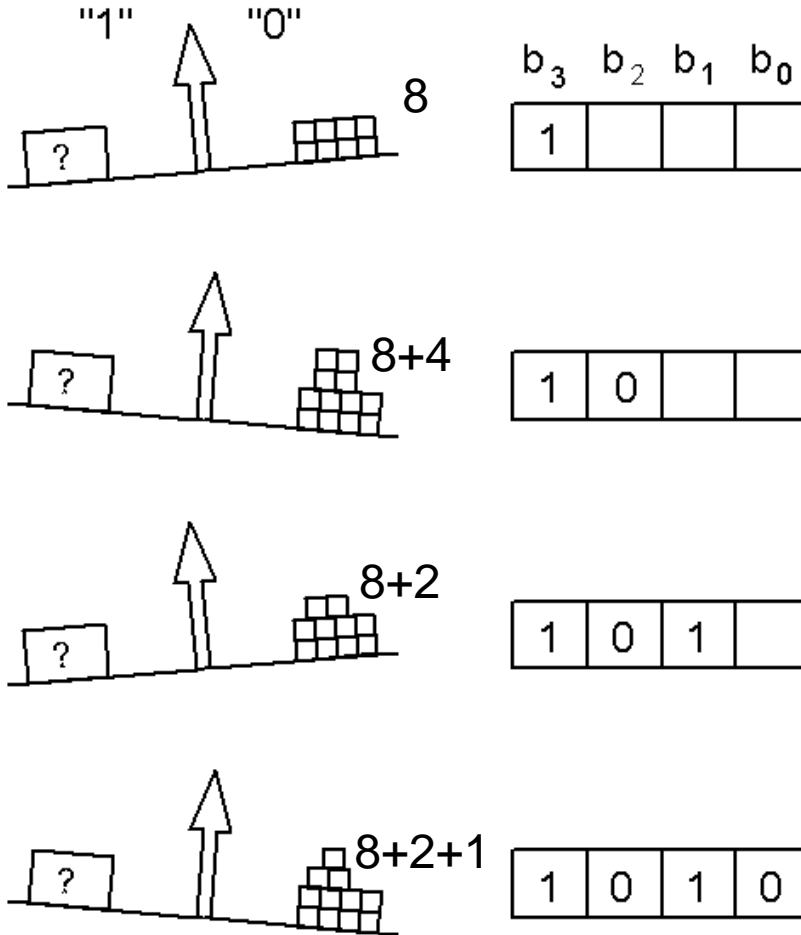

AD conversion takes time. For each bit higher resolution a comparison one step further is required.




# An AD-converter, 14 channels

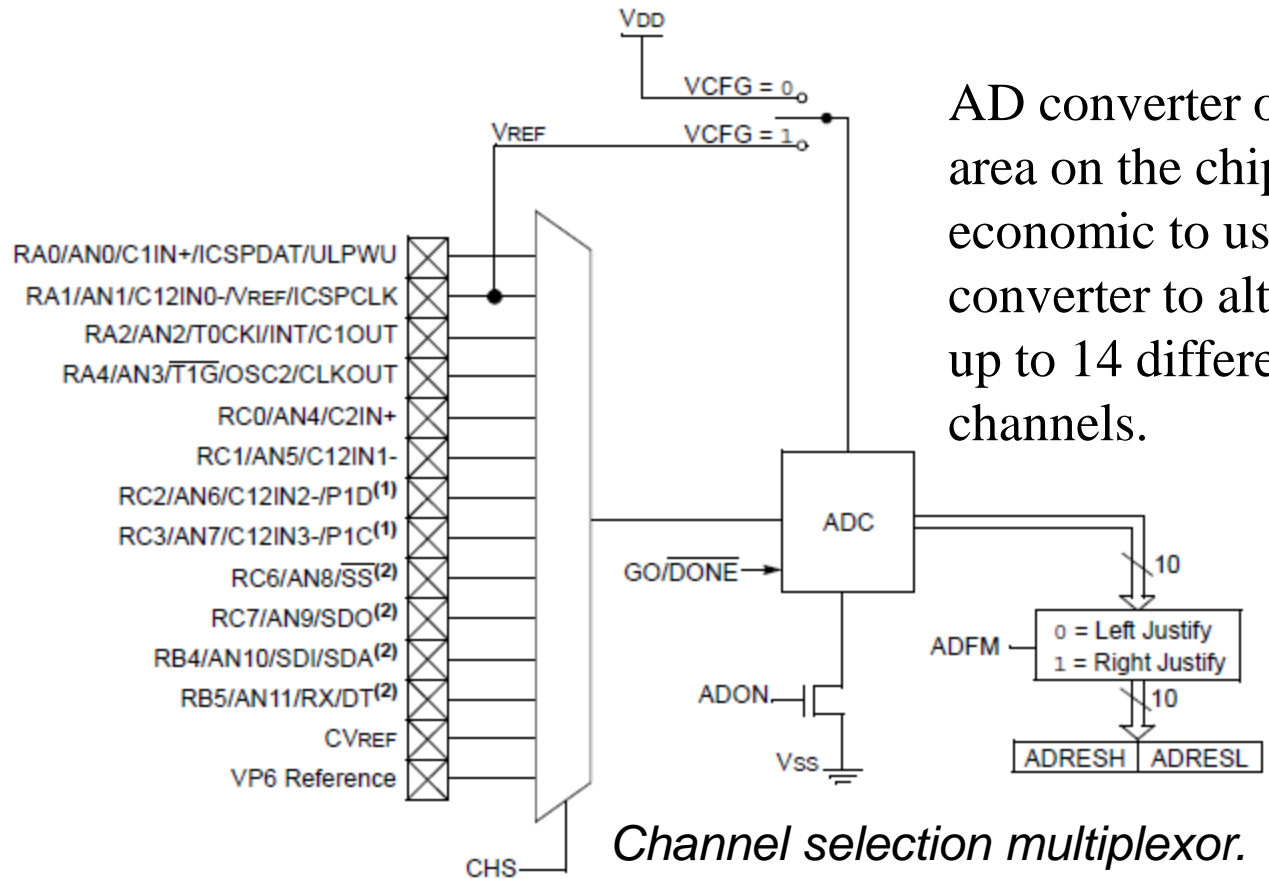

AD converter occupies a large area on the chip - so it is economic to use the same converter to alternately measure up to 14 different sources, channels.

The PIC-processor has a 10-bits AD-converter


# Supply voltage as reference

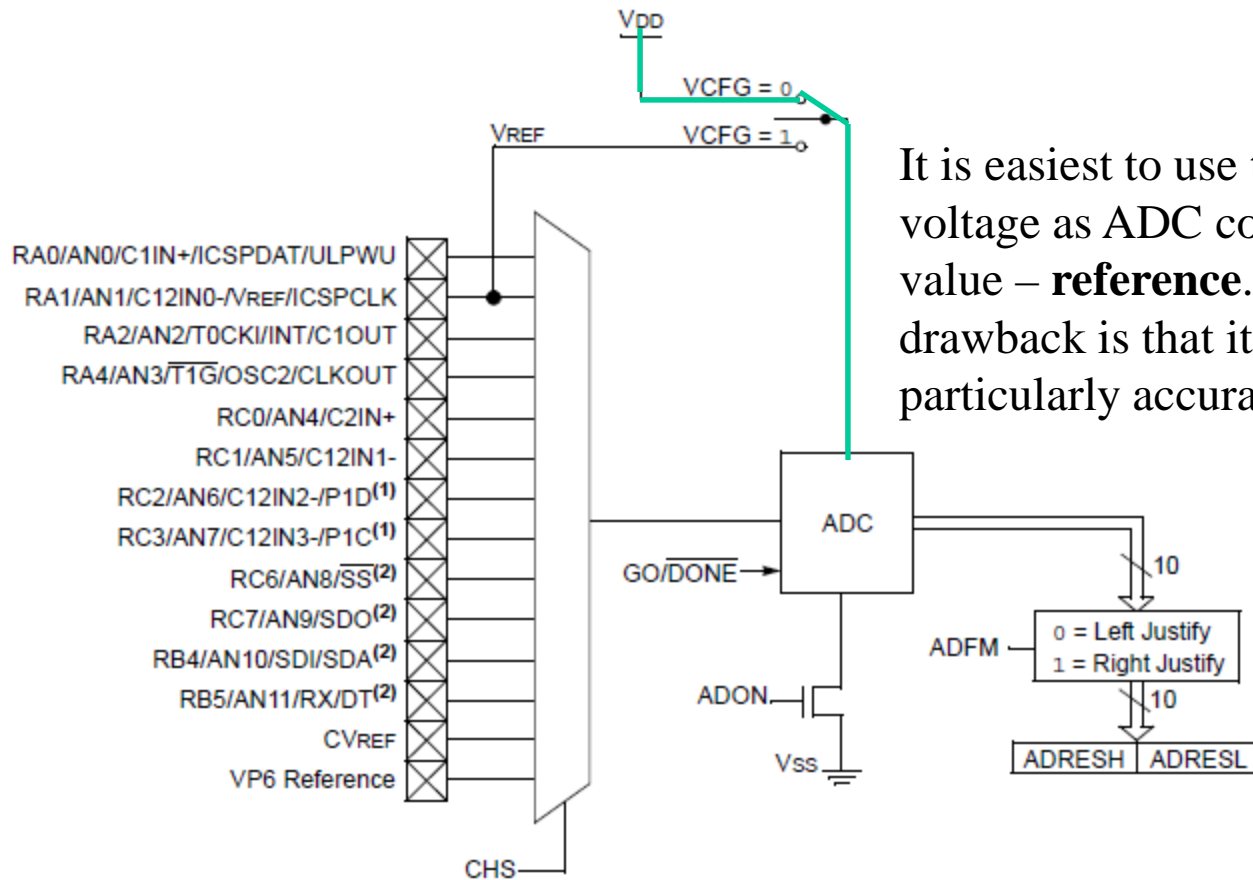


It is easiest to use the supply voltage as ADC comparison value – **reference**. The drawback is that it is not particularly accurate.

# Internal or external reference?


Why external reference?

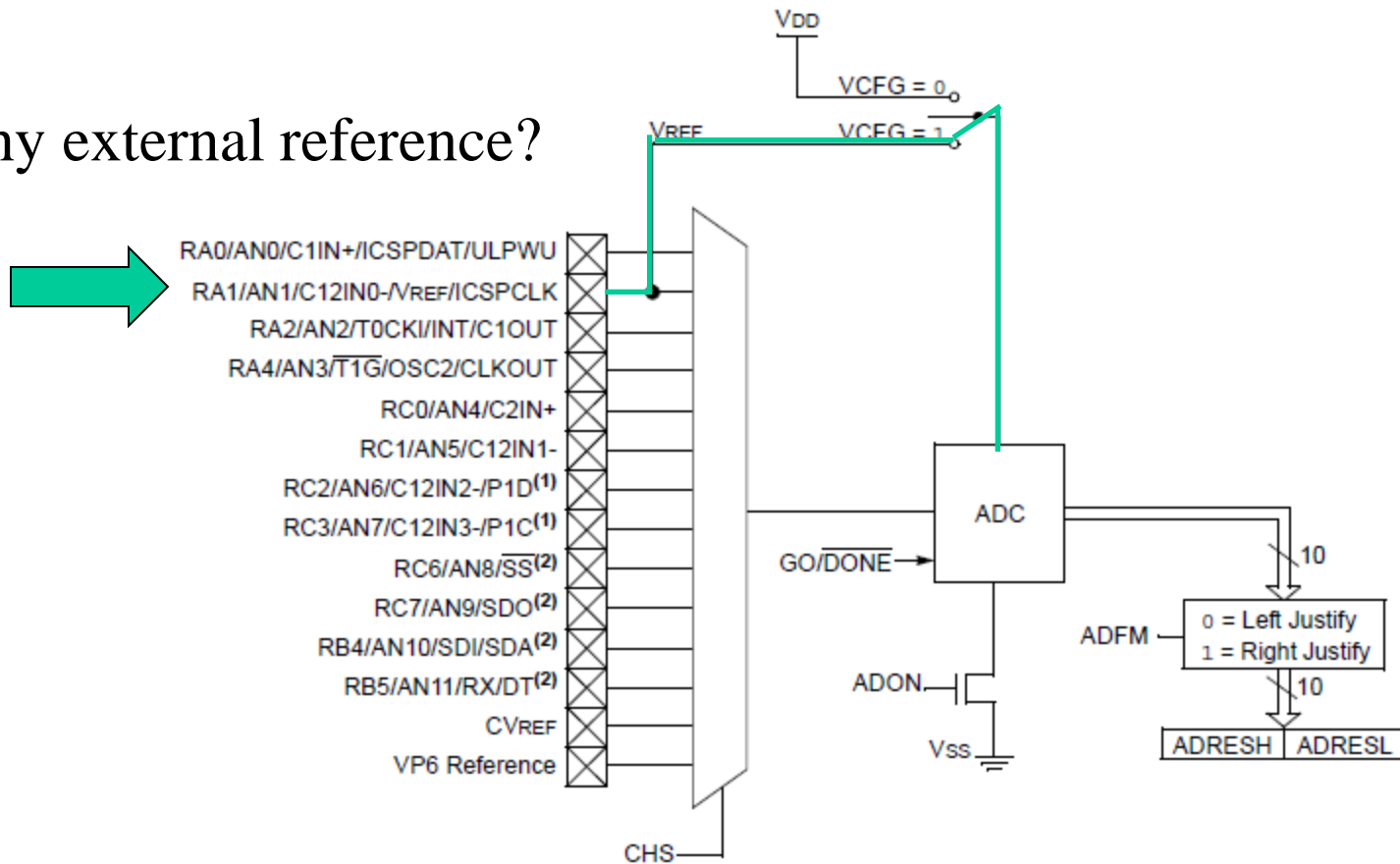


# Stabilized reference 4,096 V

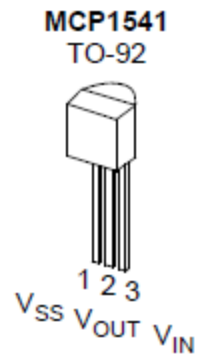

## MCP1541

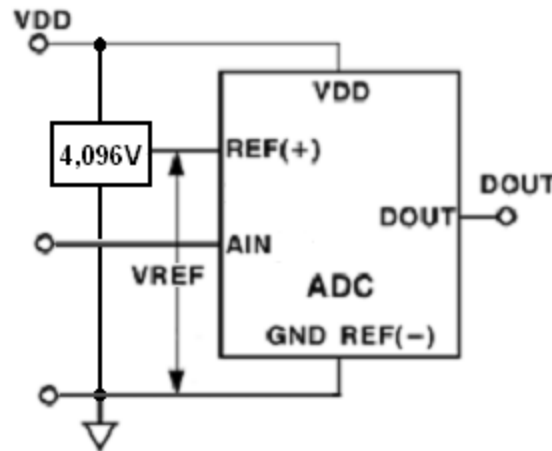


## Temperature Drift

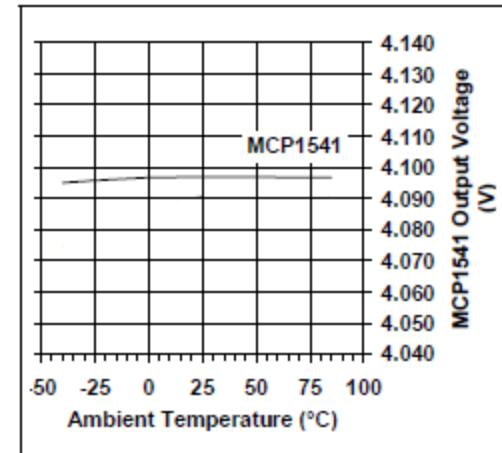

If you buy a stabilized reference circuit you can perhaps choose the value 4,096 V ( $4096=2^{12}$ ) which gives a 10-bit AD-converter exact 4 mV-steps, *without* the need to scale the measured result with multiplications and divisions.


# Ratiometric connection

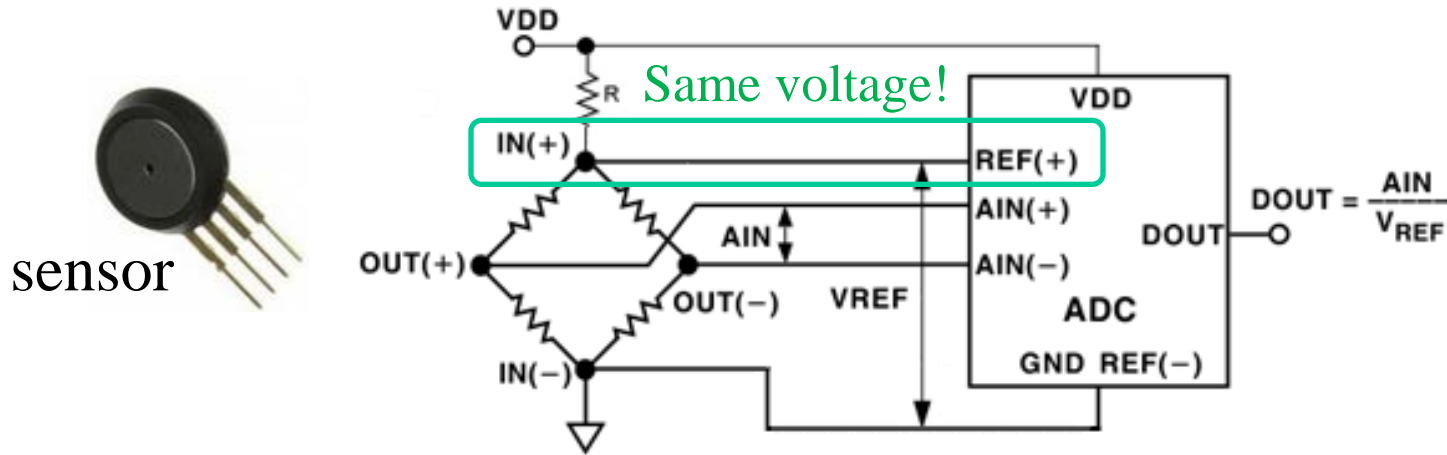


If a sensor measurement value depends on its supply voltage, you can either have stabilized supply (expensive) – or easier, use so-called ratiometric connection. If the sensor supply voltage and AD converter reference voltage **are the same**, then changes in this voltage will be the same for both, and the AD converted measured value will remain intact!
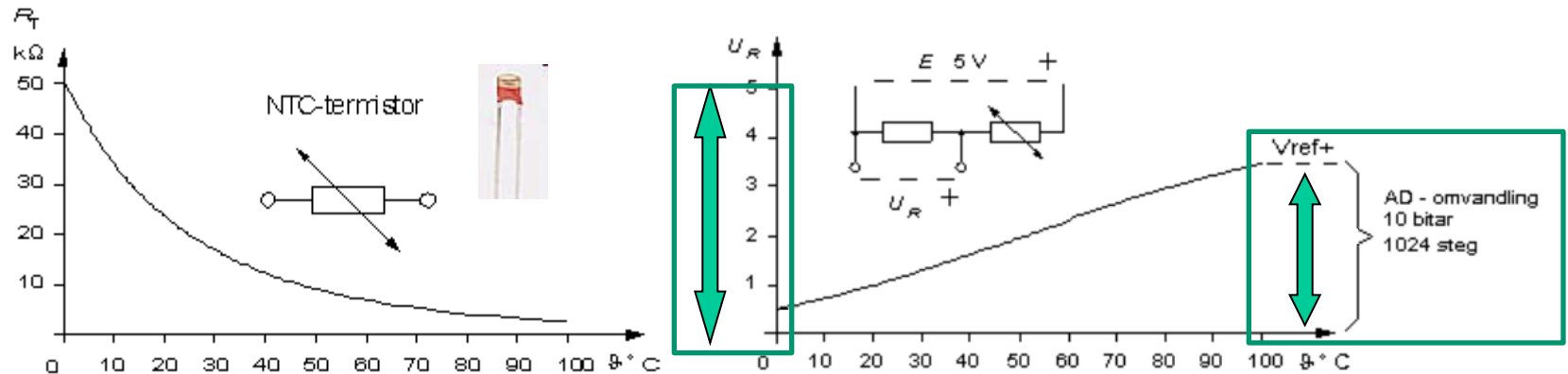
# Adapt measuring range

An NTC thermistor has a high sensitivity but a non-linear temperature relationship.



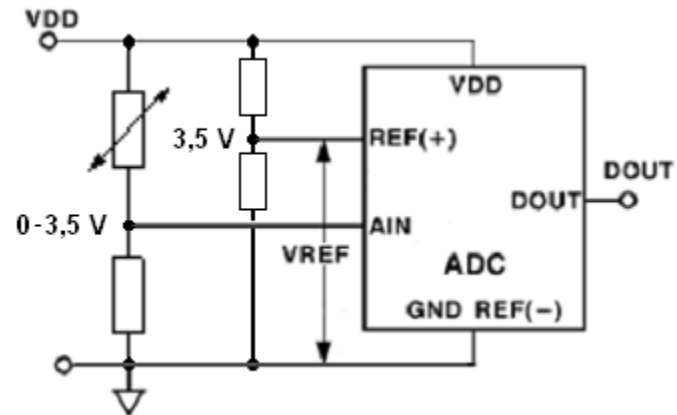One linearize with a resistor – and then get the measuring range 0 ...3,5 V. If the reference is 3,5 V instead of 5 V then one utilizes the entire ADC range for the measurement.





# Are 10-bit resolution required?

$b_9 b_8 b_7 b_6 b_5 b_4 b_3 b_2 b_1 b_0$

AD converter is 10 bits.

What does a sensor cost that has 10-bit resolution?

100 \$ ?

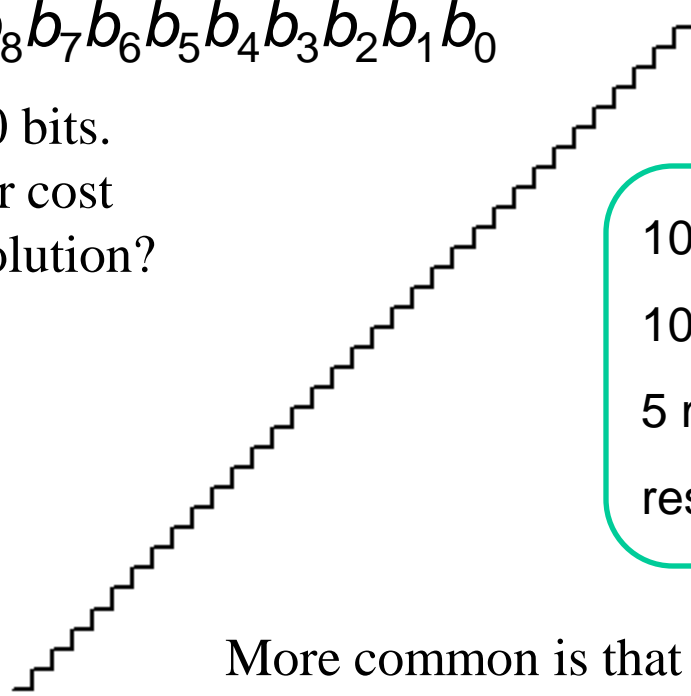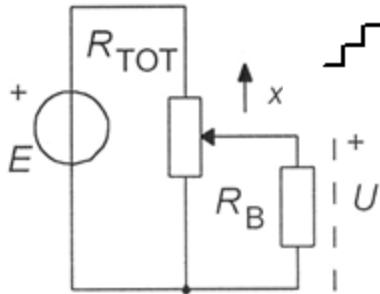

10 bits

1024 steps

5 mV/step


resolution  $\approx 0,1\%$

More common is that you can afford an 8-bit sensor. ( PIC processor itself costs 2 \$ ).

The picture shows a resistive position sensor that can take advantage of 10-bit resolution.

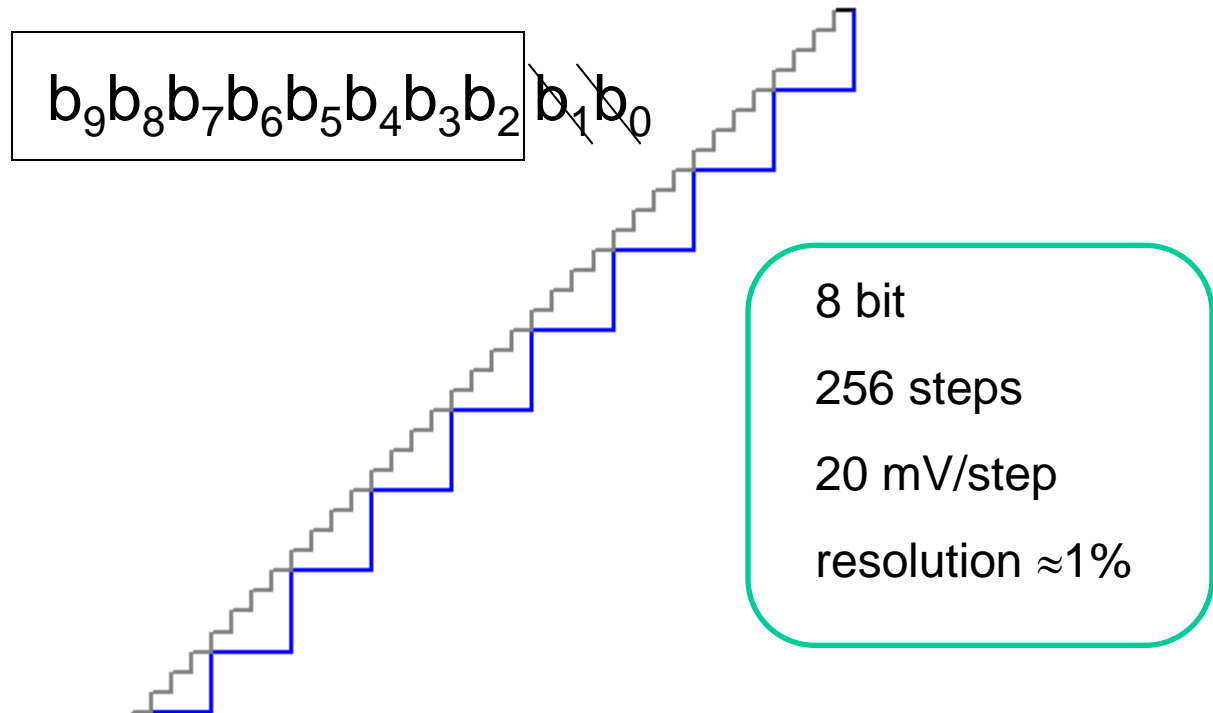
# 8-bit program

If one need only 8 bit resolution one can ignore the two least significant bits and handle the result as a byte.





# 8-bit program

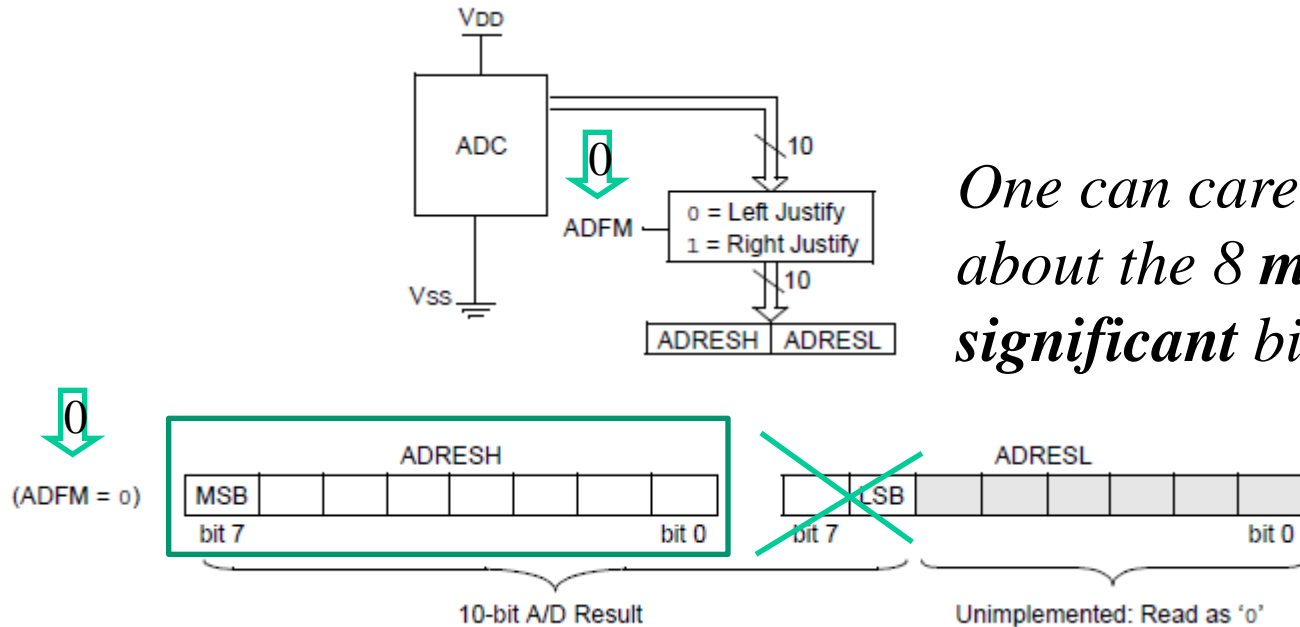


```
ADFM=0;  
char value;  
value = ADRESH; /* 8-bit measurement */
```

# Avoid amplifier


If one only need 8 bit resolution one can still use the 10-bit resolution to avoid the need to amplify the sensor signal, the two most significant bits becomes constant. One can therefore ignore to read them.

~~1~~ ~~0~~  $b_7 b_6 b_5 b_4 b_3 b_2 b_1 b_0$

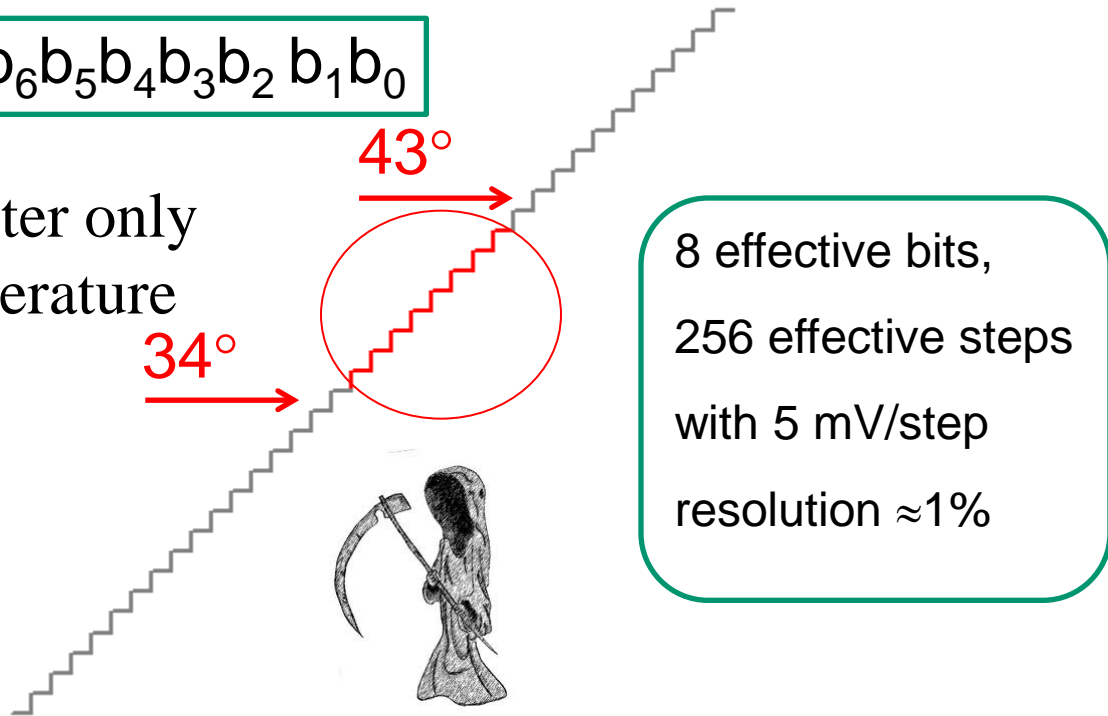A fever thermometer only need a small temperature range  $34^\circ \dots 43^\circ$  (right?)



# 8-bit program (10 bit)

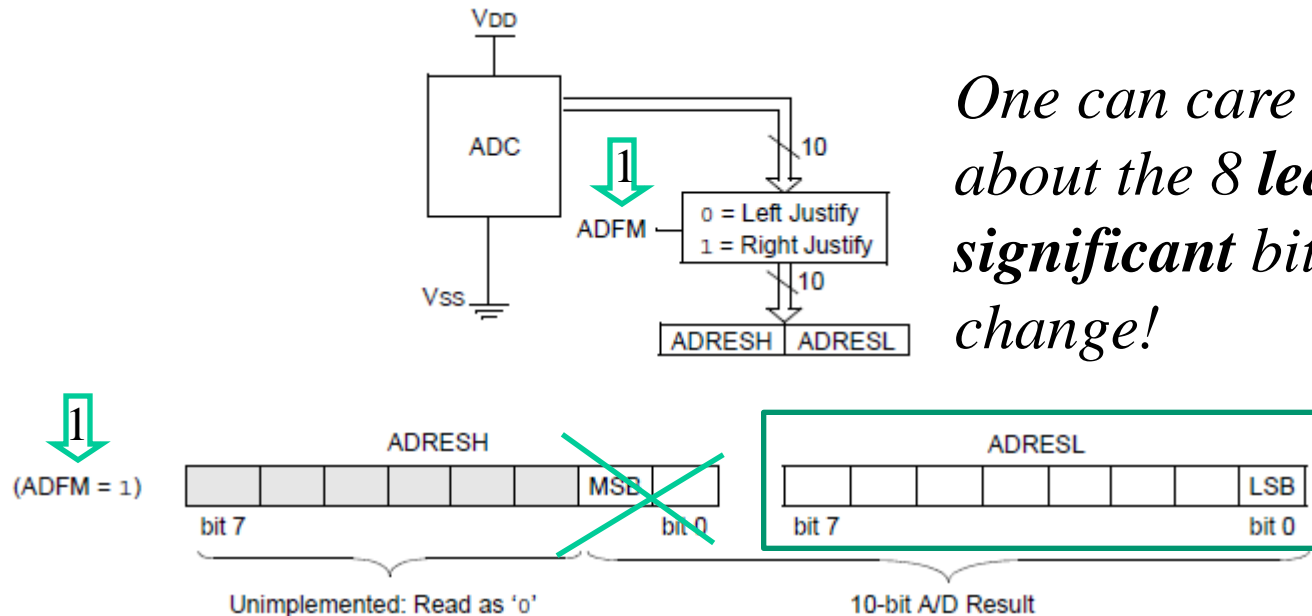


*One can care only about the 8 least significant bits that change!*


```
ADFM=0;  
char value;  
value = ADRESL; /* 8-bit measurement */
```
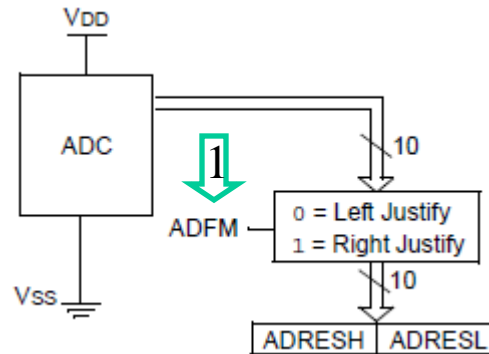
# 16-bit program

10-bits  
1024 steps  
5 mV/step  
resolution  $\approx 0,1\%$



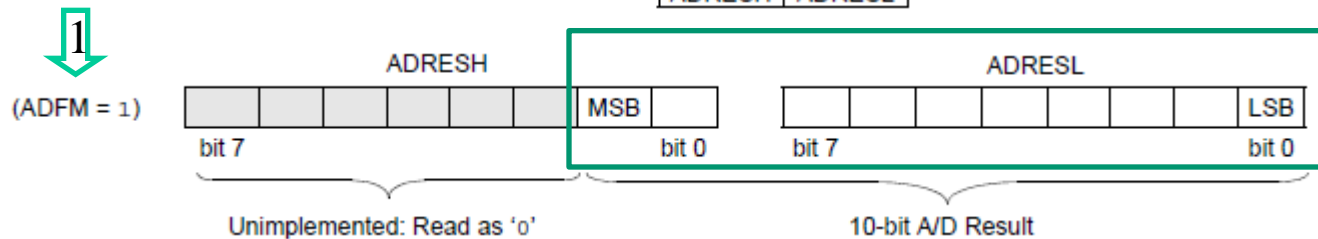*When you really need  
10 bits in a 16-bit  
variable.*




```
ADFM=1;  
unsigned long value;  
value = ADRESH * 256;  
value += ADRESL; /* 10-bit measurement */
```


William Sandqvist [william@kth.se](mailto:william@kth.se)
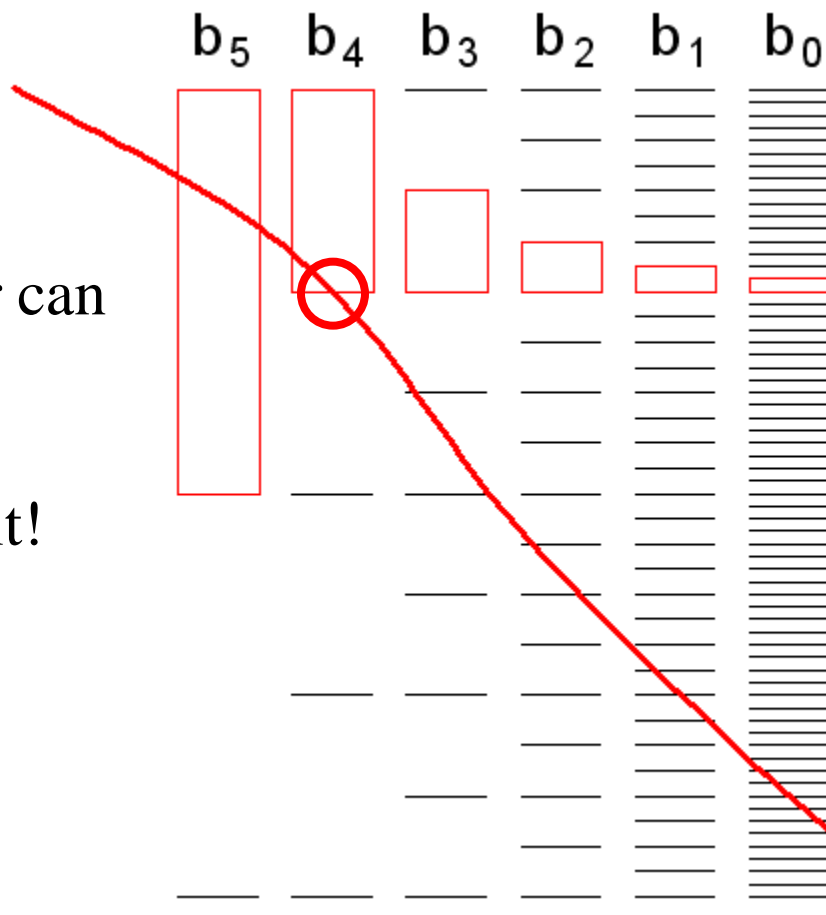
# What happens if the signal changes during conversion?

AD converter can not "undo" a previously determined bit!



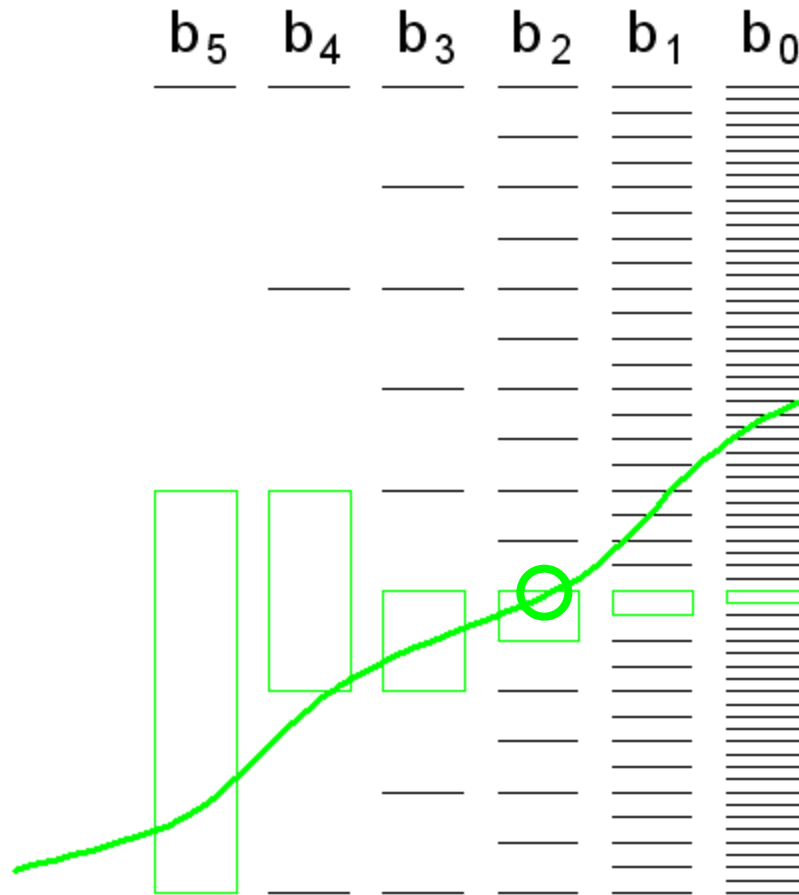The result is a value that has occurred during the conversion, but at an unspecified time!




## The problem

The time for the sampling is indeterminate!
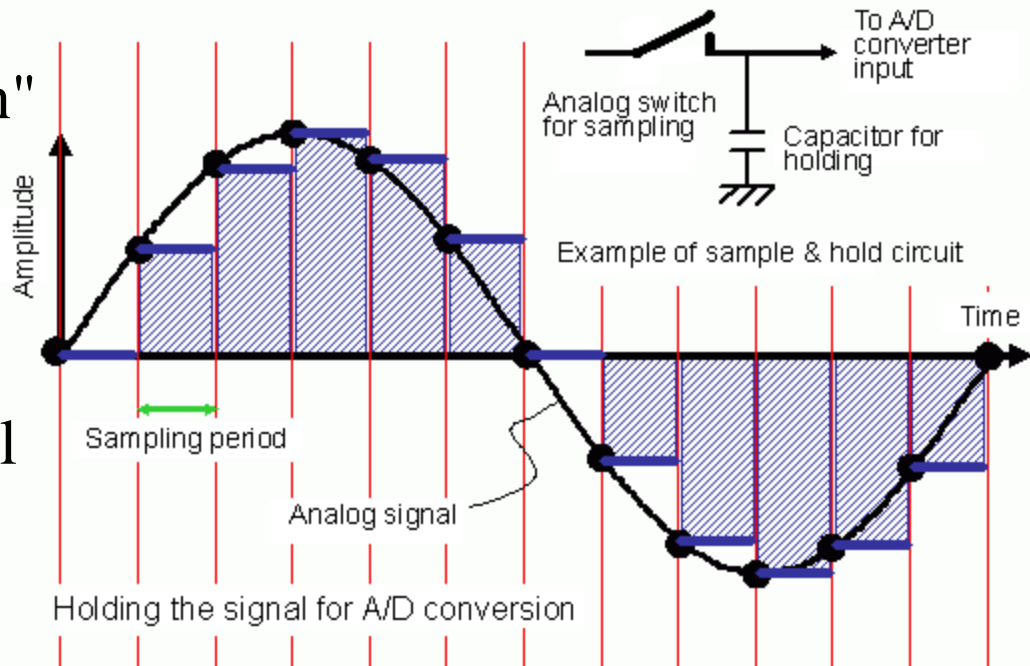
# Sample & Hold - circuit

The solution is that the analog signal is "frozen" during the conversion.

At the AD conversion start a switch is taking a "sample" of the signal and stores it in a capacitor.




The course PIC processor, the sampling capacitor has capacitance  $\approx 10\text{pF}$ .




# Acquisition time $t_{ACQ}$

Every time one has **chosen/changed channel** the **sampling capacitor**  $C_{HOLD}$  must have time to recharge to the analog voltage. **This will take about 5  $\mu$ s.**

## ANALOG INPUT MODEL

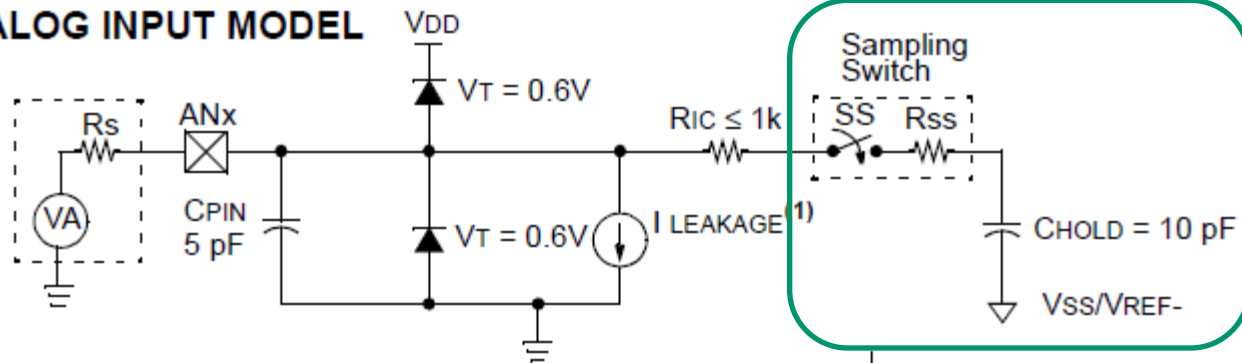

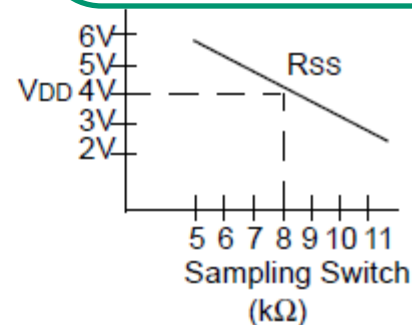**Legend:** CPIN = Input Capacitance  
VT = Threshold Voltage  
I LEAKAGE = Leakage current at the pin due to various junctions  
RIC = Interconnect Resistance  
SS = Sampling Switch  
CHOLD = Sample/Hold Capacitance



A 5  $\mu$ s delay can simply be programmed as:

```
nop2(); nop2(); nop(); /* 5 us 4 MHz clock */;
```

# AD-clock pulses

AD-converter can use a maximum clock frequency of 250 kHz. If the PIC processor clock is **4 MHz** this must first be divided 16 times before it can be used as AD-clock. This frequency divider is provided.

REGISTER 9-2: ADCON1: A/D CONTROL REGISTER 1

|       |       |       |       |     |     |     |       |
|-------|-------|-------|-------|-----|-----|-----|-------|
| U-0   | RW-0  | RW-0  | RW-0  | U-0 | U-0 | U-0 | U-0   |
| —     | ADCS2 | ADCS1 | ADCS0 | —   | —   | —   | —     |
| bit 7 |       |       |       |     |     |     | bit 0 |

**ADCS<2:0>**: A/D Conversion Clock Select bits

000 = FOSC/2

001 = FOSC/8

010 = FOSC/32

x11 = FRC (clock derived from a dedicated internal oscillator = 500 kHz max)

100 = FOSC/4

101 = FOSC/16

110 = FOSC/64

**ADCON1=0b0.101.0000;**

$$1010000_2 = 80_{10} \quad T_{AD} = 4\mu\text{s} \quad f_{AD} = 500\text{kHz}$$

# Start AD and wait for done

REGISTER 9-1: ADCON0: A/D CONTROL REGISTER 0

|       |       |       |       |       |       |         |       |
|-------|-------|-------|-------|-------|-------|---------|-------|
| R/W-0 | R/W-0 | R/W-0 | R/W-0 | R/W-0 | R/W-0 | R/W-0   | R/W-0 |
| ADFM  | VCFG  | CHS3  | CHS2  | CHS1  | CHS0  | GO/DONE | ADON  |
| bit 7 |       |       |       |       |       |         | bit 0 |

Start AD-  
conversion:


```
GO = 1;
```

Wait for AD-  
conversion done:

```
while(GO) ;
```

# AD-conversion takes time

FIGURE 9-2: ANALOG-TO-DIGITAL CONVERSION  $T_{AD}$  CYCLES

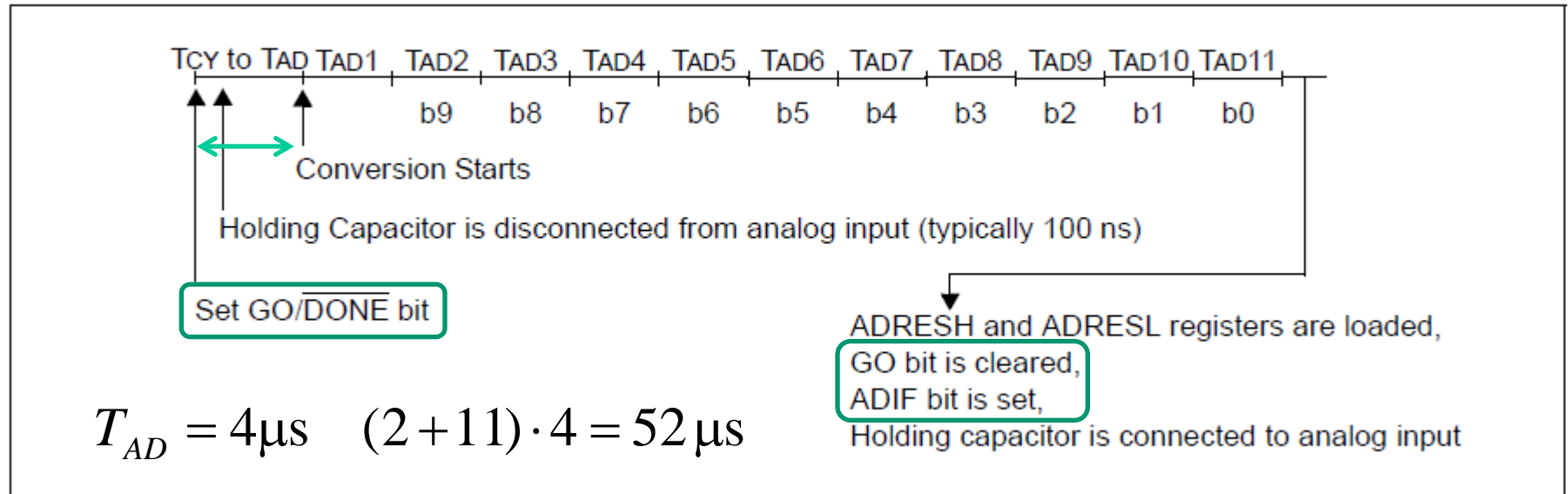

The conversion takes approximately 2 + 11 AD clock pulses. If one ignores the fact that the PIC processor must do something (?) With the AD-converted value (which also takes time), then the theoretically maximum sampling rate becomes:

$$f_{S \max} = \frac{1}{52\mu\text{s}} = 19,2 \text{ kHz}$$

# AD-conversion takes time

If one converts alternating two channels (stereo?) then there will also be the setting time of sampling capacitor  $T_{ACQ} = 5 \mu\text{s}$ .

$$f_{S_{\max}} = \frac{1}{52 + 5 + 52 + 5 [\mu\text{s}]} = 8,8 \text{ kHz}$$

The PIC processor can handle most industrial control processes - but it is of course totally inadequate as a "signal processor" for sound effects!

# Many setup possibilities

**TABLE 9-2: SUMMARY OF ASSOCIATED ADC REGISTERS**

| Name   | Bit 7                         | Bit 6  | Bit 5  | Bit 4  | Bit 3  | Bit 2  | Bit 1   | Bit 0  | Value on POR, BOR | Value on all other Resets |
|--------|-------------------------------|--------|--------|--------|--------|--------|---------|--------|-------------------|---------------------------|
| ADCON0 | ADFM                          | VCFG   | CHS3   | CHS2   | CHS1   | CHS0   | GO/DONE | ADON   | 0000 0000         | 0000 0000                 |
| ADCON1 | —                             | ADCS2  | ADCS1  | ADCS0  | —      | —      | —       | —      | -000 ----         | -000 ----                 |
| ANSEL  | ANS7                          | ANS6   | ANS5   | ANS4   | ANS3   | ANS2   | ANS1    | ANS0   | 1111 1111         | 1111 1111                 |
| ANSELH | —                             | —      | —      | —      | ANS11  | ANS10  | ANS9    | ANS8   | ---- 1111         | ---- 1111                 |
| ADRESH | A/D Result Register High Byte |        |        |        |        |        |         |        | xxxx xxxx         | uuuu uuuu                 |
| ADRESL | A/D Result Register Low Byte  |        |        |        |        |        |         |        | xxxx xxxx         | uuuu uuuu                 |
| INTCON | GIE                           | PEIE   | T0IE   | INTE   | RABIE  | T0IF   | INTF    | RABIF  | 0000 000x         | 0000 000x                 |
| PIE1   | —                             | ADIE   | RCIE   | TXIE   | SSPIE  | CCP1IE | TMR2IE  | TMR1IE | -000 0000         | -000 0000                 |
| PIR1   | —                             | ADIF   | RCIF   | TXIF   | SSPIF  | CCP1IF | TMR2IF  | TMR1IF | -000 0000         | -000 0000                 |
| PORTA  | —                             | —      | RA5    | RA4    | RA3    | RA2    | RA1     | RA0    | --xx xxxx         | --uu uuuu                 |
| PORTB  | RB7                           | RB6    | RB5    | RB4    | —      | —      | —       | —      | xxxx ----         | uuuu ----                 |
| PORTC  | RC7                           | RC6    | RC5    | RC4    | RC3    | RC2    | RC1     | RC0    | xxxx xxxx         | uuuu uuuu                 |
| TRISA  | —                             | —      | TRISA5 | TRISA4 | TRISA3 | TRISA2 | TRISA1  | TRISA0 | --11 1111         | --11 1111                 |
| TRISB  | TRISB7                        | TRISB6 | TRISB5 | TRISB4 | —      | —      | —       | —      | 1111 ----         | 1111 ----                 |
| TRISC  | TRISC7                        | TRISC6 | TRISC5 | TRISC4 | TRISC3 | TRISC2 | TRISC1  | TRISC0 | 1111 1111         | 1111 1111                 |

**Legend:** x = unknown, u = unchanged, — = unimplemented read as '0'. Shaded cells are not used for ADC module.

# AD-conversion – step by step

1. Configure Port:
  - Disable pin output driver (See TRIS register)
  - Configure pin as analog (See ANSEL register).
2. Configure the ADC module:
  - Select ADC conversion clock (ADCON1, ADCS<2:0>).
  - Configure voltage reference (ADCON0, VCFG).
  - Select ADC input channel (ADCON0, CHS<3:0>).
  - Select result format (ADCON0, ADFM).
  - Turn on ADC module (ADCON0, ADON)
3. Start conversion set the GO/DONE bit. (ADCON0, GO)
4. Wait for ADC conversion to complete, polling the GO/DONE bit. (ADCON0, GO)
5. Read ADC Result (ADRESH, ADRESL)

William Sandqvist [william@kth.se](mailto:william@kth.se)