
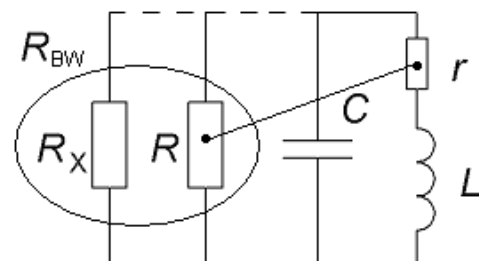
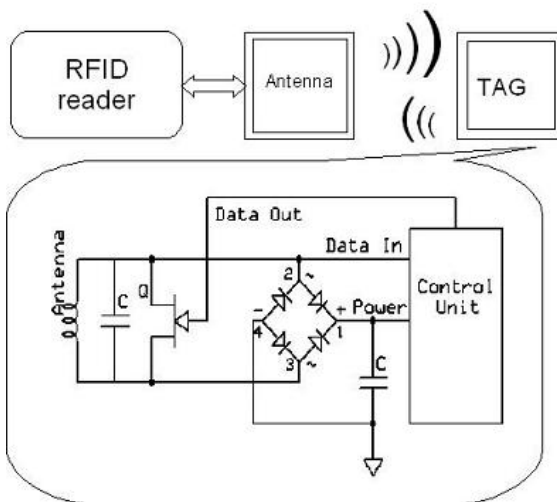
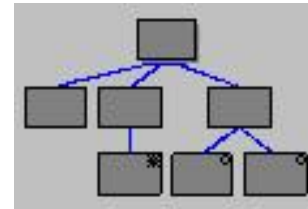
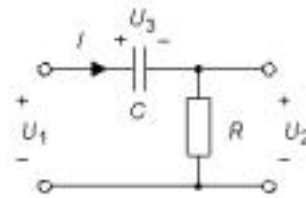


Embedded Electronics exercises

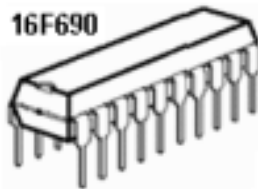


Equivalent resistance, Resistivity and resistor temperature depends, Serial – parallel circuits, Batteries, Kirchoff's current law/voltage law, Kirchoff's laws, Node analysis – potential, Thevenin and Norton Equivalents, Transients, Capacitance, Magnets – Inductance, Phasors, phasor charts $j\omega$ -method, Resonance, Filters, Transformer, Inductive coupling.

© William Sandqvist 2014

Equivalent resistance

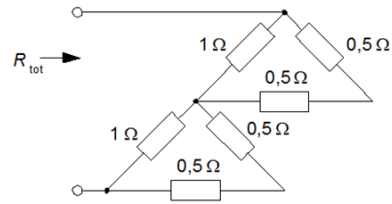1.1

How much will the equivalent resistance R_{tot} for this circuit be ?
(Given resistors with resistance values $1\ \Omega$ and $0,5\ \Omega$ connected as shown).



$$R_{tot} = ? \text{ [}\Omega\text{]}$$

1.2

How much will the equivalent resistance R_{tot} for this circuit be?


Given:

$$R_1 = 1\ \Omega$$

$$R_2 = 21\ \Omega$$

$$R_3 = 42\ \Omega$$

$$R_4 = 30\ \Omega$$

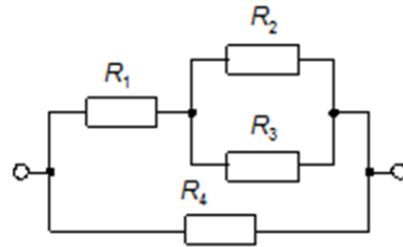


$$R_{tot} = ? \text{ [}\Omega\text{]}$$

1.3

How much will the equivalent resistance R_{ERS} for this circuit be.

$$R_1 = 1\ \Omega, R_2 = 4\ \Omega, R_3 = 6\ \Omega, R_4 = 1\ \Omega, R_5 = 2\ \Omega$$

$$R_{ERS} = ? \text{ [}\Omega\text{]}$$

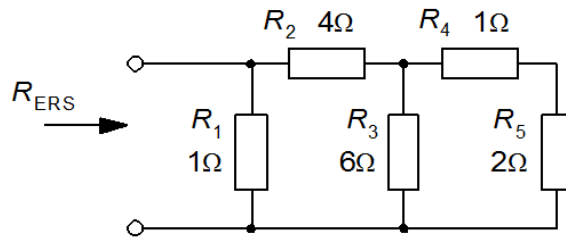


1.4

Calculate the equivalent resistance R_{ERS} for this circuit.


Resistors have the values $0,5\ \Omega$, $1,6\ \Omega$, $5,2\ \Omega$, $2,7\ \Omega$, $7\ \Omega$ and $3\ \Omega$.

$$R_{ERS} = ? \text{ [}\Omega\text{]}$$

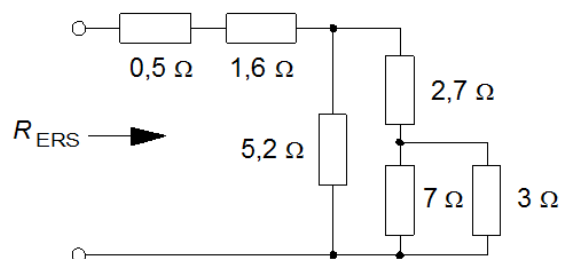

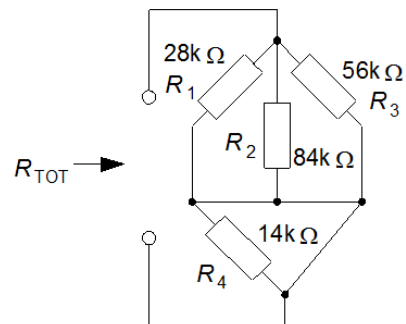
1.5

How much will the equivalent resistance R_{tot} for this circuit with 4 resistors?



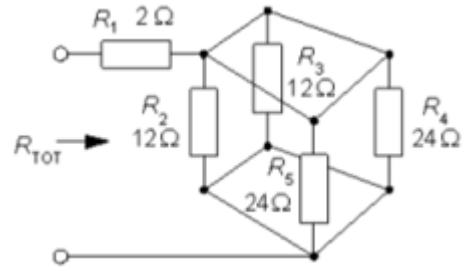
1.6

How much will the equivalent resistance R_{tot} for this circuit consisting of 5 soldered resistors?



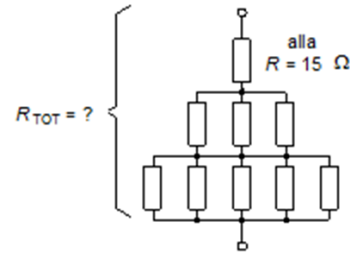
1.7

One builds a "pyramid" of resistors $R = 15 \Omega$. See the figure. How much will the equivalent resistance R_{TOT} be?



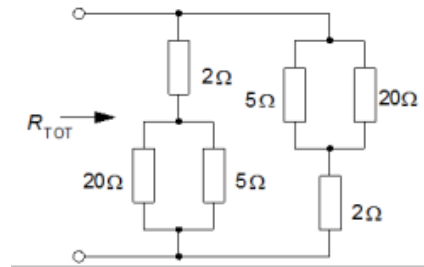
1.8

How much will the equivalent resistance R_{TOT} for this circuit with 6 resistors?
 $R_{TOT} = ? [\Omega]$




1.9

Set up an expression, and calculate the replacement resistance R_{tot} . (use || to denote the parallel connection).
 $R_1 = 2\Omega, R_2 = 20\Omega, R_3 = 2\Omega, R_4 = 6\Omega, R_5 = 6\Omega, R_6 = 4\Omega, R_7 = 3\Omega$.

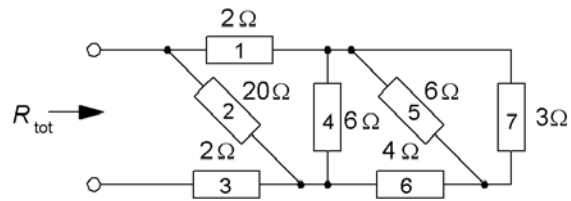



1.10

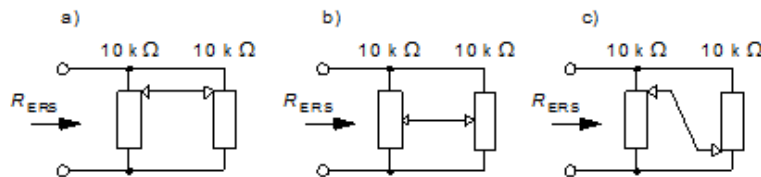

Two potentiometers with total resistance of $10 \text{ k}\Omega$ are connected as shown. How large is the replacement resistance when:

- a) both potentiometers are in the upper position. $R_{ERS} = ? [\Omega]$
- b) both potentiometers are in the middle position. $R_{ERS} = ? [\Omega]$
- c) one potentiometer is in the upper position, the other in the lower end position. $R_{ERS} = ? [\Omega]$

1.11

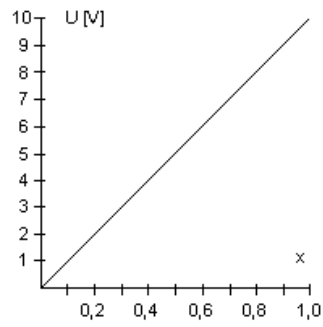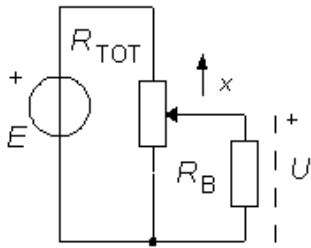

Potentiometer with total resistance $R_{TOT} = 10 \text{ k}\Omega$ is connected to a measuring instrument which has the internal resistance $R_B = 1 \text{ k}\Omega$. This is far too low load resistance, so the instrument draws current from the potentiometer sensor so that the linearity is lost.

The graph shows the ideal relationship between U and x . Sketch (rough) in the diagram how the deviation from the ideal curve will become. Suppose $E = 10 \text{ V}$ and that $0 < x < 1$.

Resistor resistivity and temperature dependency


2.1

How long is the cable? An electrical installation company usually give their trainees following mission – in the store is a large and heavy cable on a reel, how long is the cable?

A cable consists of two conductors. A leader and a return conductor. The two leaders in the cable end that is wrapped in the back of the roll has been stripped and twisted together. The second cable end is directly accessible. On the cable reel side are stamped conductors cross-sectional area $A = 2,5 \text{ mm}^2$.

The resistivity of copper $\rho = 0,018 \text{ } [\Omega\text{mm}^2/\text{m}]$.

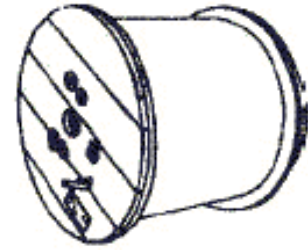(This number is known by hart of many in the electrical industry).




2.2

With a radiation thermometer one can measure temperature contactlessly. In order to check such a thermometer one directs it against a bright light bulb and then it showed the temperature $280 \text{ }^\circ\text{C}$. The bulb had a Wolfram Wire and were fed with voltage of 20 V . It consumed the current 0.11 A .

Previously, the cold lamp resistance had been measured at room temperature $22 \text{ }^\circ\text{C}$ to $98 \text{ } \Omega$. The temperature coefficient for Wolfram is $\alpha = 4,5 \cdot 10^{-3}$.

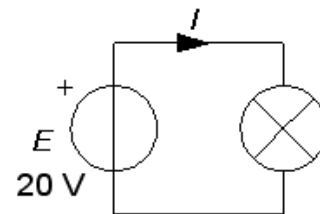Calculate the filament temperature of the lamp [$^\circ\text{C}$] and compare it to the temperature reading. Did the radiation thermometer showed the correct temperature value?



2.3


An immersion heater, with resistance $R = 50 \text{ } \Omega$ at room temperature $25 \text{ }^\circ\text{C}$, used in conjunction with an adjustable resistor R_1 , adjustable between 0 och $100 \text{ } \Omega$.

The heater resistance wire is made of nickel. Nickel has temperature coefficient $\alpha = 6,7 \cdot 10^{-3}$. The two resistors are connected to a stable voltage source $E = 12 \text{ V}$. See the figure.

a) One adjusts R_1 until the water begins to boil ($100 \text{ }^\circ\text{C}$). What is the value of the resistance R then? $R = ? \text{ } [\Omega]$

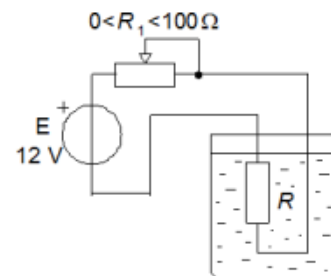
b) One measures $R_1 = 25 \text{ } \Omega$.

Which heating power is supplied to the water via R ? $P = ? \text{ } [\text{W}]$



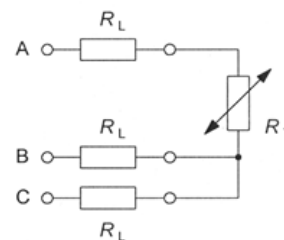2.4


Describe the principle of three terminal sensing.



Serial – parallel circuits

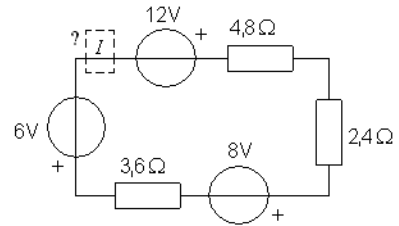
3.1

Determine the current I in magnitude and direction.



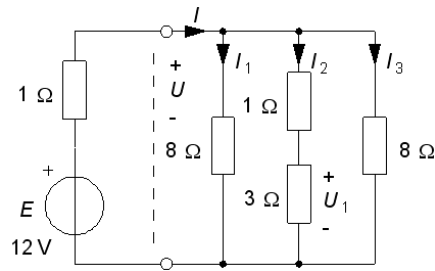
3.2

- Calculate the resultant resistance R_{RES} for the three parallel connected branches.
- Calculate current I and voltage U .
- Calculate the three currents I_1 , I_2 and I_3 and the voltage U_1 over 3 Ω-resistor.



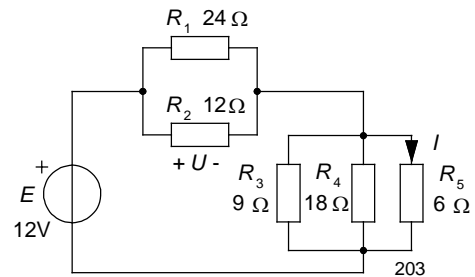
3.3

Calculate current I and voltage U for the serial-parallel circuit in the figure.



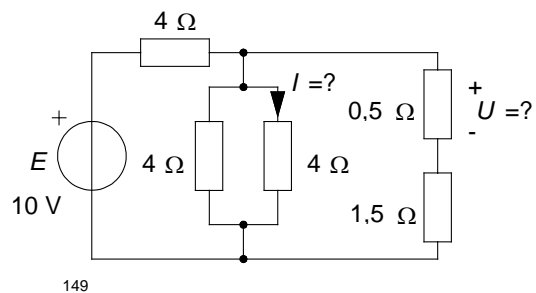
3.4

Calculate current $I = ?$ and voltage $U = ?$ for the serial-parallel circuit in the figure.



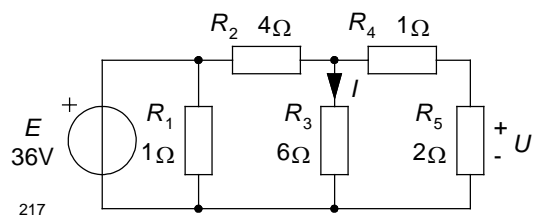3.5


Calculate current I and voltage U for the serial-parallel circuit in the figure.



3.6

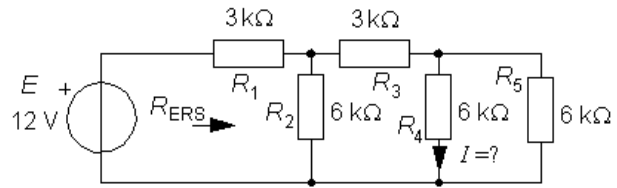- a) Set up an expression of, and calculate the replacement resistance R_{ERS} .
 b) Set up an expression, and calculate the current I .

$R_1 = 3 \text{ k}\Omega$ $R_2 = 6 \text{ k}\Omega$ $R_3 = 3 \text{ k}\Omega$
 $R_4 = 6 \text{ k}\Omega$ $R_5 = 6 \text{ k}\Omega$




Batteries

4.1

A battery has the capacity number $C_{20} = 60 \text{ Ah}$. The capacity number is based on laboratory measurements.

- a) How long time did the discharge last, and wich discharge current was used at this laboratory measurement?
 b) Suppose that the battery with the capacity number $C_{20} = 60 \text{ Ah}$ is used to a lap that consumes the current 1 A. How long will the battery last?
 c) Suppose that the battery runs a start motor with the current 300 A. How long will the battery last? (expect the capacity number to be reduced by 30% at this high current).

4.2

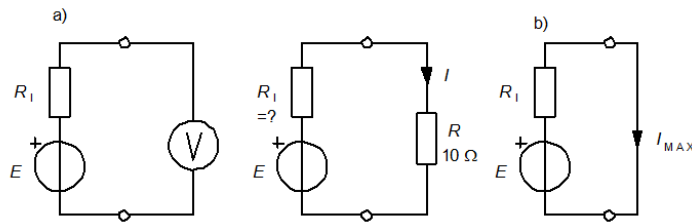

In order to determine a battery's internal resistance R_1 two measurements were made. see figure above to left.

First the battery emf was measured with a good voltmeter $E = 1,4 \text{ V}$, and then the battery was loaded with a resistor $R = 10 \Omega$ and then the current I through the resistor was measured to $I = 123 \text{ mA}$.


- a) What was the battery's internal resistance? $R_1 = ? [\Omega]$
 b) What is the maximum current I_{MAX} the battery could deliver if it was short circuited? $I_{MAX} = ? [\text{mA}]$

4.3

A battery-powered equipment is powered by a rechargeable battery. The battery consists of a number (n pieces) NiCad cells.

(The figure is simplified with only two of the n cells shown.)
The Cells has $E = 1,1 \text{ V}$ and $R_i = 0,2 \Omega$. The capacity number for each cell is $C = 3000 \text{ mAh}$.

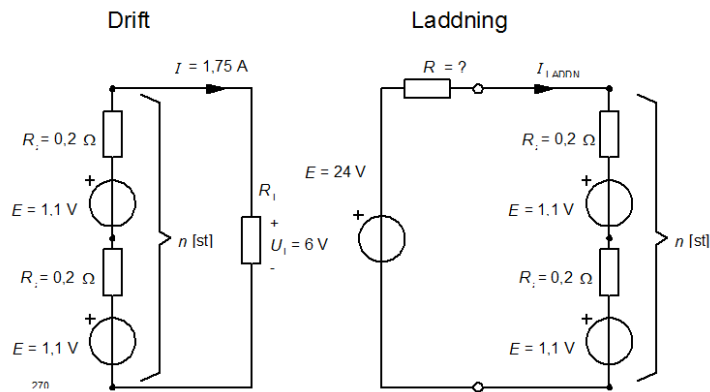The equipment consumes 1.75 A at 6 V , how many cells are needed?



a) $n = ?$

The battery is charged from a 24 V battery. What a charging current I_{LADDN} should you have if you want the battery to be charged rapidly in an hour? (From empty to full, assuming that the cell E is constant during charging).

b) $I_{\text{LADDN}} = ?$

What value should R have in order to receive this charging current?


c) $R = ?$

4.4

Three similar batteries $E = 10 \text{ V}$ and internal resistance 6Ω are connected in parallel to supply current to a resistor with resistance 2Ω .

a) How great will current I and voltage U be?


$I = ? \text{ [A]}$
 $U = ? \text{ [V]}$

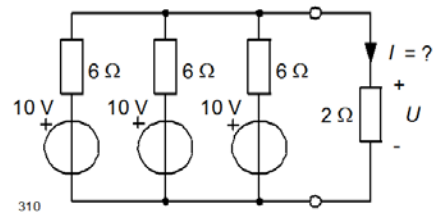

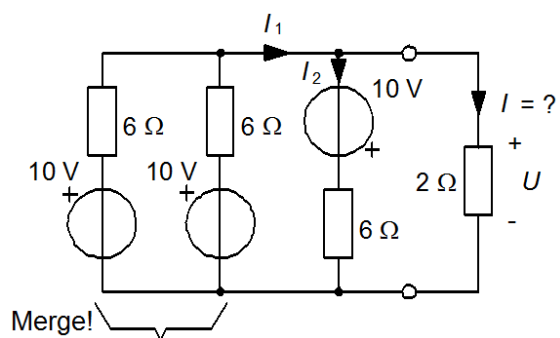b) Accidentally one happens to turn one of the batteries wrong. Use Kirchoff's laws to determine the currents I_1 , I_2 , and I magnitude and direction (sign). Determine U .

The task is simplified if you "merge" the two of the batteries to one battery in a similar way as in a.


$I_1 = ? \text{ [A]}$
 $I_2 = ? \text{ [A]}$
 $I = ? \text{ [A]}$
 $U = ? \text{ [V]}$



Kirchoff's current law and voltage law

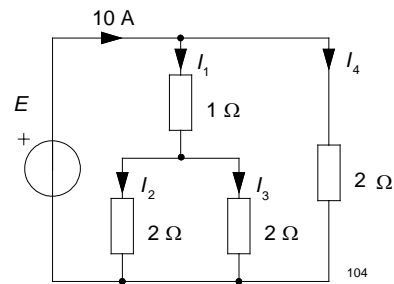5.1


Calculate the four currents I_1 , I_2 , I_3 och I_4 .



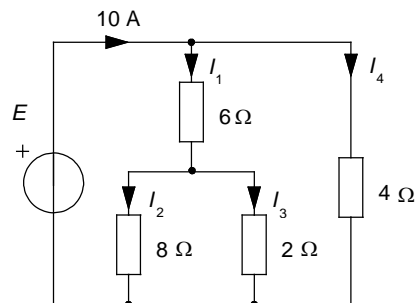5.2


We know that the current I from, E , to circuit is 10 A. How big are the currents I_1 , I_2 , I_3 , I_4 ? What value has E ?

- $I_1 = ?$
- $I_2 = ?$
- $I_3 = ?$
- $I_4 = ?$
- $E = ?$



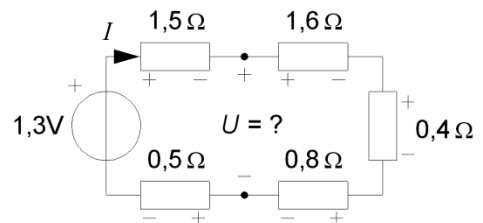5.3

Use Kirchoff's voltage law to calculate $U = ?$



Kirchoff's laws, equation system


6.1

Use Kirchoff's laws to determine the three currents amount and direction (sign).

$$I_1 = ?, I_2 = ?, I_3 = ?.$$

An interpretation of the circuit:

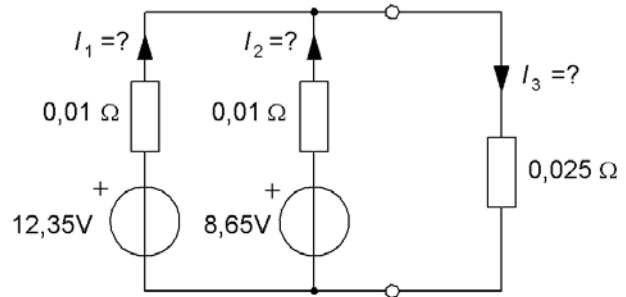A car owner parallel connects his poor battery (8,65V) with a borrowed good battery (12,35V) to boost the starter motor (0,025Ω) a cold winter day. Having solved the task do you know if he had any advantage of the poor battery?



6.2

Use Kirchoff's laws to determine the three currents I_1 , I_2 , and I_3 their amount and direction (sign)..

Given:

$$E_1 = 5V \quad R_1 = 1 \Omega$$

$$E_2 = 21V \quad R_2 = 2 \Omega$$


$$E_3 = 4V \quad R_3 = 2 \Omega$$

$$R_4 = 15 \Omega$$

$$I_1 = ? \text{ [A]}$$

$$I_2 = ? \text{ [A]}$$

$$I_3 = ? \text{ [A]}$$

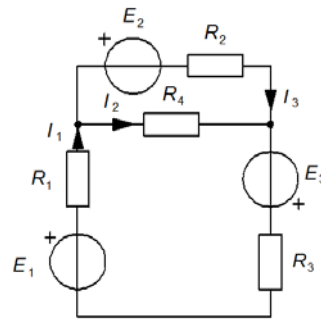


6.3

Use Kirchoff's laws to

a) Determine the voltage across R_2 (18Ω resistor).


b) Determine the current I_2 to the amount and direction.

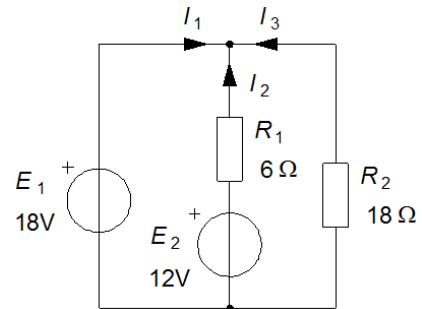c) Determine the current I_1 to the amount and direction.



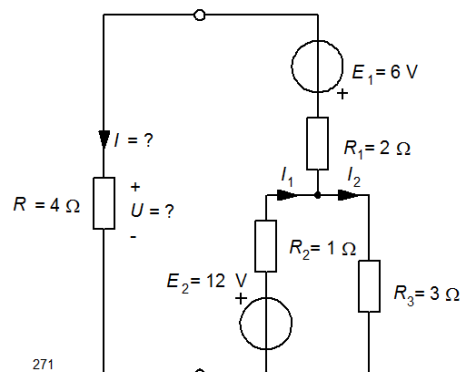6.4

Use Kirchoff's laws to determine the current I 's and the voltage U 's sizes and directions (sign).




6.5

a) Use Kirchoff's two laws to set up an equation system by which the three currents I_1 , I_2 and I_3 can be calculated. (You need not solve the system of equations)

If equationsystem is solved one gets:

$$I_1 = 1,87 \quad I_2 = -10,4 \quad I_3 = 8,55 \text{ [A].}$$

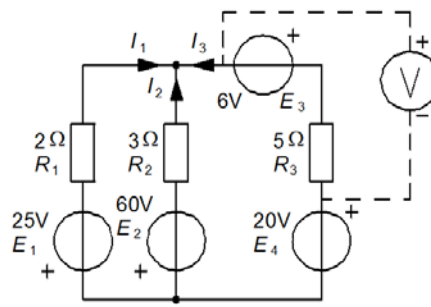b) What does the voltmeter at the right in the figure show (give both amount and sign) [V]?




6.6

Use Kirchoff's laws to calculate the currents I_1 , I_2 , and I_3 to magnitude and direction (sign).

$$I_1 = ? \text{ [A]}$$

$$I_2 = ? \text{ [A]}$$

$$I_3 = ? \text{ [A]}$$

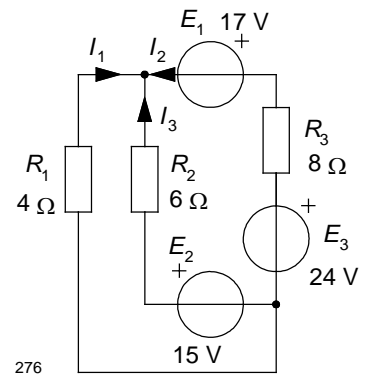


Potential, nodal analysis, depending generators

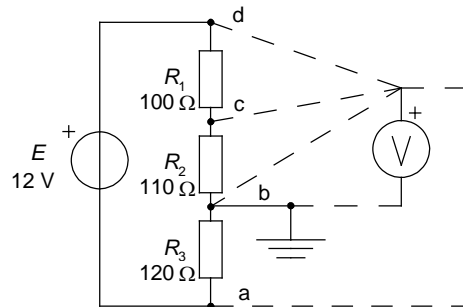7.1

A voltage divider consists of three resistors $R_1 = 100 \Omega$, $R_2 = 110 \Omega$, $R_3 = 120 \Omega$, it is fed with an emf $E = 12 \text{ V}$. One measures the potential (the voltage relative to ground) at the different sockets of the voltage divider.

Voltmeter negative terminal is all the time connected to the socket b, ground, while the voltmeter positive terminal median voltmeters pluspol in turn connected to the sockets a, b, c, and d.




What will voltmeter show? Fill in the table below.

Socket	a)	b)	c)	d)
Voltmeter [V]				

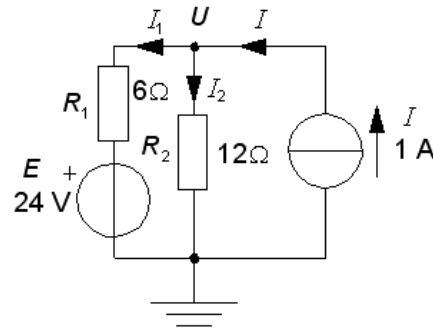
7.2

Use node analysis to calculate the currents I , I_1 , and I_2 .



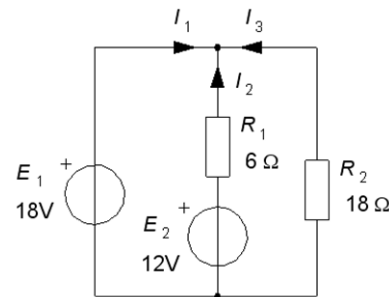7.3

Use nodal analysis to determine the currents I_1 , I_2 och I_3 to magnitude and direction.




7.4 Depending generator

Use Kirchoff's laws to determine the three currents amount and direction (sign).

$I_1=?$, $I_2=?$, $I_3=?$.


Note that E is a dependent emf.

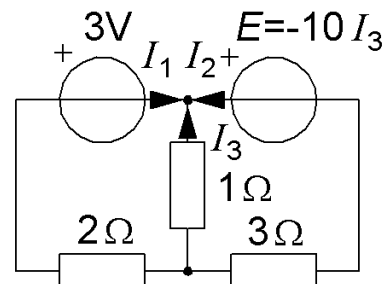The dependent emf E depends on the current through the 1Ω resistor according to the relationship $E = -10 \cdot I_3$.




Thevenin and Norton Equivalent circuits

8.1

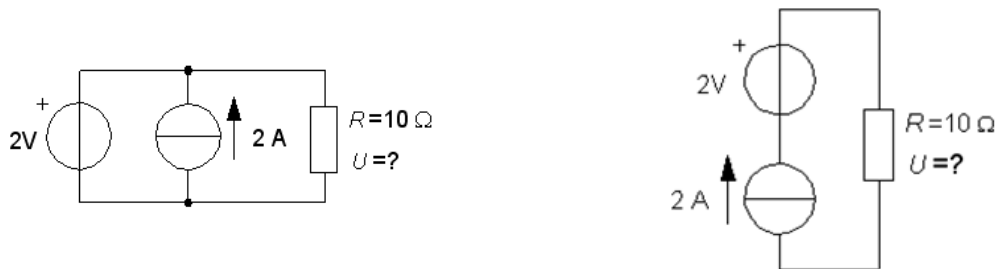

What value should voltage U get in these idealized and usually unrealistic circuits?


8.2

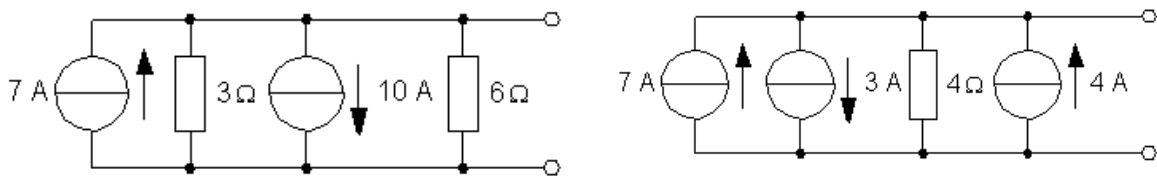


Simplify the circuits.

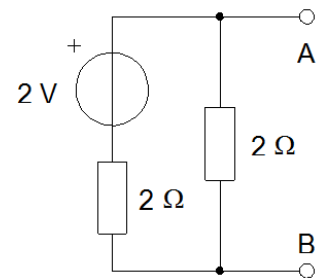8.3

Replace the given two port circuit with a simpler one having an emf in series with a resistor.




8.4

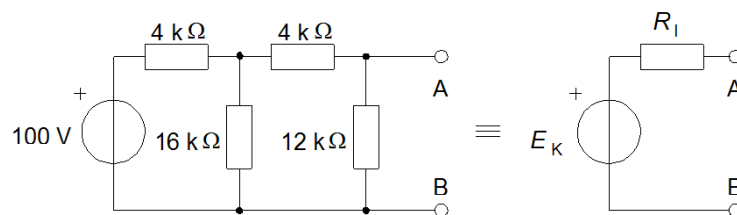

- Determine the voltage between A and B (the open circuit voltage).
- Determine the current that would go through a conductor with very little resistance, if it is connected directly between A and B in the figure (the so-called short-circuit current.)
- Determine a circuit consisting of an emf E_K in series with a resistor R_1 (according to figure) which is equivalent to the given circuit if viewed from points A and B.
- Determine the maximum power which can be obtained in a resistor connected between points A and B. (Use the result from task c.)

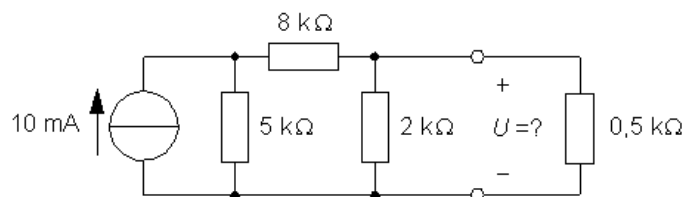8.5


Use Norton and Thevenin equivalents to gradually reduce the circuit, and then calculate the voltage $U = ?$




8.6

a) Develop an Thévenin equivalent, E_0 R_I , to the circuit with the two voltage sources (7V) and current source (12 mA).

$E_0 = ?$ [V] $R_I = ?$ [k Ω]

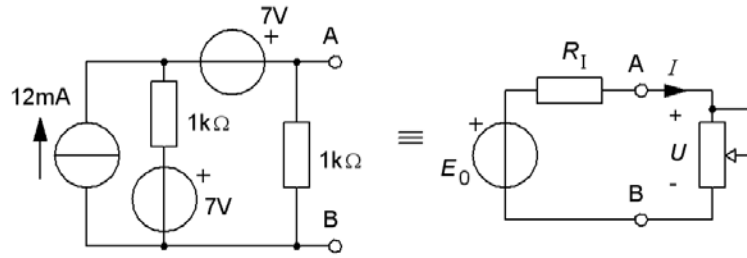


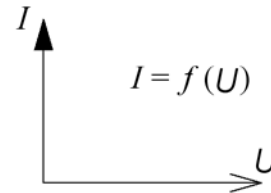b) The circuit AB is connected to a variable resistor. One measures voltage and current to draw the circuit's characteristic curve I as a function of U . Draw this graph. grade axes.




8.7 superposition

Use superposition to solve $I = ?$.

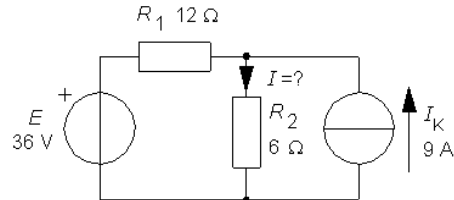


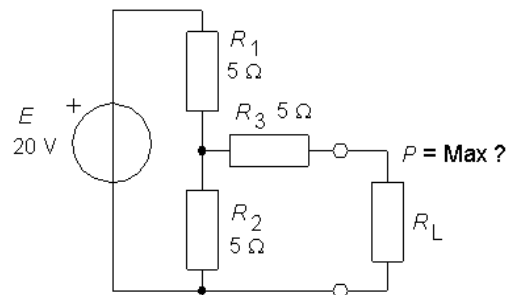8.8

Choose the load resistor R_L to dissipate the maximum power.
How big is this power?




8.9

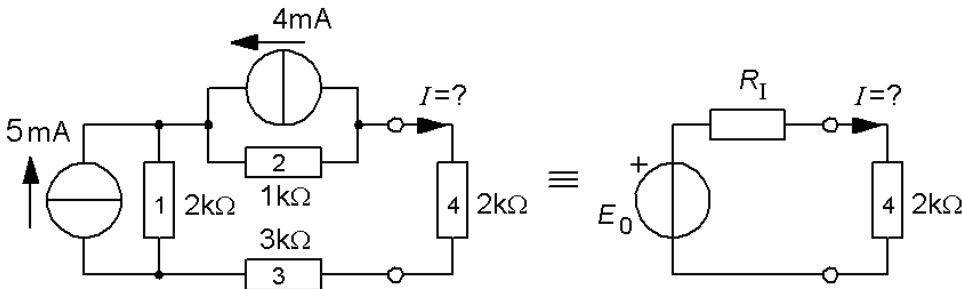

a) Develop the equivalent Thévenin circuit, E_0 R_I , to the net with the two current sources.


b) Then calculate what current I one would get if a resistor $R_4 = 2$ k Ω is connected to the original (or equivalent) net.

8.10

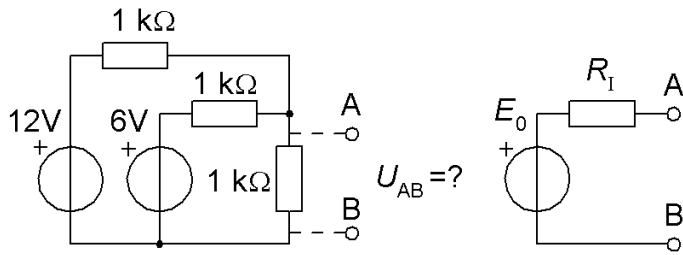

- Develop the equivalent Thévenin circuit, $E_0 R_I$, to the circuit with the two emf and the three resistors.
- How big is the voltage drop U_{AB} over $1\text{ k}\Omega$ resistor in the original circuit?

8.11

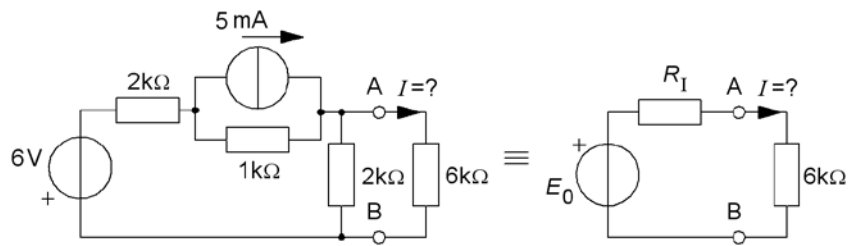


- Develop the equivalent Thévenin circuit, $E_0 R_I$, to the circuit with the voltage source and the current source and the three resistors. ($6\text{ k}\Omega$ resistor is not included in the circuit)
- How large current would flow in a $6\text{ k}\Omega$ resistor if it is connected between A-B? Calculate current I magnitude and direction (positive current direction defined in the figure).

Capacitance, magnetism, inductance

9.1

The figure shows a principle view of a camera flash.

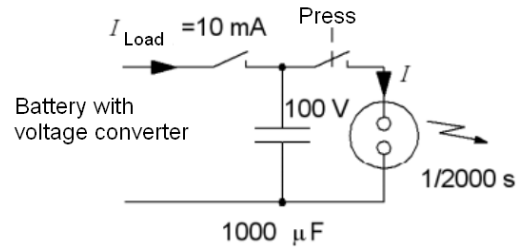- a) How much electrical energy is stored in the capacitor W ?
- b) How big is the charge in capacitor Q ?
- c) How big is the lightning current (mean value) I ?
- d) How big is the power during flash discharge P ?
- e) How long must you wait for the next flash t_{Load} ?



9.2

The backup capacitors of the type "Supercap" can be used as a power backup for memories - if one for example needs to move the phone from one room to another without the phone forgetting its settings.


Make a rough estimate of how long the charge on the capacitor will last? Assume that $C = 1$ F and U is initially 5V. The equipment draws $I = 10$ mA and operates down to 2.5V.

9.3

Two capacitors are parallel-connected. What about equivalent capacitance and rated voltage?

$$C_1 = 4 \mu\text{F } 50\text{V}$$

$$C_2 = 2 \mu\text{F } 75\text{V}$$

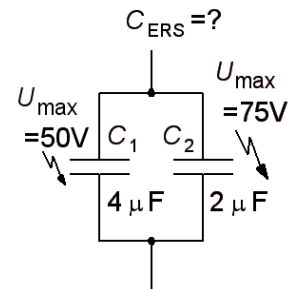


9.4

Two capacitors are connected in series. Calculate the equivalent capacitance and specify how the voltage is divided between the capacitors.

$$E = 10 \text{ V}$$

$$C_1 = 6 \mu\text{F}$$

$$C_2 = 12 \mu\text{F}$$

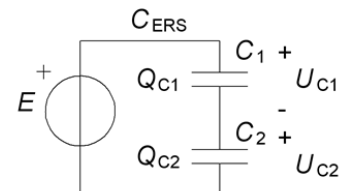


9.5

Three permanent magnets are placed in a row as shown. Draw the magnetic force lines in the figure. Mark with arrows the magnetic field direction.



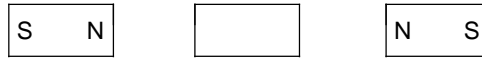
9.6

Two permanent magnets are placed on either side of an equally large piece of metal. See Fig. The metal piece, in the center, is of a material having permeability $\mu_r = 1$. Draw the magnetic force lines in the figure. Mark with arrows the magnetic field direction.



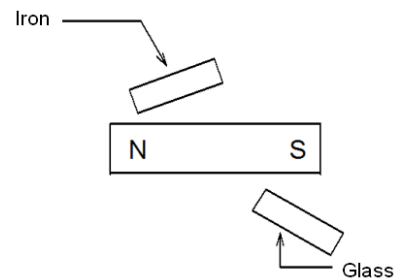9.7


Sketch the magnet's field lines in the figure, and how these are affected by the iron piece and the glass piece in the magnet proximity. Also mark the direction of the field.



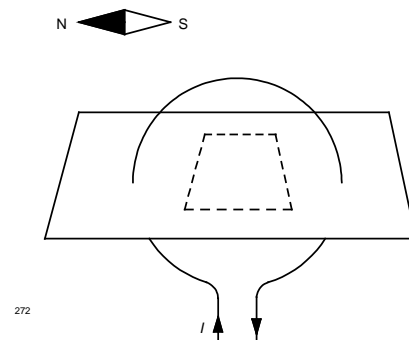9.8


A copper wire is formed as a loop through a paper. See the figure. Through the loop, a current of a few Amperes flows in the direction of the arrows.

- Draw the magnetic field (the magnetic lines of force) around the wires in the plane of the paper. Mark field direction of arrows.
- Assume that a compass needle is placed in the hatched area on the paper. Draw how the compass needle will align itself in the magnetic field of the wire loop.



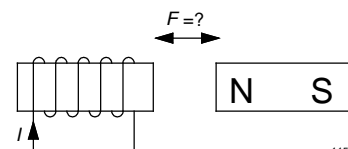9.9

A current is flows through the coil. Amagnet is nearby outside the coil. See the fig. Wich direction has the resulting force F , is it attractive or repulsive?




115a

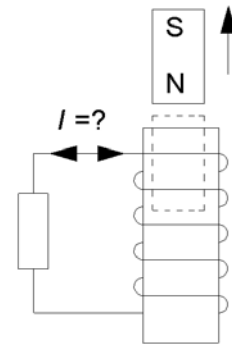
9.10

Lens law.

We draw out the magnet (as a cork from a bottle) from the coil. Which direction will the current I have?



9.11

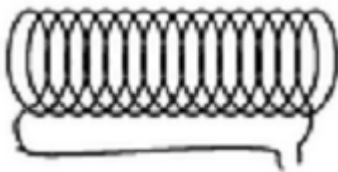

$$L = \frac{N^2 \cdot \mu \cdot A}{l} \quad K = \frac{\mu \cdot A}{l} \quad L = K \cdot N^2$$


Suppose that a coil is wound with $N = 100$ turns and then have the inductance 1 H. How many turns has to be unwound if you want to change the coil so that the inductance becomes $\frac{1}{2}$ H?

Transients with RC and L/R

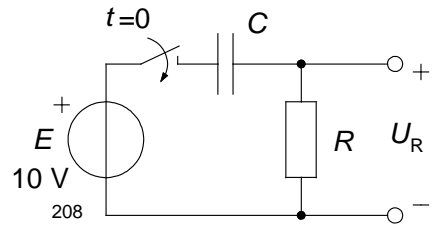10.1

At time $t = 0$ the contact between voltage source $E = 10 \text{ V}$ and the capacitor $C = 500 \text{ } \mu\text{F}$ which is series connected to the resistor $R = 500 \text{ } \Omega$.


- How long time will it take for the voltage across the resistor $U_R = 2 \text{ V}$?
- After how long time will the voltage across the capacitor be 2 V ?



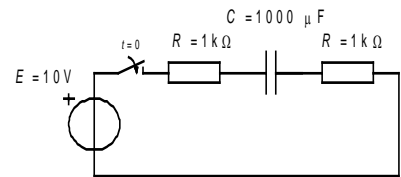10.2

A capacitor $C = 1000 \text{ } \mu\text{F}$ is connected in series with two resistors with the resistance $R = 1 \text{ k}\Omega$. At time $t = 0$ a voltage source with the constant voltage $E = 10 \text{ V}$ is connected to the circuit.


At what time ($t = ?$) has the three components the same voltage across them?



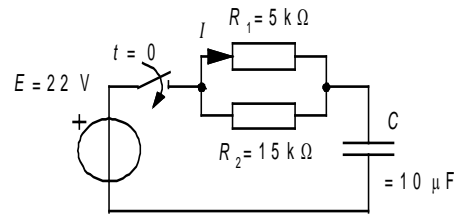10.3

A capacitor, $C = 10 \text{ } \mu\text{F}$, is charged from a constant voltage source $E = 22 \text{ V}$. The charging current is limited by two parallel connected resistors $R_1 = 5 \text{ k}\Omega$ and $R_2 = 15 \text{ k}\Omega$. The charging is started by the switch closing at time $t = 0$.


- What time constant τ has the circuit during the charge?
- How long time will it take until the current I through R_1 has passed below 3 mA ?



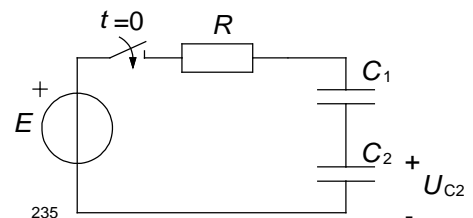10.4

Two serial connected capacitors, $C_1 = 25 \text{ } \mu\text{F}$ and $C_2 = 15 \text{ } \mu\text{F}$, are charged from a constant voltage source $E = 15 \text{ V}$. The charging current is limited by a resistor $R = 330 \text{ k}\Omega$. The charge is started by the switch closed at time $t = 0$.


- What time constant τ has the circuit during charge?
- How long will it take before the voltage U_{C_2} reaches 2 V ?



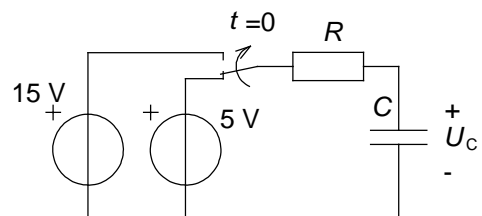10.5

Before time $t = 0$ is the capacitor via a switch connected to $+5 \text{ V}$. At the time $t = 0$ the switch is changed and the capacitor will be connected to $+15 \text{ V}$. Suppose $R = 2000 \text{ } \Omega$ and $C = 1000 \text{ } \mu\text{F}$.


- How long will it take after $t = 0$ for voltage U_C to reach $+10 \text{ V}$?
- How long time after $t = 0$ do you estimate it will take for current through R to cease? (For a technician less than 1% is nothing.)



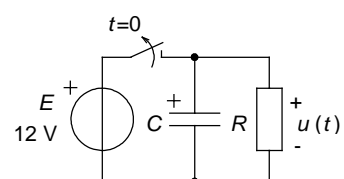10.6

before time $t = 0$ a constant voltage $E = 12 \text{ V}$ is connected to R and C . At time $t = 0$ the connection to the voltage E is removed. Suppose $R = 110 \text{ } \Omega$ and that $C = 10000 \text{ } \mu\text{F}$.


- How long time will it take after $t = 0$ for the voltage $u(t)$ across the resistor to drop to 2 V ?
- How long time after $t = 0$ do you estimate it will take for current through R to cease? (For a technician less than 1% is nothing.)



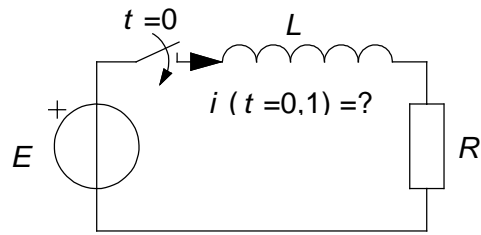10.7

A coil with inductance $L = 0,8 \text{ H}$ and the internal resistance $R = 12 \Omega$ is connected to a constant voltage source $E = 12 \text{ V}$ with a switch. At time $t = 0$ the switch is closed.


- What value will the current i through the circuit have after one tenth of a second? $i(t = 0,1) = ? \text{ [A]}$
- What value will the current have after one tenth of a second if R would be twice as large $R = 2 \cdot 12 = 24 \Omega$? $i_{2R}(t = 0,1) = ? \text{ [A]}$



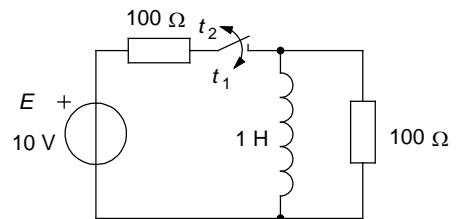10.8



E is a constant voltage source. At time t_1 the switch is closed.

- How large is the current through the coil in the first moment?
 - How large is the current through the coil after a long time?
- Later, at time t_2 the switch will be opened.
- Write down the expression for the current through the coil as a function of time t for the time after t_2 . (Suppose that the switch is opened at time $t = t_2 = 0$).



166

10.9

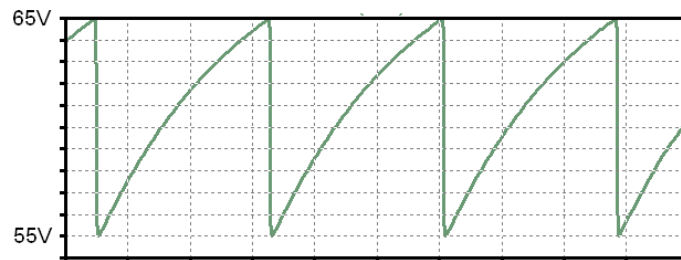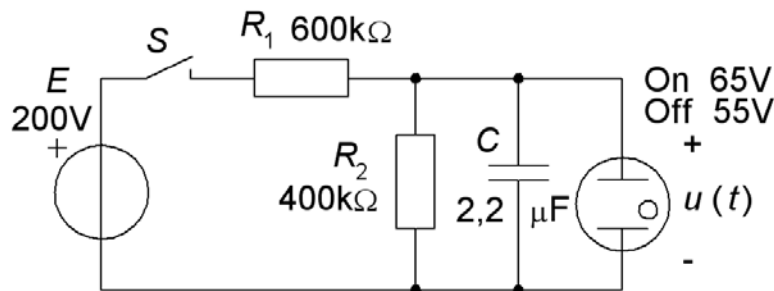


$E = 200\text{V}$ $R_1 = 600\text{k}\Omega$ $R_2 = 400\text{k}\Omega$ $C = 2,2\mu\text{F}$ On 65V Off 55 V


The circuit above flashes with a **neon lamp** (this was a common component at the time before the LEDs). Capacitor is charged. Neon lamp will "ignite" when the voltage across it reaches 65 V. It will quickly discharge the capacitor to 55 V, and then the light will "go off".

- From the beginning the capacitor is discharged. Calculate how long time it will take, after having hit the switch S , until the first light pulse will appear.
- Then the circuit will flash at a constant rate, see the oscilloscope-graph. Calculate how long time there will be between the flashes?
- Suppose one **removes** the resistor R_2 from the circuit. How long time will it then be between the flashes?

10.10

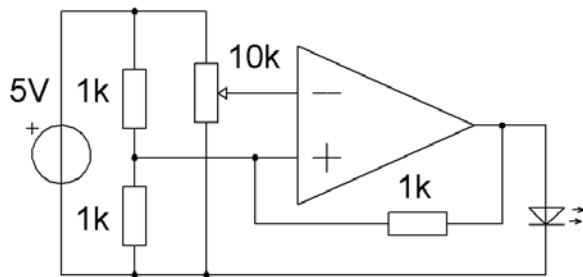

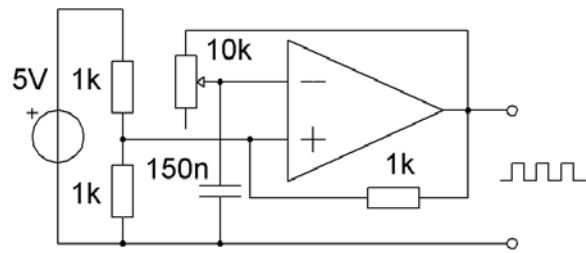a) Calculate the Schmitt trigger trig levels.



b) Calculate the Schmitt trigger oscillator frequency. The potentiometer is set to $R = 5k$.

10.11

A resistance thermometer is used for measuring the temperature of the surface of an internal combustion engine.


When the engine is hot one measures 176Ω , and when the engine has cooled down for 10 minutes one measures 139Ω . After a long time (very long) the engine will be cooled down to ambient temperature which is measured to be 25°C .

The temperature $\vartheta [^\circ \text{C}]$ during cool down follows an exponential function with a time constant τ , use the "equation for exponential changes".

For the resistance thermometer (with platinum) has the relationship:

$$R(\vartheta) = 100 \cdot (1 + 3,85 \cdot 10^{-3} \cdot \vartheta) [\Omega]$$

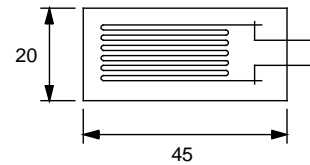- Determine the time constant for cool down.
 $\tau = ?$ [minutes]



Alternating voltage and current, phasors


11.1

A sinusoidal entity has the maximum value A 6,0 and becomes 0 2000 times per second. The time $t = 0$ is chosen so that the entity at that time has the value 3,0 and is rising towards 6,0. State the entity

- mathematically
- wave graph
- phasor

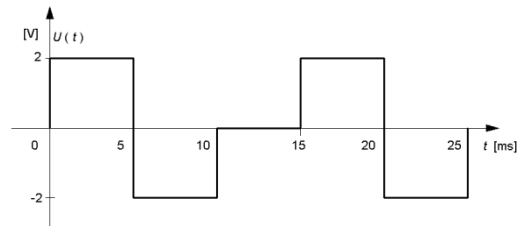11.2

Calculate for this periodic alternating voltage its rms value – which is the equivalent DC voltage that would produce the same effect in a resistor.




11.3

What is the relationship between the amplitude, the peak value and the RMS value of a sine voltage?

Phasor charts

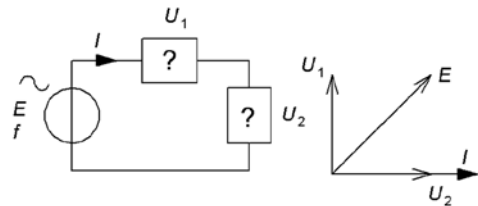
11.4

Identify what components that have given the voltage phasors U_1 and U_2 .



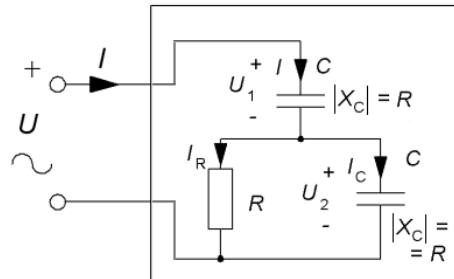11.5


Draw the phasor chart with all volages and currents for this circuit. Estimate the impedance Z as the ratio between the lengths of U och I . Estimate the impedance phase angle φ as the angle between U and I phasors.



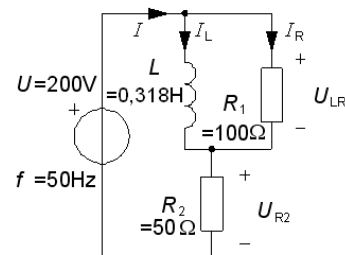11.6

The circuit of the figure is supplied with a sinusoidal alternating voltage $U = 200$ V, $f = 50$ Hz. The solenoid has the inductance $L = 0,318$ H and the two resistors $R_1 = 100$ Ω and $R_2 = 50$ Ω .

- Calculate X_L .
- Draw the phasor chart for this circuit. The phasor chart shall contain U , U_{LR} , U_{R2} , I , I_L , I_R . Suggestion: use U_{LR} as the reference phase (horizontal, angle 0°). Phasor lengths must be at least a rough, proportionate. Mark angle φ in the phasor chart, the angle between I and U .




11.7

Draw the phasor chart for the circuit in the figure. At the actual frequency applies that $|X_C| = R$ and $|X_L| = R/2$.

The phasor chart should contain U U_1 U_2 I I_R I_C .

Mark angle φ in the phasor chart, the angle between I and U .

U_2 is a suitable reference phase.

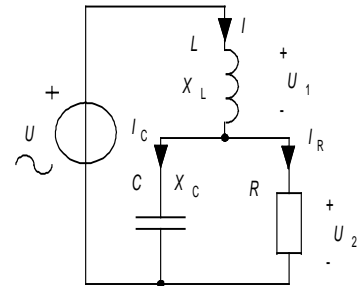


11.8

The figure shows a voltage divider. This is fed with an alternating voltage U_1 and the output voltage is U_2 . At the actual frequency applies that $|X_L| = 2R$.

Draw the phasor with I_1 , U_1 och U_2 .

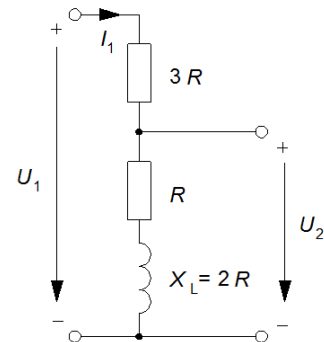Use I_1 as reference phase (= horizontal). (Strive to get the right proportions of phasors)




Alternating voltage and current, $j\omega$ -method

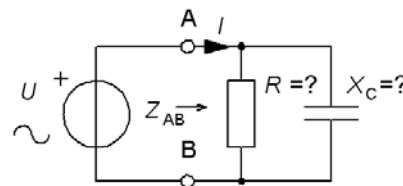12.1

Set up the complex expression for current I expressed in U R C ω .


Let U be reference phase which means a real number. Reply with an expression of the form $a+jb$.



12.2

How can the impedance Z look like that has given rise to this phasors? Draw the circuit diagram and calculate the components.

$U = 220$ V, $f = 50$ Hz.

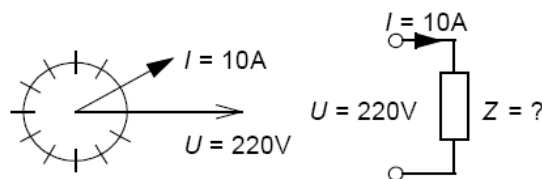


12.3

U_1 is a sinusoidal alternating voltage with the angular frequency ω .


Determine product $R \cdot C$.

(No current is drawn at U_2)

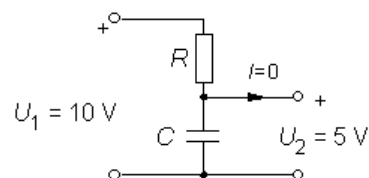

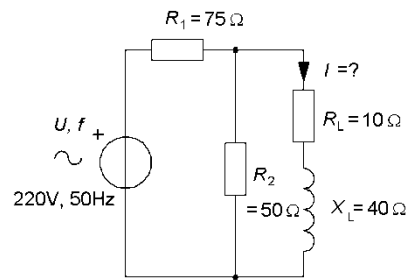
12.4

Determine the current I .
Use Thevenine equivalent.



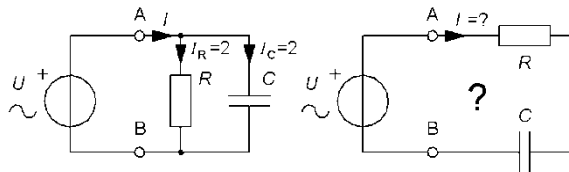
12.5

When a resistor R and a capacitor C are connected in parallel to a AC voltage source U each of the two components gets the current 2A.
How big would the current be if the two were series connected to the voltage source?



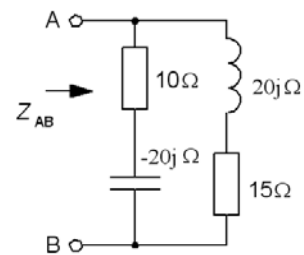12.6

Determine the complex impedance Z_{AB} for the circuit.




12.7

Derive an expression for complex current I (with U as reference phase).


Note! One does not always have to give the answer in the form $a+jb$. The same information, but with less effort, is if the answer is expressed as a ratio of complex numbers. Amount and arguments can if needed be taken from the numerator and the denominator directly.

$$\underline{I} = \frac{a + jb}{c + jd} \quad I = \frac{|a + jb|}{|c + jd|} \quad \arg(\underline{I}) = \arg(a + jb) - \arg(c + jd)$$

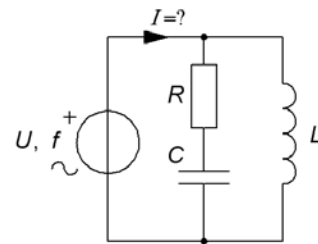

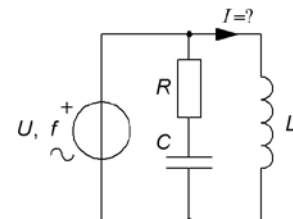12.8

Derive an expression for complex current I (with U as reference phase).




12.9

Calculate impedance Z .

Calculate current I .

Calculate I_C (use current branching formula).

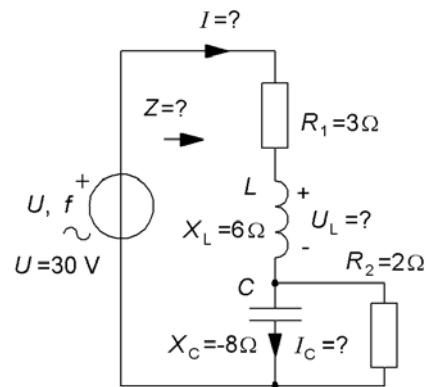
Calculate U_L (use voltage division formula).



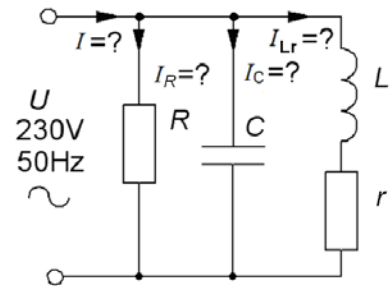12.10

An AC circuit is connected to the AC mains with $U = 230\text{ V}$ and $f = 50\text{ Hz}$. $R = 46\ \Omega$, $\omega L = R$, $r = 32,5\ \Omega$ and $C = 69\ \mu\text{F}$.

- Calculate I_R
- Calculate I_C
- Calculate I_{Lr}
- Calculate I




12.11

An AC voltage U_{IN} with the frequency $f = 1000\text{ Hz}$ feeds a circuit with an inductance $L = 10\text{ mH}$ in series with a resistor $R = 50\ \Omega$. In parallel with these are a resistor $R_S = 100\ \Omega$.

Given is voltage $U_{UT} = 6,28\text{ V}$.

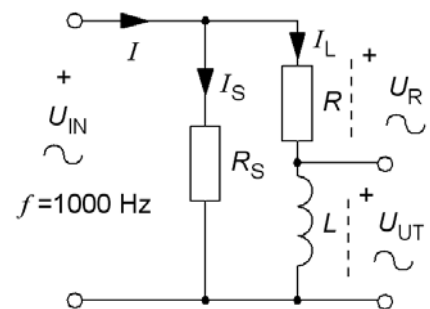- Calculate I_L
- Calculate U_R
- Calculate U_{IN}
- Calculate I




Resonance

13.1

In a circuit R , L and C are series connected. One measures the same voltage drop, 1 V, across all of the three components. How big is the supply voltage U ?


(NOTE! trick question)

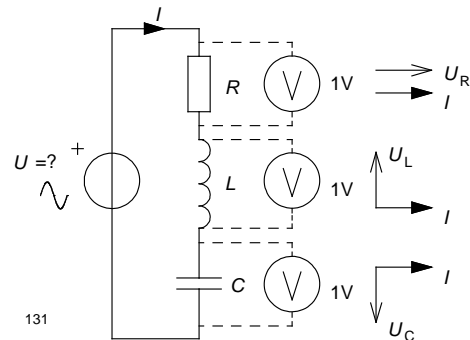

13.2


In a circuit R , L and C are in parallel. One measures the same current, 1 A, in the three parallel branches. How big is the current, I , that is taken from the supply voltage?

(NOTE! trick question)

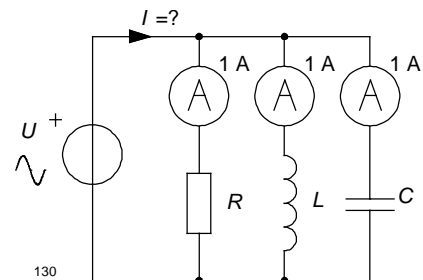

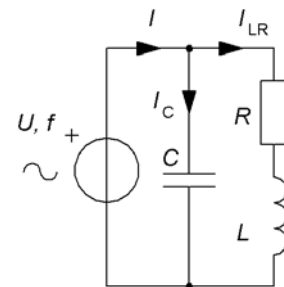13.3

At which frequency (expressed in R , L and C) has the current I and voltage U the same phase?



13.4


A serial resonance circuit has the resonance frequency $f_0 = 2000$ Hz and the bandwidth $BW = 200$ Hz.

- Calculate the circuit Q-value.
- One measures the coil resistance to $R_s = 2 \Omega$. What value has X_L (at the resonance frequency)?
- Calculate L and C .
- Estimate the lower and upper limits of the bandwidth. Check that the estimate was reasonable.

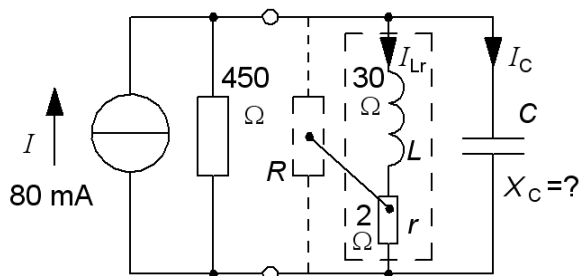
13.5

A parallel resonant circuit is supplied from a current generator which supplies 80 mA at the resonant frequency $f_0 = 20$ kHz.

- Check that the inductor has $Q > 10$. Transform the seriesresistance r to a parallel resistance R .
- How large is the resulting impedance (source + resonant circuit) at the resonance frequency?
- Calculate currents I_{Lr} and I_C .
- What values has L and C ?
- Calculate resulting Q-value and bandwidth.





13.6

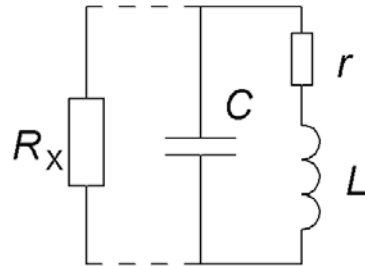

Stores theft buttons contains a resonant circuit with a high Q value, consisting of a small coil $L + r$ and a capacitor C . $L = 5 \mu\text{H}$ $r = 0,5 \Omega$ and $C = 25 \text{ pF}$.

- Which resonant frequency has the circuit?
- Which Q -value has the coil at resonance frequency?
- one wishes to adjust the resulting Q -value of the resonance circuit to exact $Q = 500$ by connecting a parallel resistor R_X . What value should R_X have?

13.7

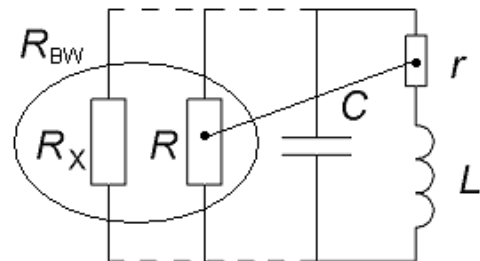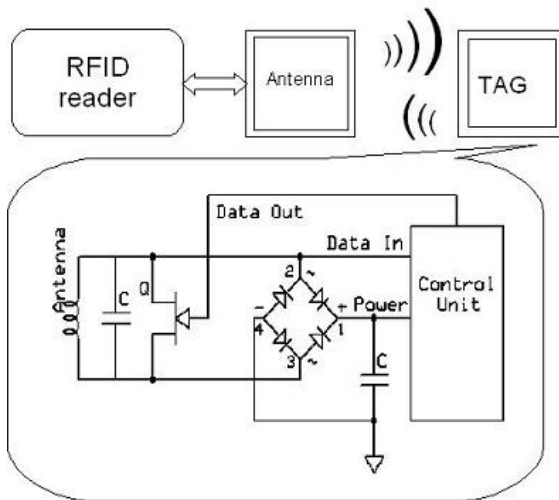


SL's access-card contains a so called RFID-tag. It communicates with a reader at the turnstyle at the frequency of 13.56 MHz and the data rate of 70 kHz. To "read" the data signal with this speed the resonance circuits included in the card and the reader needs to have a bandwidth at least twice the data rate ie $2 \cdot 70 = 140 \text{ kHz}$.

(You only need to understand the resonant circuit $r L C$ in order to solve the task, not the RFID technology).

In figure is $L = 2,5 \mu\text{H}$ and $r = 1,5 \Omega$ the embedded coil. C is the capacitance of the resonant circuit. The circuit parallel resistance R_X symbolises the processor connected to the resonant circuit, which consumes power from the resonant circuit.

- Calculate the value of C that gives the wished resonance frequency?
- What Q -value has the coil at resonance frequency?
- Transform the coils serial resistans r to a parallel resistans R .
- Suppose now that the coil only has parallel resistance.
What value should a parallel resistance R_{BW} have for the bandwidth to be 140 kHz?
- What value could the resistance R_X in parallel with R have for the bandwidth to be 140 kHz?
($R_{BW} = R_X || R$)

13.8

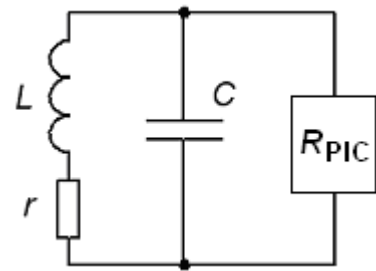

RFID-key-tags are used instead of door phone for access to apartment buildings. The communication is with radio frequency. The key tag contains a printed coil L r and a capacitor C , that forms a resonance circuit for the communication frequency. The resonance circuit is also loaded with a processor R_{PIC} .

$L = 0,43 \text{ mH}$ $r = 4 \Omega$ $C = 3,77 \text{ nF}$ $R_{PIC} = 20 \text{ k}\Omega$

- What is the resonance frequency of the key tag? $f = ?$ [kHz]
- What Q -value has the printed coil at resonance frequency? $Q_L = ?$ [times]
- What resulting Q -value (with the processor included) will the resonance circuit have? $Q_{res} = ?$ [times]
- What is the resulting bandwidth of the resonance circuit? $BW = ?$ [kHz]


Filters

14.1

The figure shows a simple filter with L and R .


- Derive the filter's transfer function.
- Enter the filter magnitude function and phase function.
- Give an expression for the filter cut-off frequency f_G .
- What kind of filters is it LP HP BP BS ?

$$\frac{\underline{U}_2}{\underline{U}_1} = ? \quad \left| \frac{\underline{U}_2}{\underline{U}_1} \right| = ? \quad \arg\left(\frac{\underline{U}_2}{\underline{U}_1}\right) = ? \quad f_G = ? \quad LP \ HP \ BP \ BS ?$$

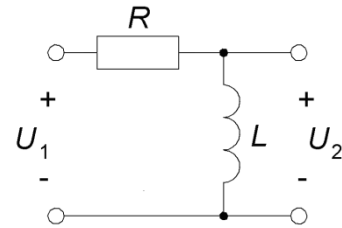

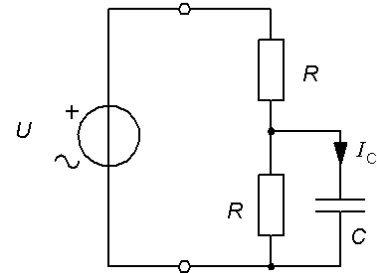14.2

Set up an expression for $I_C(U, \omega, R, C)$.



14.3

The figure shows a simple filter with a capacitor C and two resistors R_1 and R_2 .


- Derive the filter transfer function, the ratio between the complex voltages

$$\frac{\underline{U}_2}{\underline{U}_1}$$

- What values of the transfer function magnitude and phase angle going towards at the low frequencies?

What values of the transfer function magnitude and phase angle going towards at the very high frequencies?

What kind of filters is it, LP HP BP BS?

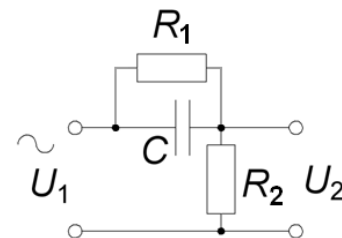

- Set up an expression of the filter cutoff frequency (then the numerator real part and imaginary part are equal)?


- Suppose that $R_1 = 1 \text{ k}\Omega$ and $R_2 = 2 \text{ k}\Omega$ and $C = 1 \text{ }\mu\text{F}$. Calculate cut off frequency.

14.4

The figure shows a simple filter with L C and R .

- Derive the filter's transfer function.
- Derive the filter magnitude function and phase function.
- At what frequency will the numerator be purely real? Give an expression for this frequency f_x .
- What is the value of the magnitude function at this frequency? What value does the phase function have at this frequency?
- Examine the filter's magnitude and phase for very small frequencies ($f \approx 0$) and for very high frequencies ($f \approx \infty$). What kind of filters is it, LP HP BP BS ?

$$\frac{\underline{U}_2}{\underline{U}_1} = ? \quad \left| \frac{\underline{U}_2}{\underline{U}_1} \right| = ? \quad \arg\left(\frac{\underline{U}_2}{\underline{U}_1}\right) = ? \quad f_x = ? \quad LP \ HP \ BP \ BS ?$$

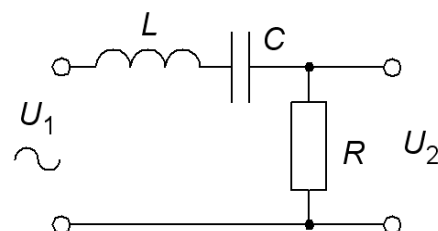


14.5

Wien bridge often occur as feedback networks in amplifiers. (The two R , and the two C are the same).

What value does $\frac{U_2}{U_1}$ approach at high, respective low frequencies?

For what value of f (expressed in R and C) does U_2 and U_1 has the same phase angle?

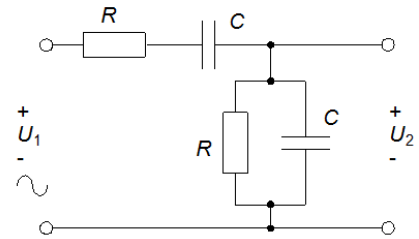
How big is the ratio $\frac{U_2}{U_1}$ at this frequency?



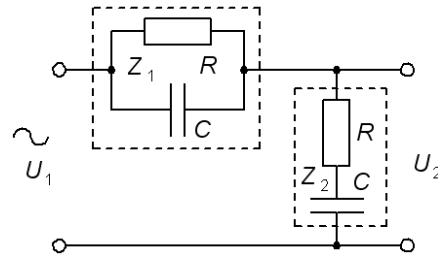14.6

The figure shows the Wien bridge "backwards".

- Derive the filter's transfer function.
- (Sketch magnitude function and phase function.)
- What amount and phase angle has the transfer function when $\omega = 1/RC$?




14.7

The figure shows a simple filter with two R and a L .

- Derive the filter's complex transfer function $\underline{U}_2 / \underline{U}_1$.
- At what angular frequency ω_x will the magnitude function be $|\underline{U}_2| / |\underline{U}_1| = 1/\sqrt{2}$?

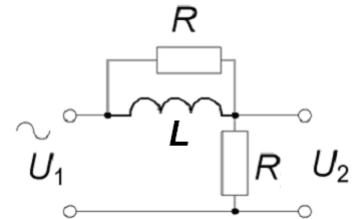Give an expression for this frequency ω_x with RL .




- What value is the transfer function magnitude going towards at the low frequencies, $\omega \approx 0$? What value has the phase function at very low frequencies?
- What value is the transfer function magnitude going towards at very high frequencies, $\omega \approx \infty$? What value has the phase function at very high frequencies?

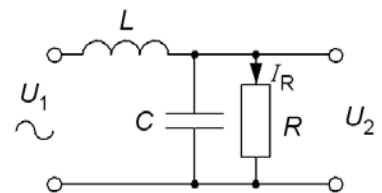14.8

The figure shows a simple filter with L C and R .

- Derive the filter's transfer function $\underline{U}_2 / \underline{U}_1$.
- At what angular frequency ω_x will denominator be purely imaginary? Give an expression for this frequency ω_x with RL and C .



- What value has the transfer function magnitude at this angular frequency, ω_x ?
- What value has the phase function at this angular frequency, ω_x ?
- Give an expression for the transfer function $\underline{I}_R / \underline{U}_1$. (Note! You already have $\underline{U}_2 / \underline{U}_1$ from a)

a) $\frac{U_2(\omega)}{U_1(\omega)} = ?$ b) $\omega_x(R, L, C) = ?$ c) $\left| \frac{U_2(\omega_x)}{U_1(\omega_x)} \right| = ?$ d) $\arg\left(\frac{U_2(\omega_x)}{U_1(\omega_x)} \right) = ?$ e) $\frac{I_R(\omega)}{U_1(\omega)} = ?$

Transformer, inductive coupling

15.1

For a transformer in operation the following data was measured:

Primary			Secondary		
N_1	U_1	I_1	N_2	U_2	I_2
600	225 V	?	200	?	9 A

Calculate the two missing values.

15.2

For a transformer in operation the following data was measured:

Primary			Secondary		
N_1	U_1	I_1	N_2	U_2	I_2
?	230 V	2 A	150	?	12 A

Calculate the two missing values.

15.3


For a transformer in operation the following data was measured:

Primary			Secondary		
N_1	U_1	I_1	N_2	U_2	I_2
600	225 V	?	?	127 V	9 A


Calculate the two missing values.

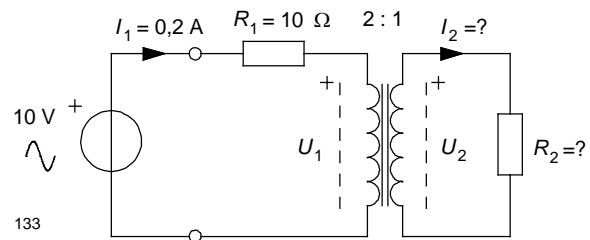15.4

$U = 10$ V, 50 Hz and $I_1 = 0,2$ A. Calculate I_2 and R_2 .



15.5

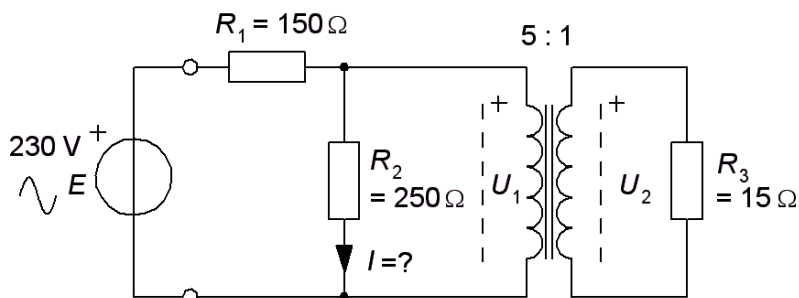


A transformer with a ratio of 5: 1 is connected to the mains $E = 230$ V via a voltage divider $R_1 = 150$ Ω and $R_2 = 250$ Ω . The secondary side of the transformer has the load $R_3 = 15$ Ω .

Calculate the current I through resistor R_2 .

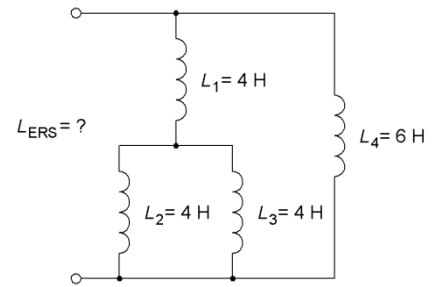15.6

Four coils are connected as shown. They are totally independent of each other, they have no common flow.
How large is the resulting inductance $L_{ERS} = ?$




15.7


Calculate the total inductance of three series connected coils placed so that they access portions of each flow.

$L_1 = 5$ [H], $L_2 = 10$ [H], $L_3 = 15$ [H],
 $M_{12} = 2$ [H], $M_{23} = 3$ [H], $M_{13} = 1$ [H].

$L_{TOT} = ?$ [H].

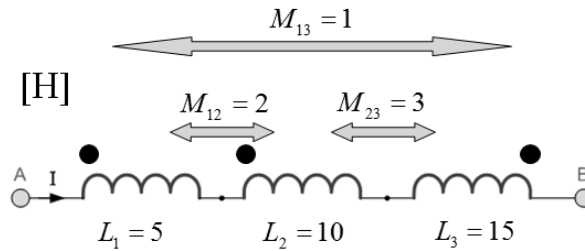

15.8

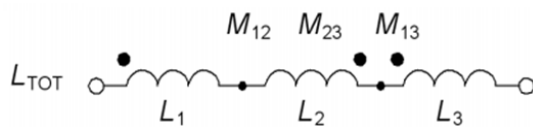


Three inductors $L_1 = 12$, $L_2 = 6$, $L_3 = 5$ [H] are series connected.

When inductors are close to each other the placement on the circuit board can be important. In the figure to the left a) will inductors to have a portion of the magnetic lines in common. They then have the mutual inductances $M_{12} = 3$, $M_{23} = 1$, $M_{13} = 1$ [H].

In the figure to the right b) the inductors are mounted three dimensional so that there are no shared power magnetic lines.

a) Calculate the total inductance for the arrangement in figure a). $L_{TOT} = ?$

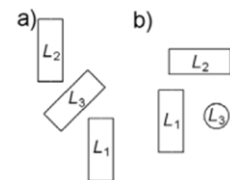b) Calculate the total inductance for the arrangement in figure b). $L_{TOT} = ?$



Solutions

Equivalent resistance

1.1

$$R_{\text{tot}} = 2 \cdot \left(\frac{1 \cdot (0,5 + 0,5)}{1 + 0,5 + 0,5} \right) = 1 \Omega$$

1.2

$$R_{\text{tot}} = \frac{R_4 \left(R_1 + \frac{R_2 \cdot R_3}{R_2 + R_3} \right)}{R_4 + \left(R_1 + \frac{R_2 \cdot R_3}{R_2 + R_3} \right)} = \frac{30 \cdot \left(1 + \frac{21 \cdot 42}{21 + 42} \right)}{30 + \left(1 + \frac{21 \cdot 42}{21 + 42} \right)} = \frac{30(1+14)}{30+1+14} = \frac{30 \cdot 15}{45} = 10 \Omega$$

1.3

$$R_{45} = 1 + 2 = 3 \quad R_{345} = \frac{6 \cdot 3}{6 + 3} = 2 \quad R_{2345} = 4 + 2 = 6 \quad R_{\text{ERS}} = R_{12345} = \frac{1 \cdot 6}{1 + 6} = 0,86 \Omega$$

1.4

$$R_{\text{ERS}} = 0,5 + 1,6 + \frac{5,2 \left(2,7 + \frac{7 \cdot 3}{7 + 3} \right)}{5,2 + 2,7 + \frac{7 \cdot 3}{7 + 3}} = 4,6 \Omega$$

1.5

The three resistors $R_1 \dots R_3$ are connected in parallel

$$[\text{k}\Omega]: R_{1,2,3} = \frac{1}{\frac{1}{28} + \frac{1}{84} + \frac{1}{56}} = 15,27. \quad \text{The resistor } R_4 \text{ is in parallel with a "short circuit wire" } (R=0),$$

$$\frac{0 \cdot R_4}{0 + R_4} = 0. \quad \text{Totally we get } R_{\text{tot}} = R_{1,2,3} + 0 = 15,27 \text{ k}\Omega.$$

1.6

The four resistors $R_2 \dots R_5$ are in parallel.

$$R_{2,3,4,5} = \frac{1}{\left(\frac{1}{12} + \frac{1}{12} + \frac{1}{24} + \frac{1}{24} \right)} = 4 \Omega \quad \text{and thereafter connected in series with } R_1. \quad R_{\text{tot}} = 4 + 2 = 6 \Omega.$$

1.7

$$R_{\text{TOT}} = 15 + \frac{1}{\frac{1}{15} + \frac{1}{15} + \frac{1}{15}} + \frac{1}{\frac{1}{15} + \frac{1}{15} + \frac{1}{15} + \frac{1}{15} + \frac{1}{15}} = 15 + 5 + 3 = 23 \Omega$$

1.8

The circuit consists of two equal parallel branches. One of the branches have:


$$R_{\text{ERS}} = \frac{20 \cdot 5}{20 + 5} + 2 = 6. \quad \text{Then the total equivalent resistance is: } R_{\text{TOT}} = \frac{6 \cdot 6}{6 + 6} = 3 \Omega$$

1.9


$$R_{\text{tot}} = \left(\left(\left((R_7 \parallel R_5) + R_6 \right) \parallel R_4 \right) + R_1 \right) \parallel R_2 + R_3$$

$$R_{5,7} = \frac{6 \cdot 3}{6 + 3} = 2 \quad R_{4,5,6,7} = \frac{(2 + 4) \cdot 6}{2 + 4 + 6} = 3$$
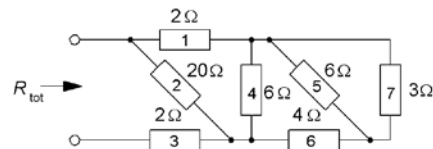
$$R_{1,2,4,5,6,7} = \frac{(3 + 2) \cdot 20}{3 + 2 + 20} = 4 \quad R_{\text{tot}} = 4 + 2 = 6 \Omega$$




1.10

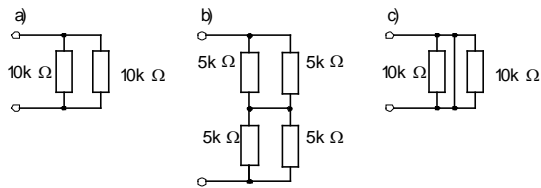



a) $10/2 = 5k$ b) $5/2+5/2 = 5k$ c) 0

1.11

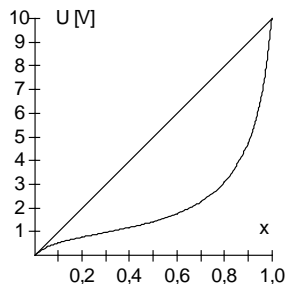

Resistivity and resistors temperature dependence

2.1

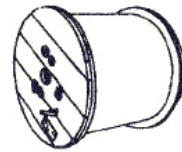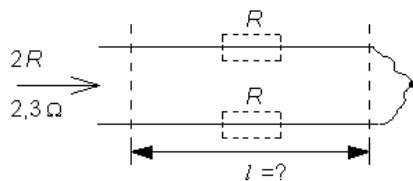

A smart trainee goes and gets a Ω -meter and measures the resistance in the two series connected wires of the cable. This measurement gives $2R = 2,3 \Omega$.

Each wire then has the resistance $R = 1,15 \Omega$.

The length l of the cable can be calculated:

$$l = (R \times A) / \rho = 1,15 \times 2,5 / 0,018 = 159,7 \text{ m}$$

It had been troublesome to measure out the length of the cable with measuring tape!

2.2

$$R_2 = \frac{U}{I} = \frac{20}{0,11} = 182 \Omega \quad R_1 = 98 \Omega \quad \alpha = 4,5 \cdot 10^{-3} \quad t_1 = 98 \text{ }^\circ\text{C}$$

$$R_2 = R_1 + R_1 \cdot \alpha (t_2 - t_1) \Leftrightarrow t_2 = \frac{182 - 98}{98 \cdot 4,5 \cdot 10^{-3}} + 22 = 212,5 \text{ }^\circ\text{C}$$

The radiation thermometer thus showed 60° improper!

2.3

$$\text{a) } \alpha_{\text{NI}} = 6,7 \cdot 10^{-3}$$


$$R_{\text{koka}} = R_{\text{rum}} + R_{\text{rum}} \cdot \alpha_{\text{NI}} (t_{\text{koka}} - t_{\text{rum}}) = 50 + 50 \cdot 6,7 \cdot 10^{-3} \cdot 75 = 75,1 \Omega$$

$$\text{b) } I = \frac{E}{R + R_1} = \frac{12}{75,1 + 25} = \frac{12}{100,1} = 0,12 \text{ A} \Leftrightarrow P = I^2 \cdot R = 0,12^2 \cdot 75,1 = 1,08 \text{ W}$$

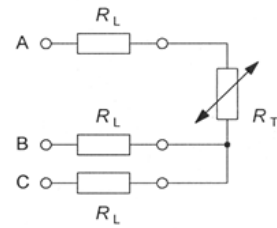2.4



Describe the principle of so-called three wire connection.

At three-wire measurement, measure first the resistance between A and B. Then you get with $2 \cdot R_L$ too much. By measuring the resistance between B and C you find out how much $2 \cdot R_L$ is and is thereby able to correct the first reading.



Serial – parallel circuits

3.1

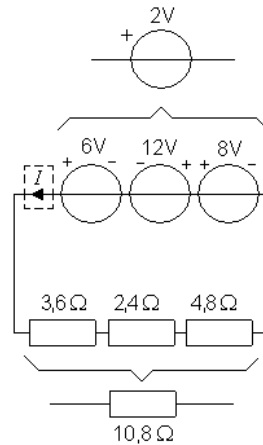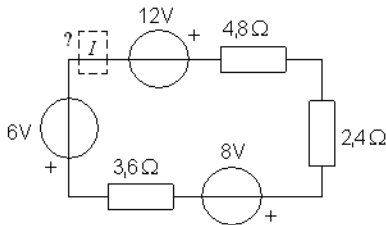

$$8 + 6 - 12 = 2 \quad 3,6 + 2,4 + 4,8 = 10,8 \quad I = \frac{2}{10,8} = 0,19 \text{ A}$$

3.2

a) $R_{\text{RES}} = 2\Omega$ b) $I = 4 \text{ A}$, $U = 8 \text{ V}$ c) $I_1 = 1 \text{ A}$, $I_2 = 2 \text{ A}$, $I_3 = 1 \text{ A}$, $U_1 = 6 \text{ V}$

3.3

We calculate two equivalent resistances.

$$R_{1,2} = \frac{24 \cdot 12}{24 + 12} = 8\Omega \quad R_{3,4,5} = \frac{1}{\frac{1}{9} + \frac{1}{18} + \frac{1}{6}} = 3\Omega$$

U can be calculated with the voltage division formula:

$$U_{R_2} = E \frac{R_{1,2}}{R_{1,2} + R_{3,4,5}} = 12 \frac{8}{8 + 3} = 8,73 \text{ V}$$

Voltage over $R_{3,4,5} = E - U = 12 - 8,73 = 3,27 \text{ V}$ and then $I = \frac{E - U}{R_5} = 3,27 / 6 = 0,55 \text{ A}$.

3.4

$$R_{\text{tot}} = 4 + \frac{\frac{4}{2} \cdot (0,5 + 1,5)}{\frac{4}{2} + (0,5 + 1,5)} = 5 \quad I_{\text{tot}} = \frac{E}{R_{\text{tot}}} = \frac{10}{5} = 2 \text{ A}$$

The current is divided between three parallel branches: $4//4//2$. Over these is the voltage =

$$= E - I_{\text{tot}} \cdot 4 = 10 - 2 \cdot 4 = 2 \text{ V}. \text{ We get } I = \frac{2}{4} = 0,5 \text{ A} \text{ and } U = 2 \frac{0,5}{0,5 + 1,5} = 0,5 \text{ V}$$

3.5

We calculate an equivalent resistance. $\frac{6 \cdot (1+2)}{6+1+2} = 2$

$U_{R1} = 36 \text{ V}$. U_{R3} can be calculated with the voltage division rule: $36 \frac{2}{4+2} = 12$

then $I = I_{R3} = \frac{U_{R3}}{R_3} = 12 / 6 = 2 \text{ A}$

Voltage U over R_5 can be calculated by voltage division rule: $12 \frac{2}{1+2} = 8$

3.6


a) $R_{ERS} = R_1 + (R_2 \parallel (R_3 + (R_4 \parallel R_5))) =$

$$R_{45} = \frac{6 \cdot 6}{6+6} = 3 \quad R_{345} = 3+3 = 6$$

$$R_{2345} = \frac{6 \cdot 6}{6+6} = 3 \quad R_{ERS} = R_{12345} = 3+3 = 6$$

$$\text{b) } I_{R1} = \frac{E}{R_{ERS}} = \frac{12}{6} = 2 \quad I_{R3} = \frac{I_{R1}}{2} = \frac{2}{2} = 1$$
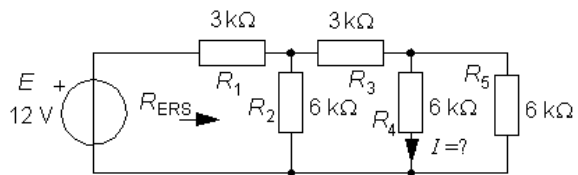
$$I_{R4} = \frac{I_{R3}}{2} = \frac{1}{2} = 0,5 \text{ [mA]}$$



Batteries

4.1

a) $C_{20} = 60 \text{ Ah}$ means that the discharge has been ongoing for 20 hours and that the battery capacity $I \times t$ was 60 Ah. The constant discharge current I that was used was then $60/20 = 3 \text{ A}$.

b) The capacity number is developed at the current 3 A. Then one can assume that the battery capacity is unchanged at the nearby current value of 1 A. We get $t = C/I = 60/1 = 60 \text{ h}$.

c) The high current 300 A is a completely different operating condition than that used by the manufacturer to develop the capacity number. From experience (here given) we know that the capacity gets lower at high currents. Therefore, it is expected that the capacity's reduced till 70%. $C' = 0,7 \times C = 0,7 \times 60 = 42$.

We get $t = C'/I = 42/300 = 0,14 \text{ h}$ $0,14 \times 60 = 8,4 \text{ min}$.

4.2

$$\text{a) } I = \frac{E}{R_1 + R} \Leftrightarrow 0,123 = \frac{1,4}{R_1 + 10} \Leftrightarrow R_1 = \frac{1,4}{0,123} - 10 = 1,38 \Omega$$

$$\text{b) } I_{\text{MAX}} = \frac{E}{R_1} = \frac{1,4}{1,38} = 1,01 \text{ A}$$

4.3

$$\text{a) } U = 6 \quad I = 1,75 \quad n \cdot E - n \cdot R_i \cdot I - U = 0 \quad n = \frac{U}{E - I \cdot R_i} = \frac{6}{1,1 - 1,75 \cdot 0,2} = 8 \text{ st}$$

b) At serial connection the voltage is increased but the capacity will be the same. $C = 3000 \text{ mAh}$.

$$C = I \cdot t \Rightarrow I = \frac{C}{t} = \frac{3}{1} = 3 \text{ A}$$

$$\text{c) } 24 - 8 \cdot 1,1 - R \cdot 3 - 8 \cdot 0,2 \cdot 3 = 0 \quad R = \frac{24 - 8 \cdot 1,1 - 8 \cdot 0,2 \cdot 3}{3} = 3,47 \Omega$$

4.4

Three equal batteries can be merged into one with $E = 10\text{V}$ and $R_1 = 6/3 = 2 \Omega$.

a) $I = 10/(2 + 2) = 2,5 \text{ A}$. $U = 2 \cdot 2,5 = 5 \text{ V}$.

b) Two equal batteries can be merged to one with $E = 10\text{V}$ and $R_1 = 6/2 = 3 \Omega$.

Kirchoff's current law gives:

- $I_1 - I_2 - I = 0$

Kirchoff's voltage law around two meshes gives:

- $10 - 3 \cdot I_1 + 10 - 6I_2 = 0 \Leftrightarrow -3I_1 - 6I_2 + 0I = -20$

- $6I_2 - 10 - 2I = 0 \Leftrightarrow 0I_1 + 6I_2 - 2I = 10$

On matrix form:

$$\begin{pmatrix} 1 & -1 & -1 \\ -3 & -6 & 0 \\ 0 & 6 & -2 \end{pmatrix} \cdot \begin{pmatrix} I_1 \\ I_2 \\ I \end{pmatrix} = \begin{pmatrix} 0 \\ -20 \\ 10 \end{pmatrix} \quad I_1 = 2,78 \text{ A} \quad I_2 = 1,94 \text{ A} \quad I = 0,83 \text{ A}$$

$$U = I \cdot 2 = 0,83 \cdot 2 = 1,67 \text{ V}$$

Kirchoff's laws will be next in course!

Kirchoff's current law and voltage law

5.1

$I_1 = 5 \text{ A}$, $I_2 = 2,5 \text{ A}$, $I_3 = 2,5 \text{ A}$ och $I_4 = 5 \text{ A}$.

5.2

$$E = R_{TOT} \cdot I = 2,62 \cdot 10 = 26,2 \text{ V}$$

$$I_4 = \frac{E}{4} = \frac{26,2}{4} = 6,55 \text{ A} \quad I_1 = I - I_4 = 10 - 6,55 = 3,45 \text{ A}$$

$$I_3 = \frac{5,5}{2} = 2,75 \text{ A}$$

5.3


$$I = \frac{1,3}{1,5 + 1,6 + 0,4 + 0,8 + 0,5} = 0,27$$

$$U_{0,5} = 0,5 \cdot 0,27 = 0,14$$

$$U_{1,5} = 1,5 \cdot 0,27 = 0,41$$

$$U = -0,14 + 1,3 - 0,41 = 0,76 \text{ V}$$
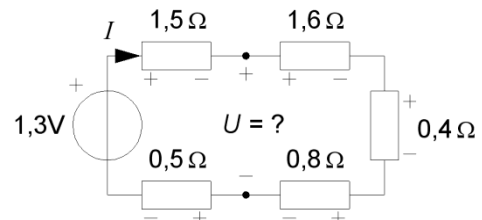
$$\text{or } U = 0,27 \cdot (0,8 + 0,4 + 1,6) = 0,76 \text{ V}$$




Kirchoffs lagar, ekvationsystem

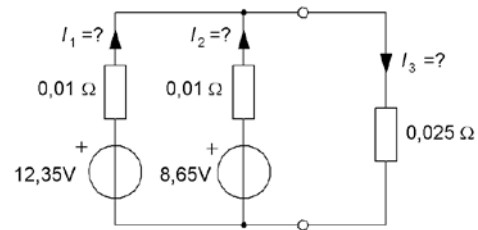6.1

Kirchoff's current law:

$$I_1 + I_2 - I_3 = 0 \Rightarrow I_3 = I_1 + I_2$$



Kirchoff's voltage law:

$$12,35 - 0,01I_1 - 0,025I_3 = 0 \Leftrightarrow 12,35 - 0,01I_1 - 0,025(I_1 + I_2) = 0 \Leftrightarrow 0,035I_1 + 0,025I_2 = +12,35$$

Kirchoff's voltage law:

$$8,65 - 0,01 \cdot I_2 - 0,025I_3 = 0 \Leftrightarrow 8,65 - 0,01 \cdot I_2 - 0,025(I_1 + I_2) = 0 \Leftrightarrow 0,025I_1 + 0,035I_2 = 8,65$$

two equations, two unknowns, thus solvable.

$$\begin{pmatrix} 0,035 & 0,025 \\ 0,025 & 0,035 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} 12,35 \\ 8,65 \end{pmatrix} \quad I_1 = 360 \text{ A} \quad I_2 = -10 \text{ A} \quad I_3 = I_1 + I_2 = 350 \text{ A}$$

The bad battery degrades the starting current with 10 A!

6.2

Kirchoff's current law gives:

$$\bullet \quad -I_1 + I_2 + I_3 = 0$$

Kirchoff's voltage law around two meshes gives:

$$\bullet \quad E_1 - I_1 \cdot R_1 - I_2 \cdot R_4 - E_3 - I_1 \cdot R_3 = 0 \Leftrightarrow -3I_1 - 15I_2 + 0I_3 = -9$$

$$\bullet \quad -E_2 - I_3 \cdot R_2 + I_2 \cdot R_4 = 0 \Leftrightarrow 0I_1 + 15I_2 - 2I_3 = 21$$

On matrix form:

$$\begin{pmatrix} -1 & 1 & 1 \\ -3 & -15 & 0 \\ 0 & 15 & -2 \end{pmatrix} \cdot \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0 \\ -9 \\ 21 \end{pmatrix} \quad \text{solution:} \quad I_1 = -2 \text{ A} \quad I_2 = 1 \text{ A} \quad I_3 = -3 \text{ A}$$

6.3

a) Over 18Ω-resistor is E_1 18 V.

($I_3 = -18/18 = -1$ A in opposite direction than stated in figure)

$$b) \quad E_2 - R_1 I_2 - E_1 = 0 \Rightarrow I_2 = -\frac{E_1 - E_2}{R_1} = -\frac{16 - 12}{6} = -1 \text{ A}.$$

I_2 has opposite direction than stated in figure.

$$c) \quad I_1 + I_2 + I_3 = 0 \quad I_1 = 1 + 1 = 2 \text{ A}$$

6.4

Kirchoff's current law gives:

$$\bullet \quad I_1 - I_2 - I = 0$$

Kirchoff's voltage law around two meshes gives:

$$\bullet \quad -I_2 \cdot R_3 + E_2 - I_1 \cdot R_2 = 0 \Leftrightarrow I_1 + 3I_2 + 0 \cdot I = 12$$

$$\bullet \quad I_2 \cdot R_3 - I \cdot R_1 - E_1 - I \cdot R = 0 \Leftrightarrow 0I_1 + 3I_2 - 6I = 6$$

On matrix form:

$$\begin{pmatrix} 1 & -1 & -1 \\ 1 & 3 & 0 \\ 0 & 3 & -6 \end{pmatrix} \cdot \begin{pmatrix} I_1 \\ I_2 \\ I \end{pmatrix} = \begin{pmatrix} 0 \\ 12 \\ 6 \end{pmatrix} \quad \text{solution:} \quad I_1 = 3,33 \text{ A} \quad I_2 = 2,89 \text{ A} \quad I = 0,44 \text{ A}$$

$$\Rightarrow U = I \cdot R = 4 \cdot 0,44 = 1,78 \text{ V}$$

6.5

Kirchoff's current law:

$$I_1 + I_2 + I_3 = 0$$

Kirchoff's voltage law (left):

$$-25 - 2 \cdot I_1 + 3 \cdot I_2 + 60 = 0$$

reorder:

$$-2 \cdot I_1 + 3 \cdot I_2 + 0 \cdot I_3 = -35$$

Kirchoff's voltage law (right):

$$-60 - 3 \cdot I_2 + 6 + 5 \cdot I_3 - 20 = 0$$

reorder:

$$0 \cdot I_1 - 3 \cdot I_2 + 5 \cdot I_3 = 74$$

Equation system on matrix form:

$$\begin{pmatrix} 1 & 1 & 1 \\ -2 & 3 & 0 \\ 0 & -3 & 5 \end{pmatrix} \cdot \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0 \\ -35 \\ 74 \end{pmatrix}$$

$$\text{a) } \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 1,87 \\ -10,4 \\ 8,55 \end{pmatrix}$$

$$\text{b) Voltage at voltmeter } U = -E_3 - R_3 \cdot I_3 = -6 - 5 \cdot 8,55 = -48,75 \text{ V}$$

6.6

Kirchoff's current law:

$$\bullet \quad I_1 + I_2 + I_3 = 0$$

Kirchoff's voltage law around two meshes gives:

$$\bullet \quad -I_1 \cdot R_1 + I_3 \cdot R_2 - E_2 = 0 \Leftrightarrow -4I_1 + 0I_2 + 6I_3 = 15$$

$$\bullet \quad E_2 - I_3 \cdot R_2 + E_1 + I_2 \cdot R_3 - E_3 = 0 \Leftrightarrow 0I_1 + 8I_2 - 6I_3 = -8$$

On matrix form:

$$\begin{pmatrix} 1 & 1 & 1 \\ -4 & 0 & 6 \\ 0 & 8 & -6 \end{pmatrix} \cdot \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0 \\ 15 \\ -8 \end{pmatrix}$$

$$\text{solution: } \quad I_1 = -1,56\text{A} \quad I_2 = 0,1\text{A} \quad I_3 = 1,46\text{A}$$

Potential, node analysis, dependent sources

7.1

$$U_{R1} = 12 \cdot \frac{100}{100 + 110 + 120} = 3,64 \text{ V} \quad U_{R2} = 12 \cdot \frac{110}{100 + 110 + 120} = 4 \text{ V} \quad U_{R3} = 12 \cdot \frac{120}{100 + 110 + 120} = 4,37 \text{ V}$$

Socket	a)	b)	c)	d)
Voltmeter [V]	-4,37	0	+4	4+3,64 = 7,64

7.2

$$-I_1 - I_2 + 1 = 0 \quad I_1 + I_2 = 1$$

$$I_2 = \frac{U}{R_2} = \frac{U}{12}$$

$$I_1 = \frac{U - E}{R_1} = \frac{U - 24}{6}$$

$$1 = \frac{U}{12} + \frac{U - 24}{6} = \frac{2 \cdot U - 48 + U}{12} \Leftrightarrow 12 = 3 \cdot U - 48$$

$$U = 20 \text{ V}$$

$$I_2 = \frac{20}{12} = 1,67$$

$$I_1 = \frac{20 - 24}{6} = -0,67$$

$$I_1 + I_2 = 1 \quad -0,67 + 2,67 = 1$$

7.3 Node analysis

$$I_1 + I_2 + I_3 = 0 \quad I_1 = -I_2 - I_3$$


$$E_1 = 18 \text{ V}$$

$$I_3 = -\frac{(E_1 - 0)}{R_2} = -\frac{18}{18}$$

$$= -1 \text{ A}$$

$$I_2 = -\frac{(E_1 - E_2)}{R_1} = -\frac{(18 - 12)}{6} = -1 \text{ A}$$
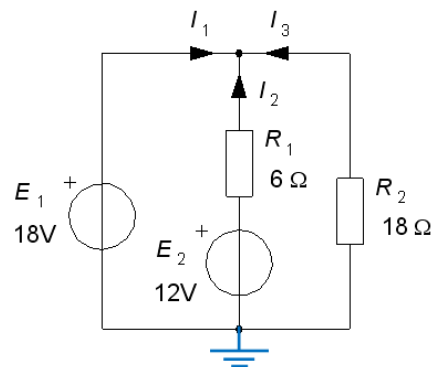
$$I_1 = -I_2 - I_3 = -(-1) - (-1) = 2 \text{ A}$$



7.4 Dependent source


Kirchoff's current law: $I_1 + I_2 + I_3 = 0$

Kirchoff's voltage law (not dependent emf):

$$-2I_1 - 3 + 1I_3 = 0 \Leftrightarrow -2I_1 + 0I_2 + 1I_3 = 3$$

Kirchoff's voltage law (with the dependent emf):
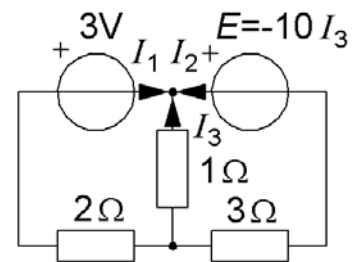
$$-1I_3 - (-10I_3) + 3I_2 = 0 \Leftrightarrow 0I_1 + 3I_2 + 9I_3 = 0$$







$$\begin{pmatrix} 1 & 1 & 1 \\ -2 & 0 & 1 \\ 0 & 3 & 9 \end{pmatrix} \cdot \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0 \\ 3 \\ 0 \end{pmatrix} \quad I_1 = -2 \quad I_2 = 3 \quad I_3 = -1$$


(numerical values are the same as in the course throughout lecture example ...)

Thevenin and Norton equivalents, superposition

8.1

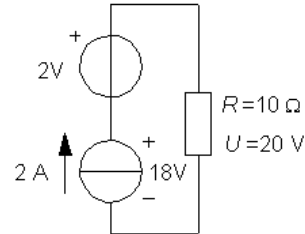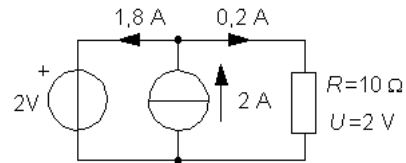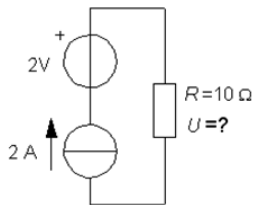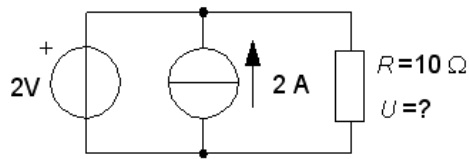


8.2

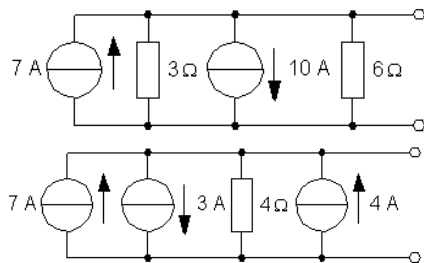

$$7 - 10 = -3$$

$$\frac{3 \cdot 6}{3 + 6} = 2$$

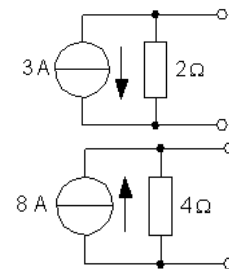

8.3 $E_K = 1 \text{ V}, R_1 = 1 \Omega$


8.4

$$\text{a) } U_{R16} = 100 \cdot \frac{16 \cdot (4+12)}{4 + \frac{16 \cdot (4+12)}{16+4+12}} = 100 \cdot \frac{8}{12} = 66,67 \quad U_{R12} = 66,67 \cdot \frac{12}{4+12} = 50 \text{ V}$$

$$\text{b) c) } R_I = 12 \parallel (4 + 4 \parallel 16) = \frac{12 \left(4 + \frac{4 \cdot 16}{4+16} \right)}{12 + 4 + \frac{4 \cdot 16}{4+16}} = 4,5 \text{ k}\Omega \Rightarrow I_K = \frac{50}{4,5} = 11,1 \text{ mA}$$


$$\text{d) } R_X = R_I \Rightarrow P = \frac{E_0^2}{4 \cdot R_I} = \frac{50^2}{4 \cdot 4,5 \cdot 10^3} = 0,114 \text{ W}$$

8.5

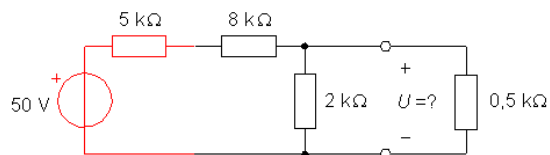


$$\frac{2 \cdot (5+8)}{2+5+8} = 1,73$$

$$50 \cdot \frac{2}{2+5+8} = 6,67$$

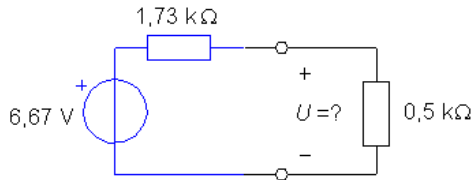


$$U = 6,67 \cdot \frac{0,5}{0,5 + 1,73} = 1,49 \text{ V}$$


8.6

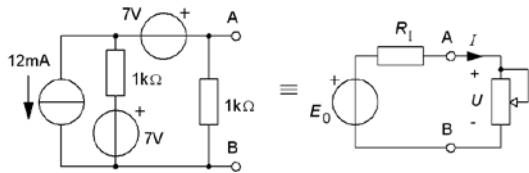

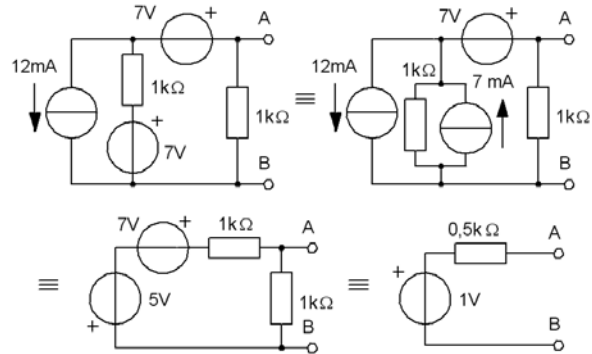
a) 7V and 1k transforms to a current source, 7 mA and 1k. Then two current sources can be merged into one 5 mA and 1k. Transform to voltage source 5V and 1k. Total 2 V with a voltage divider. Last 1V and 0,5 k.



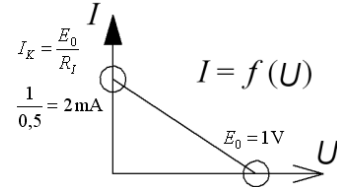b) The two port $I = f(U)$ is a line. Dry run $U = E_0 = 1\text{V}$ and short circuit $I_K = E_0/R_1 = 2 \text{ mA}$ are two points on the line.




8.7 superposition

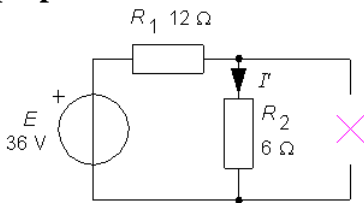

$$I' = \frac{E}{R_1 + R_2} = \frac{36}{12 + 6} = 2$$

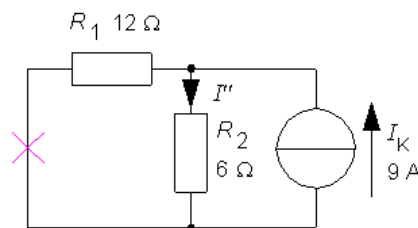A turned down current source is a circuit break!
I' one can calculate with OHM's law.



$$I'' = I_K \cdot \frac{R_1}{R_1 + R_2} = 9 \cdot \frac{12}{12 + 6} = 6$$

A turned down voltage source is a circuit short cut.
I'' one can calculate with current branching.



$$I = I' + I'' = 2 + 6 = 8 \text{ A}$$

8.8


$$R_1 = R_3 + \frac{R_1 \cdot R_2}{R_1 + R_2} = 5 + \frac{5 \cdot 5}{5 + 5} = 7,5$$

$$E_0 = E \cdot \frac{R_2}{R_1 + R_2} = 20 \cdot \frac{5}{5 + 5} = 10$$
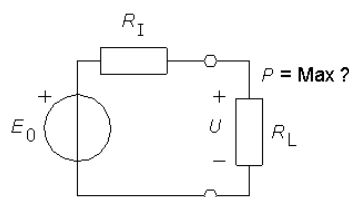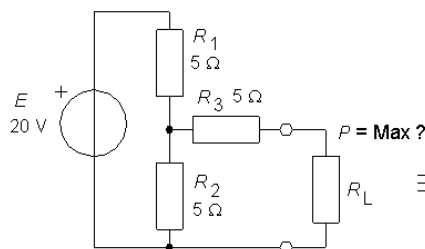
$$P_{\text{MAX}} = \frac{E_0^2}{4 \cdot R_1} = \frac{10^2}{4 \cdot 7,5^2} = 3,33 \text{ W}$$




8.9

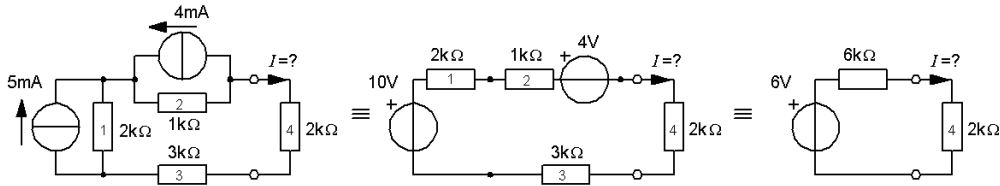

$$5\text{mA} \parallel 2\text{k}\Omega \Leftrightarrow 10\text{V} + 2\text{k}\Omega, \quad 4\text{mA} \parallel 1\text{k}\Omega \Leftrightarrow 4\text{V} + 1\text{k}\Omega \Rightarrow 6\text{V} + 6\text{k}\Omega$$

$$I = \frac{E_0}{R_I + R_L} = \frac{6}{6 + 2} = 0,75 \text{ mA}$$

8.10

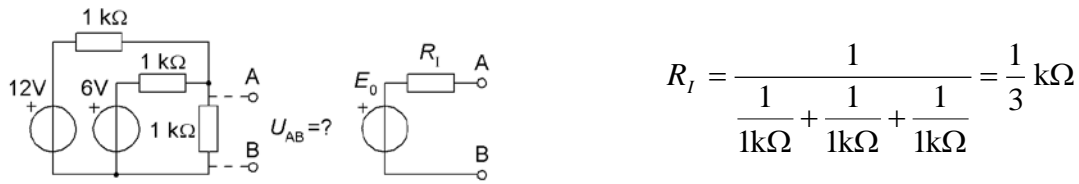


$$R_I = \frac{1}{\frac{1}{1\text{k}\Omega} + \frac{1}{1\text{k}\Omega} + \frac{1}{1\text{k}\Omega}} = \frac{1}{3} \text{ k}\Omega$$

Suppose A and B short cut. The third 1 kΩ resistor is then without current.

$$I_K = \frac{12\text{V}}{1\text{k}\Omega} + \frac{6\text{V}}{1\text{k}\Omega} = 18 \text{ mA} \quad I_K = \frac{E_0}{R_I} \Rightarrow E_0 = I_K \cdot R_I = 18 \cdot \frac{1}{3} = 6\text{V}$$

The voltage U_{AB} has the same value as E_0 .

8.11

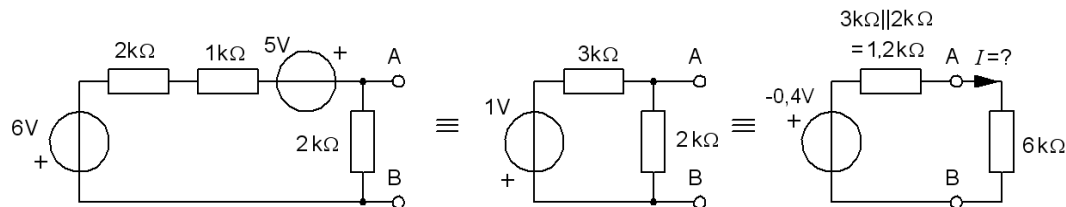

The current source and 1 kΩ resistor can be transformed into a voltage source. The whole circuit will be a 1V voltage source with a voltage divider.

$$E_0 = 1 \cdot \frac{2}{3 + 2} = 0,4 \text{ V} \quad R_I = \frac{3 \cdot 2}{3 + 2} = 1,2 \text{ k}\Omega$$

The unloaded voltage will be 0,4V, and the internal resistance $3\text{k}\Omega \parallel 2\text{k}\Omega = 1,2\text{k}\Omega$. Note that the voltage source 0,4V is counter defined in the original figure.

At last the the current (with electronics prefixes: mA kΩ V) $I = -0,4 / (1,2 + 2) = -0,125 \text{ [mA]}$

Capacitance, magnetism, inductance

9.1

$$W = \frac{1}{2} \cdot C \cdot U^2 \quad \text{a) } W = \frac{1}{2} \cdot C \cdot U^2 = \frac{1}{2} \cdot 1000 \cdot 10^{-6} \cdot 100^2 = 5 \text{ J, Ws}$$

$$Q = C \cdot U \quad \text{b) } Q = C \cdot U = 1000 \cdot 10^{-6} \cdot 100 = 0,1 \text{ C, As}$$

$$I = \frac{Q}{t} \quad \text{c) } I = \frac{Q}{t} = \frac{0,1}{1/2000} = 200 \text{ A}$$

$$P = \frac{W}{t} \quad \text{d) } P = \frac{W}{t} = \frac{5}{1/2000} = 10 \text{ kW}$$

$$\text{d) } U = \frac{Q}{C} = \frac{I_{\text{Ladda}} \cdot t_{\text{Ladda}}}{C} \Rightarrow t_{\text{Ladda}} = \frac{C \cdot U}{I_{\text{Ladda}}} = \frac{1000 \cdot 10^{-6} \cdot 100}{10 \cdot 10^{-3}} = 10 \text{ s}$$

9.2

$$\Delta Q = C \cdot \Delta U = 1 \cdot (5 - 2,5) = 2,5 \text{ As} \quad t = \frac{\Delta Q}{I} = \frac{2,5}{10 \cdot 10^{-3}} = 250 \text{ s} = 4 \text{ min}$$

9.3

Capacitance values are added, parallel connection is the same thing as if capacitor areas are added. The capacitor with the lowest withstanding voltage determines the equivalent capacitor rated voltage. It is in that capacitor the impact will occur.

$$C_{\text{ERS}} = C_1 + C_2 = 4 + 2 = 6 \mu\text{F} \quad 50\text{V}$$


9.4

No current or charge can pass through a capacitor. Two series connected capacitors must always have the same charge! $Q_{C1} = Q_{C2}$.


$$Q_{C1} = Q_{C2} = Q = C_{\text{ERS}} \cdot E = C_1 \cdot U_{C1} = C_2 \cdot U_{C2}$$

$$C_{\text{ERS}} = \frac{6 \cdot 12}{6 + 12} = 4 \mu\text{F} \quad Q = 4 \cdot 10^{-6} \cdot 10 = 40 \mu\text{C}$$
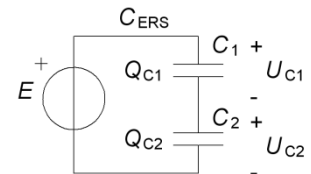
$$U_{C1} = \frac{Q}{C_1} = \frac{40 \cdot 10^{-6}}{6 \cdot 10^{-6}} = 6,66 \text{ V} \quad U_{C2} = E - U_{C1} = 10 - 6,66 = 3,33 \text{ V}$$



9.5

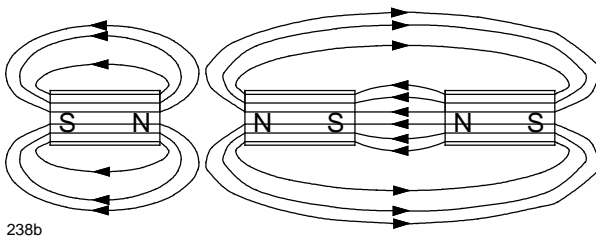


238b

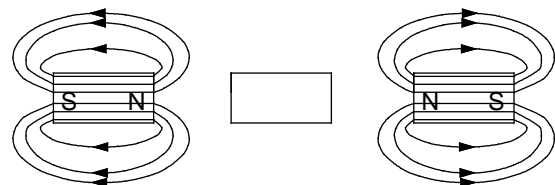9.6


The metal part has the permeability $\mu_r = 1$, which is the same as for air. It does not influence the magnets in any way.

The magnets distance from each other is large, so the magnetic fields is the same as from completely alone magnets.




238c

9.7

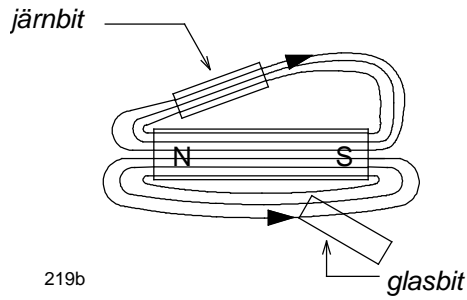

9.8

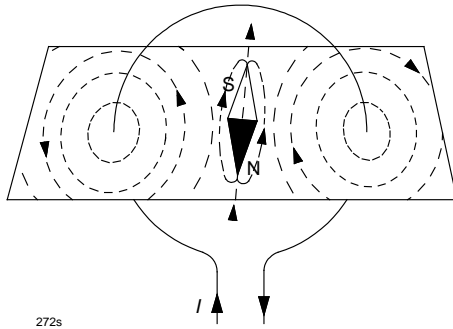


9.9

Right hand rule:


"If you keep on the coil with your right hand so that the fingers pointing in the direction of the current, the thumb is pointing toward the north end."

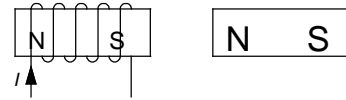This force is attractive because the electromagnet and permanent magnet face different poles to each other.



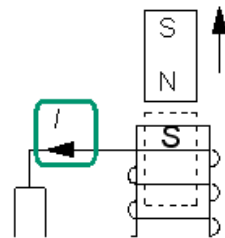9.10

The current is to counteract the movement. So will it be if the magnet leaves the coil at the "south side" (= attraction between the coil and magnet). Right hand rule then gives the current direction out from the winding.



9.11

$$L = 1 = 100^2 \cdot K \Rightarrow K = 10^{-4}$$

$$0,5 = N_x^2 \cdot 10^{-4} \Rightarrow N_x = \sqrt{5000} = 71 \quad 71 - 100 = 29$$

Unwind 29 turns (100-71) for the inductance to decrease by half.

Transients with RC and L/R

10.1

The circuit has the time constant $\tau = R \cdot C = 500 \cdot 500 \cdot 10^{-6} = 0,25$ s. Capacitor is at first moment uncharged, when connected it will charge to + 10 V. For the voltages Kirchoff's voltage law applies $E + U_C + U_R = 0$.

At time $t = 0$: $10 + 0 + U_R = 0$. At time $t = \infty$: $10 + 10 + U_R = 0$.

We get for U_R :

$$u_{\infty} = 0 \quad u_0 = 10.$$

$$a) \quad x(t) = x_{\infty} - (x_{\infty} - x_0)e^{-\frac{t}{\tau}} \Rightarrow u_R(t) = 0 - (0 - 10)e^{-\frac{t}{0,25}} = 10e^{-4t}$$

$$2 = 10e^{-4t} \Leftrightarrow 0,2 = e^{-4t} \Leftrightarrow \ln 0,2 = \ln e^{-4t} = -4t \Rightarrow t = -\frac{\ln 0,2}{4} = 0,4 \text{ s}$$

b) When the voltage over C is 2 V it will be 8 V over R .

$$8 = 10e^{-4t} \Leftrightarrow 0,8 = e^{-4t} \Leftrightarrow \ln 0,8 = \ln e^{-4t} = -4t \Rightarrow t = -\frac{\ln 0,8}{4} = 0,06 \text{ s}$$

10.2

When the three components has the same voltage it will be $\frac{1}{3}10 = 3,33$ V.

The two resistors can be merged to one $R' = 2\text{k}\Omega$. We let $U_C(t)$ be $x(t)$ in the formula for exponential process. Startvalue $U_C(t) = 0$ (from the beginning the capacitor is empty)

Endvalue $U_C(t = \infty) = 10$ V (the capacitor is charged to the full voltage after a long time)

$$\tau = R \cdot C = 2 \cdot 10^3 \cdot 1000 \cdot 10^{-6} = 2 \text{ s}.$$

$$x(t) = x_{\infty} - (x_{\infty} - x_0)e^{-\frac{t}{\tau}}$$

$$U_C(t) = 10 - (10 - 0)e^{-\frac{t}{2}} \Rightarrow U_C(t) = 10 - 10e^{-\frac{t}{2}}$$

$$0,667 = e^{-0,5 \cdot t} \Leftrightarrow \ln(0,667) = -0,5 \cdot t \Rightarrow t = \frac{0,405}{0,5} = \mathbf{0,81 \text{ s}}$$

10.3

The two resistors can be merged to one $R = \frac{R_1 \cdot R_2}{R_1 + R_2} = \frac{5 \cdot 15}{5 + 15} = 3750 \Omega$.

a) Timeconstant is: $\tau = R \cdot C = 3750 \cdot 10 \cdot 10^{-6} = \mathbf{0,038 \text{ s}}$.


b) When current through R_1 is 3 mA it will be 1 mA through R_2 . Both resistors are in parallel and has the same voltage over them. Currents will then be inversely proportional to the resistances. The total current is $I_{\text{TOT}} = 4$ mA. Use $x = I_{\text{TOT}}$ in the formula for exponential process. From the beginning the capacitor is empty

and then $I_{\text{TOT}} = \frac{E}{R} = 5,9 \cdot 10^{-3}$. After a long time the capacitor will be full and

then $I_{\text{TOT}} = 0$.

$$I_{\text{TOT}}(t) = 0 - (0 - \frac{E}{R})e^{-\frac{t}{\tau}} \Rightarrow I_{\text{TOT}}(t) = 5,9 \cdot 10^{-3} e^{-\frac{t}{0,038}}$$
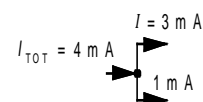
$$4 \cdot 10^{-3} = 5,9 \cdot 10^{-3} e^{-26,3t} \Leftrightarrow \ln(\frac{4}{5,9}) = -26,3 \cdot t \Rightarrow t = \frac{2,69}{26,3} = \mathbf{0,014 \text{ s}}$$



$$x(t) = x_{\infty} - (x_{\infty} - x_0)e^{-\frac{t}{\tau}}$$

10.4

a) Series connected capacitors:

$$C = \frac{C_1 \cdot C_2}{C_1 + C_2} = \frac{25 \cdot 15}{25 + 15} \cdot 10^{-6} = 9,38 \cdot 10^{-6} = 9,38 \mu\text{F}$$

$$\tau = R \cdot C = 330 \cdot 10^3 \cdot 9,38 \cdot 10^{-6} = \mathbf{3,1 \text{ s}}$$

$$b) x(t) = x_\infty - (x_\infty - x_0) e^{-\frac{t}{\tau}}$$

After long time ($t = \infty$) there will be $E = 15 \text{ V}$ over the series connected capacitors. The charge Q is the same in both capacitors (no charge can pass through a capacitor).

$$E = \frac{Q}{C} \Rightarrow Q = E \cdot C = 15 \cdot 9,38 \cdot 10^{-6} = 141 \mu\text{C} \quad u_{C2}(t = \infty) = \frac{Q}{C_2} = \frac{143 \cdot 10^{-6}}{15 \cdot 10^{-6}} = 9,38 \text{ V}$$

At beginning the capacitors are empty. $u_{C2}(t = 0) = 0$. We get:

$$u_{C2}(t) = u_{C2_\infty} - (u_{C2_\infty} - u_{C2_0}) e^{-\frac{t}{\tau}} \Leftrightarrow u_{C2}(t) = 9,38(1 - e^{-0,32t})$$

$$u_{C2}(t) = 2 \text{ vid } t = ?$$

$$2 = 9,38(1 - e^{-0,32t}) \Leftrightarrow \left(\frac{2}{9,38} - 1\right) = -e^{-0,32t} \Leftrightarrow \ln(0,79) = \ln(e^{-0,32t}) \Leftrightarrow -0,24 = -0,32 \cdot t \Rightarrow t = \mathbf{0,75 \text{ s}}$$

10.5

The capacitor is first charged to 5 V, at the change of the circuit it will be further charged towards 15 V.

We get $u_\infty = 15$ $u_0 = 5$. The time constant of the circuit is $\tau = R \cdot C = 2000 \cdot 1000 \cdot 10^{-6} = 2 \text{ s}$.

$$x(t) = x_\infty - (x_\infty - x_0) e^{-\frac{t}{\tau}} \Rightarrow u(t) = 15 - (15 - 5) e^{-\frac{t}{2}} = 15 - 10e^{-\frac{t}{2}}$$

$$10 = 15 - 10 e^{-\frac{t}{2}} \Leftrightarrow -5 = -10 e^{-\frac{t}{2}} \Leftrightarrow \ln \frac{5}{10} = \ln e^{-\frac{t}{2}} = -\frac{t}{2} \Rightarrow t = -2 \ln \frac{5}{10} = 1,39 \text{ s}$$

When the capacitor is fully charged the current will cease. This will happen after about 10 s (5 time constants).

10.6

$$u(t) = 2 \quad u_\infty = 0 \quad u_0 = 12 \quad \tau = R \cdot C = 110 \cdot 10000 \cdot 10^{-6} = 1,1 \text{ s}$$

$$x(t) = x_\infty - (x_\infty - x_0) e^{-\frac{t}{\tau}} \Rightarrow 2 = 0 - (0 - 12) e^{-\frac{t}{1,1}}$$

$$\frac{2}{12} = e^{-\frac{t}{1,1}} \Leftrightarrow 1,1 \cdot \ln\left(\frac{1}{6}\right) = -t \Rightarrow t = 1,97 \approx \mathbf{2 \text{ s}}$$

An exponentially process can be considered as terminated after $5 \cdot \tau = 5 \cdot 1,1 = \mathbf{5,5 \text{ s}}$.

10.7

x_0 = entity start value $i(0) = 0$

$$x_\infty = \text{entity end value} \quad i(\infty) = \frac{E}{R} = \frac{12}{12} = 1 \quad b) \frac{12}{24} = 0,5$$

$$\tau = \text{time constant} = \frac{L}{R} = \frac{0,8}{12} = 0,06 \quad b) \frac{0,8}{24} = 0,03$$

$$x(t) = x_\infty - (x_\infty - x_0) e^{-\frac{t}{\tau}}$$

$$a) i(t) = 1 - (1 - 0) e^{-\frac{t}{0,06}} = 1 - e^{-\frac{t}{0,06}} \Rightarrow i(t = 0,1) = 1 - e^{-\frac{0,1}{0,06}} = \mathbf{0,81 \text{ A}}$$

$$b) i(t) = 0,5 - (0,5 - 0) e^{-\frac{t}{0,03}} = 0,5 \cdot (1 - e^{-\frac{t}{0,03}}) \Rightarrow i(t = 0,1) = 0,5 \cdot (1 - e^{-\frac{0,1}{0,03}}) = \mathbf{0,48 \text{ A}}$$

10.8

a) The inductor has a current inertia so at the beginning the current stays at 0.

b) After a long time the current through the inductor is constant (no change), $\frac{di}{dt} = 0$, and the emf over the inductor is then $e = L \frac{di}{dt} = 0$. The inductor zero emf short circuits the parallel 100 Ω resistor. Current is

limited by the series resistor with the value 100 Ω . $I = \frac{10}{100} = 0,1 \text{ A}$.

c) When the switch breaks the circuit the current will subside to zero with a time constant of

$$\tau = \frac{L}{R} = \frac{1}{100} = 0,01 \text{ s}$$

$$x(t) = x_{\infty} - (x_{\infty} - x_0) e^{-\frac{t}{\tau}} \Rightarrow i_L(t) = 0 - (0 - 0,1) e^{-\frac{t}{0,01}} = 0,1 e^{-\frac{t}{0,01}}$$

10.9

The circuit has the Thevenin equivalent: $R_1 = 600 \parallel 400 = 240 \text{ k}\Omega$ $E_0 = 200 \cdot 400 / 1000 = 80 \text{ V}$

a)

$$\tau = R_1 \cdot C = 240 \cdot 10^3 \cdot 2,2 \cdot 10^{-6} = 0,528$$

$$t = \tau \cdot \ln \frac{\text{all}}{\text{the rest}} = 0,528 \cdot \ln \frac{80 - 0}{80 - 65} = 0,88 \text{ s}$$

b)

$$\tau = 0,528$$


$$t = \tau \cdot \ln \frac{\text{all}}{\text{the rest}} = 0,528 \cdot \ln \frac{80 - 55}{80 - 65} = 0,27 \text{ s}$$

c)


If R_2 is gone E will not be voltage divided. $E = 200$. Time constant will change.

$$\tau = R_1 \cdot C = 600 \cdot 10^3 \cdot 2,2 \cdot 10^{-6} = 1,32$$
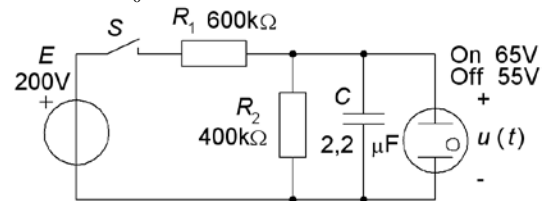
$$t = \tau \cdot \ln \frac{\text{all}}{\text{the rest}} = 1,32 \cdot \ln \frac{200 - 55}{200 - 65} = 0,094 \text{ s}$$




10.10

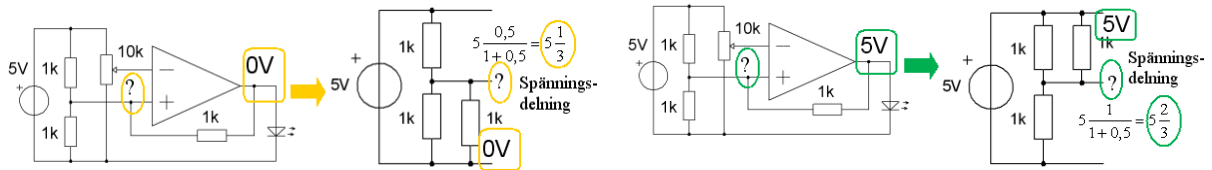

$$U_{TH-} = 5 \frac{1}{3} \approx 1,67 \text{ V}$$
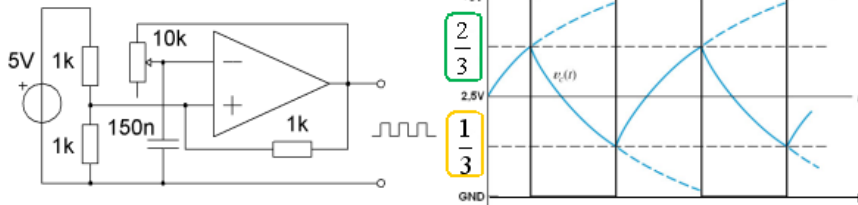
$$U_{TH+} = 5 \frac{2}{3} \approx 2,33 \text{ V}$$



$$\tau = R \cdot C = 5 \cdot 10^3 \cdot 150 \cdot 10^{-9} = 0,75 \cdot 10^{-3}$$

$$t_1 = \tau \cdot \ln \frac{\text{all}}{\text{the rest}} = 0,75 \cdot 10^{-3} \cdot \ln \frac{5 - \frac{1}{3} \cdot 5}{\frac{1}{3} \cdot 5} = 0,75 \cdot 10^{-3} \cdot \ln 2 = 5,2 \text{ ms}$$

$$t_2 = t_1 \quad T = 2 \cdot t_1 = 2 \cdot 5,2 \cdot 10^{-3} = 10,4 \text{ ms} \quad f = \frac{1}{T} = \frac{1}{10,4 \cdot 10^{-3}} = 962 \text{ Hz}$$

We can shorten away the supply voltage 5V. The frequency is thus independent of the supply voltage!

10.11

$$R(\vartheta) = 100 \cdot (1 + 3,85 \cdot 10^{-3} \cdot \vartheta) [\Omega]$$

$$R_0 = 176 \Omega$$

$$R(t = 10 \text{ min}) = 139 \Omega$$

$$R_\infty = R(\vartheta = 25^\circ) = 100 \cdot (1 + 3,85 \cdot 10^{-3} \cdot 25) = 109,6 [\Omega]$$

$$x(t) = x_\infty - (x_\infty - x_0) e^{-\frac{t}{\tau}} \Rightarrow R(t = 10 \text{ min}) = 139 = 109,6 - (109,6 - 176) e^{-\frac{10}{\tau}}$$


$$0,443 = e^{-\frac{10}{\tau}} \Leftrightarrow \ln(0,443) = -\frac{10}{\tau} \Rightarrow \tau = \frac{10}{0,815} = 12,3 \text{ minuter}$$

AC voltage and current, phasor

11.1


a) $x(t) = 6 \sin(2000\pi \cdot t + \pi/6)$

b)

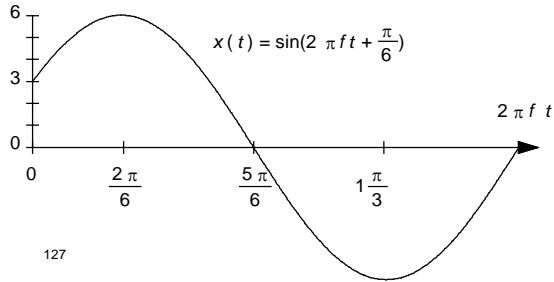


127

c)

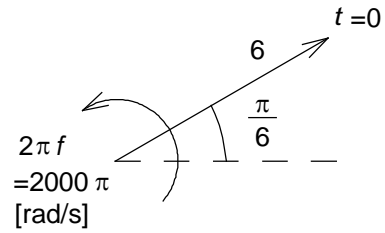

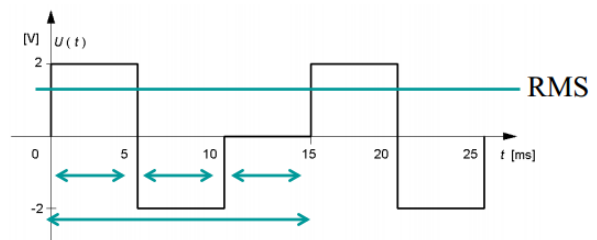11.2

$$U = \sqrt{\frac{\int_0^T u(t)^2 dt}{T}} = \sqrt{\frac{(2^2 + (-2)^2 + 0) \cdot 5 \cdot 10^{-3}}{15 \cdot 10^{-3}}} = \sqrt{\frac{8 \cdot 5 \cdot 10^{-3}}{15 \cdot 10^{-3}}} = 1,63 \text{ V}$$



11.3


$$U = \sqrt{\frac{\int_0^T u(t)^2 dt}{T}} = \hat{U} \sqrt{\frac{\int_0^T \sin^2(\omega t) dt}{T}} = \hat{U} \sqrt{\frac{\int_0^T \sin^2\left(\frac{2\pi t}{T}\right) dt}{T}} = \hat{U} \sqrt{\frac{1}{2}} = \frac{\hat{U}}{\sqrt{2}}$$

Phasor chart


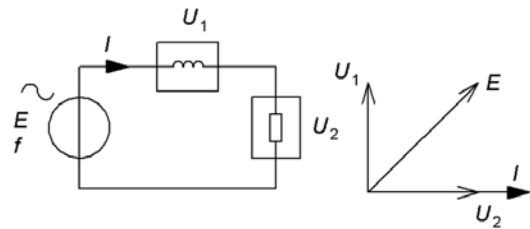
11.4

I identify what components that have given the voltage phasors U_1 and U_2 .

U_2 has the same phase as the current so it is a resistor that has given the voltage phasor. U_1 is earlier in phase than I so here we have a component with a current inertia, an inductance.



11.5

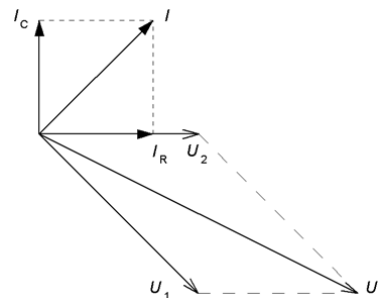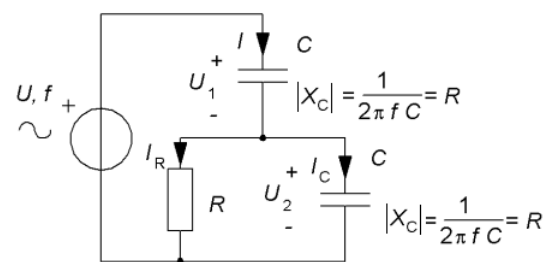

1) U_2 reference phase (=horizontal)

2) $\bar{I}_R \parallel \bar{U}_2 \xrightarrow{U_R} I_R$


3) $\bar{I}_C \perp \bar{U}_2 \quad I_C = I_R = \frac{U_2}{R}$

4) $\bar{I} = \bar{I}_R + \bar{I}_C \quad I = \sqrt{2} \cdot I_C$

5) $\bar{U}_1 \perp \bar{I}$


$U_1 = I \cdot R = I_C \cdot \sqrt{2} \cdot R \Rightarrow U_1 = \sqrt{2} \cdot U_2$

6) $\bar{U} = \bar{U}_1 + \bar{U}_2$

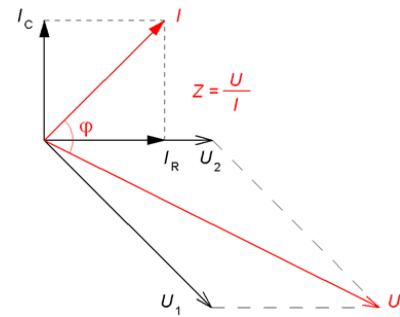

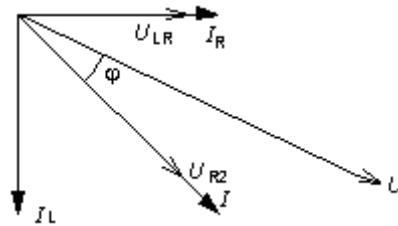11.6


$X_L = 2 \cdot \pi \cdot f \cdot L = 2 \cdot \pi \cdot 50 \cdot 0,318 = 100 \Omega$. We choose U_{LR} as reference phase. Current I_R has the same direction as U_{LR} . Current I_L is 90° after U_{LR} and has a equally long phasor as I_R because R_1 and L has the same resistance to the alternating current ($X_L = 100 \Omega, R_1 = 100 \Omega$). The two currents I_L and I_R can be added as vectors to a vector $I, \bar{I} = \bar{I}_R + \bar{I}_L$. I is $\sqrt{2}$ times longer than I_L and I_R (Pythagorean Theorem). Current I passes through the lower resistor R_2 . The voltaged rop over U_{R2} will have the same direction as I and is $\sqrt{2}$ times bigger than U_{LR} (because the resistors are equal and the current is so many times larger). The voltage U can finally determined as the vector sum of U_{LR} och U_{R2} ;
 $\bar{U} = \bar{U}_{LR} + \bar{U}_{R2}$.



The angle φ is the angle between voltage U over the whole circuit and the current I flowing in to it.

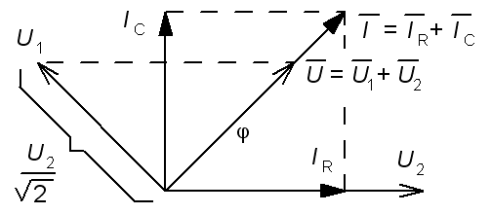
11.7

Start with U_2 as reference phase. The current I_R has the same direction as U_2 . ($U_2 = I_R \cdot R$)
 Current I_C is 90° before U_2 and is equally big as I_R (because $X_C = R$)
 Currents I_C and I_R are summed to $I. \bar{I} = \bar{I}_R + \bar{I}_C \quad I = \sqrt{2} \cdot I_R$ (Pythagorean Theorem)
 U_1 is 90° before $I. U_1 = I \cdot X_L = \sqrt{2} \cdot I_R \cdot \frac{R}{2} = \frac{I_R \cdot R}{\sqrt{2}}$



The voltages U_1 and U_2 are summed to the voltage $U. \bar{U} = \bar{U}_1 + \bar{U}_2$.
 (One can se that U will get equally big as U_1 !)

11.8

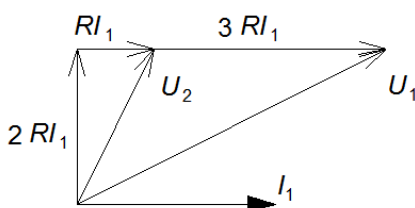

Alternating voltage and current, $j\omega$ -method

12.1

$$\underline{I} = \underline{I}_R + \underline{I}_C = \frac{U}{R} + \frac{U}{\frac{1}{j\omega C}} = \frac{U}{R} + j\omega C \cdot U$$

12.2

$$\underline{Z} = \frac{U}{\underline{I}} = \frac{220}{10 \cdot \cos(30^\circ) + 10j \cdot \sin(30^\circ)} = \frac{220}{8,6 + 5j} \cdot \frac{(8,6 - 5j)}{(8,6 - 5j)} = \frac{1892 - 1100j}{99} = 19,1 - 11,1j$$

this impedance could be a resistor $R = 19,1 \Omega$ in series with a capacitor with the reactance $X_C = -11,1 \Omega$.

$$X_C = -\frac{1}{\omega C} = -11,1 \Rightarrow C = -\frac{1}{2\pi \cdot 50 \cdot (-11,1)} = 287 \mu\text{F}$$


12.3

$$\underline{U}_2 = \underline{U}_1 \cdot \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \cdot \frac{(j\omega C)}{(j\omega C)} = \underline{U}_1 \cdot \frac{1}{1 + j\omega RC} \Rightarrow \frac{U_1}{U_2} = \sqrt{1 + R^2 \omega^2 C^2} = \frac{10}{5} = 2$$

$$1 + R^2 \omega^2 C^2 = 4 \Leftrightarrow R\omega C = \sqrt{3} \Leftrightarrow RC = \frac{\sqrt{3}}{\omega}$$

12.4

$$\underline{I} = \frac{U}{\underline{Z}} \Rightarrow I = \frac{88}{|(30 + 10) + j40|} = \frac{88}{\sqrt{(30 + 10) + 40^2}} = 1,56 \text{ A}$$

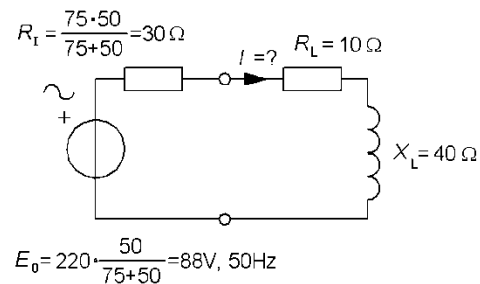

12.5

Parallel connection:

$$\underline{I} = \underline{I}_R + \underline{I}_C = \frac{U}{R} + U \cdot j\omega C$$

$$I_R = \frac{U}{R} \quad I_C = U\omega C$$

$$\underline{I} = 2 + 2j$$

Serial connection:

$$\underline{I} = \frac{U}{R + \frac{1}{j\omega C}} \Rightarrow I = \frac{U}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}}$$

$$R = \frac{1}{\omega C} = \frac{E}{2} \Rightarrow I = \frac{U}{U \cdot \sqrt{\frac{1}{4} + \frac{1}{4}}} = \sqrt{2} \text{ A}$$

12.6

$$\underline{Z}_{AB} = \frac{(15 + j20) \cdot (10 - j20)}{15 + j20 + 10 - j20} = \frac{550 - j100}{25} = 22 - j4 [\Omega]$$

12.7

$$\underline{Z} = \frac{(R + \frac{1}{j\omega C}) \cdot j\omega L}{R + j\omega L + \frac{1}{j\omega C}} = \frac{\frac{L}{C} + j\omega LR}{R + j(\omega L - \frac{1}{\omega C})} \quad \underline{I} = \frac{U}{\underline{Z}} = U \cdot \frac{R + j(\omega L - \frac{1}{\omega C})}{\frac{L}{C} + j\omega LR}$$

12.8

Voltage U is directly over the parallel branch with the inductance L .

$$\underline{I} = \frac{U}{j\omega L} = -j \frac{U}{\omega L}$$

12.9

$$\underline{Z}_{R2C} = \frac{2 \cdot (-8j) \cdot (2+8j)}{2-8j \cdot (2+8j)} = 1,88 - 0,47j$$

$$\underline{Z} = 3 + 6j + 1,88 - 0,47j = 4,88 + 5,53j \quad Z = \sqrt{4,88^2 + 5,53^2} = 7,38 \Omega$$

$$\underline{I} = \frac{U}{\underline{Z}} = \frac{30}{4,88 + 5,53j} \cdot \frac{(4,88 - 5,53j)}{(4,88 - 5,53j)} = \frac{146,5 - 165,9j}{54,41} = 2,7 - 3j \quad I = \sqrt{2,7^2 + 3^2} = 4 \text{ A}$$


$$\underline{I}_C = \frac{2(2,7 - 3j) \cdot (2+8j)}{2-8j \cdot (2+8j)} = 0,86 + 0,46j \quad I_C = \sqrt{0,86^2 + 0,46^2} = 0,98 \text{ A}$$

$$\underline{U}_L = 30 \frac{6j}{3+6j+(1,88-0,47j)} = 30 \frac{6j}{4,88+5,53j} \cdot \frac{(4,88-5,53j)}{(4,88-5,53j)} = 18,3 + 16,2j \quad U_L = 24,4 \text{ V}$$

12.10

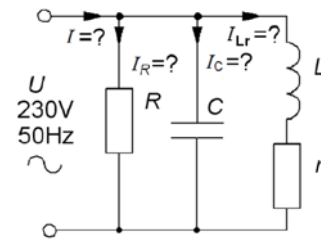a) \underline{U} and \underline{I}_R are in phase and will be our reference phase with, $\arg(\underline{U}) = 0$

$$U = R \cdot I_R \Rightarrow I_R = \frac{U}{R} = \frac{230}{46} = 5 \text{ A}$$



b)

$$\underline{U} = \frac{1}{j\omega C} \underline{I}_C \Rightarrow U = \frac{1}{\omega C} I_C \Rightarrow I_C = U \cdot \omega C = 230 \cdot 2 \cdot \pi \cdot 50 \cdot 69 \cdot 10^{-6} \approx 5 \text{ A}$$

$$\arg(\underline{I}_C) = \arg(\underline{U}) + \arg(j\omega C) = 0^\circ + 90^\circ = 90^\circ$$

c)

$$\underline{U} = \underline{Z}_{Lr} \cdot \underline{I}_{Lr} = (r + j\omega L) \cdot \underline{I}_{Lr} \Rightarrow I_{Lr} = \frac{U}{\sqrt{r^2 + (\omega L)^2}} = \frac{230}{\sqrt{32,5^2 + (32,5)^2}} \approx 5 \text{ A}$$

$$\arg(\underline{I}_{Lr}) = \arg(\underline{U}) - \arg(\underline{Z}_{Lr}) = 0^\circ - \arctan \frac{32,5^2}{32,5^2} = -45^\circ$$


d)

$$\underline{I} = \underline{I}_C + \underline{I}_R + \underline{I}_{Lr}$$

$$I = \sqrt{(I_C - I_{Lr} \cdot \sin 45^\circ)^2 + (I_R + I_{Lr} \cdot \cos 45^\circ)^2} =$$

$$= \sqrt{(5 - 5 \cdot 0,71)^2 + (5 + 5 \cdot 0,71)^2} =$$
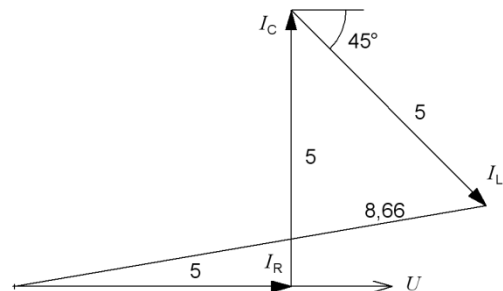
$$= \sqrt{1,46^2 + 8,54^2} = \sqrt{75} \approx 8,66 \text{ A}$$



12.11

a) \underline{U}_{UT} are chosen as reference phase, $\arg(\underline{U}_{UT}) = 0$

$$\underline{U}_{UT} = j\omega L \cdot \underline{I}_L \quad \underline{U}_{UT} = U_{UT} = 6,28$$

$$\underline{I}_L = \frac{\underline{U}_{UT}}{j\omega L} = \frac{6,28}{j \cdot 2\pi \cdot 1000 \cdot 10 \cdot 10^{-3}} = -0,1j$$

$$I_L = 0,1 \text{ A}$$



b) $\underline{U}_R = R \cdot \underline{I}_L = -50 \cdot 0,1j = -5j \quad U_R = 5 \text{ V}$

c) $\underline{U}_{IN} = \underline{U}_R + \underline{U}_{UT} = 6,28 - 5j \quad U_{IN} = \sqrt{6,28^2 + 5^2} = 8,0 \text{ V}$

$$\underline{I}_S = \frac{\underline{U}_{IN}}{R_S} = \frac{6,28 - 5j}{100} = 0,063 - 0,05j$$

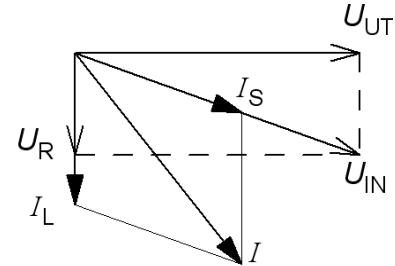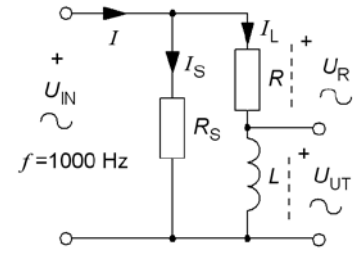d) $\underline{I} = \underline{I}_L + \underline{I}_S = -0,1j + 0,063 - 0,05j = 0,062 - 0,15j$

$$I = \sqrt{0,063^2 + 0,15^2} = 0,16 \text{ A}$$



Resonance

13.1

Because $|U_C| = |U_L|$ there is resonance. The voltage drops over L and C will cancel each other and left over will be 1 V over R .

$$U = 1 \text{ V.}$$

13.2

Because $|I_C| = |I_L|$ there is resonance. $I = 1 \text{ A}$, the current in L and C is a circulating current, $I_C = -I_L$.

13.3

$$\underline{I} = \underline{I}_C + \underline{I}_{LR} = \frac{U}{j\omega C} + \frac{U}{R + j\omega L} \cdot \frac{(R - j\omega L)}{(R - j\omega L)} = U \cdot \left(j\omega C + \frac{R - j\omega L}{R^2 + (\omega L)^2} \right) =$$

$$= U \cdot \left(\frac{R}{R^2 + (\omega L)^2} + j \left(\omega C - \frac{\omega L}{R^2 + (\omega L)^2} \right) \right)$$

We have here chosen U as reference phase, real. Current I must then also be real to be in phase with voltage.

This provides the condition that $\text{Im}[\underline{I}] = 0$.

$$\omega C = \frac{\omega L}{R^2 + (\omega L)^2} \Rightarrow \omega^2 = \frac{1}{LC} - \frac{R^2}{L^2} \quad \omega = 2\pi f \Rightarrow f = \frac{1}{2\pi} \sqrt{\left(\frac{1}{LC} - \frac{R^2}{L^2} \right)}$$

This frequency is the **resonance frequency**.

13.4

a) Q-value. $BW = \frac{f_0}{Q} \Rightarrow Q = \frac{f_0}{BW} = \frac{2000}{200} = 10.$

b) $R_S = 2 \Omega \quad Q = \frac{X_L}{R_S} \Rightarrow X_L = Q \cdot R_S = 10 \cdot 2 = 20 \Omega$

c) $X_L = 2\pi f_0 L \Rightarrow L = \frac{X_L}{2\pi f_0} = \frac{20}{2\pi \cdot 2000} = 1,59 \text{ mH} \quad X_L = X_C$

$$X_C = \frac{1}{2\pi f_0 C} \Rightarrow C = \frac{1}{2\pi f_0 X_C} = \frac{1}{2\pi \cdot 2000 \cdot 20} = 3,98 \mu\text{F}$$

d) $f_1 \approx f_0 - \frac{BW}{2} = 1900 \quad f_2 \approx f_0 + \frac{BW}{2} = 2100$

$$f_0 = \sqrt{f_1 \cdot f_2} = \sqrt{1900 \cdot 2100} = 1997 \approx 2000 \text{ OK!}$$

13.5

a) The coil Q-value, parallel resistance. $Q = \frac{X_L}{R_S} = \frac{30}{2} = 15 \quad R = Q^2 \cdot r = 15^2 \cdot 2 = 450 \Omega$

b) $Z_{ERS} = 450 \parallel 450 = 225 \Omega$

c) $I \cdot Z_{ERS} = 80 \cdot 10^{-3} \cdot 225 = 18 \text{ V} \quad I_C = \frac{18}{-j30} \Rightarrow I_C = 0,6 \text{ A} \angle +90^\circ$

$$I_{Lr} = \frac{18}{2 + j30} \Rightarrow I_L \approx 0,6 \text{ A} \angle -86^\circ$$

d) $L = \frac{X_L}{2\pi f_0} = \frac{30}{2\pi \cdot 20 \cdot 10^3} = 0,24 \text{ mH} \quad C = \frac{1}{2\pi f_0 \cdot |X_C|} = \frac{1}{2\pi \cdot 20 \cdot 10^3 \cdot 30} = 265 \text{ nF}$

e) $Q_{TOT} = \frac{225}{30} = 7,5 \quad BW = \frac{f_0}{Q} = \frac{20 \cdot 10^3}{7,5} = 2,67 \text{ kHz}$

13.6

a) $f_0 = \frac{1}{2\pi \sqrt{L \cdot C}} = \frac{1}{2\pi \sqrt{5 \cdot 10^{-6} \cdot 25 \cdot 10^{-12}}} = 14,2 \text{ MHz}$

b) The coil Q-value

$$Q = \frac{2\pi f_0 \cdot L}{r} = \frac{2\pi \cdot 14,2 \cdot 10^6 \cdot 5 \cdot 10^{-6}}{0,5} = 894$$

c) Total parallel resistance for $Q = 500$ will be:

$$R_{Q500} = 500 \cdot 2\pi f_0 \cdot L = 500 \cdot 2\pi \cdot 14,2 \cdot 10^6 \cdot 5 \cdot 10^{-6} = 224 \text{ k}\Omega$$

The coil resistance transformed to parallel resistance will be:

$$R = Q^2 \cdot r = 894^2 \cdot 0,5 = 400 \text{ k}\Omega$$

Chose R_X so that:

$$R_{Q500} = R_X \parallel R \Rightarrow R_X = \frac{R \cdot R_{Q500}}{R - R_{Q500}} = \frac{400 \cdot 224}{400 - 224} = 507 \text{ k}\Omega$$

13.7

$$f_0 = \frac{1}{2\pi\sqrt{L \cdot C}} \Rightarrow C = \frac{1}{4\pi^2 L f_0^2} = \frac{1}{4\pi^2 \cdot 2,5 \cdot 10^{-6} \cdot (13,56 \cdot 10^6)^2} = 55 \text{ pF}$$

$$Q = \frac{\omega L}{r} = \frac{2\pi f_0 \cdot L}{r} = \frac{2\pi \cdot 13,56 \cdot 10^6 \cdot 2,5 \cdot 10^{-6}}{1,5} = 142$$

$$R = Q^2 \cdot r = 142^2 \cdot 1,5 = 30,25 \text{ k}\Omega$$

$$Q_{\text{BW}} = \frac{f_0}{\Delta f} = \frac{13,56 \cdot 10^6}{140 \cdot 10^3} = 96,86 \quad Q_{\text{BW}} = \frac{R_{\text{BW}}}{2\pi \cdot f_0 \cdot L} \Rightarrow$$

$$R_{\text{BW}} = Q_{\text{BW}} \cdot 2\pi \cdot f_0 \cdot L = 96,86 \cdot 2\pi \cdot 13,56 \cdot 10^6 \cdot 2,5 \cdot 10^{-6} = 20,63 \text{ k}\Omega$$

$$R_{\text{BW}} = R_X \parallel R \Rightarrow R_X = \frac{R \cdot R_{\text{BW}}}{R - R_{\text{BW}}} = \frac{30,25 \cdot 20,63}{30,25 - 20,63} \cdot 10^3 = 64 \text{ k}\Omega$$

If the electronics are power efficient and does not consume more current than a 64 k resistor the resonance circuit will have a bandwidth of 140 kHz. Unnecessarily large bandwidth increases sensitivity to disturbances.

13.8



$$a) f_0 = \frac{1}{2\pi\sqrt{L \cdot C}} = \frac{1}{2\pi\sqrt{0,43 \cdot 10^{-3} \cdot 3,77 \cdot 10^{-9}}} = 125 \text{ kHz}$$

$$b) Q_L = \frac{2\pi f_0 \cdot L}{r} = \frac{2\pi \cdot 125 \cdot 10^3 \cdot 4,3 \cdot 10^{-3}}{4} = 84,4$$

$$c) R_{\text{PIC}} = 20 \cdot 10^3 \quad r_{\text{PIC}} = \frac{R_{\text{PIC}}}{Q_L^2} = \frac{20 \cdot 10^3}{84,4^2} = 2,8 \Omega \quad Q_{\text{res}} = \frac{2\pi f_0 \cdot L}{r_{\text{PIC}} + r_L} = \frac{338}{4 + 2,8} = 50$$

$$d) Q_{\text{res}} = \frac{f_0}{\text{BW}} \Rightarrow \text{BW} = \frac{f_0}{Q_{\text{res}}} = \frac{125 \cdot 10^3}{50} = 2,5 \text{ kHz}$$

Interested in the function? PIC processor has "protection diodes" inside the chip – these will now act as rectifier diodes and rectify the 125-kHz signal to provide power to the CPU. A capacitor C_{PWR} keeps the supply voltage stable (the chip internal capacitance will be enough). The processor uses the 125-kHz-signal as its clock (CLKIN). One instruction takes 4 clockcycles. A program that sends a bit "1" can look like this:

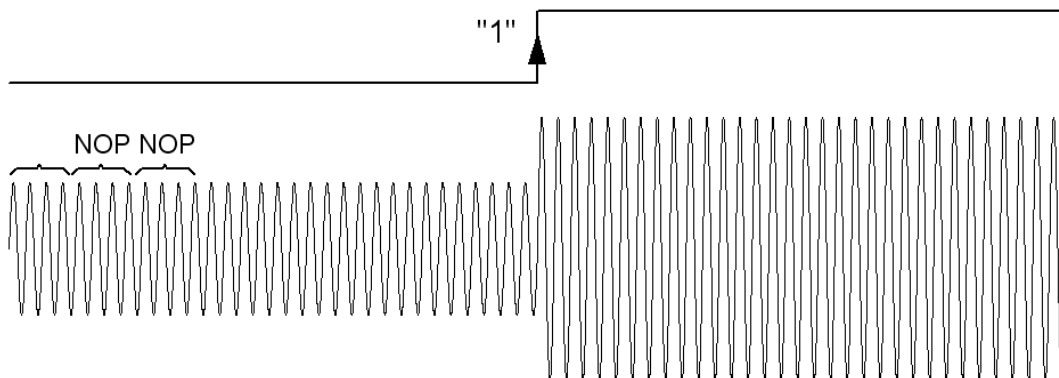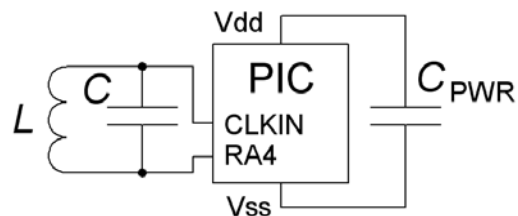

```
TRISA.5 = 1; /* CLKIN is input */
PORTA.4 = 0;
TRISA.4 = 0; /* RA4 pin at GND, RF-signal is damped */
nop(); nop(); nop(); nop(); nop(); nop(); nop();
TRISA.4 = 1; /* RA4 pin is threestate, RF-signal is undamped */
nop(); nop(); nop(); nop(); nop(); nop(); nop();
```


Filter

14.1

$$\frac{\underline{U}_2}{\underline{U}_1} = \frac{j\omega L}{R + j\omega L} = \frac{j\omega \frac{L}{R}}{1 + j\omega \frac{L}{R}} \quad \left| \frac{\underline{U}_2}{\underline{U}_1} \right| = \frac{|j\omega L|}{|R + j\omega L|} = \frac{\omega L}{\sqrt{R^2 + (\omega L)^2}}$$

$$\arg\left(\frac{\underline{U}_2}{\underline{U}_1}\right) = \arg\left(\frac{j\omega L}{R + j\omega L}\right) = \arg(j\omega L) - \arg(R + j\omega L) = 90^\circ - \arctan\left(\frac{\omega L}{R}\right) =$$
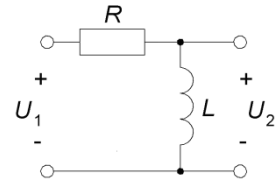
$$= \arctan\left(\frac{R}{\omega L}\right) \quad R^2 = (\omega L)^2 \quad \omega = 2\pi \cdot f_G \Rightarrow f_G = \frac{R}{2\pi L} \quad \text{HP}$$



14.2

$$R \parallel C = \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \cdot \frac{j\omega C}{j\omega C} = \frac{R}{1 + j\omega RC} \quad \underline{I}_C = \frac{\underline{U}_C}{\frac{1}{j\omega C}} = \underline{U}_C \cdot j\omega C$$

$$\underline{U}_C = U \cdot \frac{\frac{R}{1 + j\omega RC}}{R + \frac{1}{1 + j\omega RC}} \cdot \frac{1 + j\omega RC}{R} = U \frac{1}{1 + j\omega RC + 1} \Rightarrow \underline{I}_C = U \frac{j\omega C}{2 + j\omega RC}$$

14.3

$$R_1 \parallel C = \frac{R_1 \cdot \frac{1}{j\omega C}}{R_1 + \frac{1}{j\omega C}} \cdot \frac{j\omega C}{j\omega C} = \frac{R_1}{j\omega R_1 C + 1}$$

$$\frac{\underline{U}_2}{\underline{U}_1} = \frac{R_2}{R_2 + \frac{R_1}{j\omega R_1 C + 1}} \cdot \frac{j\omega R_1 C + 1}{j\omega R_1 C + 1} = \frac{R_2(j\omega R_1 C + 1)}{R_2(j\omega R_1 C + 1) + R_1} = \frac{j\omega R_1 R_2 C + R_2}{j\omega R_1 R_2 C + (R_1 + R_2)}$$




$$\omega \approx 0 \Rightarrow \frac{\underline{U}_2}{\underline{U}_1} \approx \frac{R_2}{R_1 + R_2} \quad \frac{\underline{U}_2}{\underline{U}_1} = \frac{1}{3} \quad \arg\left(\frac{\underline{U}_2}{\underline{U}_1}\right) \approx 0^\circ$$

$$\omega \rightarrow \infty \Rightarrow \frac{\underline{U}_2}{\underline{U}_1} = 1 \quad \arg\left(\frac{\underline{U}_2}{\underline{U}_1}\right) \approx 0^\circ$$

The crossover frequency is when the numerators real part is equal to its imaginary part:

$$\omega R_1 R_2 C = (R_1 + R_2) \Rightarrow \omega = \frac{(R_1 + R_2)}{R_1 R_2 \cdot C} \Rightarrow f = \frac{(R_1 + R_2)}{2\pi \cdot R_1 R_2 \cdot C}$$
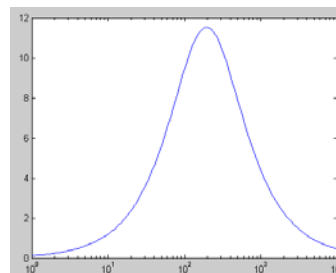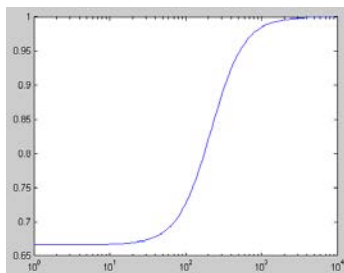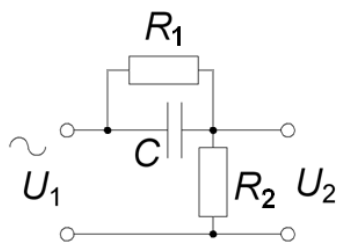
$$f = \frac{(1 \cdot 10^3 + 2 \cdot 10^3)}{2\pi \cdot 1 \cdot 10^3 \cdot 2 \cdot 10^3 \cdot 1 \cdot 10^{-6}} = 239 \text{ Hz}$$



The filter is a high pass filter, HP, that passes high frequencies but attenuates 1/3 at low frequencies. The phase shift is greatest at the "cutoff frequency" 240Hz when it amounts to ca. 12°.

14.4

$$\frac{\underline{U}_2}{\underline{U}_1} = \frac{R}{j\omega L + \frac{1}{j\omega C} + R} = \frac{R}{R + j(\omega L - \frac{1}{\omega C})} \quad \left| \frac{\underline{U}_2}{\underline{U}_1} \right| = \frac{R}{|R + j(\omega L - \frac{1}{\omega C})|} = \frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$




$$\arg\left(\frac{\underline{U}_2}{\underline{U}_1}\right) = \arg\left(\frac{R}{R + j(\omega L - \frac{1}{\omega C})}\right) = \arg(R) - \arg\left(R + j(\omega L - \frac{1}{\omega C})\right) = 0^\circ - \arctan\left(\frac{\omega L - \frac{1}{\omega C}}{R}\right)$$

$$(\omega L - \frac{1}{\omega C}) = 0 \Rightarrow \omega_x = \frac{1}{\sqrt{L \cdot C}} \quad f_x = \frac{1}{2\pi\sqrt{L \cdot C}}$$


$$f = f_x \Rightarrow \left| \frac{\underline{U}_2}{\underline{U}_1} \right| = 1 \quad \arg\left(\frac{\underline{U}_2}{\underline{U}_1}\right) = -\arctan(0) = 0^\circ$$

$$f = 0 \Rightarrow \left| \frac{\underline{U}_2}{\underline{U}_1} \right| = 0 \quad \arg\left(\frac{\underline{U}_2}{\underline{U}_1}\right) = \arg\left(\frac{1}{-\infty j}\right) = 90^\circ$$

$$f = \infty \Rightarrow \left| \frac{\underline{U}_2}{\underline{U}_1} \right| = 0 \quad \arg\left(\frac{\underline{U}_2}{\underline{U}_1}\right) = \arg\left(\frac{1}{+\infty j}\right) = -90^\circ \Rightarrow BP$$

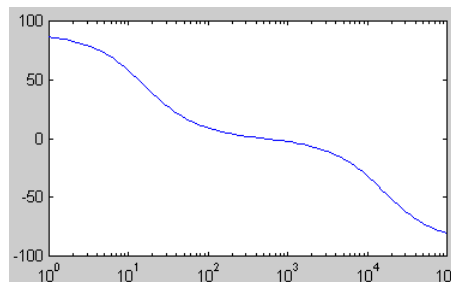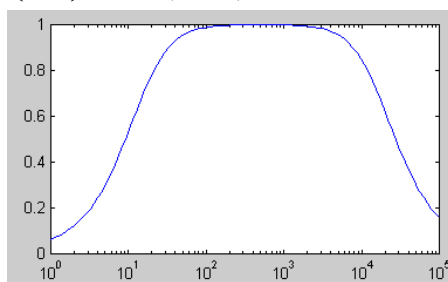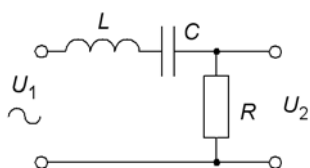

14.5

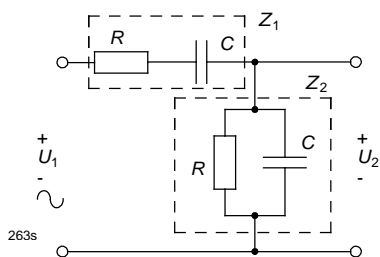

define impedances $Z_1 = R + \frac{1}{j\omega C}$ och $Z_2 = \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega RC}$


$$\frac{\underline{U}_2}{\underline{U}_1} = \frac{Z_2}{Z_1 + Z_2} = \frac{\frac{R}{1 + j\omega RC}}{R + \frac{1}{j\omega C} + \frac{R}{1 + j\omega RC}} = \frac{R}{3R + j\left(R^2 \cdot \omega C - \frac{1}{\omega C}\right)}$$

$\omega \rightarrow 0 \Rightarrow \frac{1}{\omega C} \rightarrow \infty$. När $\omega \rightarrow \infty \Rightarrow \omega C \rightarrow \infty$.

$$\left(R^2 \cdot \omega C - \frac{1}{\omega C}\right) \rightarrow \infty \Rightarrow \frac{U_2}{U_1} \rightarrow 0$$

When $R^2 \cdot \omega C - \frac{1}{\omega C} = 0$ at $\omega = \frac{1}{RC}$ then $\frac{U_2}{U_1} = \frac{1}{3}$.



14.6

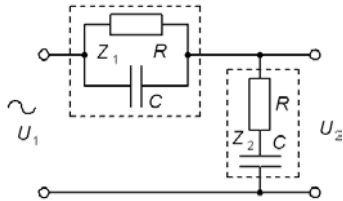

define impedanses $\underline{Z}_1 = \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega RC}$ och $\underline{Z}_2 = R + \frac{1}{j\omega C}$

$$\frac{U_2}{U_1} = \frac{R + \frac{1}{j\omega C}}{R + \frac{1}{j\omega C} + \frac{R}{1 + j\omega RC}} \cdot \frac{j\omega C(1 + j\omega RC)}{j\omega C(1 + j\omega RC)} = \dots = \frac{(1 - \omega^2 R^2 C^2) + 2j\omega RC}{(1 - \omega^2 R^2 C^2) + 3j\omega RC}$$
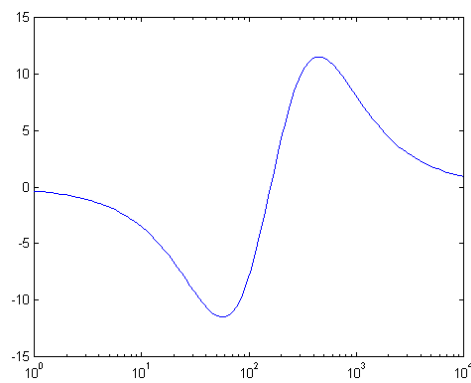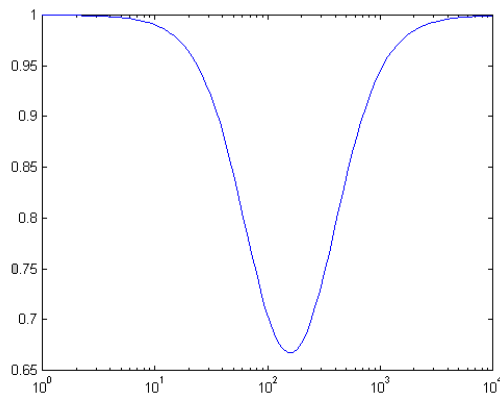
$$\omega = \frac{1}{RC} \Rightarrow \omega RC = 1 \quad \omega^2 R^2 C^2 = 1 \Rightarrow \frac{U_2}{U_1} = \frac{2}{3} \quad \arg\left(\frac{U_2}{U_1}\right) = 0$$



14.7




$$a) \quad R \parallel L = \frac{R \cdot j\omega L}{R + j\omega L} \quad \frac{U_2}{U_1} = \frac{R}{R + \frac{R \cdot j\omega L}{R + j\omega L}} = \frac{1}{1 + \frac{j\omega L}{R + j\omega L}} = \frac{R + j\omega L}{R + j\omega L + j\omega L} = \frac{R + j\omega L}{R + j2\omega L}$$

$$b) \quad \left|\frac{U_2}{U_1}\right| = \left|\frac{R + j\omega L}{R + j2\omega L}\right| = \frac{1}{\sqrt{2}} \frac{\sqrt{R^2 + (\omega L)^2}}{\sqrt{R^2 + (2\omega L)^2}} = \frac{1}{\sqrt{2}} \quad 2R^2 + 2(\omega L)^2 = R^2 + 4(\omega L)^2$$

$$R^2 = 2(\omega L)^2 \Rightarrow \omega_x = \frac{R}{L\sqrt{2}}$$

$$c) \quad \frac{R + j\omega L}{R + j2\omega L} \quad \omega \rightarrow 0 \quad \frac{R+0}{R+0} = 1 \Rightarrow \left|\frac{U_2}{U_1}\right| = 1 \quad \arg\left(\frac{U_2}{U_1}\right) = 0^\circ$$

$$d) \frac{R + j\omega L}{R + j2\omega L} \Rightarrow \frac{\frac{R}{\omega} + jL}{\frac{R}{\omega} + j2L} \quad \omega \rightarrow \infty \quad \frac{0 + jL}{0 + j2L} = \frac{1}{2} \Rightarrow \left| \frac{\underline{U}_2}{\underline{U}_1} \right| = 0,5 \quad \arg\left(\frac{\underline{U}_2}{\underline{U}_1}\right) = 0^\circ$$

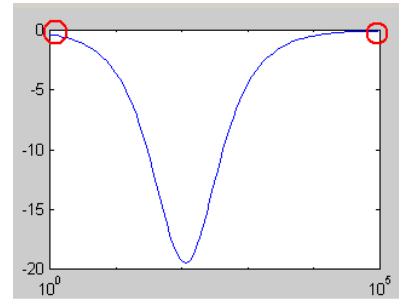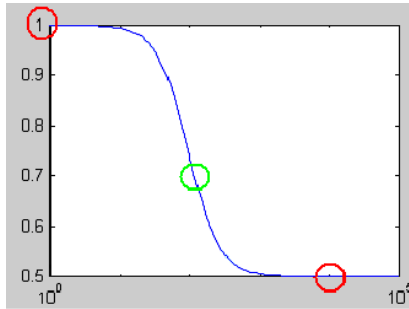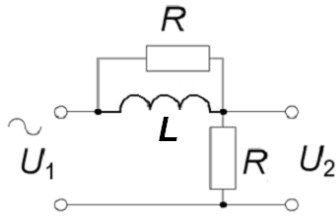

14.8

$$a) \frac{\underline{U}_2(\omega)}{\underline{U}_1(\omega)} = ? \quad b) \omega_x(R, L, C) = ? \quad c) \left| \frac{\underline{U}_2(\omega_x)}{\underline{U}_1(\omega_x)} \right| = ? \quad d) \arg\left(\frac{\underline{U}_2(\omega_x)}{\underline{U}_1(\omega_x)}\right) = ? \quad e) \frac{\underline{I}_R(\omega)}{\underline{U}_1(\omega)} = ?$$

$$a) b) \quad R \parallel C = \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \cdot \frac{j\omega C}{j\omega C} = \frac{R}{1 + j\omega RC}$$

$$\frac{\underline{U}_2}{\underline{U}_1} = \frac{\frac{R}{1 + j\omega RC}}{j\omega L + \frac{R}{1 + j\omega RC}} \cdot \frac{1 + j\omega RC}{1 + j\omega RC} = \frac{R}{j\omega L(1 + j\omega RC) + R} =$$

$$= \frac{R}{(R - \omega^2 RLC) + j\omega L} \quad \operatorname{RE}\left[\frac{\underline{U}_2}{\underline{U}_1}\right] = 0 \Rightarrow \omega^2 RLC = R \quad \omega = \frac{1}{\sqrt{LC}}$$

$$c) \frac{\underline{U}_2}{\underline{U}_1} = \frac{R}{(R - \omega^2 RLC) + j\omega L} = \left\{ \omega = \frac{1}{\sqrt{LC}} \right\} = \frac{R}{0 + j\sqrt{\frac{L}{C}}} \quad \frac{\underline{U}_2}{\underline{U}_1} = \frac{R}{\sqrt{\frac{L}{C}}} = R\sqrt{\frac{C}{L}}$$

$$d) \quad \arg\left[\frac{\underline{U}_2}{\underline{U}_1}\right] = \arg\left[\frac{R}{j\sqrt{\frac{L}{C}}}\right] = -90^\circ$$

$$e) \frac{\underline{I}_R}{\underline{U}_1} = ? \quad \underline{I}_R = \frac{\underline{U}_2}{R} \Rightarrow \frac{\underline{I}_R}{\underline{U}_1} = \frac{\underline{U}_2}{\underline{U}_1} \cdot \frac{1}{R} = \frac{1}{(R - \omega^2 RLC) + j\omega L}$$

Transformer, inductive coupling

15.1

Transformer has the voltage ratio $n = N_1/N_2 = 600/200 = 3$.

We get $U_2 = \frac{1}{n}U_1 = \frac{225}{3} = 75 \text{ V}$ and $I_1 = \frac{1}{n}I_2 = \frac{9}{3} = 3 \text{ A}$.

15.2

$$\frac{N_2}{N_1} = \frac{1}{6} \Rightarrow N_1 = 6 \cdot N_2 = 6 \cdot 150 = 900 \quad U_2 = U_1/n = 230/6 = 38,3 \text{ V}$$

15.3

Transformer has voltage ratio

$$\frac{U_1}{U_2} = \frac{N_1}{N_2} = \frac{225}{127} = 1,77 \Rightarrow N_2 = \frac{U_2}{U_1} N_1 = \frac{600 \cdot 127}{225} = 339.$$


We get $I_1 = \frac{N_2}{N_1} I_2 = \frac{339}{600} 9 = 5,08 \text{ A}$.

15.4

$$U_1 = 10 - 0,2 \cdot 10 = 8 \text{ [V]} \quad U_2 = \frac{1}{2} U_1 = 0,5 \cdot 8 = 4 \text{ [V]} \quad I_2 = \frac{2}{1} I_1 = 2 \cdot 0,2 = \mathbf{0,4 \text{ [A]}}$$

$$R_2 = \frac{U_2}{I_2} = \frac{4}{0,4} = \mathbf{10 \text{ [\Omega]}}$$

15.5

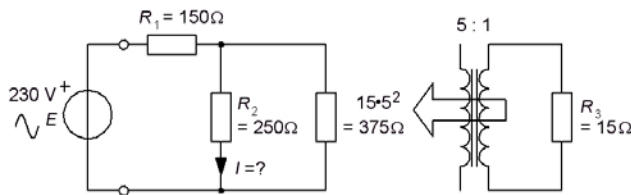


$$R_3 : R_{1 \leftarrow 2} = \left(\frac{N_1}{N_2} \right)^2 \cdot R_2 \Rightarrow 5^2 \cdot 15 = 375$$

$$250 \parallel 375 = 150 \quad I = \frac{E/2}{250} = \frac{115}{250} = 0,46 \text{ A}$$

15.6



$$L_{\text{ERS}} = \frac{\left(4 + \frac{4 \cdot 4}{4 + 4} \right) \cdot 6}{4 + \frac{4 \cdot 4}{4 + 4} + 6} = 3 \text{ H}$$

15.7

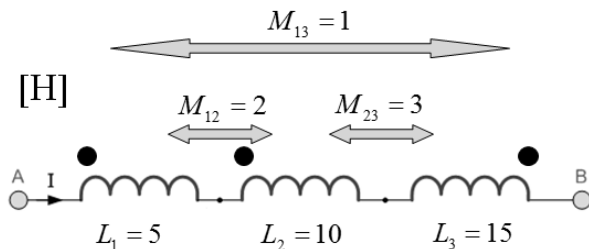

$$\begin{aligned} L_{\text{TOT}} &= \\ &L_1 + M_{12} - M_{13} + \\ &L_2 + M_{12} - M_{23} + \\ &L_3 - M_{23} - M_{13} = \\ &= 5 + 2 - 1 + 10 + 2 - 3 + 15 - 3 - 1 = 26 \text{ [H]} \end{aligned}$$

15.8

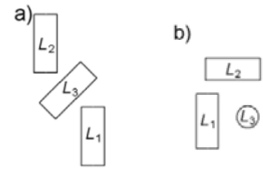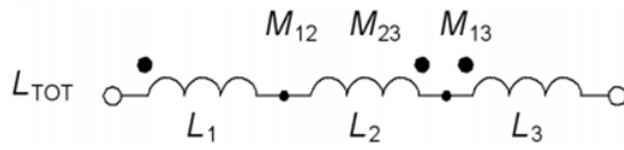

a) $L_{TOT} = L_1 - M_{12} + M_{13} + L_2 - M_{12} - M_{23} + L_3 - M_{23} + M_{13} = 12 - 3 + 1 + 6 - 3 - 2 + 5 - 1 + 1 = 16 \text{ [H]}$

b) $L_{TOT} = L_1 + L_2 + L_3 = 12 + 6 + 5 = 23 \text{ [H]}$

