



KTH Informations- och kommunikationsteknik

Written exam with solutions IE1204/5 Digital Design Friday 13/1 2017 08.00-12.00

General Information

Examiner: Ingo Sander.

Teacher: Kista, William Sandqvist tel 08-7904487

Teacher: Valhallavägen, Ahmed Hemani 08-7904469

Exam text does not have to be returned when you hand in your writing.

Aids: No aids are allowed!

The exam consists of three parts with a total of 14 tasks, and a total of 30 points:

Part A1 (Analysis) contains ten short questions. Right answer will give you one point. Incorrect answer will give you zero points. The total number of points in Part A1 is **10 points**. To **pass the Part A1 requires at least 6p**, *if fewer points we will not look at the rest of your exam.*

Part A2 (Methods) contains two method problems on a total of 10 points.

To **pass the exam** requires at least **11 points** from A1 + A2 , *if fewer points we will not look at the rest of your exam.*

Part B (Design problems) contains two design problems of a total of 10 points. Part B is corrected only if there are at **least 11p** from the exam A- Part.

NOTE ! At the end of the exam text there is a submission sheet for Part A1, which shall be separated and be submitted together with the solutions for A2 and B.

For a passing grade (**E**) requires at **least 11 points on the exam**. If exactly 10p from A1(6p)+A2(4p), (FX), completion to (E) will be offered.

Grades are given as follows:

0 –	11 –	16 –	19 –	22 –	25
F	E	D	C	B	A

The result is expected to be announced before Friday 3/2 2017.

Part A1: Analysis

Only answers are needed in Part A1. Write the answers on the submission sheet for Part A1, which can be found at the end of the exam text.

1. 1p/0p

A function $f(x, y, z)$ is described on minimized SoP form (Sum of products):


$$f(x, y, z) = \{SoP\}_{\min} = y + x \cdot \bar{z}$$

Write down the function as a minimized product of sums.

$$f(x, y, z) = \{PoS\}_{\min} = ?$$

 1. Proposed solution.


$$f(x, y, z) = \{SoP\}_{\min} = y + x \cdot \bar{z}$$



$$f(x, y, z) = \{PoS\}_{\min} = (x + y) \cdot (y + \bar{z})$$

 2. 1p/0p

Useless circuit (!). A 5-bit adder is connected to multiply a binary unsigned 4-bit number $x = x_3x_2x_1x_0$ with a constant k , $y = k \cdot x$. Let the number x be $x = 1010_2$ what will the (6 bit) sum $y = y_5y_4y_3y_2y_1y_0$ be?



2. Proposed solution.

If ignoring Carry out (5 bit sum) the circuit performs the operation $y = (2 \cdot x - 1 \cdot x) = 1 \cdot x$ the number x remains unaffected by adder ($k = 1$). $1010 \rightarrow 01010$. With Carry out (the 6 bit sum) $1010 \rightarrow 101010$.

Yes this circuit is really useless outside the exam (where it is worth 1p).

3. 1p/0p

A two's complement 16-bit number is $x_{16} = \text{FFFB}$ (hexadecimal). This number will be transferred to a 4-bit register (the number of bits will be reduced and the sign kept). Express this 4-bit number as a decimal number with sign $\pm x_{10} = ?$

3. Proposed solution.

The twelve excess sign bits are ignored $x = \mathbf{B} = 1011 = -(0100+1) = -0101_2 = -5_{10}$

4. 1p/0p

Given is a Karnaugh map for a function of four variables $Y = f(x_3, x_2, x_1, x_0)$.

Write the function Y_{\min} , as a minimized sum of products, on **SoP** form.

"-" in the map means "don't care".

		x_1x_0			
		00	01	11	10
x_3x_2	00	0 1	1 -	3 1	2 0
	01	4 -	5 1	7 1	6 0
	11	12 0	13 1	15 1	14 1
	10	8 0	9 -	11 1	10 -

4. Proposed solution.


		x_1x_0			
		00	01	11	10
x_3x_2	00	0 1	1 -	3 1	2 0
	01	4 -	5 1	7 1	6 0
	11	12 0	13 1	15 1	14 1
	10	8 0	9 -	11 1	10 -

$$Y_{\min} = f(x_3, x_2, x_1, x_0) = f(x_3, x_1, x_0) = x_0 + \overline{x_3}x_1 + x_3x_1 = x_0 + x_3 \oplus x_1$$

 5. 1p/0p

The figure below shows a circuit with two NOR gates and two NAND gates. Simplify the function

$Y = f(a, b, c, d)$ as much as possible and write the function on SoP-form.




5. Proposed solution.

$$Y = \overline{\overline{a \cdot b} + \overline{c + d}} = \{dM\} = a \cdot b \cdot (c + \overline{d}) = abc + ab\overline{d}$$

 
6. 1p/0p

Give an expression for the logical function realized by the CMOS circuit in the figure.

Write the function on SoP-form. $F = f(A, B, C, D) = ?$



6. Proposed solution.

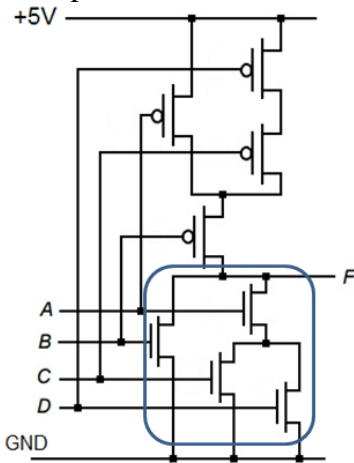

Pulldown net


$$\begin{aligned} \bar{F} &= B + A \cdot (C + D) \\ \Rightarrow F &= \overline{B + A \cdot (C + D)} = \bar{B} \cdot \overline{A \cdot (C + D)} = \\ &= \bar{B} \cdot (\bar{A} + \overline{C + D}) = \bar{B} \cdot (\bar{A} + \bar{C} \cdot \bar{D}) = \bar{B} \cdot \bar{A} + \bar{B} \cdot \bar{C} \cdot \bar{D} \end{aligned}$$

7. 1p/0p


A State Machine can be drawn either as **state diagram** or as **ASM chart** (Algorithmic State Machine chart).

This figure shows an ASM-chart. Draw the equivalent **Moore state diagram** using the circles in the right figure.

 
The same figure is also on the submission sheet.



7. Proposed solution.

 

8. 1p/0p

 

A synchronous counter starts in the state $q_2q_1q_0 = 000$. What will the state be after **four** clock pulses? $q_2q_1q_0 = ?$


8. Proposed solution.

The counter is a Moebius counter that counts the "Creeping Code".


$$q_2q_1q_0 : 000 \rightarrow 001 \rightarrow 011 \rightarrow 111 \rightarrow 110 \quad q_2q_1q_0 = 110$$

 9. 1p/0p

The figure shows a latch circuit. Complete the timing diagram. The same timing diagram is also on the submission sheet.




9. Proposed solution.

 

 10. 1p/0p

At the labs, we use chips from the 74-series. They are nowadays used as spares. These functions can instead be described using VHDL code and downloaded to programmable logic.

The circuit 7421 is shown to the right. Below are the VHDL code for the circuit. In the code, we have hidden the line `o1` from you (with characters `•`).



Write VHDL code for the line `o2 <= () ;`

```
library ieee;
use ieee.std_logic_1164.all;

entity A74XX21 is
  port (
    a1 : in  std_logic;
    b1 : in  std_logic;
    c1 : in  std_logic;
    d1 : in  std_logic;
    a2 : in  std_logic;
    b2 : in  std_logic;
    c2 : in  std_logic;
    d2 : in  std_logic;
    o1 : out std_logic;
    o2 : out std_logic );
end entity;
```

```
architecture dataflow of A74XX21 is
begin
  o1 <= ( •• ••• •• ••• •• ••• •• ) ;
  o2 <= (                                     ) ;
end architecture;
```

10. Proposed solution.

```
o2 <= ( a2 and b2 and c2 and d2 ) ;
```


Part A2: Methods

Note! Part A2 will only be corrected if you have passed part A1 ($\geq 6p$)

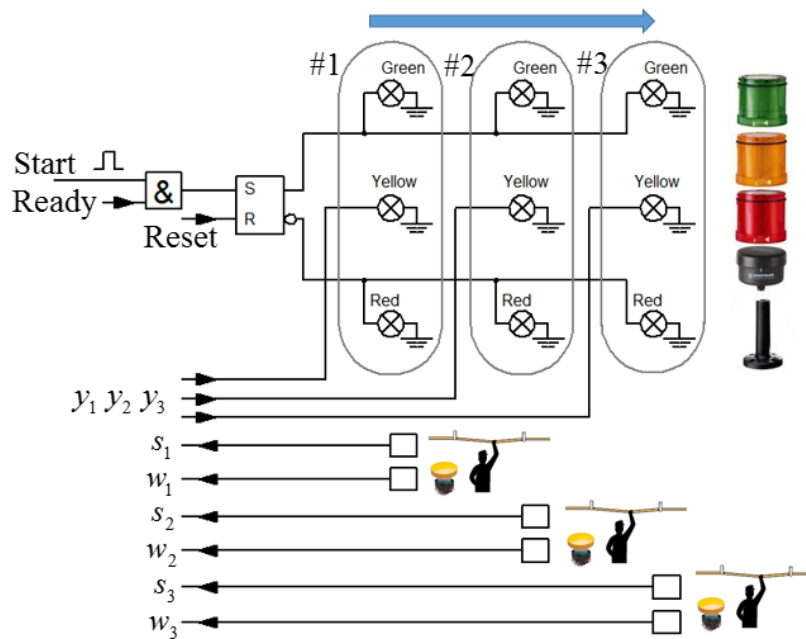11. 4p ANDON signal lights.

In production factories with assembly line a system of warning lights green (G), yellow (Y) and Red (R) are used at the assembly stations. Operators have a stop button (with a cord) that stops the assembly line and all stations then signals **red**. The operator also has an alert button to summon help. It will signal **yellow** light at the own station and for all previous stations along the assembly line, but without stopping it.

When all problems are removed, the assembly line may be started again with a short start pulse (Start). All stations then signals the green light. See the figure that shows three stations with the operator buttons and lights. The arrow indicates the transport direction of the assembly line.



a) (a+b=1p) **(Green)** A short pulse $Start = 1$ can start the assembly line if $Ready = 1$. Design a circuit that provides signal $Ready = 1$ if *none* of the stop signals $s_1 s_2 s_3$ are 1.

b) **(Red)** The assembly line is stopped if $Reset = 1$. Design a circuit that provides signal $Reset = 1$ if *any* of the signals $s_1 s_2 s_3$ is 1.




$$Reset = f(s_1, s_2, s_3) .$$

Draw the two circuits together, use a few optional gates.

   c) (2p) **(Yellow)** Operators can warn on problems by lighting a yellow lamp. The signals $w_1 w_2 w_3$ shall lit their own yellow light (y_1 at w_1 or y_2 at w_2 or y_3 at w_3), but also lit the yellow lights belonging to the stations that are earlier in the direction of assembly line (stations after shall not be warned).


Set up the truth table for $y_1 y_2 y_3 = f(w_1, w_2, w_3)$.

Derive the functions $y_1 = f(w_1, w_2, w_3)$ $y_2 = f(w_1, w_2, w_3)$ $y_3 = f(w_1, w_2, w_3)$ by inspecting the truth table or by using Karnaugh map. Design the circuit with a few optional gates.



 d) (1p) It is common with more than three workstations along a conveyor belt. In the figure, a warning signal w_{IN} from an subsequent group of stations, and a warning signal w_{OUT} to a previous group of stations, has been added.


Completed the circuit from c) with the signals signal w_{OUT} and w_{IN} in such a way that it works together with the other stations. (Rule: all previous stations must also warn with yellow light).



11. Proposed solution.

a) $Ready = \overline{s_1} \cdot \overline{s_2} \cdot \overline{s_3} = \overline{s_1 \cdot s_2 \cdot s_3} = \{dM\} = \overline{s_1 + s_2 + s_3}$

b) $Reset = s_1 + s_2 + s_3$

 

c)

w_1	w_2	w_3	y_1	y_2	y_3
0	0	0	0	0	0
0	0	1	1	1	1
0	1	0	1	1	0
0	1	1	1	1	1
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	1	1	1


w_1	w_2	w_3	y_2	
	00	01	11	10
0	0	1	1	1
1	0	1	1	1

$y_2 = \overline{w_2 w_3} = w_2 + w_3$

$y_3 = w_3$ (inspection of t-table)

$y_1 = w_1 + w_2 + w_3$ (inspection)

$y_2 = w_2 + w_3$ (K-map)

 

d) w_{IN} is or-ed together with w_3 .


$y_3 = (w_3 + w_I)$

$y_2 = w_2 + (w_3 + w_I)$

$y_1 = w_1 + w_2 + (w_3 + w_{IN})$

w_{OUT} will now be the same as y_1 .

 $w_{OUT} = y_1 = w_1 + w_2 + (w_3 + w_I)$



12. 6p Counter

A modulo-6 synchronous counter consists of three D-flip-flops and one XOR-gate and one AND-gate, see the figure.


a) (1p) Derive the expressions for next state

$$q_3^+ = ? \quad q_2^+ = ? \quad q_1^+ = ?$$

b) (1p) Set up the complete state table $q_3^+ q_2^+ q_1^+ = f(q_3 q_2 q_1)$

c) (1p) Draw the complete state diagram.

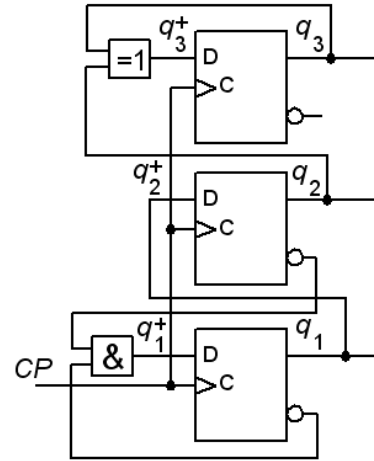d) (1p) Which states are not part of the modulo-6 sequence? What will happen if one starts from any of these states?




Redesign the circuit, maintaining the function so that it uses **two 2:1 multiplexers** in place of the gates. See figure to the right.


 
e) (2p) What signals should be connected to the multiplexer data inputs to replace the gates?

$$q_3^+ : \text{mux}_0 = ?, \quad \text{mux}_1 = ?$$

$$q_1^+ : \text{mux}_0 = ?, \quad \text{mux}_1 = ?$$



12. Proposed solution.

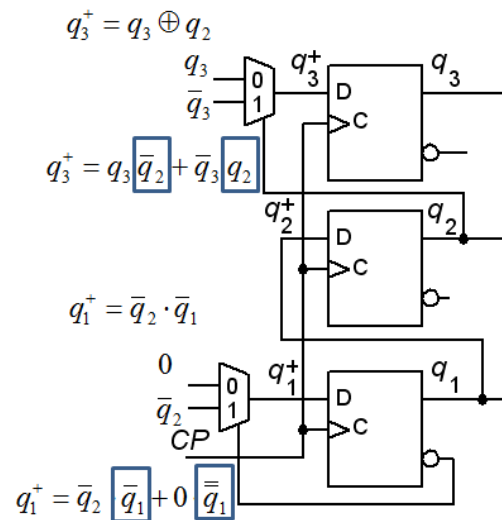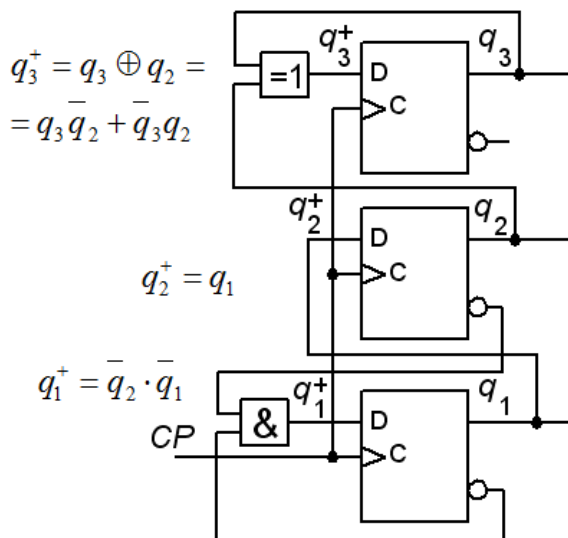

	q_2q_1		q_3^+	
q_3	00	01	11	10
0	0	0	1	1
1	1	1	0	0

$$q_3^+ = q_3\bar{q}_2 + \bar{q}_3q_2$$


	q_2q_1		q_2^+	
q_3	00	01	11	10
0	0	1	1	0
1	0	1	1	0

$$q_2^+ = q_1$$

	q_2q_1		q_1^+	
q_3	00	01	11	10
0	1	0	0	0
1	1	0	0	0

$$q_1^+ = \bar{q}_2 \cdot \bar{q}_1$$

	q_2q_1		$q_3^+q_2^+q_1^+$	
q_3	00	01	11	10
0	001	010	110	100
1	101	110	010	000


 


Part B. Design Problems

Note! Part B will only be corrected if you have passed part A1+A2 ($\geq 11p$).

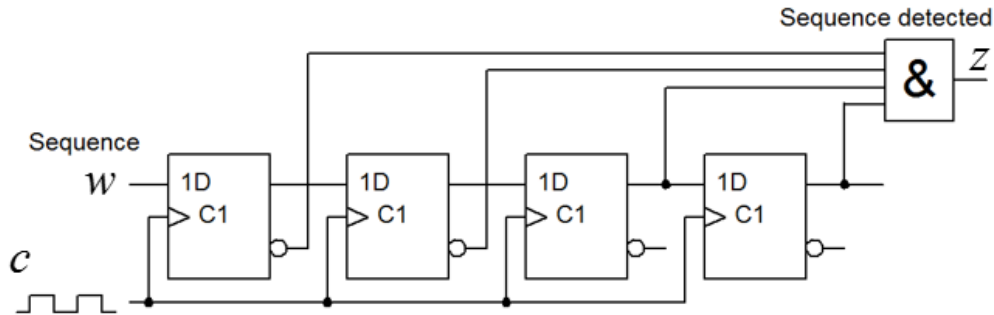 13. 5p Synchronous sequential circuit. Detector for specific event.

A shift register is used to detect when a particular sequence occurs in a sequence of bits to input w . The signal w is synchronized with the clock pulses c . Each time the correct bit sequence appears $z = 1$. At start is $w = 0$.



a) (1p) Which bit sequence is detected?

One can construct a Moore machine with fewer D-flip-flops that detects the same sequence.


b) (1p) Draw the **State Diagram** for such a sequence detector.

c) (2p) Derive the **state table** and the **coded state table**, using *binary code* as state code. Derive minimized expressions for **next state decoder** and **output decoder**. You do not need to draw any circuit diagram.

 d) (1p) Minimize the following state diagram.

Then draw the minimized **state diagram**.


Note that this is a completely independent task without any connection to the former sequence detector.



13. Proposed solution.

a) The input sequence will be $1 \rightarrow 1 \rightarrow 0 \rightarrow 0$.

b)

 

	w		z
	0	1	
a	a	b	0
b	a	c	0
c	d	b	0
d	e	b	0
e	a	b	1

c)

		$q_2^+ q_1^+ q_0^+$		z
$q_2 q_1 q_0$	w	0	1	
000	0	000	001	0
001	0	000	010	0
010	0	011	001	0
011	0	100	001	0
100	0	000	001	1

		q_2^+			
$q_2 q_1$	$q_0 w$	00	01	11	10
00	0	0	0	0	0
01	0	0	0	0	1
11	-	-	-	-	-
10	0	0	-	-	-

		q_1^+			
$q_2 q_1$	$q_0 w$	00	01	11	10
00	0	0	0	1	0
01	1	0	0	0	0
11	-	-	-	-	-
10	0	0	-	-	-


		q_0^+			
$q_2 q_1$	$q_0 w$	00	01	11	10
00	0	1	0	0	0
01	1	1	1	1	0
11	-	-	-	-	-
10	0	1	-	-	-

$$z = q_2 \quad q_2^+ = q_1 q_0 \bar{w} \quad q_1^+ = q_1 \bar{q}_0 \bar{w} + \bar{q}_1 q_0 w \quad q_0^+ = q_1 \bar{q}_0 + q_1 w + \bar{q}_0 w$$

d) Independent task.


		w		z	$(abf)(cde)$	
a	b	0	1		$a_0 \rightarrow (abf)$	$a_1 \rightarrow (cde)$
a	b	c	1	1	$b_0 \rightarrow (abf)$	$b_1 \rightarrow (cde)$
b	b	c	1	1	$f_0 \rightarrow (abf)$	$f_1 \rightarrow (cde)$
c	c	c	0	0	$(abf)(\dots)$	
d	e	a	0	0	$c_0 \rightarrow (cde)$	$c_1 \rightarrow (cde)$
e	d	f	0	0	$d_0 \rightarrow (cde)$	$d_1 \rightarrow (abf)$
f	b	c	1	1	$e_0 \rightarrow (cde)$	$e_1 \rightarrow (abf)$

$$A = (abf) \quad B = (c) \\ C = (de)$$

 

 14. 5p Registration of double edges.

Pulses are received at two inputs a and b of an asynchronous sequential circuit. As soon as a total of two positive edges (transitions from $0 \rightarrow 1$) has been submitted to the inputs then the output y becomes 1 (and then remains 1 regardless of input signals).



Two edges means that it either enters two pulses to any of the inputs, or enters one pulse to each input. The pulses may come at any time to the inputs and no assumption can be made about the length of the pulses.

At start both input signals are $a = b = 0$. No simultaneous input signal changes can occur.



a) (2p) Study the possible inputs, and set up a proper **flow table** for the sequential circuit. Draw the **state diagram**.

b) (2p) Make a suitable state assignment with an **excitation table** that provides circuits that are free from critical race (comment on how you achieved this). You will also develop the hazard free **expressions** for the **next state** (comment on how you achieved this) as well as an expression for **output**.

c) (0,5p) Draw the circuit diagram. (Use optional gates).


d) (0,5p) To be useful, the sequential circuit will need a Reset input so that it can be re-started. Complete the circuit with such a function. (Use optional gates).

14. Proposed solution. a)

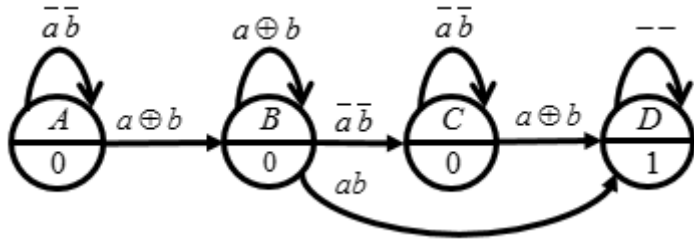 


	ab				
	00	01	11	10	y
A	A	B	-	B	0
B	C	B	D	B	0
C	C	D	-	D	0
D	D	D	D	D	1


b)

 

 B and D are on Hamming distance 2. For B $ab = 11$, unstable state C will forward B to D.



c)

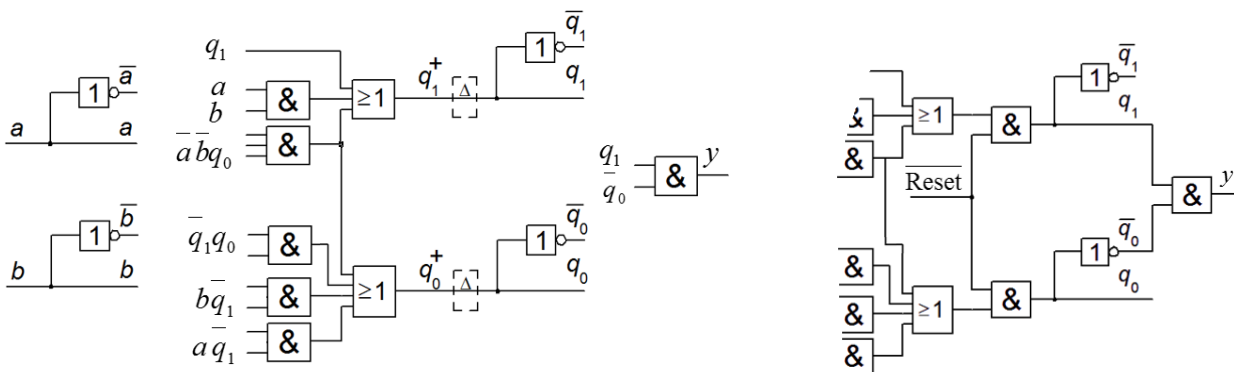

d) An active low Reset could be inserted with two and-gates as the initial state A has the code 00.

Good Luck!


 
 

 
Submission sheet for Part A1 Sheet 1

(remove and hand in together with your answers for part A2 and part B)

Last name: _____ Given name: _____

Personal code: _____ Sheet: **1**

Write down your answers for the questions from Part A1 (1 to 10)

Question	Answer
1	$f(x, y, z) = \{POS\}_{\min} = ?$
2	$x = 1010_2 \rightarrow y = k \cdot x = y_5y_4y_3y_2y_1y_0 = ?$
3	$x_{16} = FFFB \rightarrow 4\text{-bit} \rightarrow \pm x_{10} = ?$
4	$Y = \{SOP\}_{\min}$
5	$Y = f(a, b, c, d)$
6	$F = f(A, B, C, D)$
7	
8	$q_2q_1q_0 = 000 \rightarrow \rightarrow \rightarrow \rightarrow ??$
9	<div style="display: flex; align-items: center;"> <div style="margin-right: 20px;">  </div> <div> a_0^1  b_0^1  A_0^1  </div> </div>
10	$\circ 2 \leq (\quad) ;$

This table is completed by the examiner!!

Part A1 (10)	Part A2 (10)		Part B (10)		Total (30)	
Points	11	12	13	14	Sum	Grade

