 




# EP1200 Introduction to Computing Systems Engineering

## *Sequential Logic*





# Perspective on Boolean logic

Each Boolean function has a canonical representation

- expressed in terms of And, Not, Or
- And, Not, Or can be expressed in terms of Nand alone

Universal building blocks

- mass production
- unique topology



# Perspective on Boolean arithmetic

Combinational logic: time for output to be trusted?

The adder design is very basic: no parallelism

- It pays to optimize adders

The ALU is also very basic without multiplication and division

- What about more advanced math operations?
- A typical hardware/software tradeoff



# Sequential vs. combinational logic

## Combinational devices

- operate on data only
- provide calculation services (e.g. Nand ... ALU)

## Problem

- When is the output signal stable and useful?

## Sequential devices

- operate on data and a clock signal
- storage and synchronization
- called “clocked devices”

## The low-level behavior of clocked / sequential gates is tricky

- All sequential chips can be based on one low-level sequential gate
  - the “data flip flop”, or DFF
- The clock-dependency encapsulated at the low-level DFF level
- Higher-level sequential chips can be built on top of DFF gates using combinational logic only.



# Lecture plan

Clock


A hierarchy of memory chips

- Flip-flop gates
- Binary cells
- Registers
- RAM

Counters



# The clock

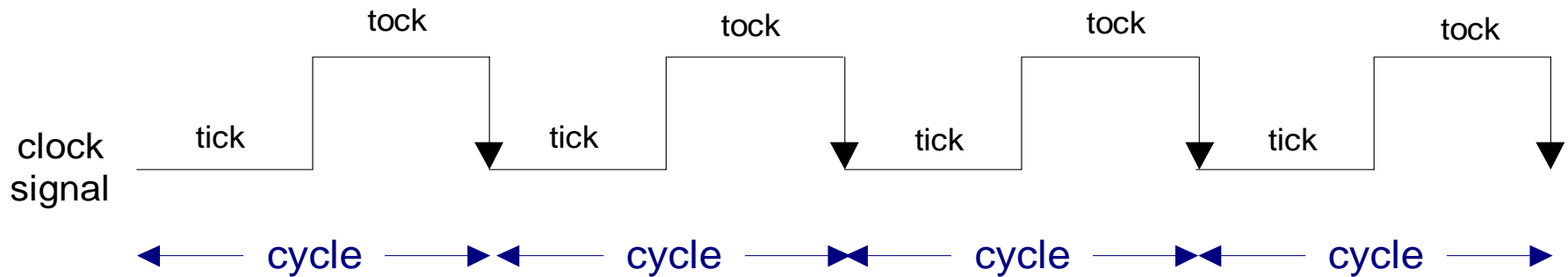

A clock cycle


- *tick*-phase (low) and a
- *tock*-phase (high)

In real hardware, the clock is implemented by an oscillator

In the hardware simulator, clock cycles generated

- manually by the user
- automatically by a test script

# Data flip-flop

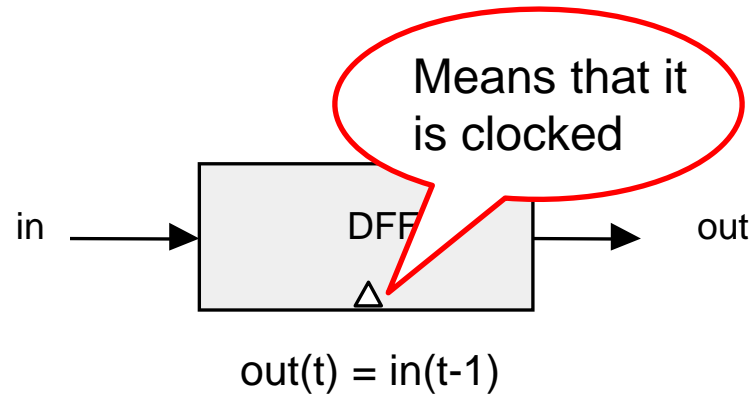

A fundamental state-keeping device


Not concerned with DFF *implementation*

- given, similarly to NAND for combinational logic

Memory devices

- many flip-flops
- regulated by the same master clock signal

# A one-bit register

 

if load(t-1) then out(t)=in(t-1)  
else out(t)=out(t-1)


A storage unit that can

- change its state to a given input
- maintain its state over time (until changed)



$out(t) = in(t-1)$

*Basic building block*

 


out(t) = out(t-1) ?  
out(t) = in(t-1) ?

***Won't work***




# A one-bit register

## Interface

 


if  $\text{load}(t-1)$  then  $\text{out}(t)=\text{in}(t-1)$   
else  $\text{out}(t)=\text{out}(t-1)$

## Implementation

 


# Multi-bit register

 

if  $\text{load}(t-1)$  then  $\text{out}(t)=\text{in}(t-1)$   
else  $\text{out}(t)=\text{out}(t-1)$


*1-bit register*

 

if  $\text{load}(t-1)$  then  $\text{out}(t)=\text{in}(t-1)$   
else  $\text{out}(t)=\text{out}(t-1)$


*w-bit register*

# RAM hierarchy

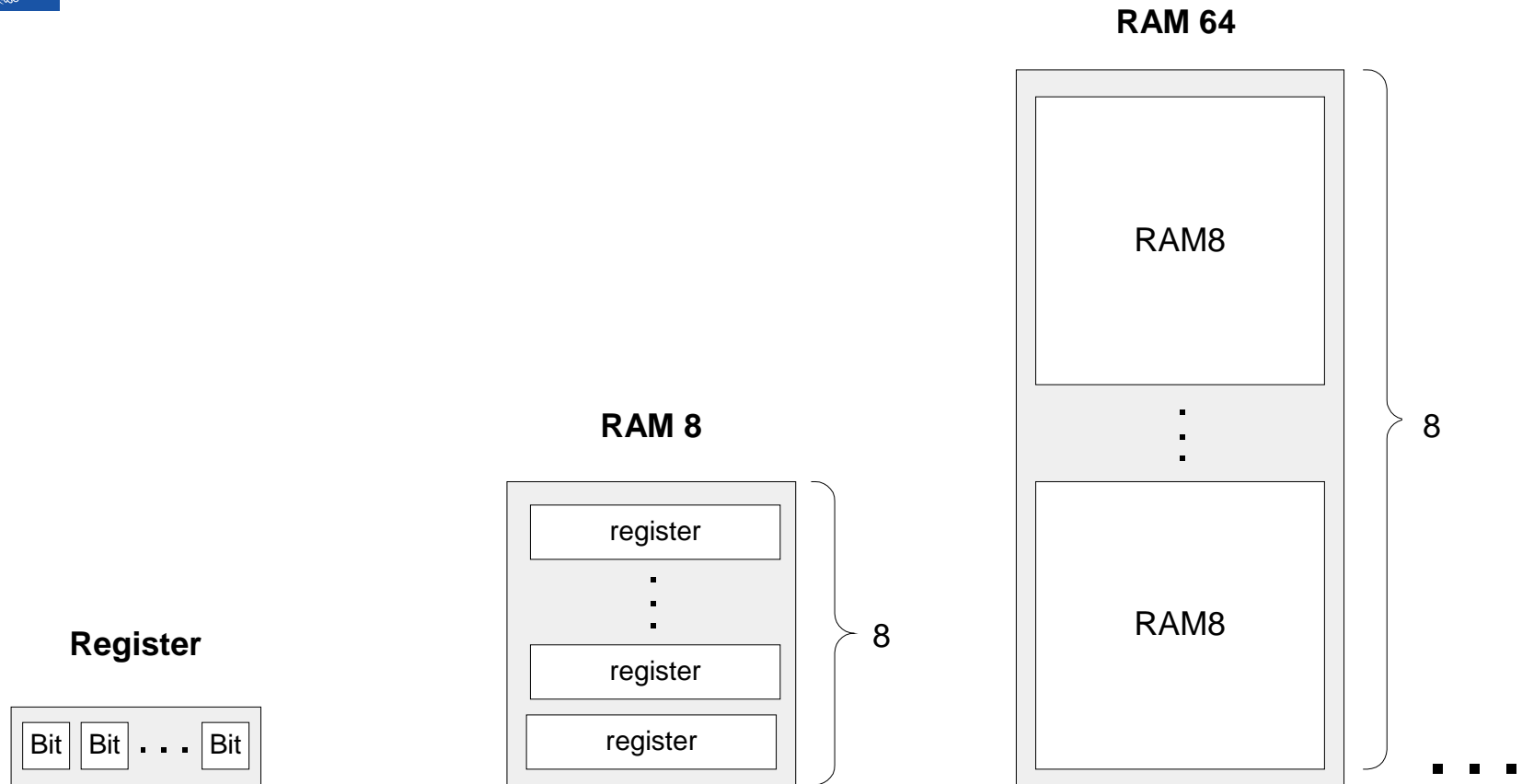



# RAM interface

 


```
Chip name: RAMn // n and k are listed below
Inputs:    in[16], address[k], load
Outputs:   out[16]
Function:  out(t)=RAM[address(t)](t)
           If load(t-1) then
             RAM[address(t-1)](t)=in(t-1)
Comment:   "=" is a 16-bit operation.
```

The specific RAM chips needed for the Hack platform are:

<u>Chip name</u>	<u>n</u>	<u>K</u>
RAM8	8	3
RAM64	64	6
RAM512	512	9
RAM4K	4096	12
RAM16K	16384	14



# Program Counter

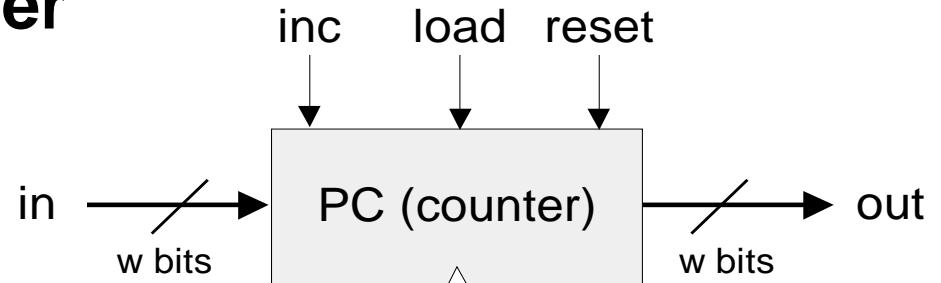

```
If reset(t-1) then out(t)=0
  else if load(t-1) then out(t)=in(t-1)
    else if inc(t-1) then out(t)=out(t-1)+1
      else out(t)=out(t-1)
```

A storage device that can

- set its state to a base value (load)
- increment the state in every clock cycle
- maintain its state (stop incrementing) over clock cycles
- reset its state

Typical function: *program counter*

Implementation: register chip + combinational logic



# For next class

1. Read
  - Chapter 3 on sequential logic
  - Appendix A, pages 289-296
2. Do project 2 from course web
  - In folders
    - projects/03/a and projects/03/b (large RAM)
  - Hints
    - Fan out, use “out=a, out=b, ...”
    - For PC, several control signals may be set at the same time
      - follow the if clauses in the definition of the chip
3. Hand in Project 3 by March 28 at 8.00