



Written exam

IE1206 Embedded Electronics

IF1330 Electrical principles

Friday 23/8 2019 14.00-18.00

General Information

Examiner: Carl-Mikael Zetterling

Responsible teacher at exam: Per-Erik Hellström 08-790 43 25

All sheets that are handed in need **your name and personal number** written on them.

Mark every sheet with the **problem it deals with**.

You cannot have more than one problem per sheet.

Aids: Calculator

The exam consists of 8 problems (5 points each) distributed over the 4 modules in the course:

Module 1: problem 1 and 2

Module 2: problem 3 and 4

Module 3: problem 5 and 6


Module 4: problem 7 and 8

To **pass the exam** requires at least **2 points** from each module and preliminary **20 points** in total.


Grades are given as follows:

Points	<20	20-23	24-27	28-31	32-35	36-40
Grades	F	E	D	C	B	A

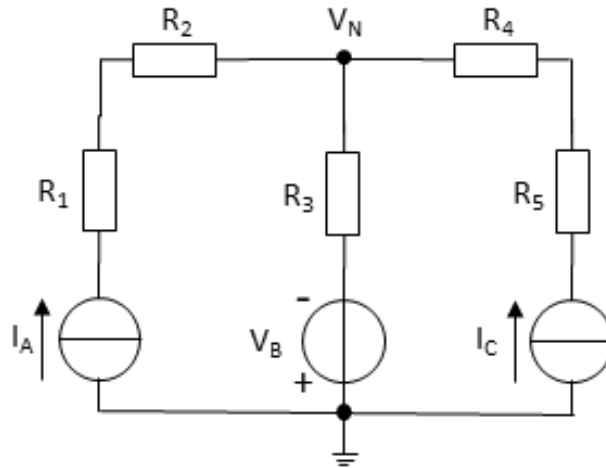
1. $R_1=2\text{ k}\Omega$, $R_2=3\text{ k}\Omega$, $R_3=2\text{ k}\Omega$, $R_4=3\text{ k}\Omega$, $R_5=0.5\text{ k}\Omega$, $I_A=1\text{ mA}$, $V_B=5\text{ V}$, $I_C=4\text{ mA}$
 (A) Determine the voltage V_N .
 (B) What is the power consumed in R_3 ?



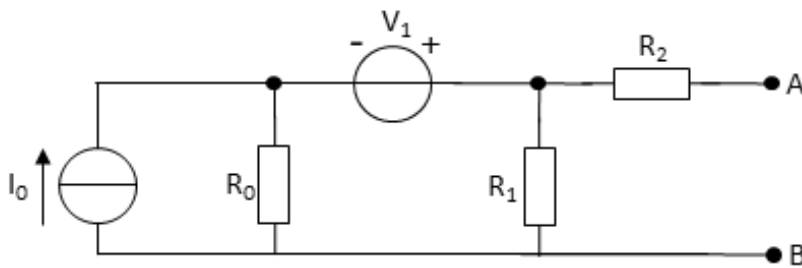2. Determine the Thévenin equivalent circuit seen at A-B.
 $I_0=3\text{ mA}$, $V_1=4\text{ V}$, $R_0=2\text{ k}\Omega$, $R_1=8\text{ k}\Omega$, $R_2=4\text{ k}\Omega$.



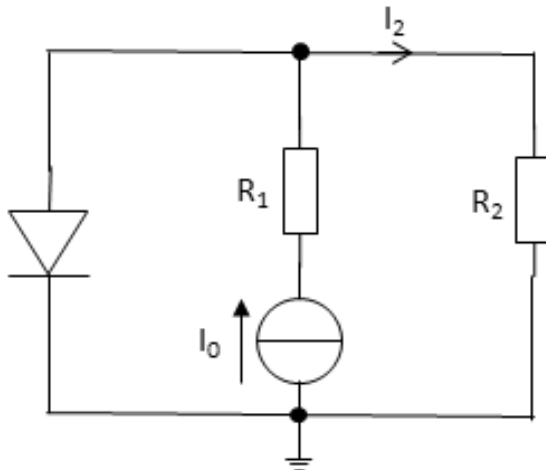
3. Determine the current I_2 . The diode can be treated as an ideal diode with a threshold voltage $V_T=0.7\text{ V}$. $I_0=500\text{ }\mu\text{A}$, $R_1=R_2=5\text{ k}\Omega$.



4. Assume that the operational amplifier is ideal. $R_1=10\text{ k}\Omega$, $R_2=30\text{ k}\Omega$ and $R_L=32\text{ k}\Omega$.

(A) Determine the power dissipated in R_L when $V_{in}=2\text{ V}$.

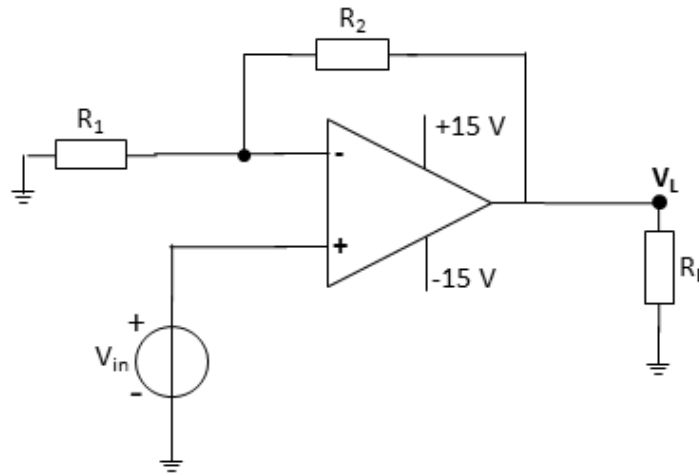
(B) Determine V_L when $V_{in}=5\text{ V}$.




5. The switch has been open for a long time. At $t=0\text{ s}$ the switch closes.

(A) Derive an expression for $I_1(t)$ for $t>0\text{ s}$ in terms of I_0 , R_0 , R_1 and C_1 .

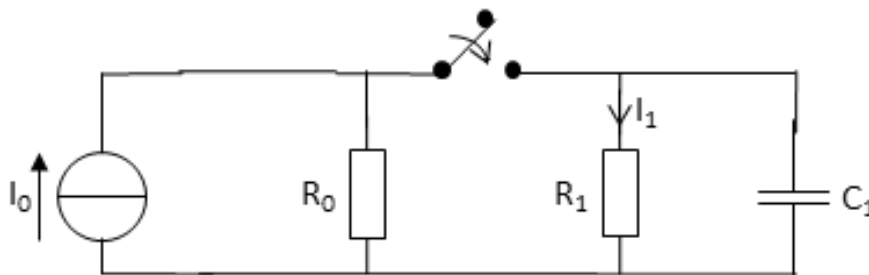
(B) At what time t_1 is $I_1(t_1)=1\text{ mA}$ assuming $I_0=12\text{ mA}$, $R_0=1\text{ k}\Omega$, $R_1=3\text{ k}\Omega$ and $C_1=20\text{ nF}$.



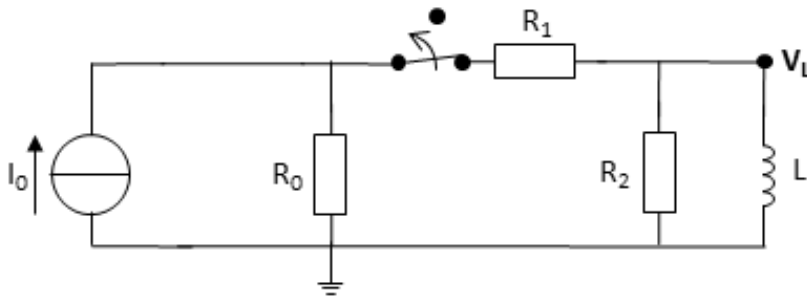
6. The switch has been closed for a long time. At $t=0$ s the switch opens.
 $I_0=30$ mA, $R_0=1$ k Ω , $R_1=9$ k Ω , $R_2=10$ Ω .
 Determine L so that $V_L(t=1$ ms) = $0.5V_L(t=0^+)$ s)



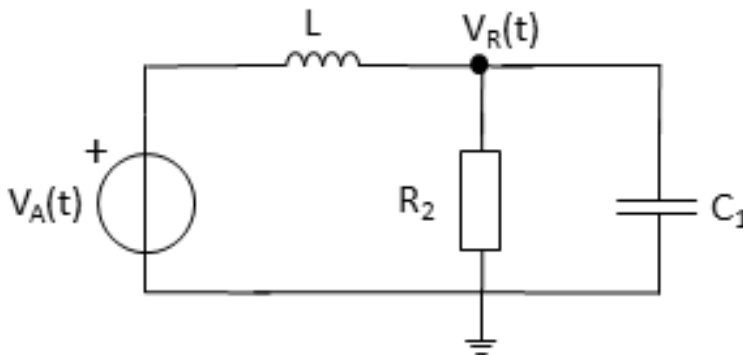7. $V_A(t)$ is a steady-state cosine voltage source with amplitude 2 V, angular frequency $\omega=10^6$ rad/s and phase angle $\phi=0^\circ$. $L=1$ mH, $R_2=1$ k Ω and $C_1=1$ nF.
 Determine $V_R(t)$.



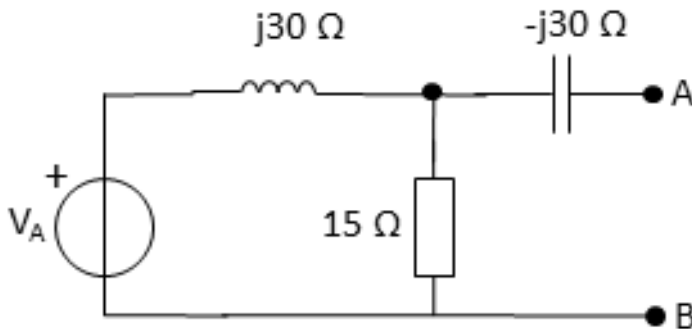8. (A) Determine the Norton equivalent circuit seen at A-B when V_A is a steady state cosine voltage source with amplitude=180 V and phase angle= 90° .
 (B) Determine the components and their values and draw the Norton equivalent circuit when $\omega=1000$ rad/s.



Answers to exam 20190823 in IE1206 and IF1330

1A: $V_N=5V$

1B: $P_{R3}=50 \text{ mW}$

2: $V_{TH}=8 \text{ V}$, $R_{TH}=6.8 \text{ k}\Omega$

3: $I_2=0.14 \text{ mA}$

4A: $P_{RL}=2 \text{ mW}$

4B: $V_L=15 \text{ V}$

5A: $I_1=I_0 \cdot (R_0/(R_1+R_0)) \cdot (1-\exp(-t/\tau))$, $\tau=(R_0/R_1) \cdot C_1$

5B: $t_1=6.1 \mu\text{s}$

6: $L=14.4 \text{ mH}$

7: $V_R(t)=2\cos(\omega t-90)$ (or $-\pi/2$)

8A: $I_{no}=3j \text{ A}$, $Z_{th}=12-24j \text{ }\Omega$.

8B: In the schematic $R=12 \text{ }\Omega$ and $C=41.6 \mu\text{F}$ and $I_{no}=3\cos(\omega t+90)$ (or $\pi/2$)