

# IE1204 Exam 20191021 Answers

## Part 1

1

$$A = 93_{10} = 01011101_2 = 5D_{16}$$

$$B = -42_{10} = 11010110_2 = D6_{16}$$

$$A + B = 00110011_2 = 51_{10}$$

2

$$C = 01011010_2 = 90_{10} = 5A_{16}$$

$$D = 00110011_2 = 51_{10} = 33_{16}$$

$$-D = 11001101_2 = -51_{10} = CD_{16}$$

$$C - D = 00100111_2 = 39_{10}$$

3

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1


		C, D			
		00	01	11	10
A, B	00	1	1	1	0
	01	1	1	1	0
	11	0	0	1	1
	10	0	0	1	0

$\bar{A}\bar{C} + CD + ABC$

Can't be further simplified!

4
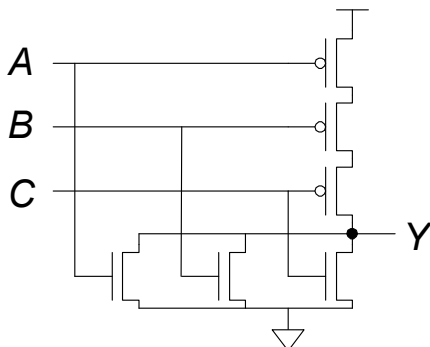
$$Z = \bar{A} \cdot \bar{B} \cdot \bar{C} = \overline{A + B + C} \quad (\text{three input NOR})$$



## Part 2


5

$$Y = \bar{A} \cdot \bar{B} \cdot C + \bar{A} \cdot \bar{B} \cdot \bar{D} + A \cdot \bar{B} \cdot C + A \cdot \bar{B} \cdot \bar{D}$$

Format: Sum of products

		C, D			
		00	01	11	10
A, B	00	1	0	1	1
	01	0	0	0	0
	11	0	0	0	0
	10	1	0	1	1

$\bar{B}\bar{D} + \bar{B}C$

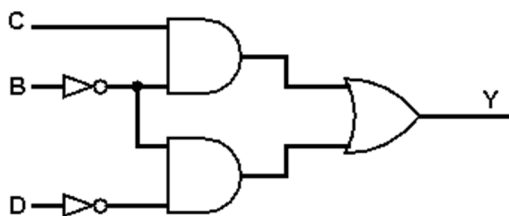


6

Format: Sum of products

		C, D			
		00	01	11	10
A, B	00	1	1	0	x
	01	x	0	1	1
	11	0	1	1	0
	10	1	1	0	x

$\bar{B}\bar{C} + \bar{A}BC + ABD$
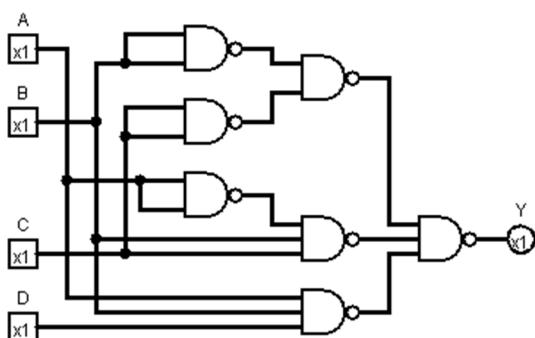
$$Y = \bar{B} \cdot \bar{C} + \bar{A} \cdot B \cdot C + A \cdot B \cdot D = \overline{\overline{\bar{B} \cdot \bar{C} + \bar{A} \cdot B \cdot C + A \cdot B \cdot D}} = \overline{\bar{B} \cdot \bar{C} \cdot \bar{A} \cdot B \cdot C \cdot A \cdot B \cdot D}$$





7

Format: Sum of products



		C, D			
		00	01	11	10
A, B	00	0	0	0	0
	01	1	1	0	0
	11	1	1	1	1
	10	0	1	0	1

$B\bar{C} + A\bar{C}D + AC\bar{D} + AB$

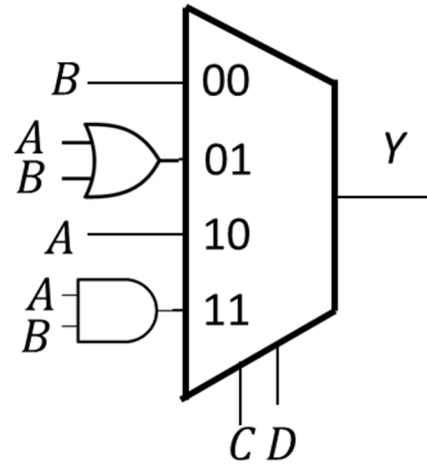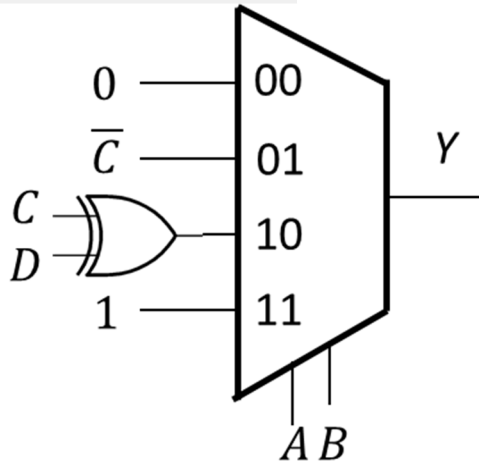

8

q3	q2	q1	q0	B4	B3	B2	B1	B0
0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0	1
0	0	1	0	0	0	0	1	0
0	0	1	1	0	0	0	1	1
0	1	0	0	0	0	1	0	0
0	1	0	1	0	0	1	0	1
0	1	1	0	0	0	1	1	0
0	1	1	1	0	0	1	1	1
1	0	0	0	0	1	0	0	0
1	0	0	1	0	1	0	0	1
1	0	1	0	1	0	0	0	0
1	0	1	1	1	0	0	0	1
1	1	0	0	1	0	0	1	0
1	1	0	1	1	0	0	1	1
1	1	1	0	1	0	1	0	0
1	1	1	1	1	0	1	0	1

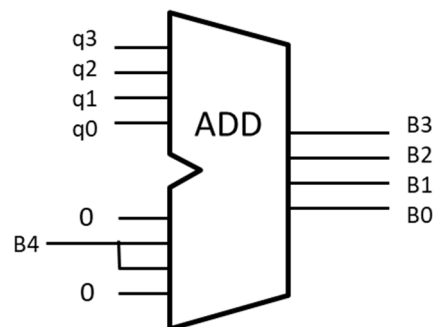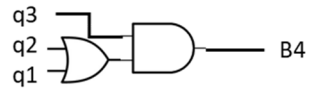

$$B4 = q3 \cdot q2 + q3 \cdot q1 = q3(q2 + q1)$$

$$B3 = q3 \cdot \bar{B4}$$

$$B2 = q2 \cdot \bar{B4} + q3 \cdot q2 \cdot q1 = \bar{q3} \cdot q2 + q3 \cdot q2 \cdot q1$$


$$B1 = q1 \oplus B4$$

$$B0 = q0$$

Or use the first expression plus an ADDER: add 6 if the value is 10 or higher (has the same effect as subtracting 10 when the carry is not used)

### Part 3

9

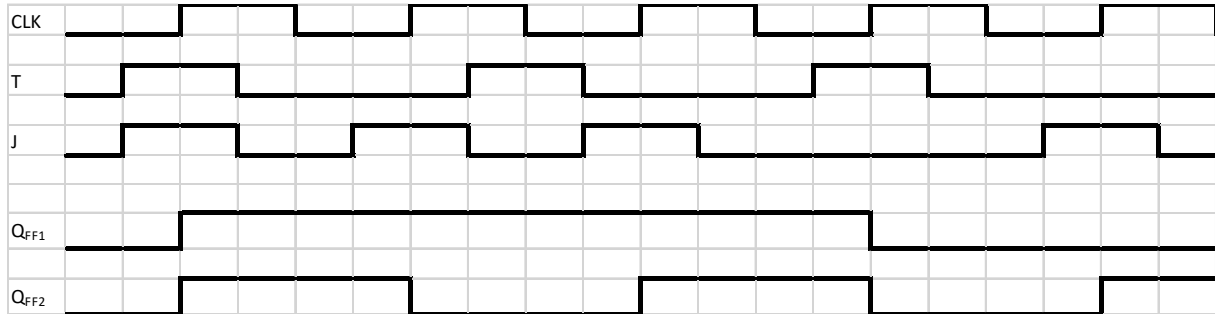


10

if  $D = 0$ :  $q_1^+ = q_1$   
 $q_0^+ = q_0$


if  $D = 1$ :  $q_1^+ = q_0$   
 $q_0^+ = \overline{q_1}$

$B = \overline{q_1 + q_0} = \overline{q_1} \cdot \overline{q_0}$   
 $H = q_1 \cdot q_0$

Present state		Next state				Out	
q1	q0	D=0		D=1		B	H
0	0	0	0	0	1	1	0
0	1	0	1	1	1	0	0
1	1	1	1	1	0	0	1
1	0	1	0	0	0	0	0

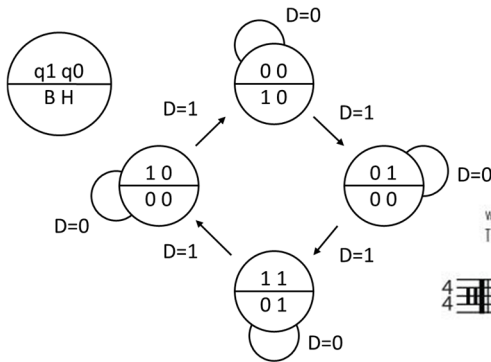

**Billie Jean**  
 by Michael Jackson

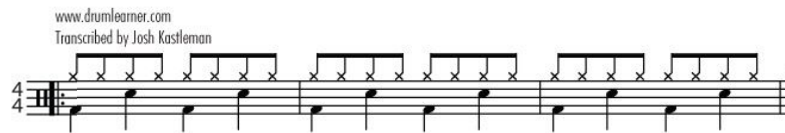

The FSM can be used as a drum machine: B = Base, H = Hi-hat, clk = Snare, D=1 drum, D=0 pause

11

Present state			Next state		
c	b	a	c+	b+	a+
0	0	0			
0	0	1			
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0			
1	0	1	1	1	1
1	1	0			
1	1	1	0	1	0

c+	ba =			
	00	01	11	10
c=0	x	x	1	0
1	x	1	0	x

b+	ba =			
	00	01	11	10
c=0	x	x	0	1
1	x	1	1	x



a+	ba =			
	00	01	11	10
c=0	x	x	1	1
1	x	1	0	x

$$c^+ = \bar{b} + \bar{c} \cdot a$$

$$b^+ = c + \bar{a}$$

$$a^+ = \bar{c} + \bar{b}$$

Present state			Next state		
c	b	a	c+	b+	a+
0	0	0	1	1	1
0	0	1	1	0	1
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	0	1	0
1	1	1	0	1	0

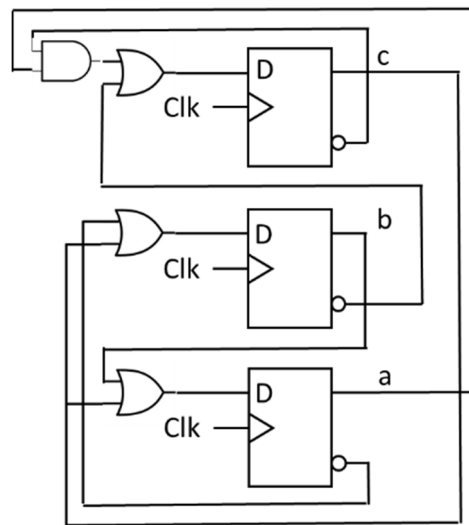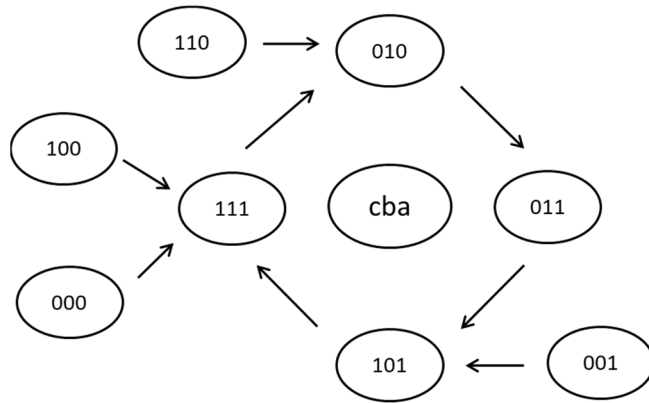

12

Present state		Next state							
		a b = 00		a b = 01		a b = 11		a b = 10	
q2	q1	q2+	q1+	q2+	q1+	q2+	q1+	q2+	q1+
0	0	0	0	1	0	1	1	0	1
0	1	0	0	0	1	1	1	0	1
1	1	1	1	0	1	1	1	0	1
1	0	0	0	1	0	1	1	1	1

q2+	a b =			
	00	01	11	10
q2q1 = 00	0	1	X	0
01	0	0	1	0
11	X	0	1	0
10	0	1	1	X

$$q_2^+ = a \cdot b + \bar{q}_1 \cdot b$$

q1+	a b =			
	00	01	11	10
q2q1 = 00	0	0	X	1
01	0	1	1	1
11	X	1	1	1
10	0	0	1	X

$$q_1^+ = q_1 \cdot b + a$$

## Part 4

13

Ripple carry critical path is  $2 \times 4 = 8$  gates.  $t_{pd} = 8 \times 40 = 320$  ps

74hc283 critical path is 6 gates.  $t_{pd} = 6 \times 40 = 240$  ps (even though the carry-chain has 5)

$$T_c \geq t_{pcq} + t_{pd} + t_{setup} = 40 + 320 + 50 = 410 \text{ ps. } f_{clock} = 1 / T_c = 2,5 \text{ GHz}$$

$$T_c \geq t_{pcq} + t_{pd} + t_{setup} = 40 + 240 + 50 = 330 \text{ ps. } f_{clock} = 1 / T_c = 3,0 \text{ GHz}$$

Hold time does not affect max clock speed.

14

$$E = 01010101_2 = 85_{10}$$

$$F = 00101010_2 = 42_{10}$$

$$G = 00010001_2 = 17_{10}$$

$$P = E \times F = 0000\ 1101\ 1111\ 0010_2 = 3570_{10} = 85 \times 42$$

$$K = E / G = 00000101_2 = 5_{10} = 85 / 17$$

15

The opcodes for the ALU is as below (did not need to be shown).

First case  $A = 1010$ ,  $B = 0011$ ,  $S_2 = 0$ ,  $S_1 = 1$ ,  $S_0 = 1$ :  $Y = A \text{ NOR } B = 0100$

Second case if  $S_2 = 1$ :  $Y = A - B = 0111$  ( $10 - 3 = 7$ , calculate decimal or binary with 2 complement)

S2	S1	S0	Operation
0	0	0	A AND B
0	0	1	A NAND B
0	1	0	A OR B
0	1	1	A NOR B
1	0	0	A + A = 2A
1	0	1	A - A = 0
1	1	0	A + B
1	1	1	A - B

16

$$A_4A_3A_2A_1A_0 = 01001$$

$$D_3D_2D_1D_0 = 0101 \text{ (diodes are zero, no inverters on this ROM)}$$

