

IE1204 Digital Design Answer Form 2020-10-16



Full Name		Personal Number		Program						
Exam Answers 2020-10-16		YYYYMMDD-XXXX		NN						
#	Answer with	Answer				Points				
1	Decimal number	-72				1				
2	8 bit two's complement binary number	0	1	1	1	0	1	0	1	1
3	8 bit two's complement binary number	1	1	1	0	0	1	1	1	1
4	Boolean expression, Y =	$A \cdot C \cdot D$				1				
5	Boolean expression, Y =	$(A + B + C)(A + \bar{B} + \bar{C})(\bar{A} + B + \bar{C})$				1				
6	Boolean expression, Y = OR $A \cdot C + \bar{A} \cdot \bar{B} \cdot \bar{D} + B \cdot \bar{C} \cdot D$	$(\bar{C} + \bar{D})(\bar{B} + D)(\bar{A} + B)$				1				
7	MUX connections	1				1				
	Row CD = 00	$\overline{A \oplus B}$								
	Row CD = 01	\bar{B}								
	Row CD = 10	$A + B$								
	Row CD = 11									
8	Timing diagram					1				
9	Timing diagram					1				
10	Setup condition	<input checked="" type="checkbox"/> Yes	<input type="checkbox"/> No		1					
	Hold condition	<input type="checkbox"/> Yes	<input checked="" type="checkbox"/> No							
11	Boolean expression	$B \cdot \bar{C}$				1				
12	16 bit two's complement binary number, MSB	1	1	1	1	1	1	0	1	
	LSB	1	0	0	0	1	1	0		1
13	8 bit two's complement binary number	1	1	1	0	0	1	1	1	1
14	Number interval	-16 to 15.875				1				
15	5 result bits (S4 S3 S2 S1 S0)	1	0	1	0	1				
16	4 flag bits (V C N Z)	1	1	0	0					
TOTAL POINTS		Examiner sign CMZ				16				

IE1204 Digital Design Exam 2020-10-16 K-maps

4 CMOS

Swedish: Bestäm den logiska funktionen $Y = f(A, B, C)$ för CMOS-grindnätet. Förenkla så långt som möjligt.

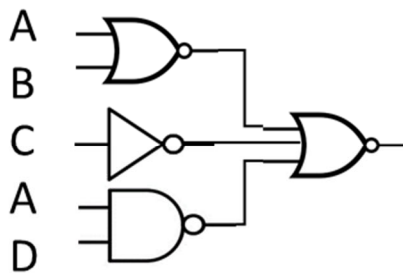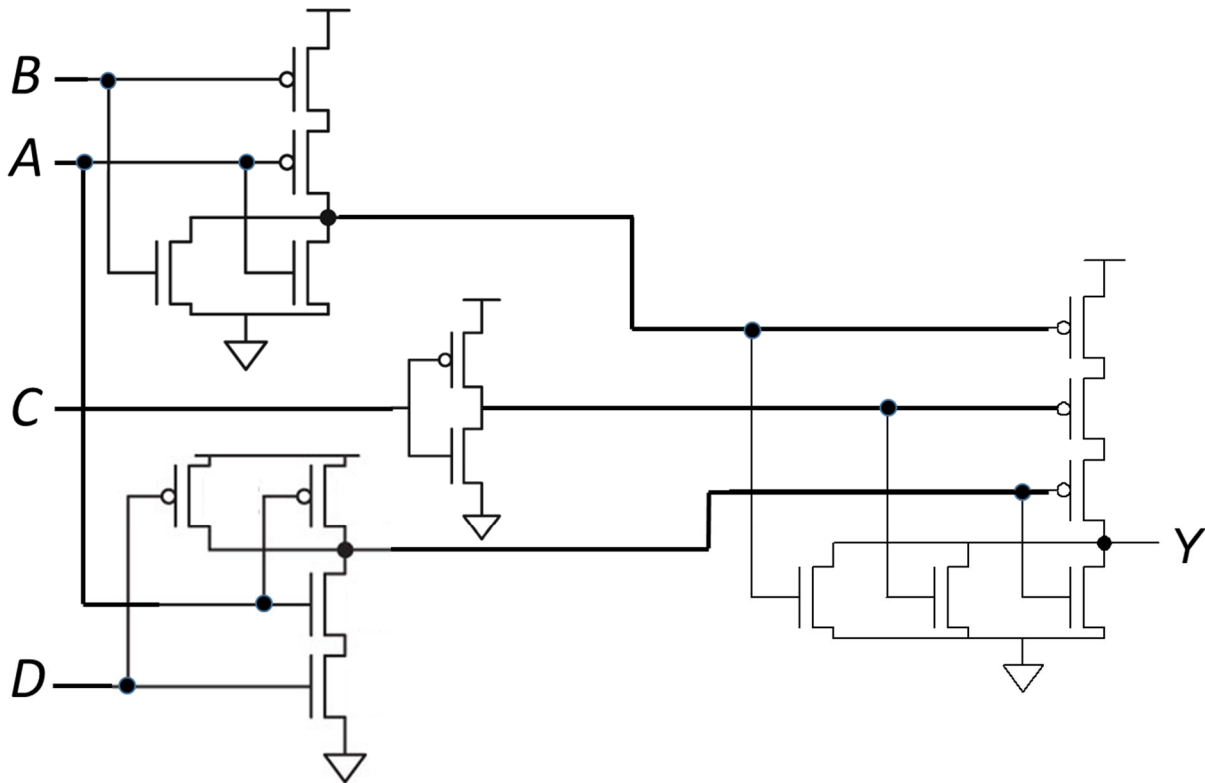English: Determine the logic function $Y = f(A, B, C)$ for the CMOS-circuit. Simplify as much as possible.



$$Y = \overline{\overline{(A + B) + \overline{C} + \overline{(A \cdot D)}}} = A \cdot C \cdot D$$

5 SoP / PoS

Swedish: Ta fram booleskt uttryck på PoS form för sanningstabellen nedan.

English: Derive the Boolean expression in PoS form for the truth table below.

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

		AB			
		00	01	11	10
C	0	0	1	1	1
	1	1	0	1	0

$$Y = (A + B + C)(A + \bar{B} + \bar{C})(\bar{A} + B + \bar{C})$$

6 K-map



Swedish: Uttnyttja x = don't care.

Ta fram enklast möjliga booleska uttryck från K-map.

English: Use x = don't care.

Derive simplest possible Boolean expression from the K-map.

Y	CD 00	CD 01	CD 11	CD 10
AB 00	1	1	0	1
AB 01	X	1	0	0
AB 11	0	1	0	0
AB 10	X	0	0	0

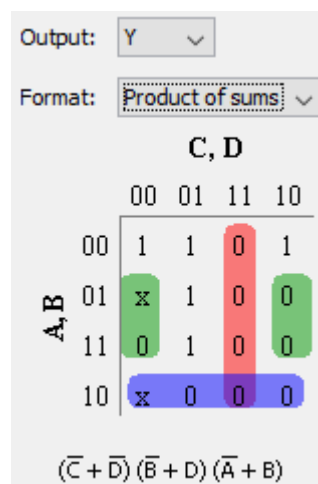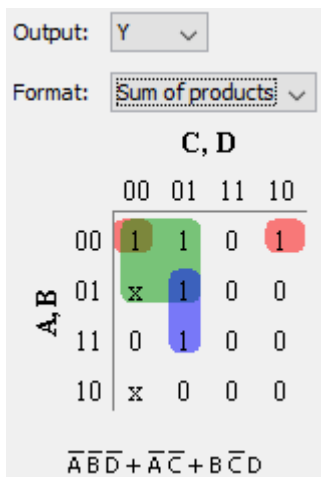

IE1204 Digital Design Exam 2020-10-16 Solutions


17 Analysis of Combinational Circuit

Swedish:

1. Ta fram booleskt uttryck för kretsen nedan.
2. Rita K-map för kretsen med variabelordning som i figuren.
3. Förenkla uttrycket med hjälp av K-map.
4. Rita ny krets med enbart 2- och 3-ingångars NOR-grindar.

English:

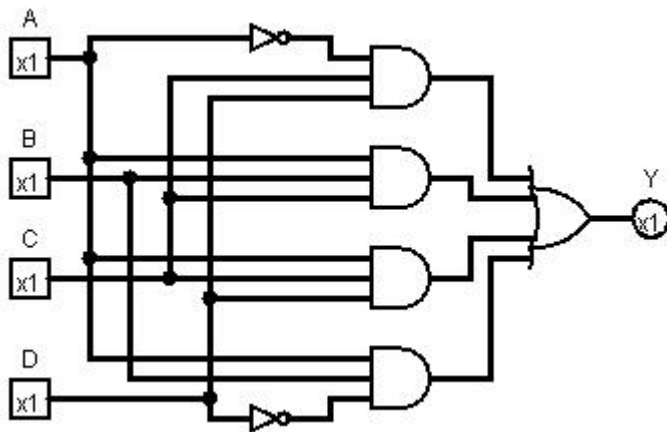1. Derive the Boolean expression for the circuit below.
2. Draw a K-map for the circuit with variables as in the figure.
3. Simplify the expression using the K-map.
4. Draw a new circuit using only 2 and 3 input NOR gates.




$$\bar{A}CD + ABC + ACD + AB\bar{D}$$

$$\sim A C D + A B C + A C D + A B \sim D$$

Use POS for NOR only (inverters are ok if you note that they can be made with a NOR)

Format: Sum of products		Format: Product of sums	
C, D		C, D	
	00 01 11 10		00 01 11 10
A, B	00 0 0 1 0	A, B	00 0 0 1 0
	01 0 0 1 0		01 0 0 1 0
	11 1 0 1 1		11 1 0 1 1
	10 0 0 1 0		10 0 0 1 0
CD + AB \bar{D}		(A + D)(B + D)(C + \bar{D})	

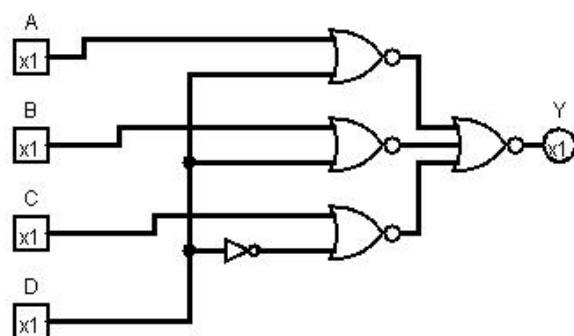

18 Design of Combinational Circuit

Swedish:

Designa en kombinatorisk krets för $Y=f(Q_3, Q_2, Q_1, Q_0)$ där

$Y = x$ (don't care) för talet 1

$Y = x$ (don't care) för alla jämna tal som är tvåpotenser, dvs 2, 4 och 8

$Y = 1$ för alla udda primtal, dvs 3, 5, 7, 11, och 13

$Y = 0$ för alla övriga udda tal

$Y = 0$ för alla övriga jämna tal

1. Rita sanningstabellen.
2. Rita K-map för sanningstabellen med variabelordning som i figuren.
3. Uttnyttja $x = \text{don't care}$. Ta fram enklast möjliga booleska uttryck från K-map.
4. Rita en krets för uttrycket med enbart 2- och 3-ingångars NAND-grindar.

English:

Design a combinational circuit for $Y=f(Q_3, Q_2, Q_1, Q_0)$ where

$Y = x$ (don't care) for the number 1

$Y = x$ (don't care) for all even numbers that are powers of 2, i.e. 2, 4, and 8

$Y = 1$ for all odd prime numbers, i.e. 3, 5, 7, 11, and 13

$Y = 0$ for all other odd numbers

$Y = 0$ for all other even numbers

1. Draw the truth table.
2. Draw a K-map for the truth table with variables as in the figure..
3. Use $x = \text{don't care}$. Derive simplest possible Boolean expression from the K-map.
4. Draw a circuit for the expression using only 2 and 3 input NAND-gates.

$Q_1Q_0 =$	00	01	11	10
$Q_3Q_2 =$ 00				
01				
11				
10				



Rita om K-map i dina inlämnade svar.

Redraw the K-map in your answer sheets.


(Answer on next page)

18 Design of Combinational Circuit

Q3	Q2	Q1	Q0	Y
0	0	0	0	0
0	0	0	1	x
0	0	1	0	x
0	0	1	1	1
0	1	0	0	x
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	x
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

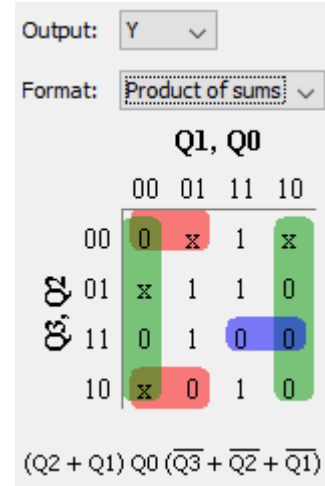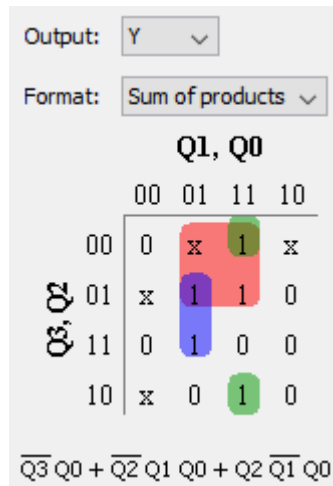

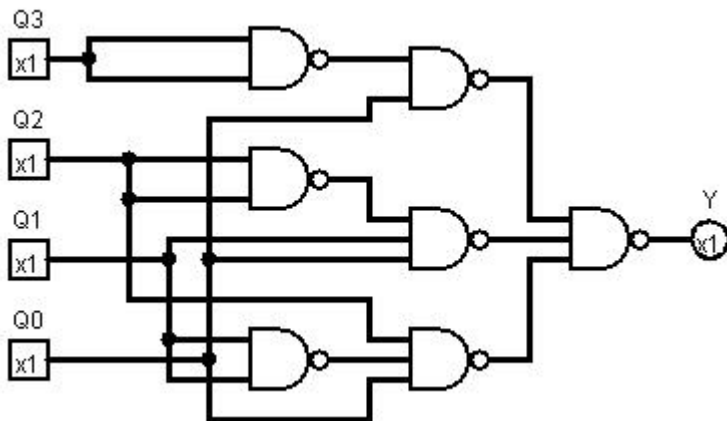Use SOP for NAND only (inverters are ok if you note that they can be made with a NAND)




19 Analysis of FSM

Swedish: Analysera vad nedanstående tillståndsmaskin (FSM) utför.

1. Ta fram Boolska uttryck för nästa tillstånd.
2. Rita tillståndstabell.
3. Rita tillståndsdigram.

English: Analyze the state machine (FSM) below.

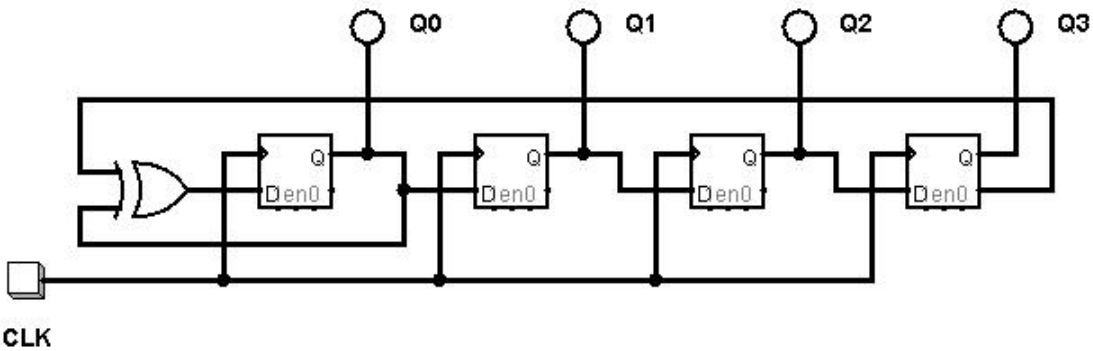1. Derive Boolean expressions for next state.
2. Draw a state table.
3. Draw a state diagram.




$$Q3+ = Q2$$

$$Q2+ = Q1$$

$$Q1+ = Q0$$

$$Q0+ = \overline{Q3} \oplus Q1 = Q3 \cdot Q1 + \overline{Q3} \cdot \overline{Q1}$$

Present state				Next state			
Q3	Q2	Q1	Q0	Q3+	Q2+	Q1+	Q0+
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	1	0	0	1
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	0
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	1
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	1
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	1

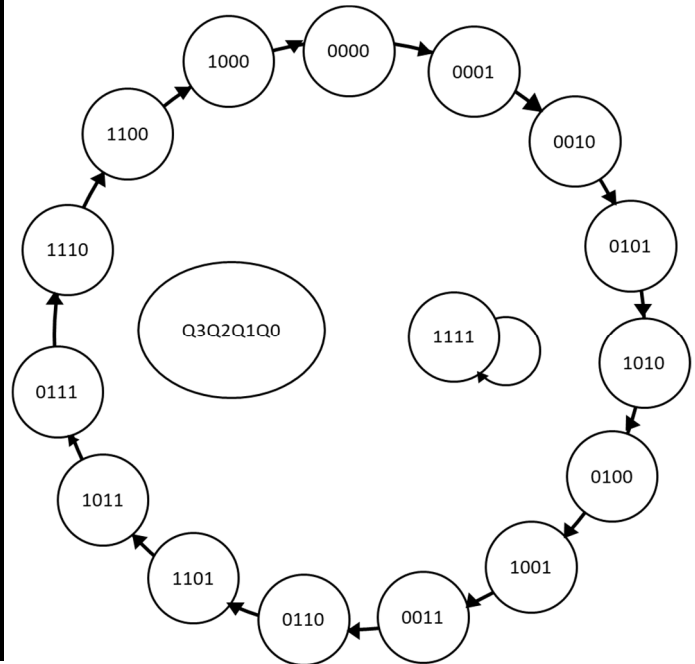


20 Design of FSM

Swedish: Konstruera en tillståndsmaskin (FSM) enligt tillståndsdigrammet nedan.

1. Rita tillståndstabell.
2. Ta fram K-map för nästa tillstånd och utsignal.
3. Ta fram minimerade uttryck för nästa tillstånd och utsignal.
4. Rita kretsschema för en FSM med DFFs och vilka grindar som helst.

English: Design a state machine (FSM) according to the state diagram below.

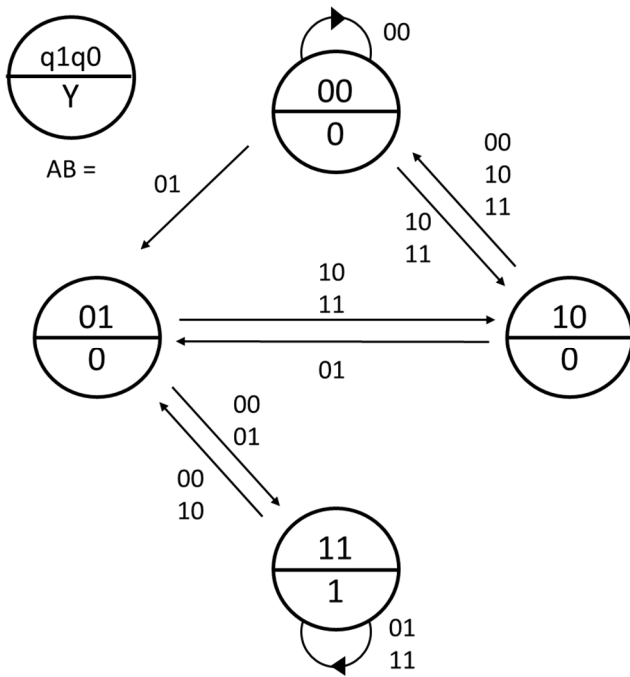1. Draw a state table.
2. Derive K-maps for next state and output.
3. Derive minimized expressions for next state and output.
4. Draw the FSM circuit diagram with DFFs and any gates.



q1q0 = 00	A B =			
	00	01	11	10
01				
11				
10				

Rita om K-map i dina inlämnade svar.

Redraw the K-map in your answer sheets.

Present state		Next state								Out
		AB = 00		AB = 01		AB = 11		AB = 10		
q1	q0	q1+	q0+	q1+	q0+	q1+	q0+	q1+	q0+	Y
0	0	0	0	0	1	1	0	1	0	0
0	1	1	1	1	1	1	0	1	0	0
1	1	0	1	1	1	1	1	0	1	1
1	0	0	0	0	1	0	0	0	0	0

q1+	AB=				
q1q0	00	01	11	10	
00	0	0	1	1	
01	1	1	1	1	
11	0	1	1	0	
10	0	0	0	0	

q0+	AB=				
q1q0	00	01	11	10	
00	0	1	0	0	
01	1	1	0	0	
11	1	1	1	1	
10	0	1	0	0	

(K-map not needed for Y)

Continues on next page

Output:

Format:

A, B

	00	01	11	10
q1, q0	0	0	1	1
01	1	1	1	1
11	0	1	1	0
10	0	0	0	0

$\bar{q}1 \bar{A} + \bar{q}1 q0 + q0 B$

Output:

Format:

A, B

	00	01	11	10
q1, q0	0	1	0	0
01	1	1	0	0
11	1	1	1	1
10	0	1	0	0

$\bar{A} B + q0 \bar{A} + q1 q0$

$$Y = q1 \cdot q0$$

